

Resistive Networks

Lecture 2

September 6th, 2018

Jae W. Lee (jaewlee@snu.ac.kr)

Computer Science and Engineering

Seoul National University

Slide credits: Prof. Anant Agarwal at MIT


Review: Lumped Matter Discipline (LMD)

- **Constraints we impose on ourselves to simplify our analysis**
 - Allows us to create the lumped circuit abstraction

$$\frac{\partial \phi_B}{\partial t} = 0 \quad \text{Outside elements}$$


$$\frac{\partial q}{\partial t} = 0 \quad \text{Inside elements}$$

wires resistors I/V sources

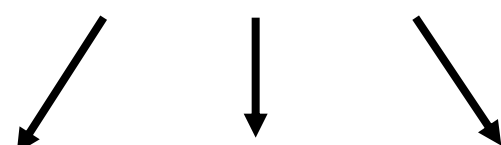

Review: Lumped Matter Discipline (LMD)

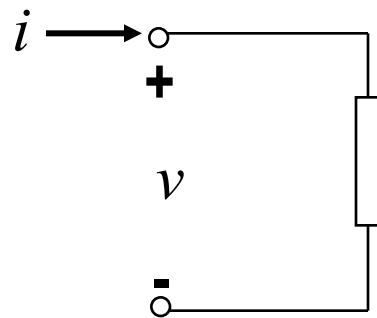- LMD allows us to create the lumped circuit abstraction



Lumped circuit element

power consumed by element = vi [Watt]

Review: Kirchhoff's Laws

- Maxwell's equations simplify to algebraic KVL and KCL under LMD!

KVL:

$$\sum_j v_j = 0$$

loop


KCL:

$$\sum_j i_j = 0$$

node

Review: Kirchhoff's Laws

■ Example

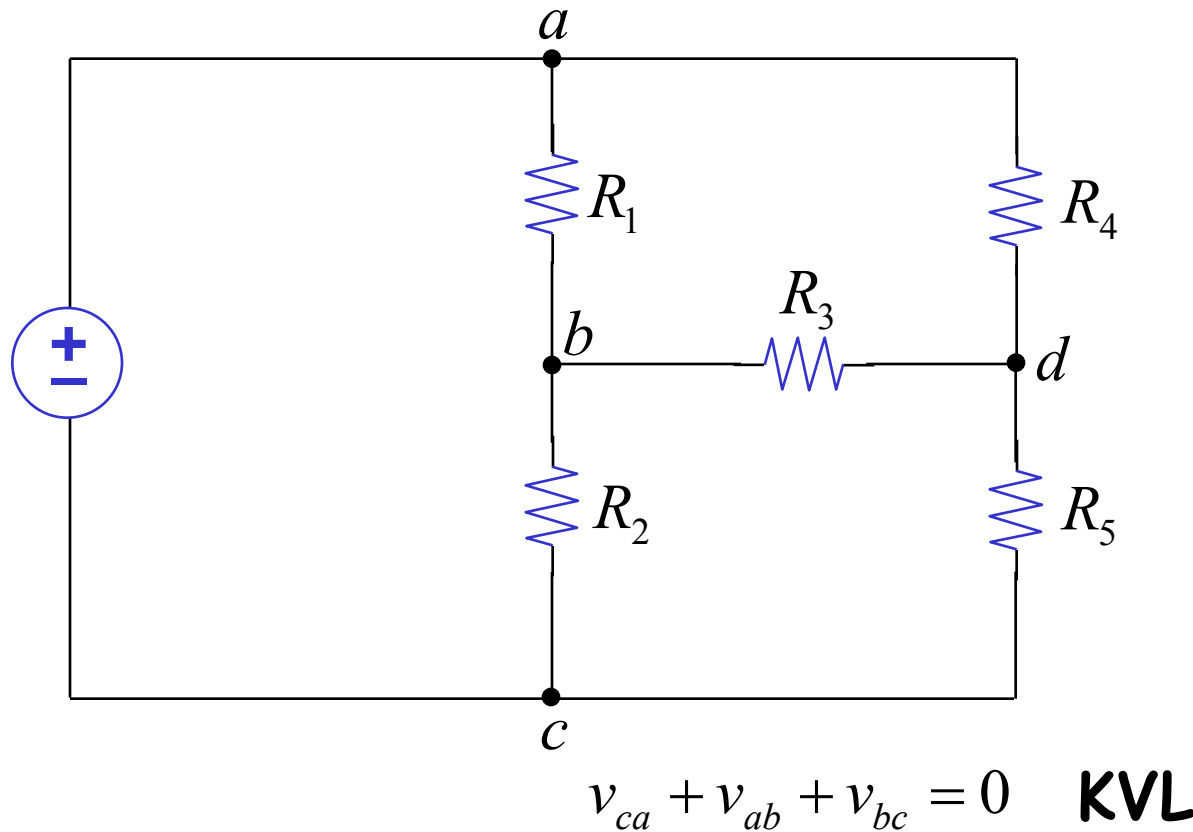

$$i_{ca} + i_{da} + i_{ba} = 0 \quad \text{KCL}$$


Outline

Textbook: Ch. 2.1-2.6

- **Kirchhoff's Laws: KCL and KVL**
- **Circuit Analysis: Basic Method**
- **Intuitive Method of Circuit Analysis: Series and Parallel Simplification**
- **Dependent Sources**

KCL (Kirchhoff's Current Law)

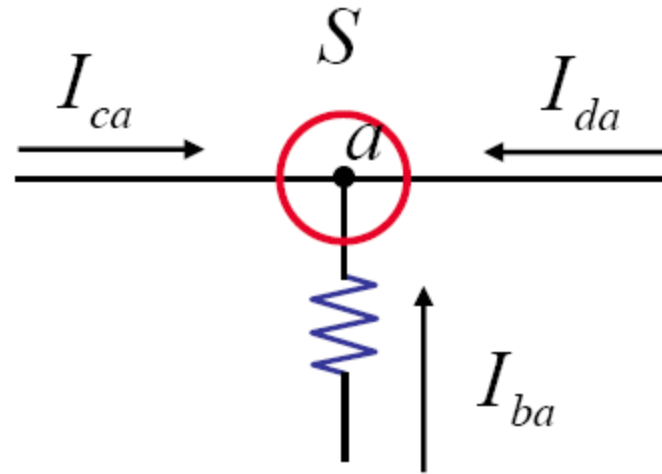- The sum of all branch currents flowing into a node is zero
– charge conservation.



$$I_{ca} + I_{ba} + I_{da} = 0$$

KCL: An Illustration

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.


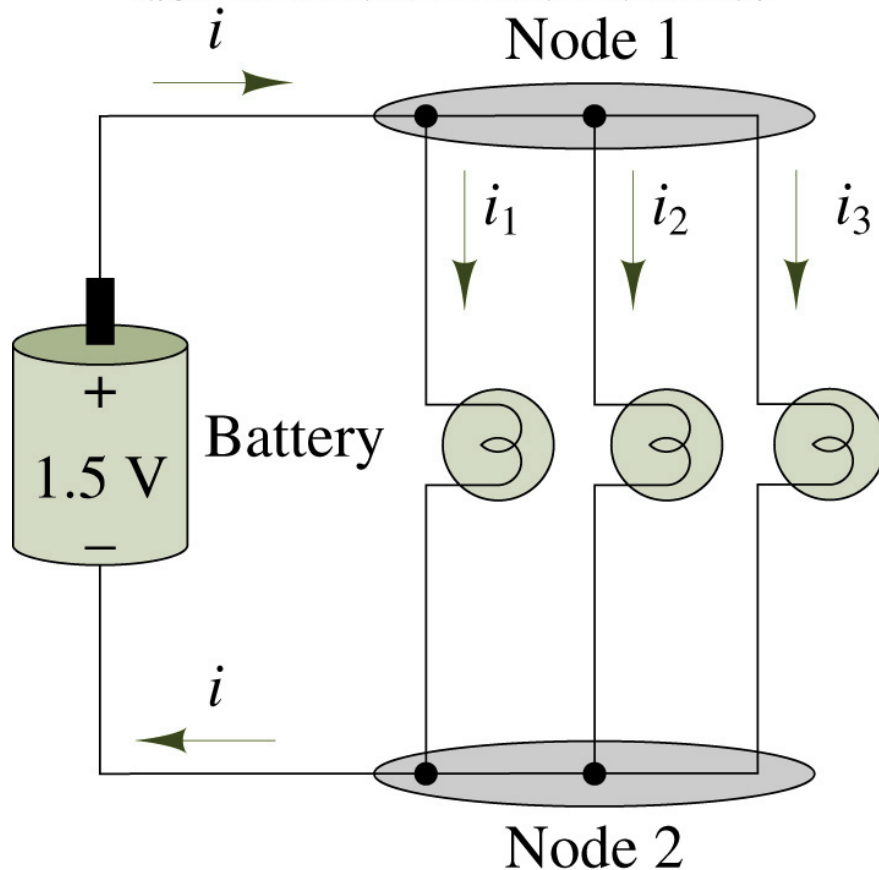


Illustration of KCL at
node 1: $-i + i_1 + i_2 + i_3 = 0$

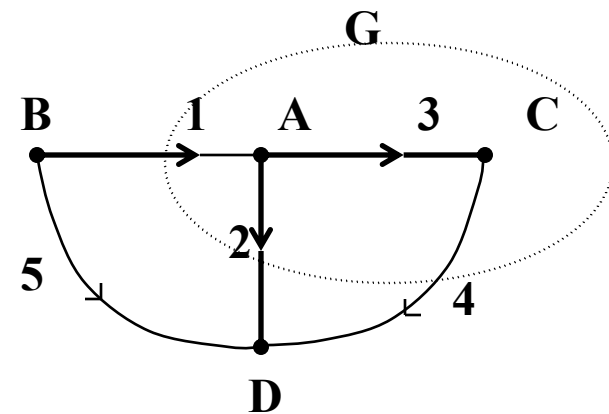


Node: $i_1 - i_2 - i_3 = 0$

G: $i_1 - i_2 - i_4 = 0$

KCL: Demonstration

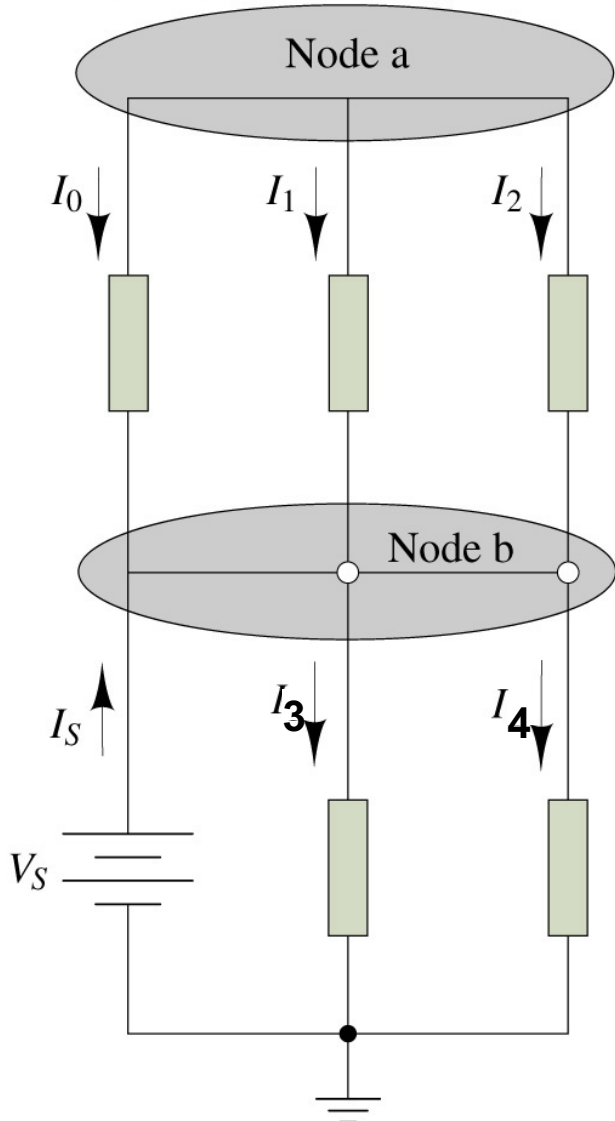Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




$$I_S = 5A, I_1 = 2A, \\ I_2 = -3A, I_3 = 1.5 A$$

Find I_0 and I_4

KCL: Example




Write down the KCL equation for **G**.

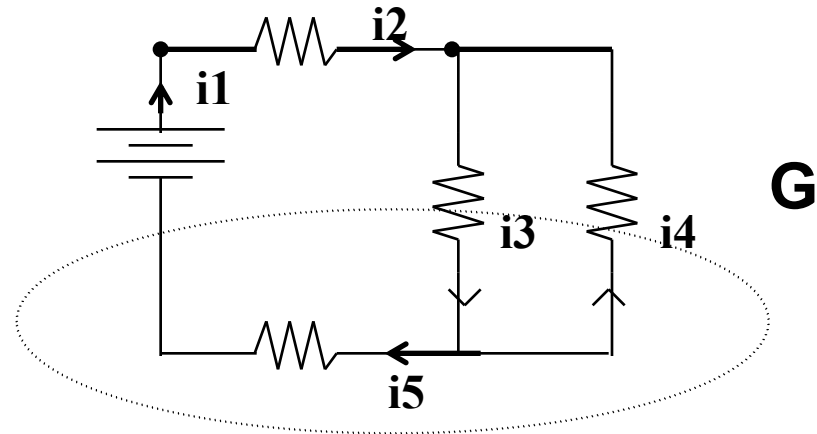


KVL (Kirchhoff's Voltage Law)

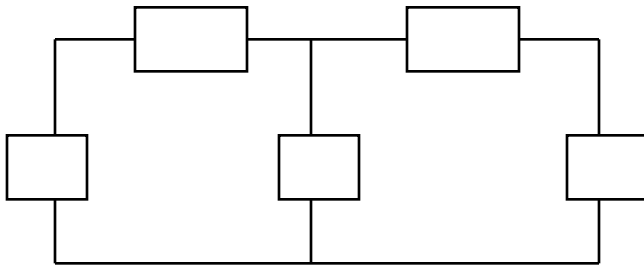- The algebraic sum of the branch voltages around any closed path in a network must be zero



(a)

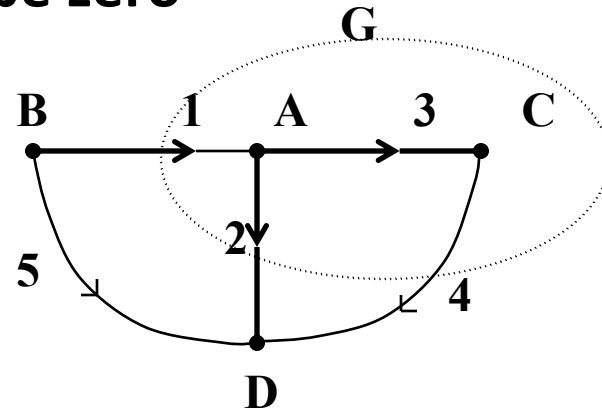

(b)


Node sequence B,A,D,B: $v_{BA} + v_{AD} + v_{DB} = 0$

Using node voltages: $v_{BA} = e_B - e_A$, $e_D = 0$

(reference node = D, reference voltage = 0)

KVL: Example

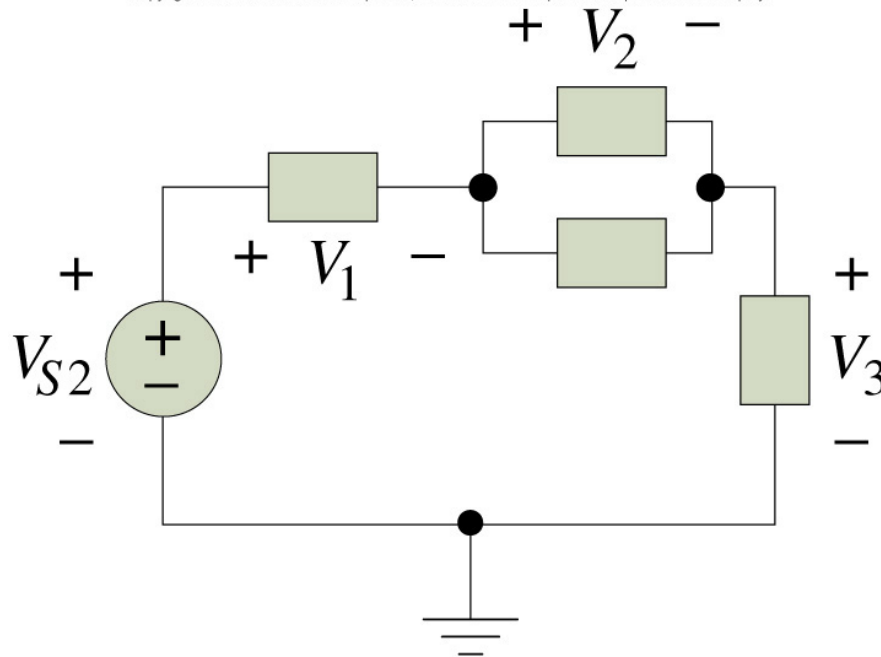Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




$$V_{S2} = 12 \text{ V}, V_1 = 6 \text{ V}, V_3 = 1 \text{ V}$$

Find V_2 .


Note: A helpful mnemonic for writing KVL equations is to assign the polarity to a given voltage in accordance with **the first sign encountered** when traversing the voltage around the loop.

Some Useful Facts

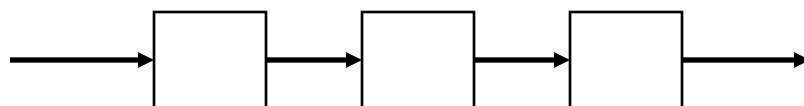- The branch currents passing through series-connected elements must be the same.



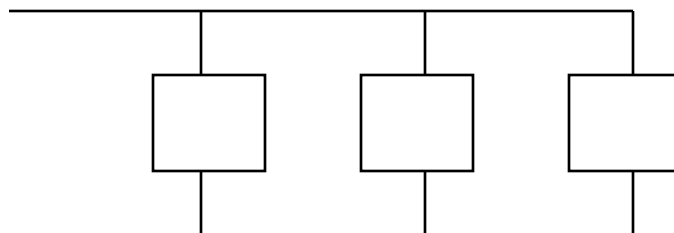- The voltages across parallel-connected elements must be the same.



Outline

Textbook: Ch. 2.1-2.6

- Kirchhoff's Laws: KCL and KVL
- **Circuit Analysis: Basic Method**
- Intuitive Method of Circuit Analysis: Series and Parallel Simplification
- Dependent Sources


Circuit Analysis: Basic Method


■ Goal: Find all element v 's and i 's


1. write element v - i relationships (from lumped circuit abstraction)
2. write KCL for all nodes
3. write KVL for all loops

Circuit Analysis: Basic Method

- **Step 1: Element relationships**
 - Example: 3 lumped circuit elements

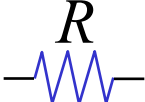For R , $V = IR$ 


For voltage source, $V = V_0$ 

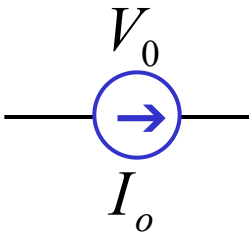For current source, $I = I_0$ 

Circuit Analysis: Basic Method

■ KVL, KCL example (Step 2 & 3)


- A demo circuit

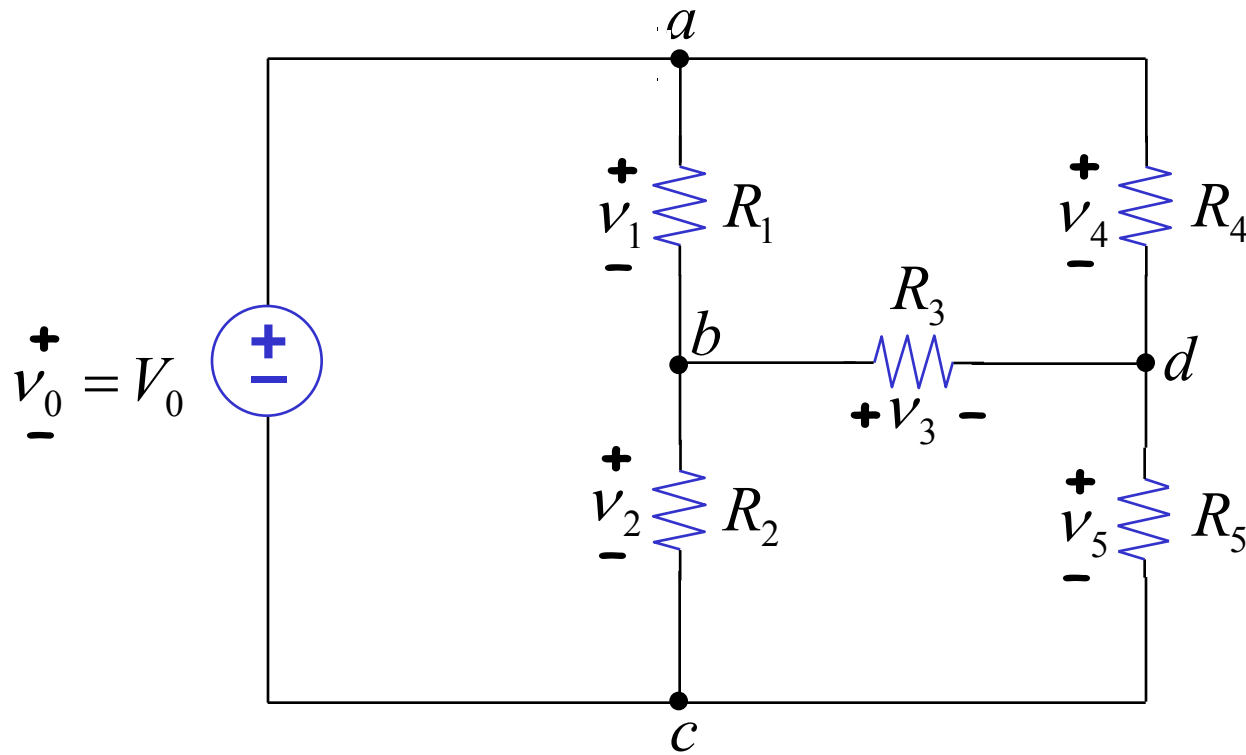

Circuit Analysis: Basic Method

■ Associated variables discipline

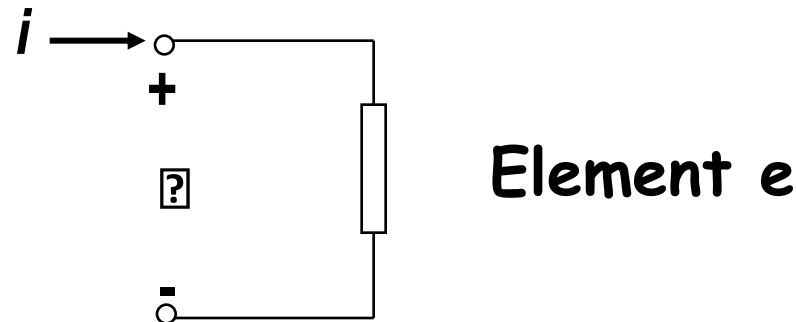- Current is taken to be positive going into the positive voltage terminal




Then power consumed by element e $\left. \vphantom{\begin{matrix} \text{Then power consumed} \\ \text{by element e} \end{matrix}} \right\} = v i$ is positive

Circuit Analysis: Basic Method

■ KVL, KCL example (Step 2 & 3)

- A demo circuit

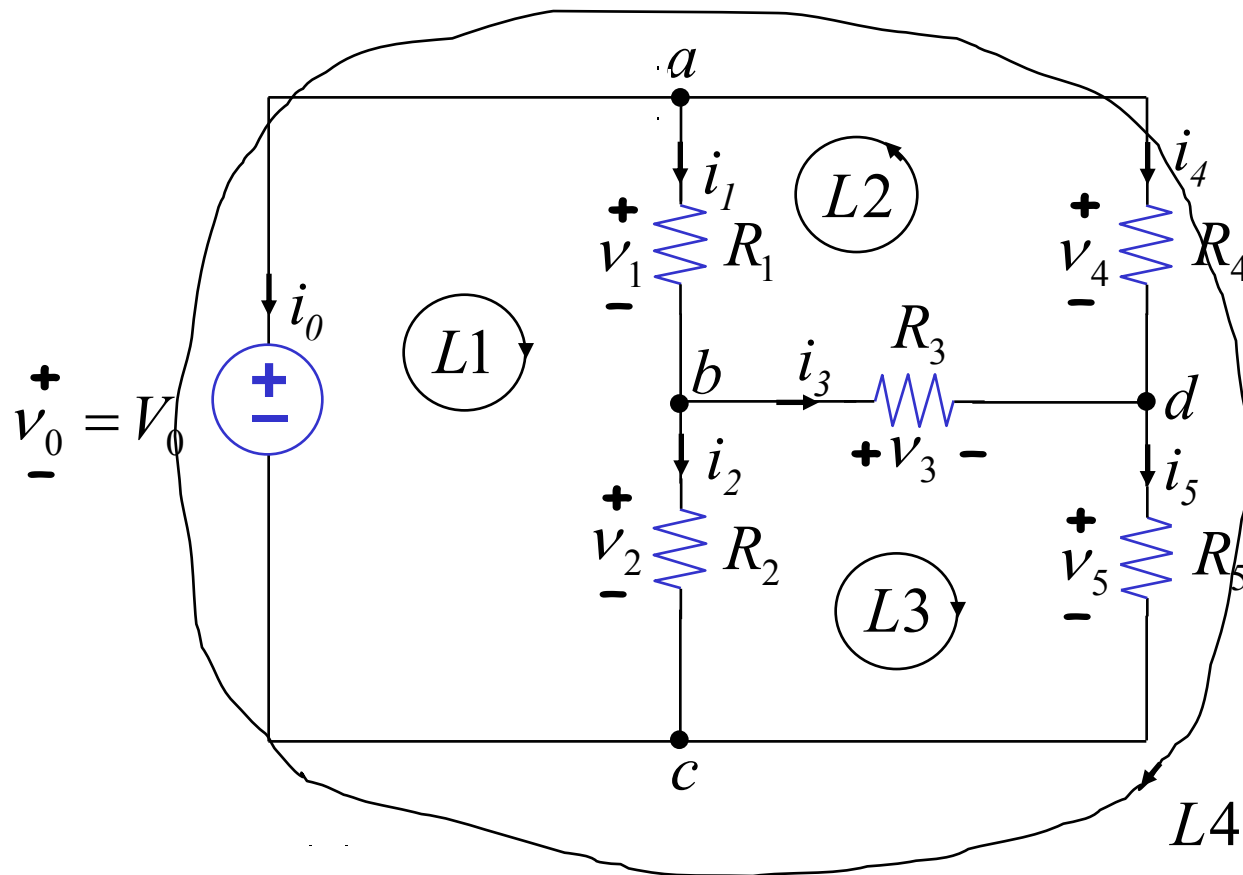

Circuit Analysis: Basic Method

■ Put all steps together!

$$V_0 \dots V_5, I_0 \dots I_5$$

12 unknowns

1. Element relationships (v, i)

$$v_0 = V_0 \leftarrow \text{given} \quad v_3 = i_3 R_3$$

$$v_1 = i_1 R_1 \quad v_4 = i_4 R_4$$

$$v_2 = i_2 R_2 \quad v_5 = i_5 R_5$$

6 equations

2. KCL at the nodes

$$\text{a: } i_0 + i_1 + i_4 = 0$$

$$\text{b: } i_2 + i_3 - i_1 = 0$$

$$\text{d: } i_5 - i_3 - i_4 = 0$$

$$\text{e: } -i_0 - i_2 - i_5 = 0 \text{ redundant}$$

3 independent equations

3. KVL for loops

$$\text{L1: } -v_0 + v_1 + v_2 = 0$$


$$\text{L2: } v_1 + v_3 - v_4 = 0$$

$$\text{L3: } v_3 + v_5 - v_2 = 0$$

$$\text{L4: } -v_0 + v_4 + v_5 = 0 \text{ redundant}$$

3 independent equations

12 equations
12 unknowns

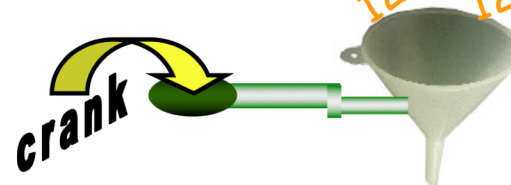

ugh @#!


Outline

Textbook: Ch. 2.1-2.6


- Kirchhoff's Laws: KCL and KVL
- Circuit Analysis: Basic Method
- **Intuitive Method of Circuit Analysis: Series and Parallel Simplification**
- Dependent Sources

Series and Parallel Simplification

■ Voltage divider and series resistors

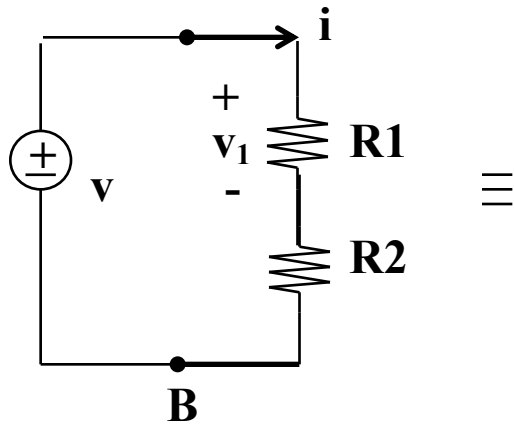

(a) Voltage divider

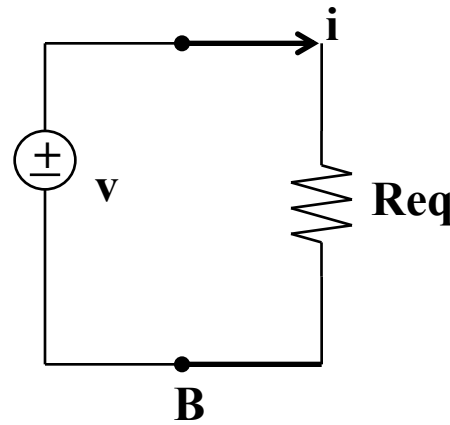

(b) Equivalent resistance

What does “equivalent” mean?

$$v_1 = \frac{R_1}{R_1 + R_2} v$$


Series and Parallel Simplification

■ Voltage divider and series resistors

$$R_1 = 10 \text{ k}\Omega, \quad R_2 = 6 \text{ k}\Omega, \\ R_3 = 8 \text{ k}\Omega$$


Find V_3 .

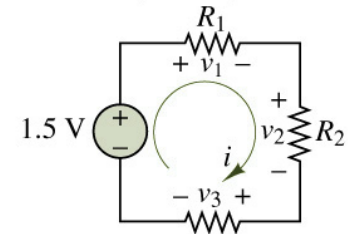Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.



The current i flows through each of the four series elements. Thus, by KVL,


$$1.5 = v_1 + v_2 + v_3$$

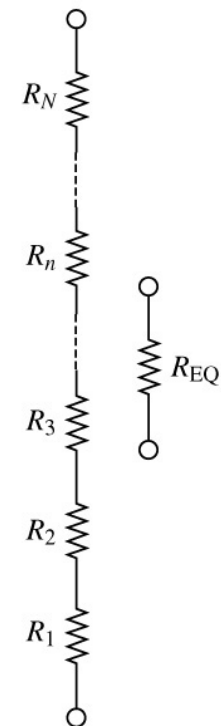

N series resistors are equivalent to a single resistor equal to the sum of the individual resistances.

Series and Parallel Simplification

■ Current divider and parallel resistors

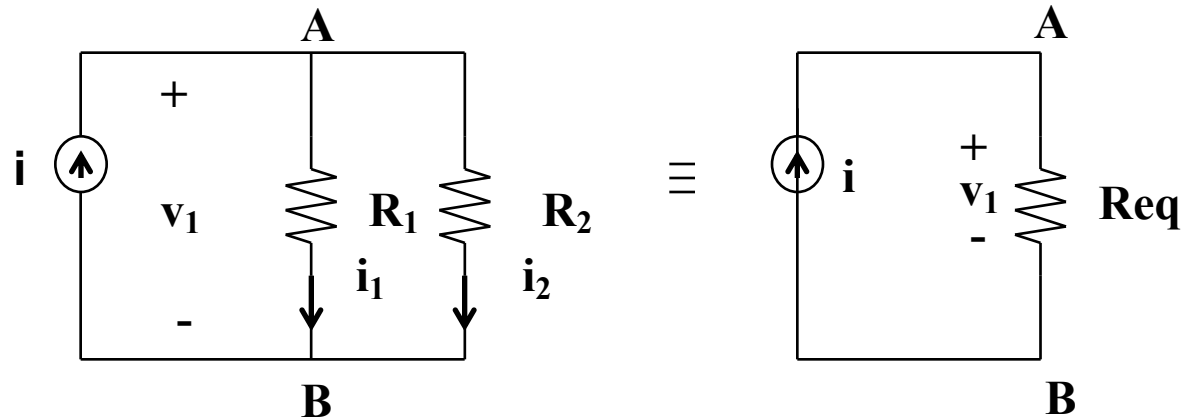

(a) Current divider



(b) Equivalent resistance

$$i_1 = \frac{G_1}{G_1 + G_2} i = \frac{R_2}{R_1 + R_2} i$$

Series and Parallel Simplification

■ Current divider and parallel resistors

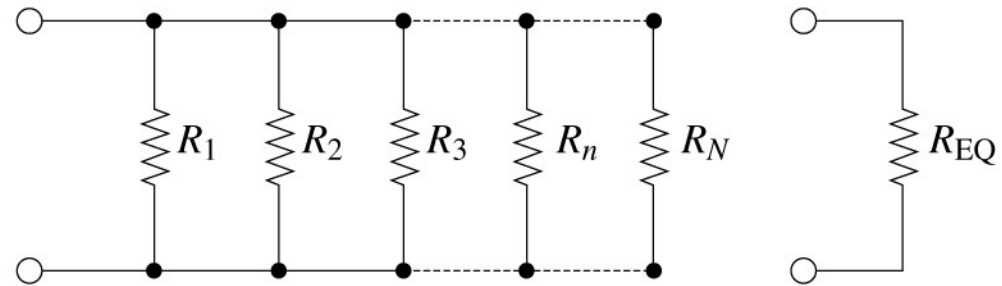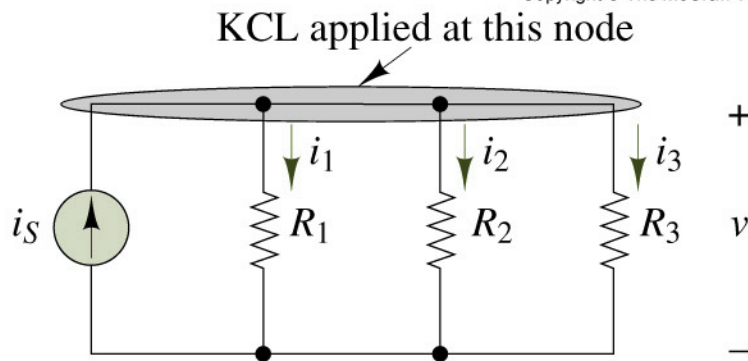
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



N resistors in parallel are equivalent to a single equivalent resistor with resistance equal to the inverse of the sum of the inverse resistances.

Series and Parallel Simplification


■ Example 1

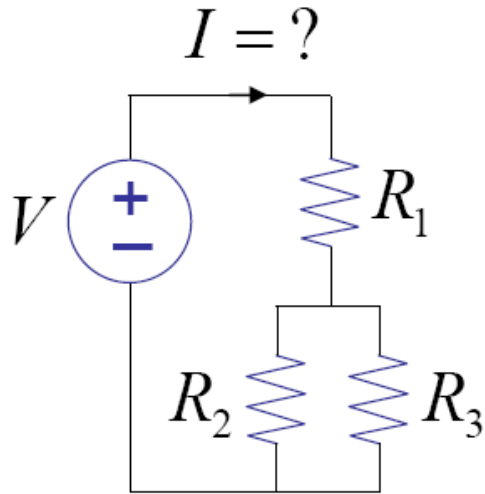

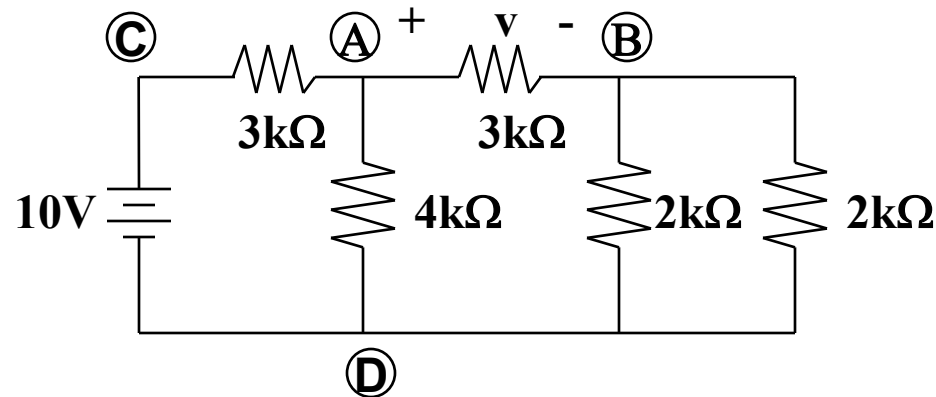Example 2







Find the voltage (v) between nodes A and B.



Series and Parallel Simplification

■ Element combination rules

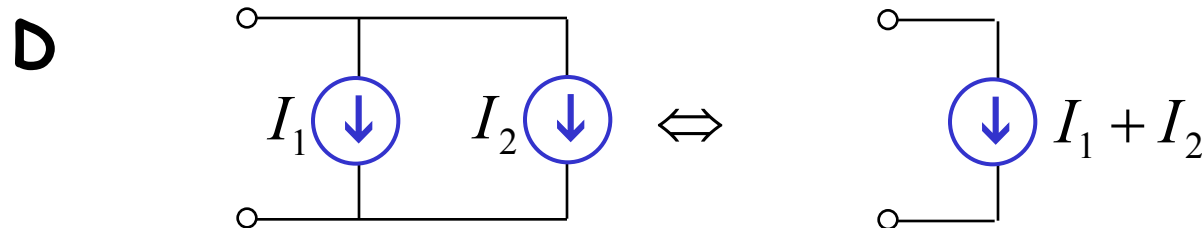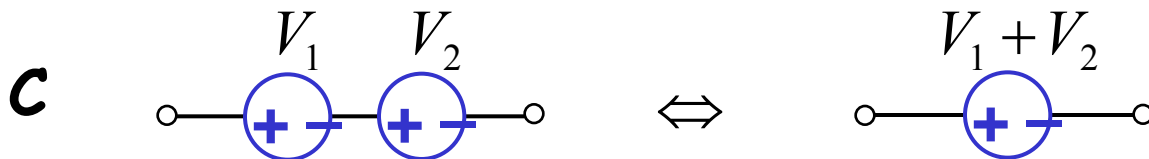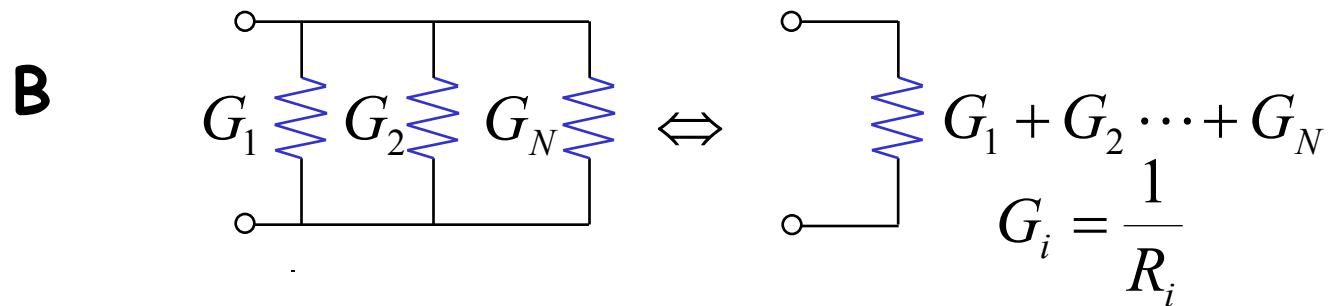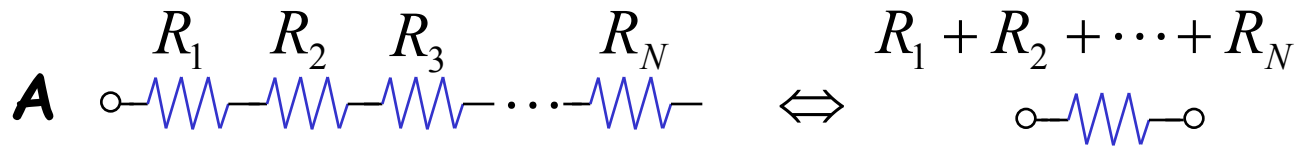

Outline


Textbook: Ch. 2.1-2.6

- Kirchhoff's Laws: KCL and KVL
- Circuit Analysis: Basic Method
- Intuitive Method of Circuit Analysis: Series and Parallel Simplification
- **Dependent Sources**

Dependent Sources


- Seen previously... **independent sources!**

Resistor

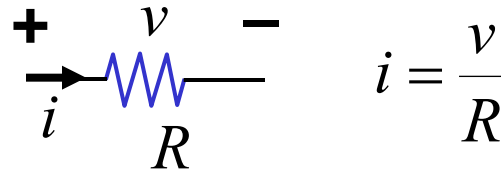

$$i = \frac{v}{R}$$

Independent
Current source

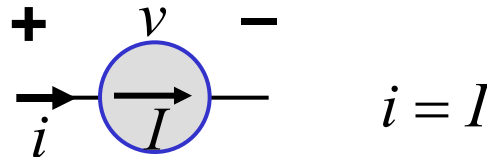


$$i = I$$

2-terminal 1-port devices

Dependent Sources

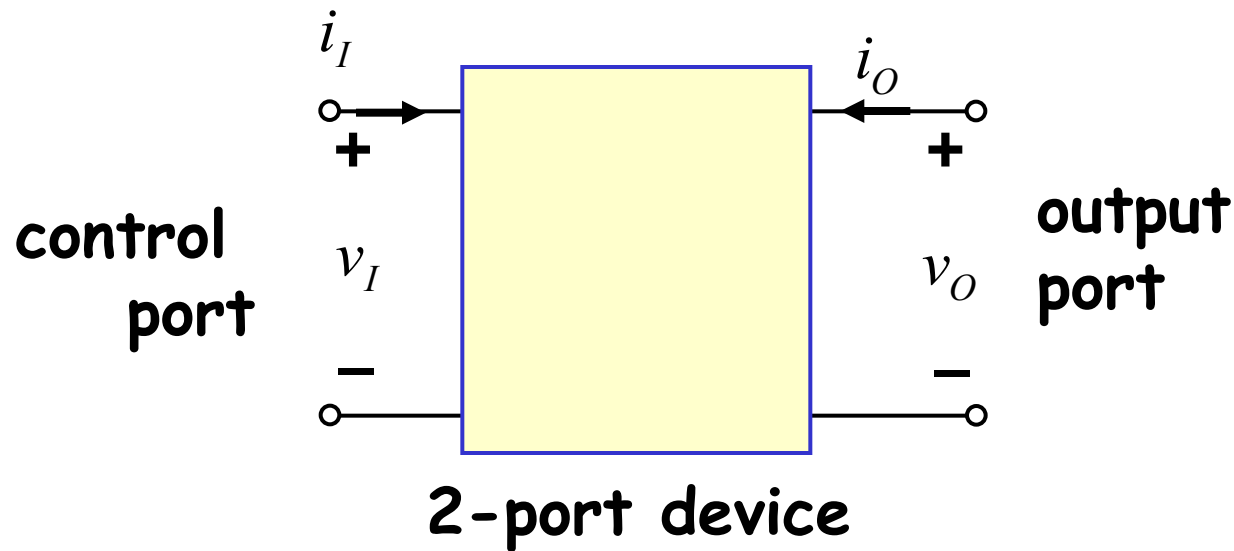- New type of device: **Dependent source**




- e.g., Voltage Controlled Current Source (VCCS)
- Current at output port is a function of voltage at the input port

Dependent Sources: Examples

Example 1: Find V

**independent
current
source**



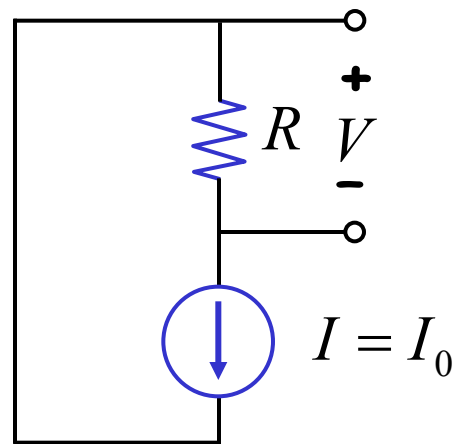


$$V = I_0 R$$

Dependent Sources: Examples

Example 2: Find V


voltage
controlled
current
source

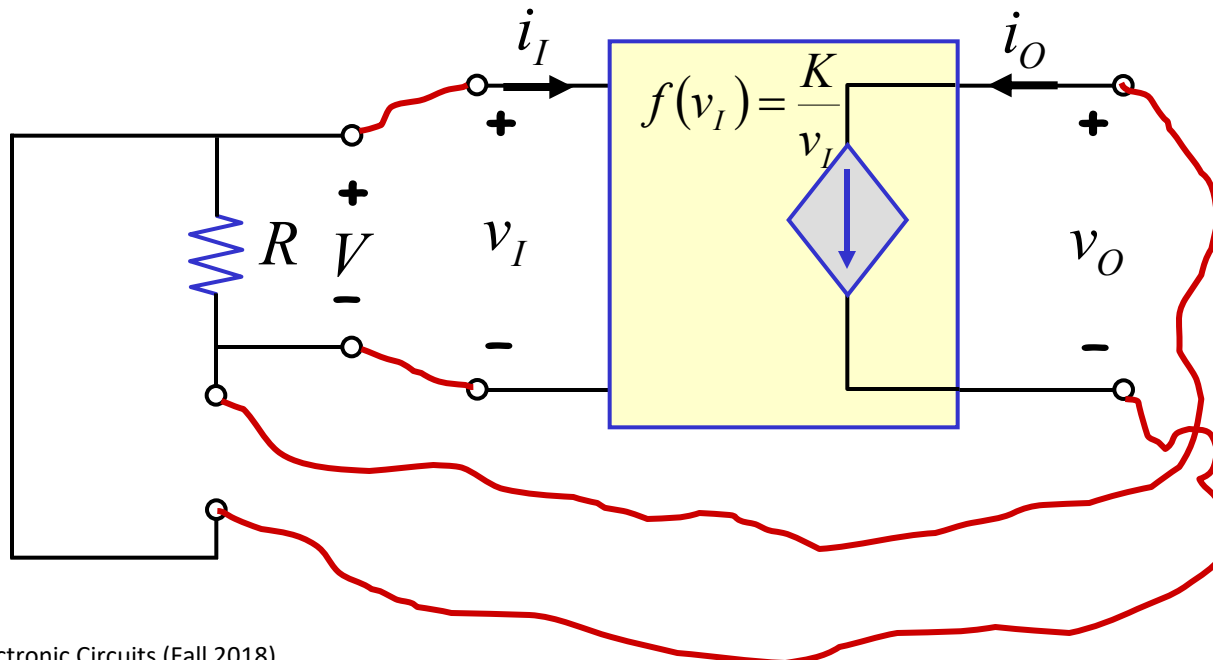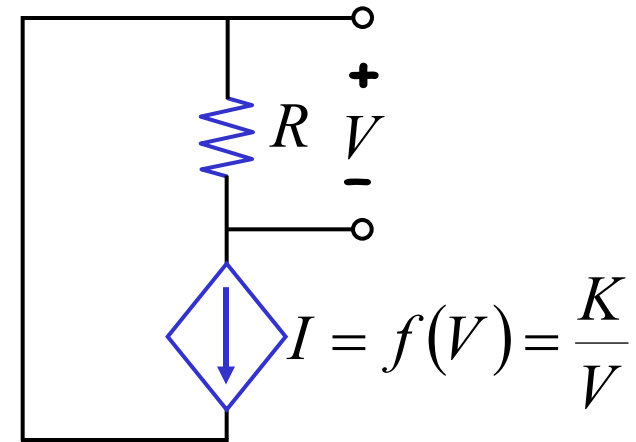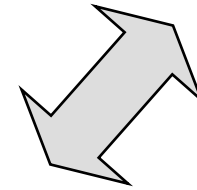

Dependent Sources: Examples

Example 2: Find V

voltage
controlled
current
source

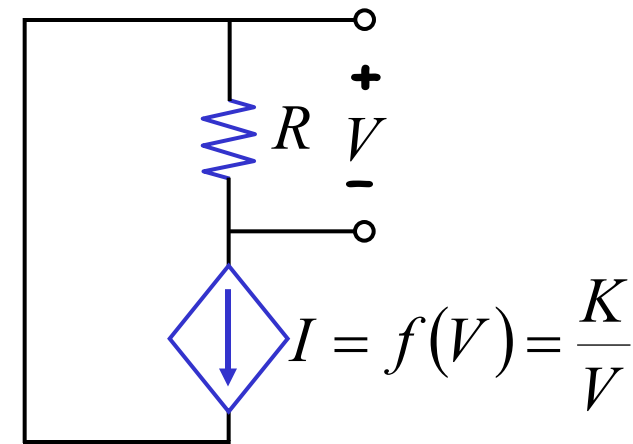

e.g. $K = 10^{-3} \text{ Amp}\cdot\text{Volt}$
 $R = 1\text{k}\Omega$

$$V = IR = \frac{K}{V} R$$

or $V^2 = KR$


or $V = \sqrt{KR}$
 $= \sqrt{10^{-3} \cdot 10^3}$
 $= 1 \text{ Volt}$


Dependent Sources

■ Symbols for (other) dependent sources

- We will heavily use them to model amplifiers (in Chapter 7)!

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

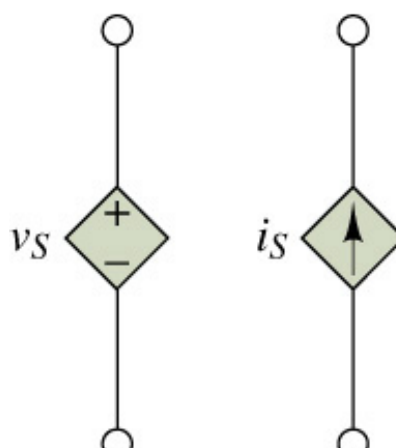
Source type		Relationship
	Voltage controlled voltage source (VCVS)	$v_S = \mu v_x$
	Current controlled voltage source (CCVS)	$v_S = r i_x$
	Voltage controlled current source (VCCS)	$i_S = g v_x$
	Current controlled current source (CCCS)	$i_S = \beta i_x$

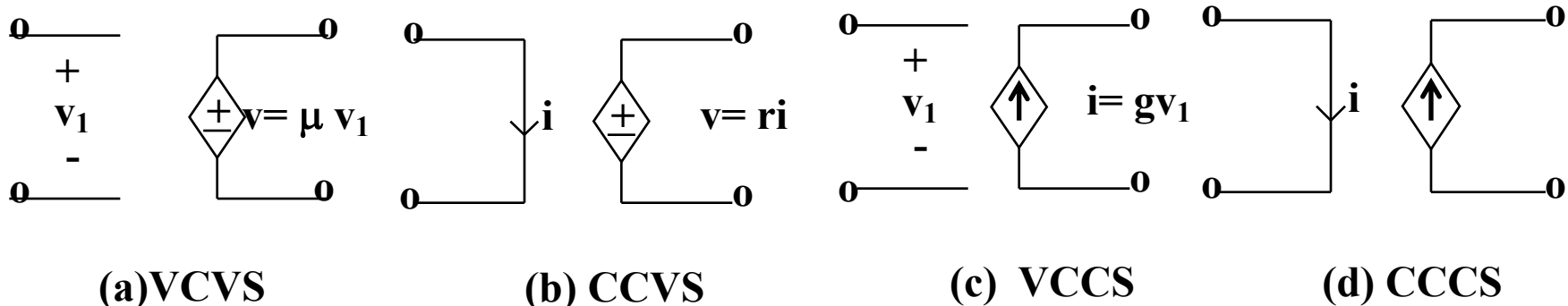

Dependent Sources: Another Example



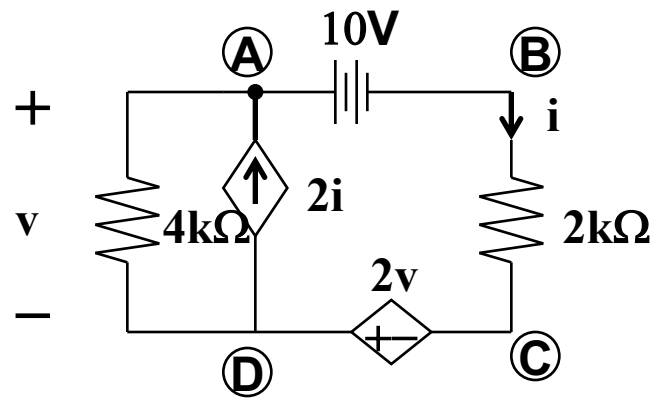Find v . How much power does $4\text{ k}\Omega$ resistor consume?



Now, the voltage source is changed from 10V to 5V.
How much power does $4\text{ k}\Omega$ resistor consume?