

Diodes

Lecture 18

December 11th, 2018

Jae W. Lee (jaewlee@snu.ac.kr)

Computer Science and Engineering

Seoul National University

Slide credits: Prof. Anant Agarwal at MIT


Outline

Textbook: 16.1, 16.2, 16.3, 16.4.1, 16.5.3

- **Diode Characteristics**
- Analysis of Diode Circuits
- Additional Example: Limiter

First, let's look at the diode

V-code: ???

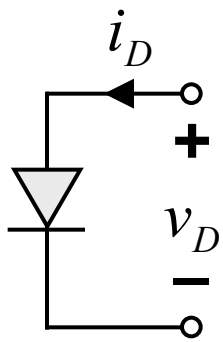



$$i_D = I_S \left(e^{\frac{v_D}{V_T}} - 1 \right)$$

$$I_S = 10^{-12} \text{ A}$$

$$V_T = 0.025 \text{ V}$$

$$V_T = \frac{kT}{q}$$

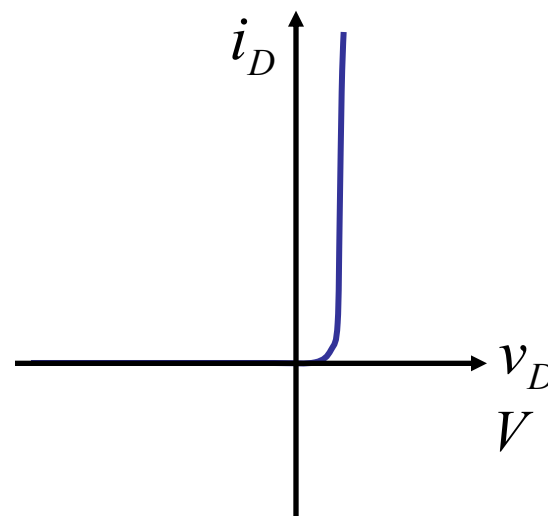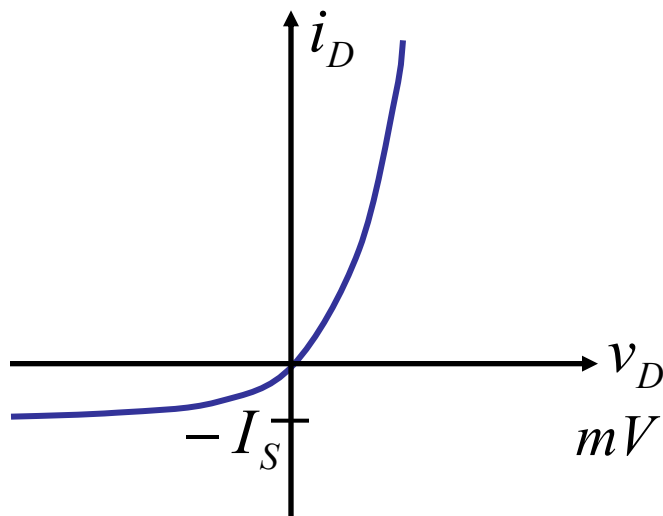Boltzmann's constant
 temperature in Kelvins
 charge of an electron



Can use this exponential model with analysis methods learned earlier:

- Analytical
- Graphical
- Incremental

Outline


Textbook: 16.1, 16.2, 16.3, 16.5.3

- Diode Characteristics
- **Analysis of Diode Circuits**
- Additional Example: Limiter


V-code: ???

Another analysis method: piecewise-linear analysis

P-L diode models:

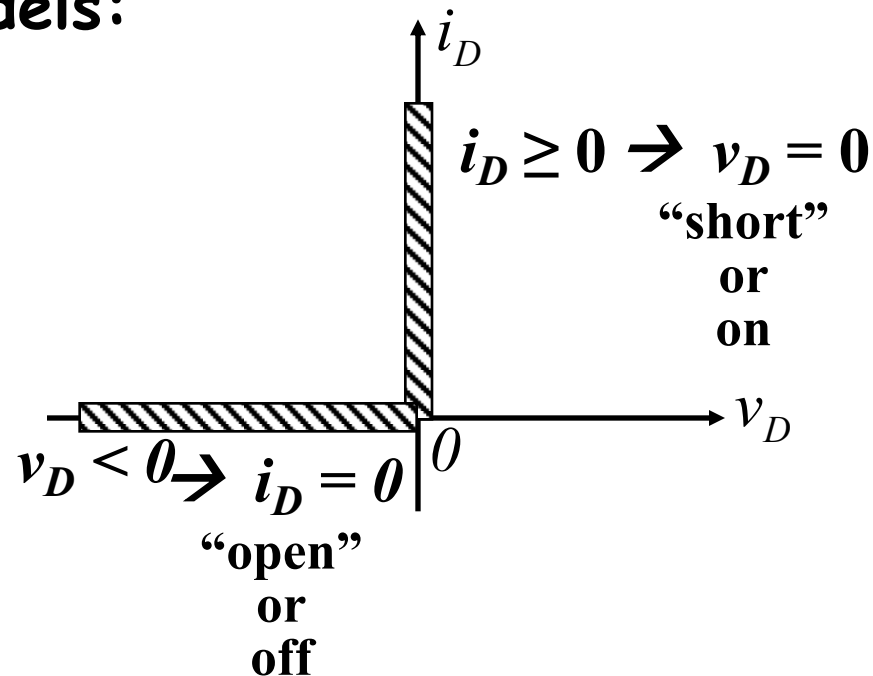



Ideal diode model

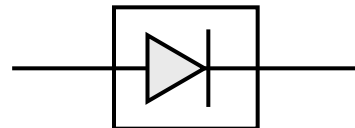

Another analysis method: piecewise-linear analysis

V-code: ???

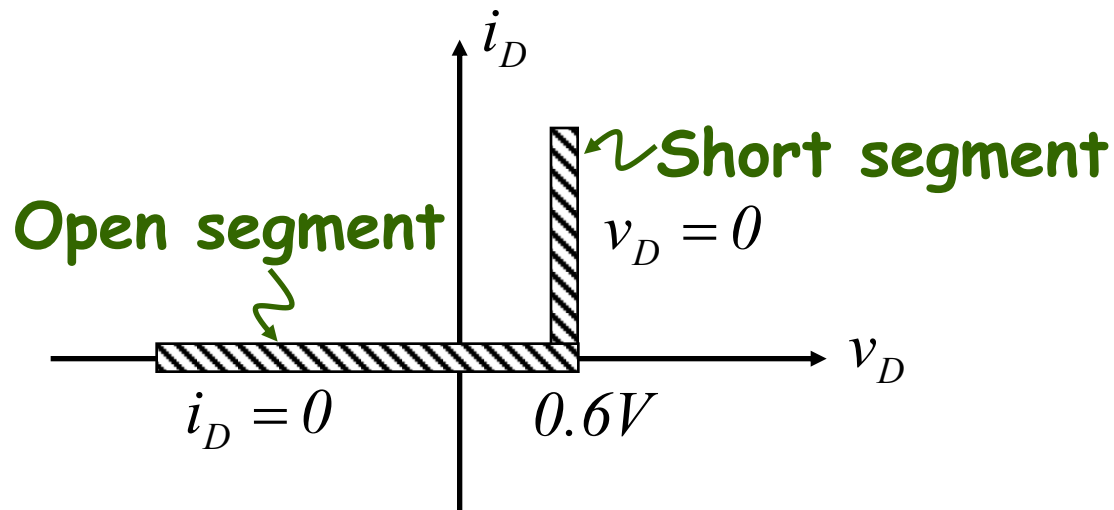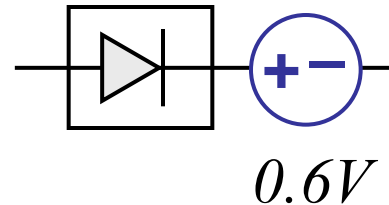“Practical” diode model
ideal with offset



Another analysis method: piecewise-linear analysis



V-code: ???

Piecewise-linear analysis method

- Replace nonlinear characteristic with linear segments.
- Perform linear analysis within each segment.

Power Conversion Circuits (PCC)

V-code: ???

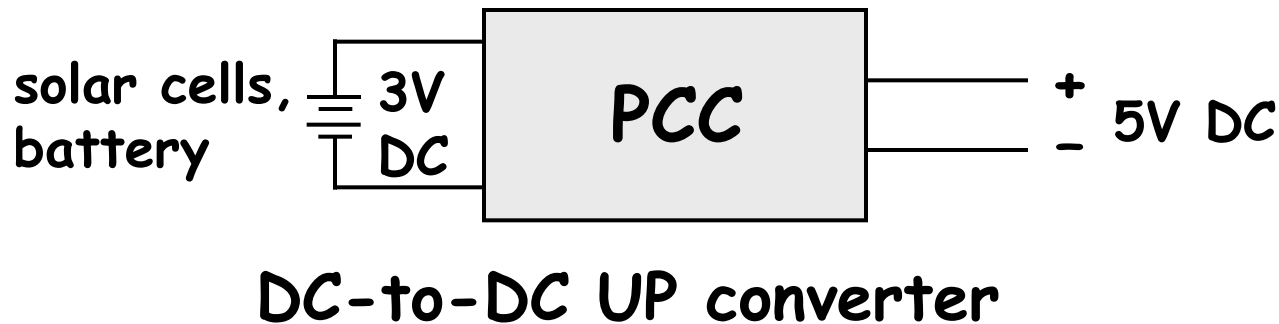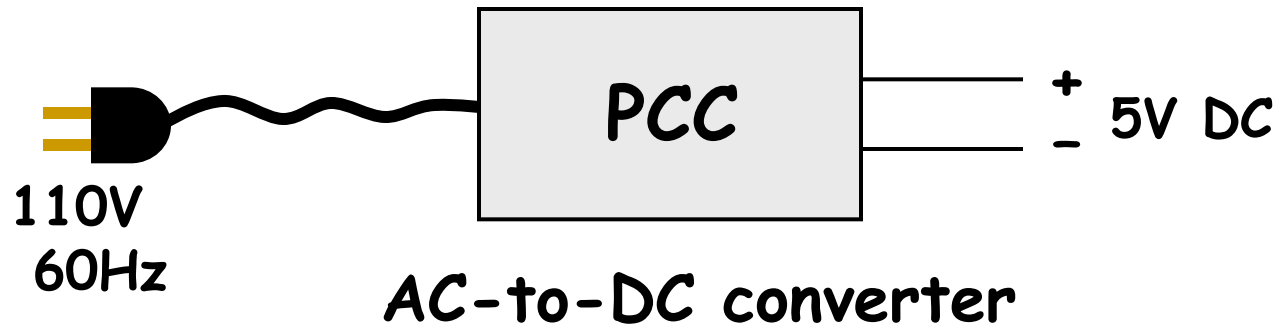

Power efficiency of converter important,
so use lots of devices:


MOSFET switches, clock circuits,
inductors, capacitors, op amps, **diodes**

Example

V-code: ???

(We will build up towards an AC-to-DC converter)


Consider

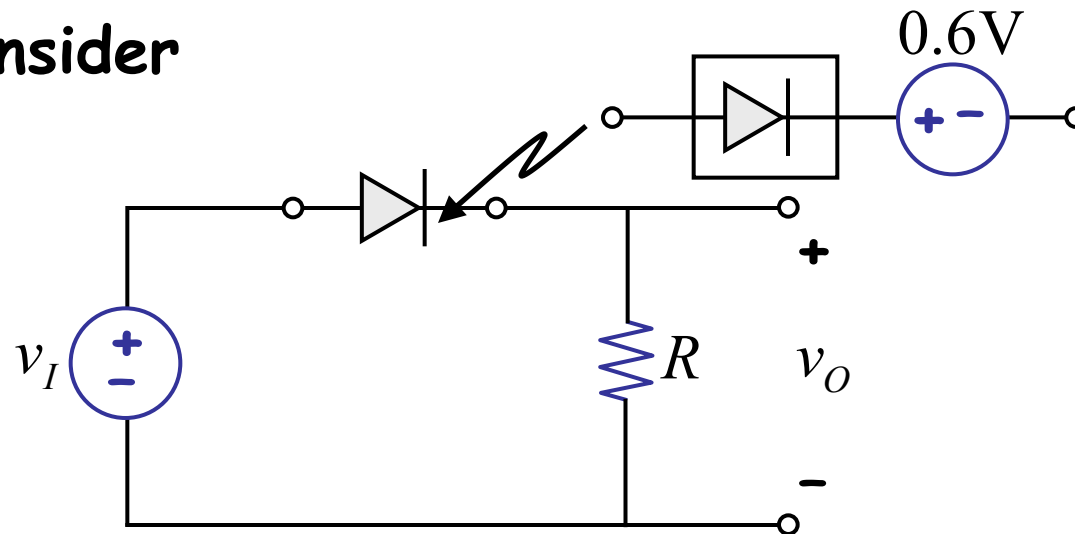

v_I is a sine wave


Example

V-code: ???

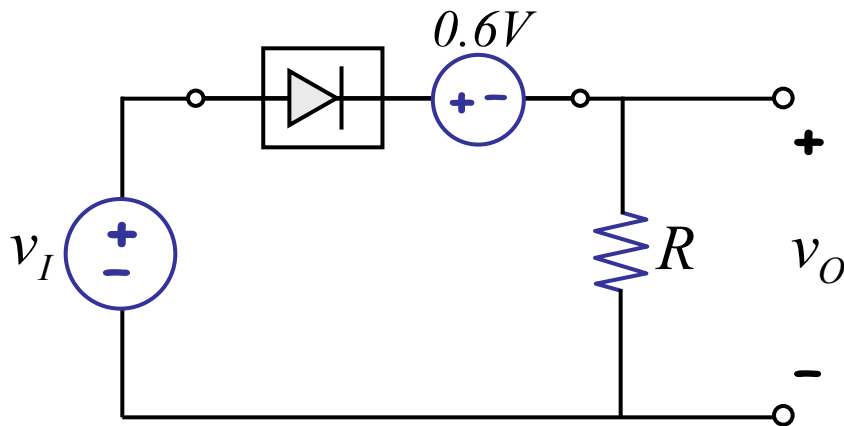


Equivalent circuit

“Short segment”:

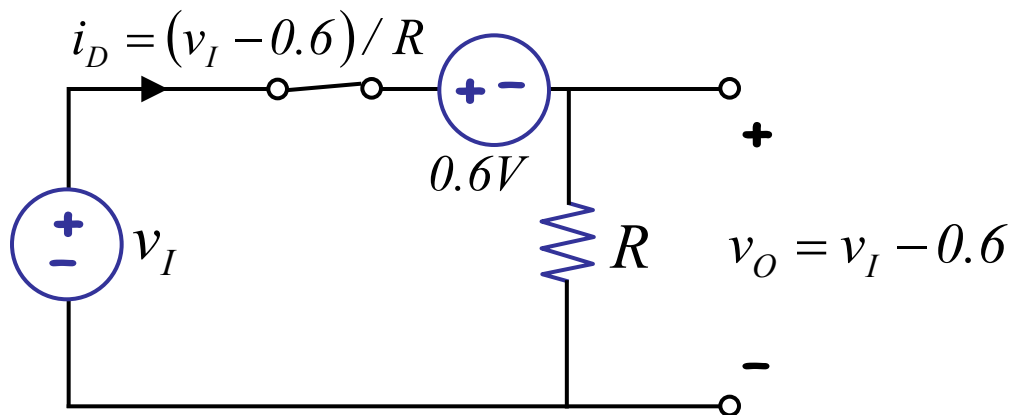

$$v_I \geq 0.6$$


“Open segment”:

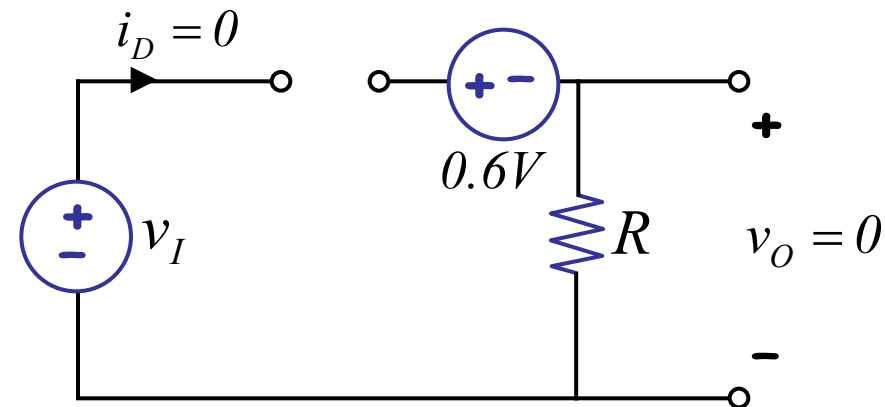

$$v_I < 0.6$$


Example

V-code: ???

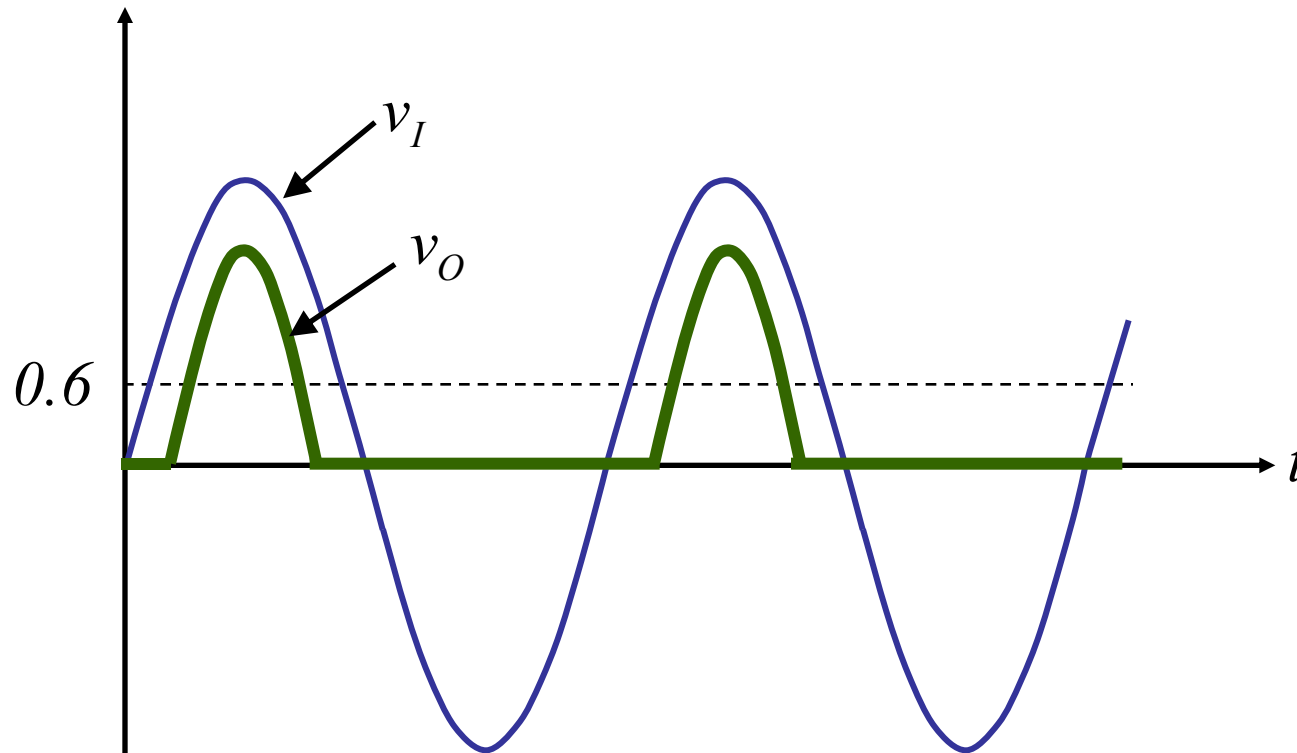


Now consider — a half-wave rectifier

V-code: ???

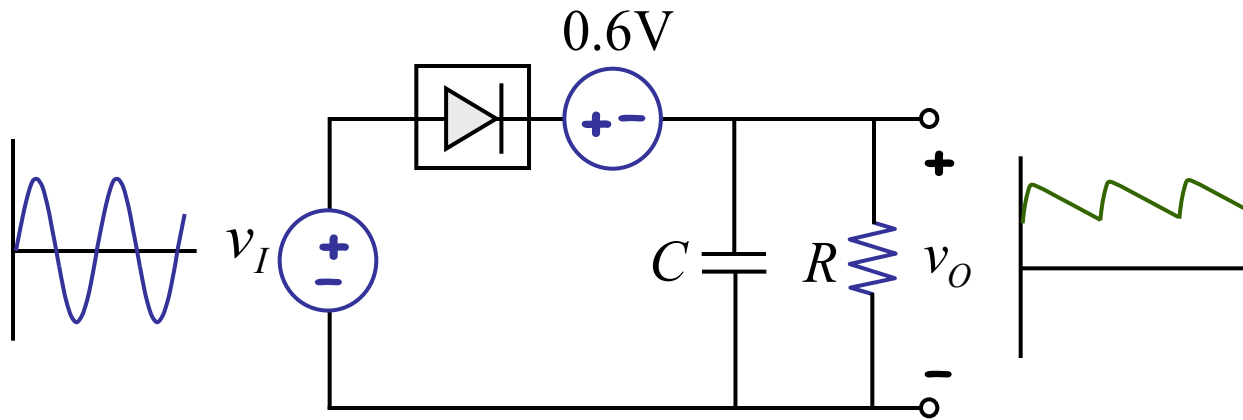

A half-wave rectifier

V-code: ???

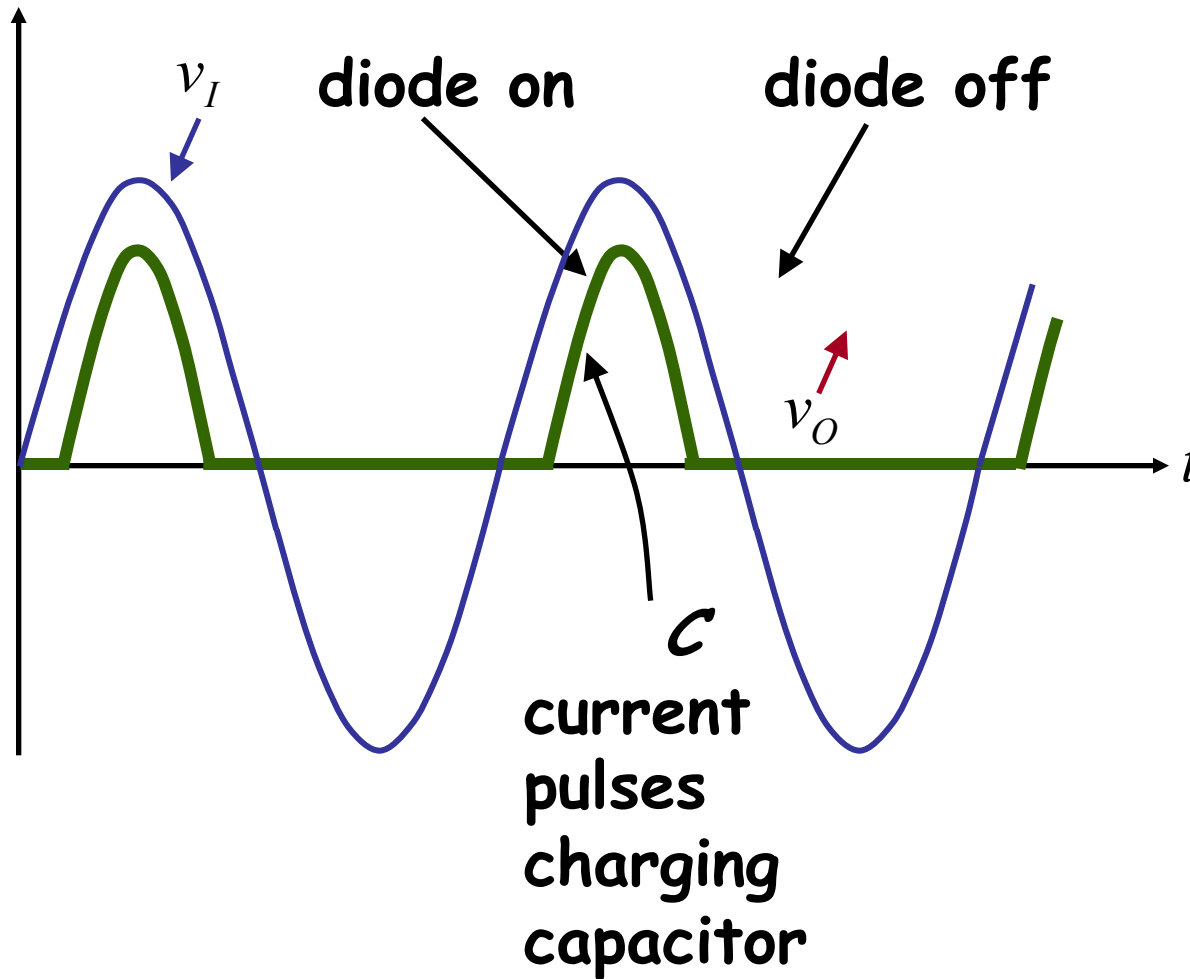


Outline

Textbook: 16.1, 16.2, 16.3, 16.5.3

- Diode Characteristics
- Analysis of Diode Circuits
- **Additional Example: Limiter**

Limter (Clipper) Circuit

V-code: ???

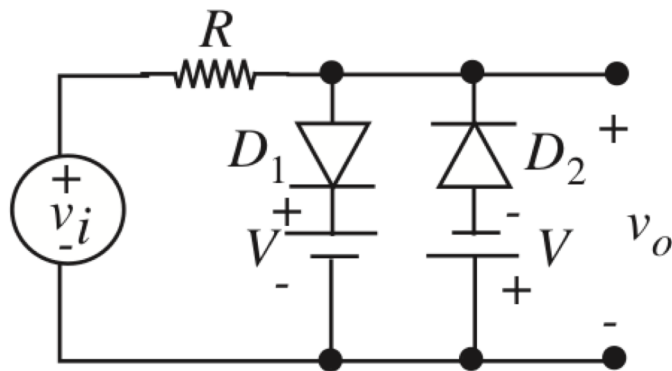

What are possible diode states?


Recall: piecewise-linear analysis

1. Draw a subcircuit for each possible state (ON or OFF) of the diodes. For one diode there are two subcircuits. For n diodes there are 2^n such states, and hence 2^n subcircuits.
2. Analyze each resulting linear circuit to find an expression for the desired output variable. Because in each subcircuit the diode is either a short or an open circuit, the subcircuits are linear. Hence linear analysis methods can be used.
3. Establish the range of validity of each of the expressions in (2); then assemble the appropriate segments to form the complete output waveform.


Limiter (Clipper) Circuit

V-code: ???

Case 1: When both diodes are OFF

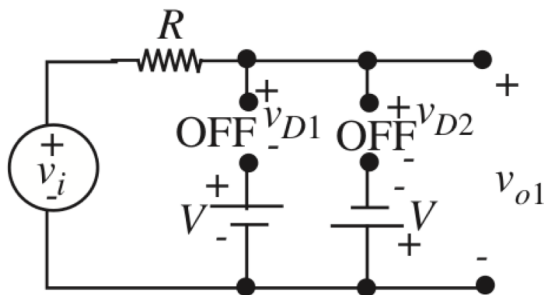

Subcircuit 1

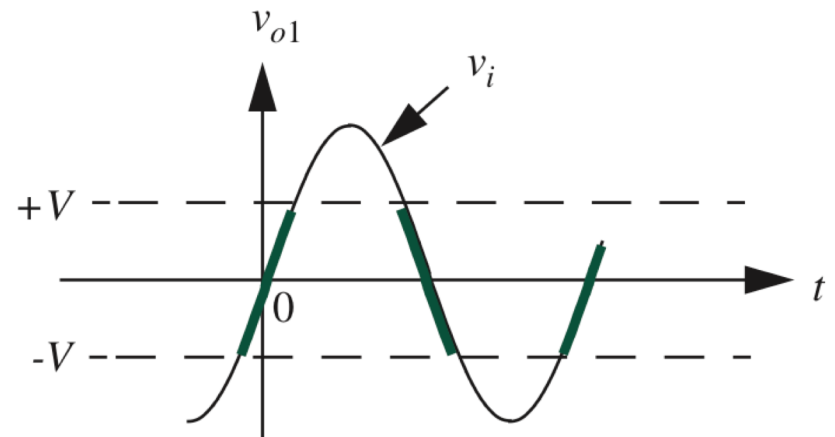


Output (V_{o1})


Limter (Clipper) Circuit

V-code: ???

Case 2: D1 is ON, D2 is OFF

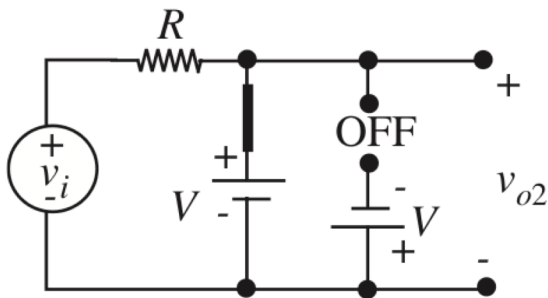

Subcircuit 2

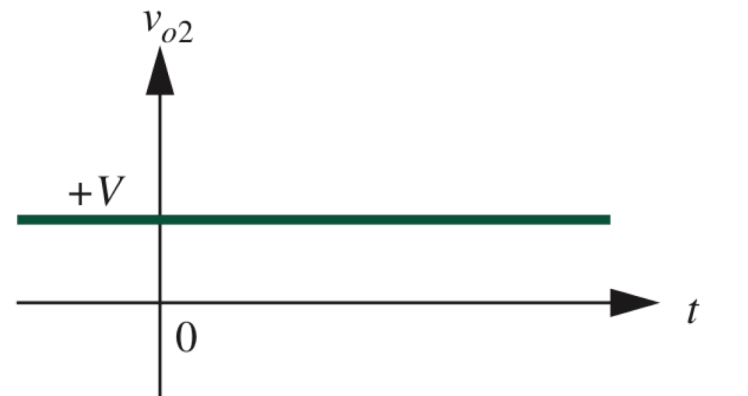


Output (V_{o2})


Limiter (Clipper) Circuit

V-code: ???

Case 3: D1 is OFF, D2 is ON

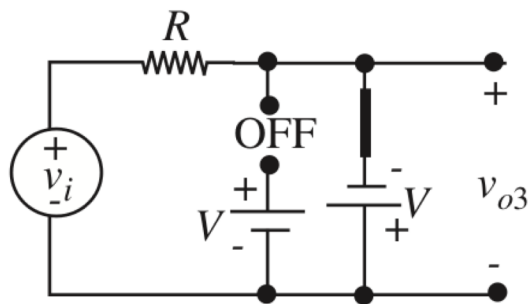

Subcircuit 3

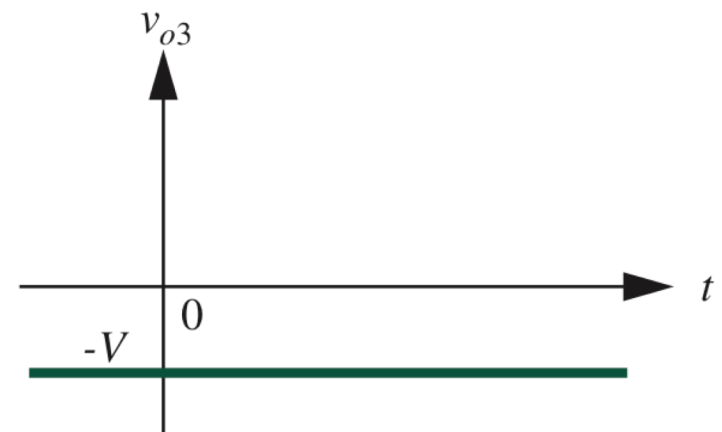


Output (V_{o3})

Limter (Clipper) Circuit

V-code: ???


Case 4: Both D1 and D2 are OFF

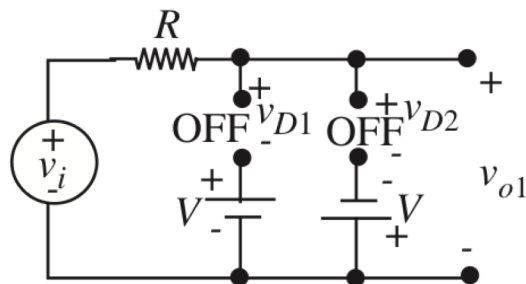

Subcircuit 4

Can this case happen??

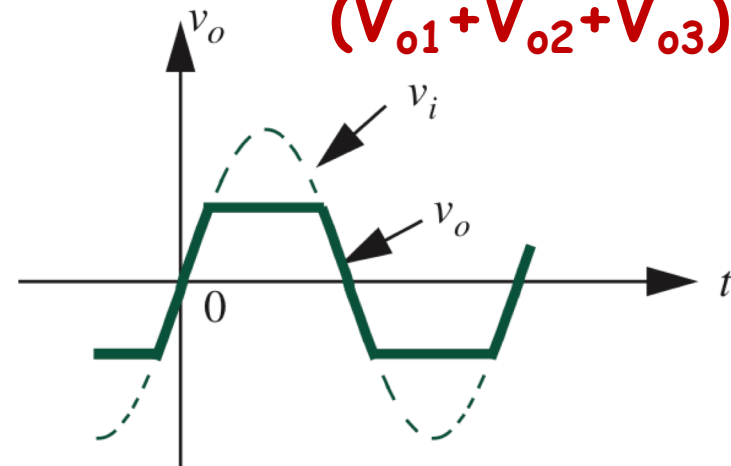Complete waveform!
($V_{o1} + V_{o2} + V_{o3}$)



Thank you!

- It was great to teach you this semester and I wish best of luck for your future endeavors!