

The Digital Abstraction

Lecture 4

September 18th, 2018

Jae W. Lee (jaewlee@snu.ac.kr)


Computer Science and Engineering

Seoul National University

Slide credits: Prof. Anant Agarwal at MIT

Review

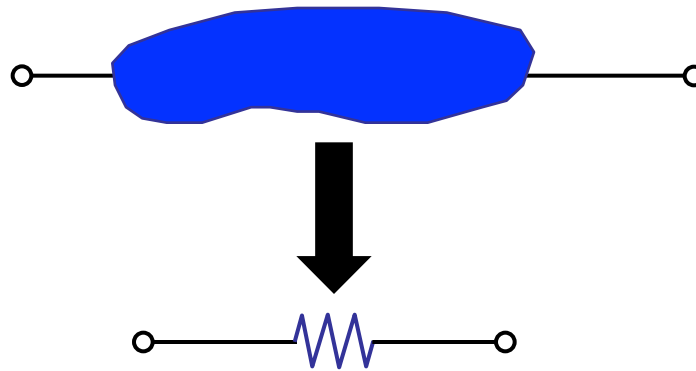- **Discretize matter** by agreeing to observe the lumped matter discipline (LMD)



Lumped Circuit Abstraction

- **Analysis tool kit: KVL/KCL, node method, superposition, Thévenin, Norton**
 - Remember superposition, Thévenin, Norton apply only for linear circuits

Today

- **Discretize value** \longrightarrow Digital abstraction
- Interestingly, we will see shortly that the tools learned in the previous three lectures are sufficient to analyze simple digital circuits

Outline


Textbook: Ch. 5.1-5.3

- **Voltage Levels and Static Discipline**
- Boolean Logic
- Combinational Gates

But first, why digital?

■ In the past ...

Analog signal processing

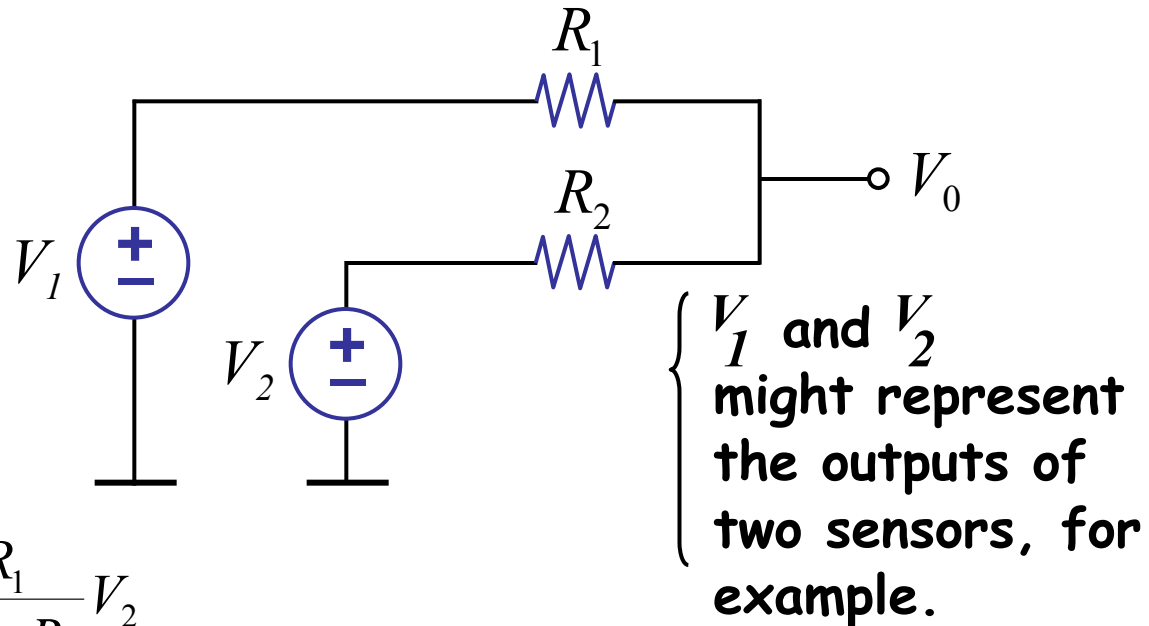

By superposition,


$$V_0 = \frac{R_2}{R_1 + R_2} V_1 + \frac{R_1}{R_1 + R_2} V_2$$

If $R_1 = R_2$,

$$V_0 = \frac{V_1 + V_2}{2}$$

The above is an “adder” circuit.

Noise Problem

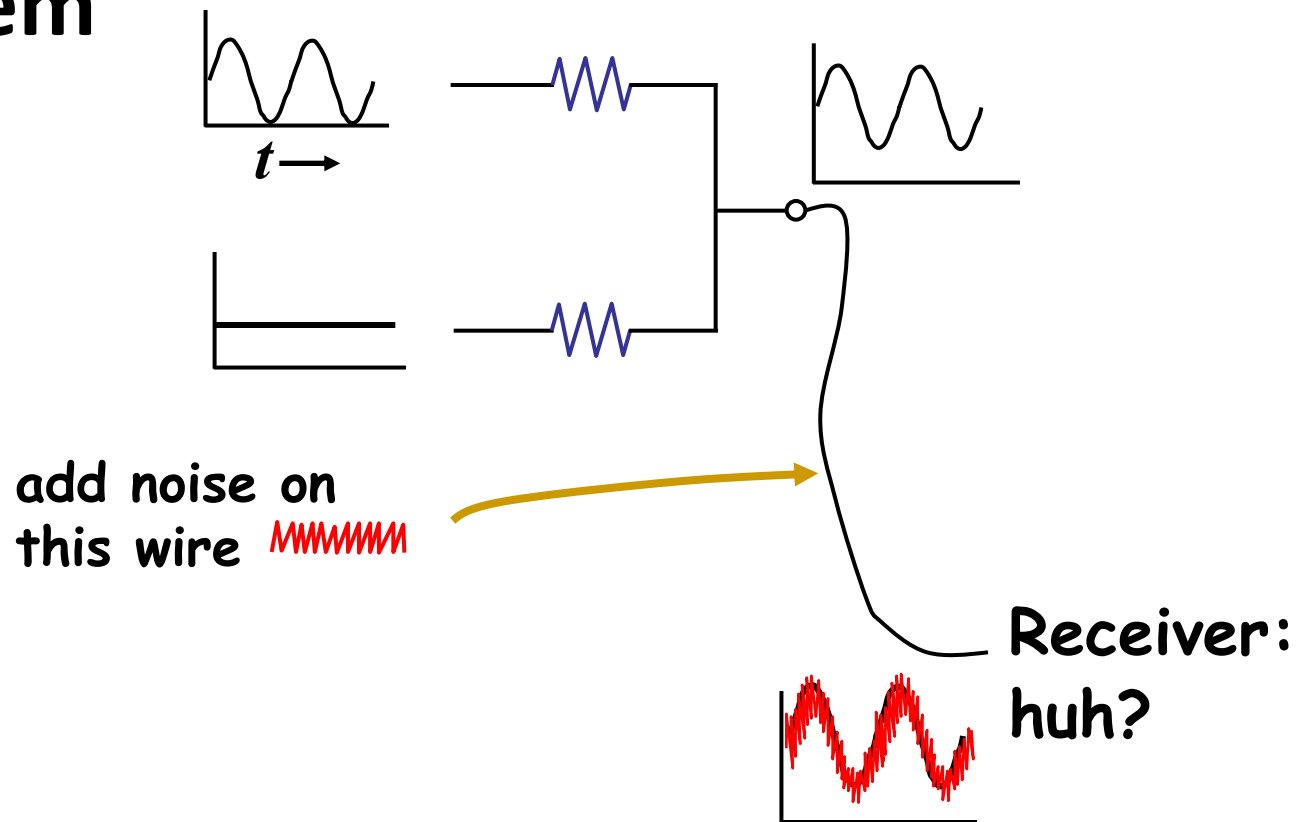

... noise hampers our ability to distinguish between small differences in value — e.g. between 3.1V and 3.2V.

Value Discretization

Restrict values to be one of two

HIGH

LOW

5V

0V

TRUE

FALSE

1


0

...like two digits 0 and 1


Why is this discretization useful?

(Remember, numbers larger than 1 can be represented using multiple binary digits and coding, much like using multiple decimal digits to represent numbers greater than 9. E.g., the binary number 101 has decimal value 5.)

Digital System

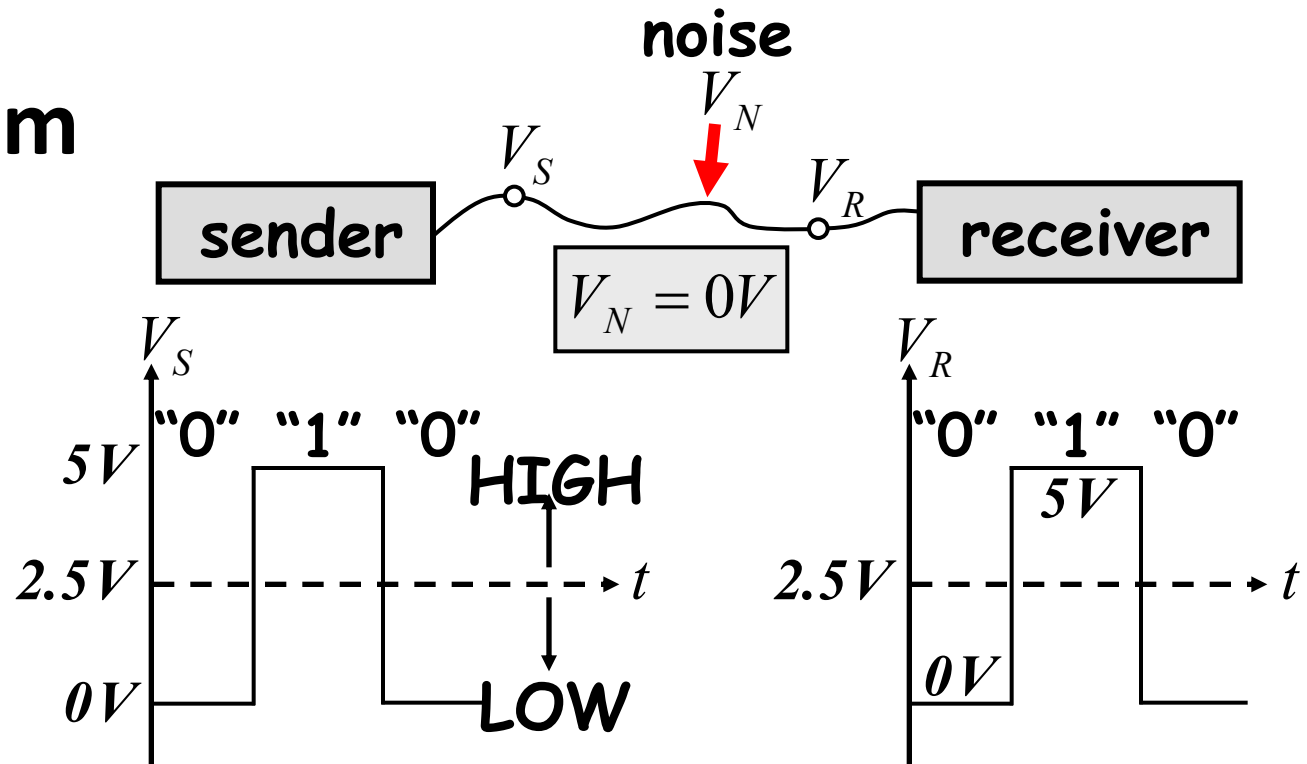

With noise

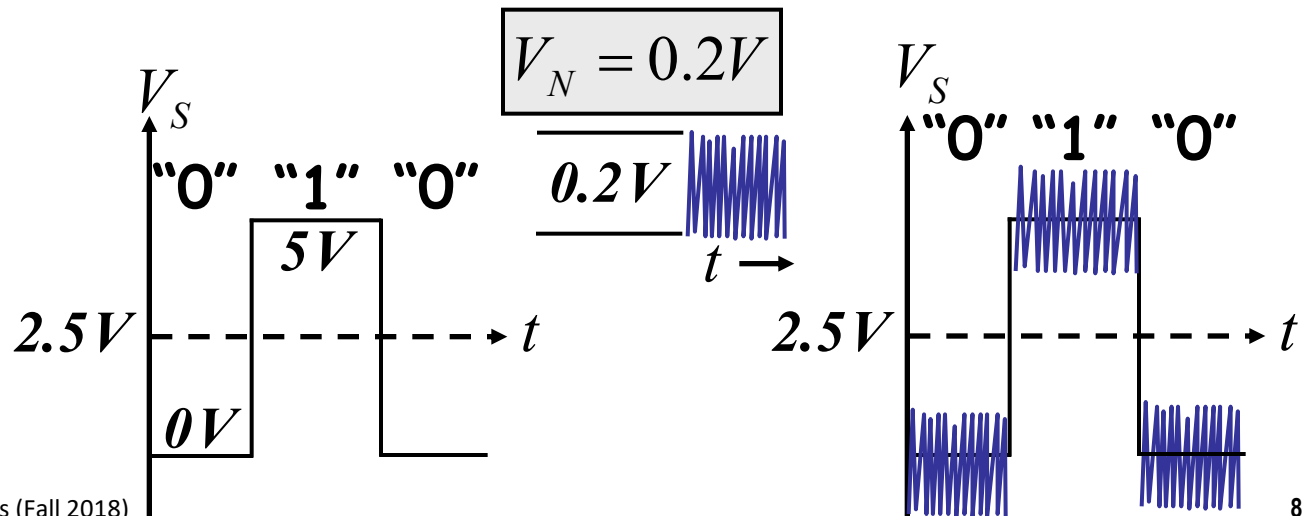


Digital System

Better noise immunity
Lots of "noise margin"

For "1": noise margin $5V$ to $2.5V = 2.5V$

For "0": noise margin $0V$ to $2.5V = 2.5V$


Voltage Thresholds and Logic Values

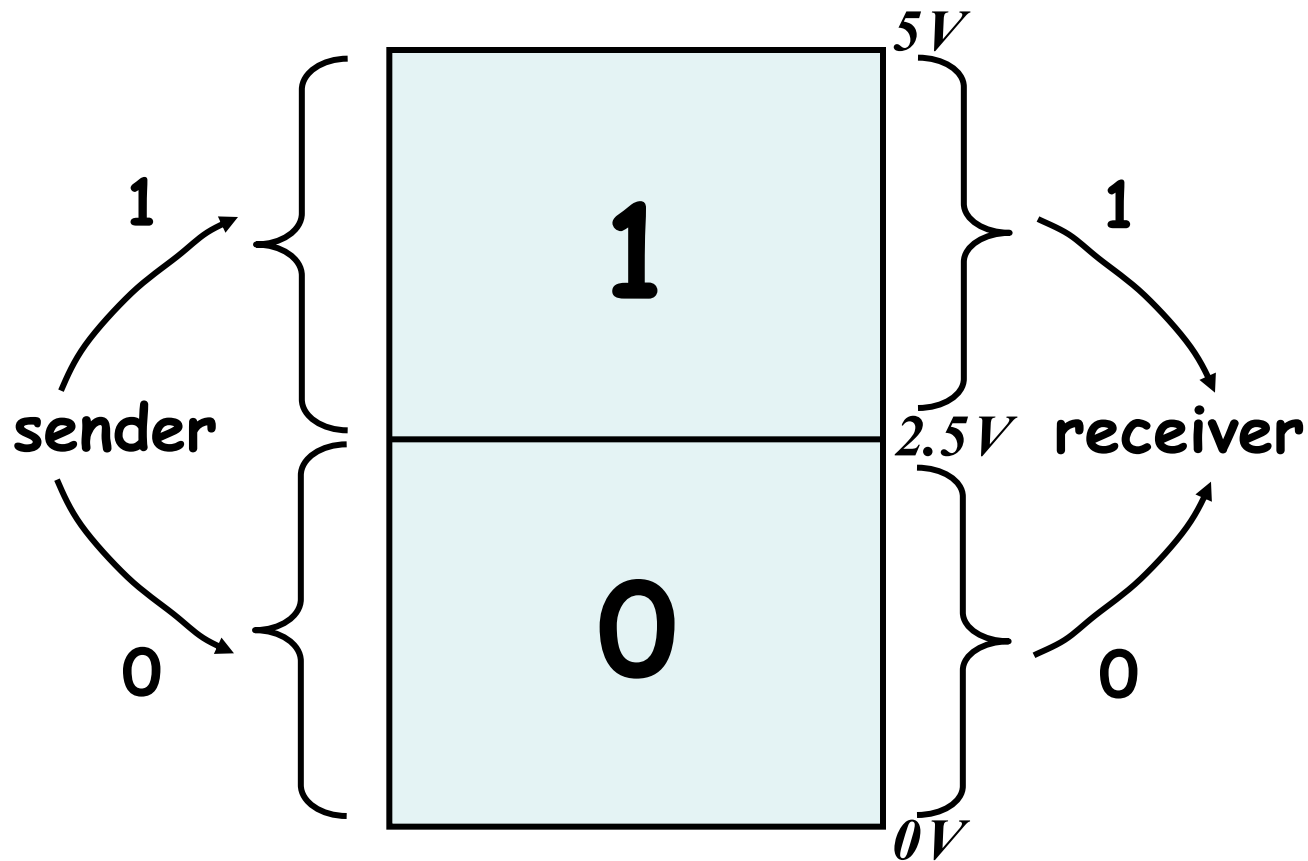

But, but, but ... What about 2.5V?

For example,

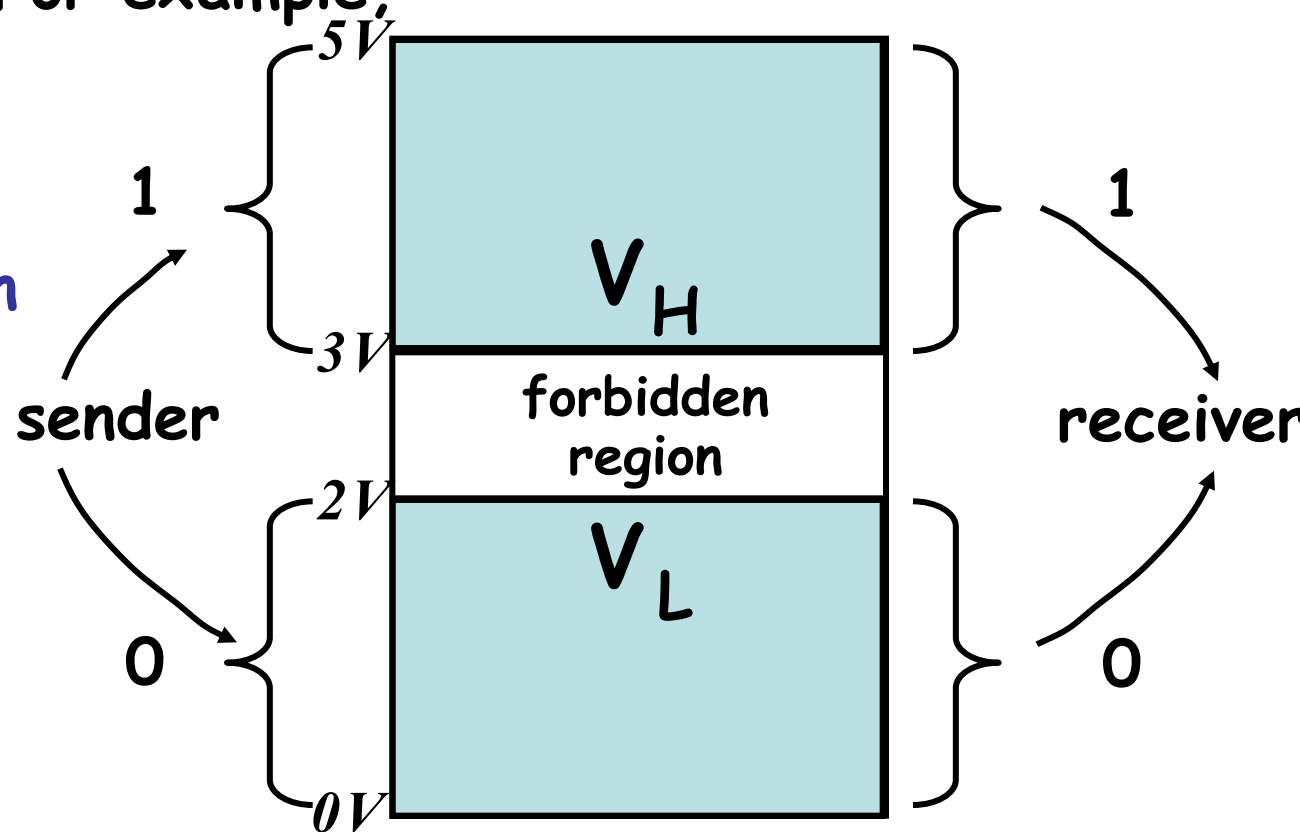Hmmm... create
"no man's land"
or forbidden region




"1" $\rightarrow V_H \rightarrow 5V$

"0" $\rightarrow 0V \rightarrow V_L$

But, but, but ... **Where's the noise margin?**

What if the sender sent 1: V_H ?


Hold the sender to
tougher standards!

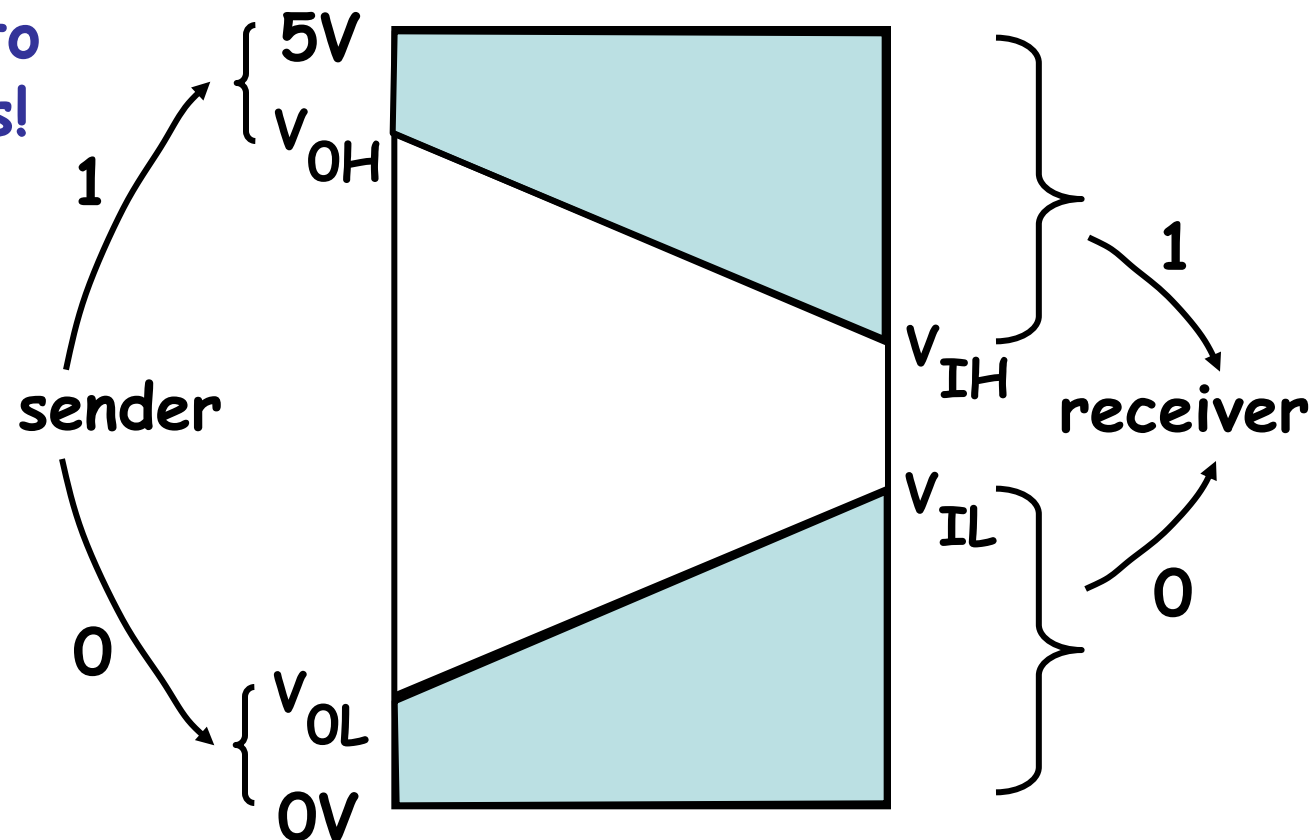



But, but, but ... Where's the noise margin?

What if the sender sent 1: V_H ?

Hold the sender to tougher standards!

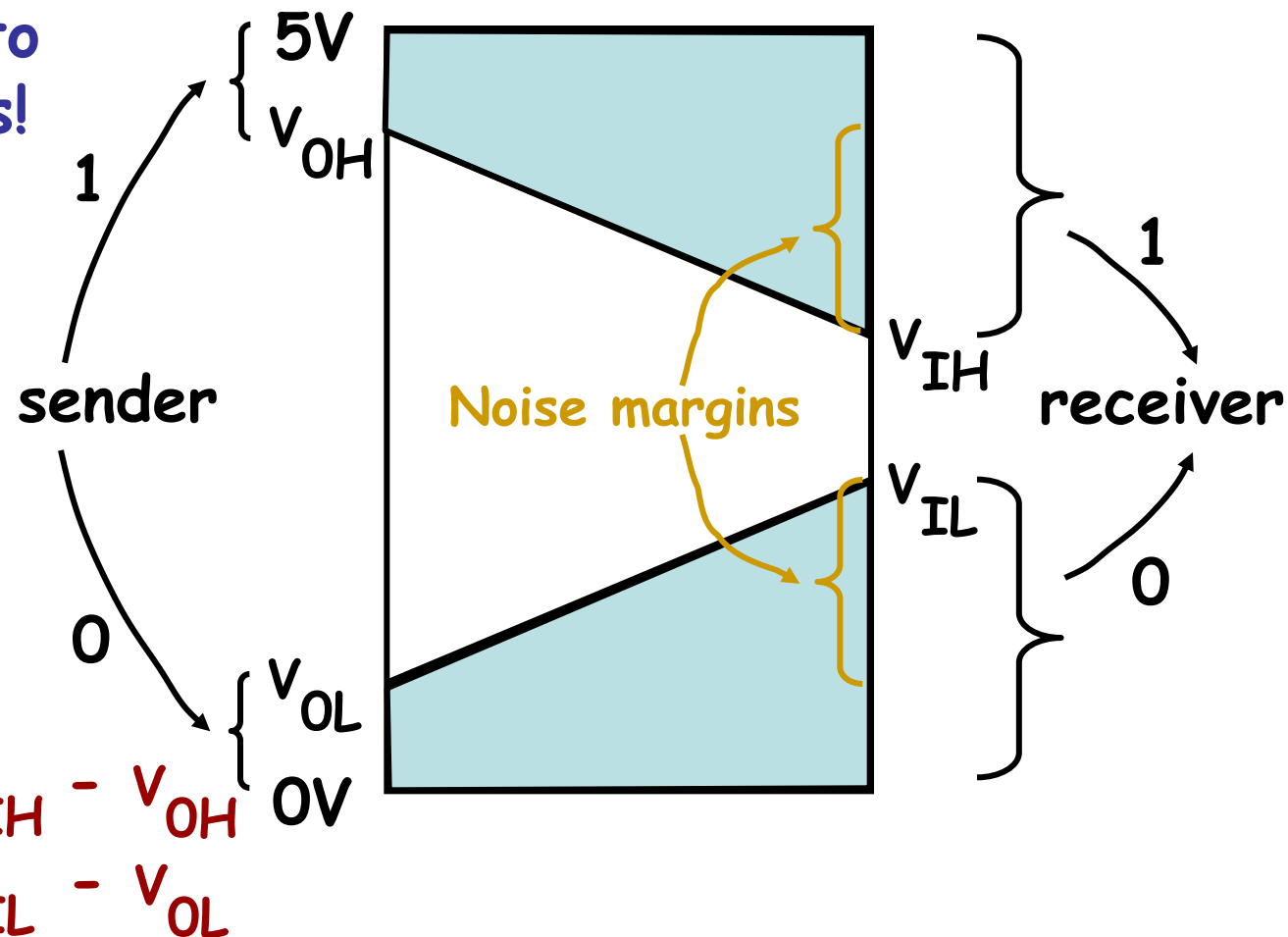

Static Discipline

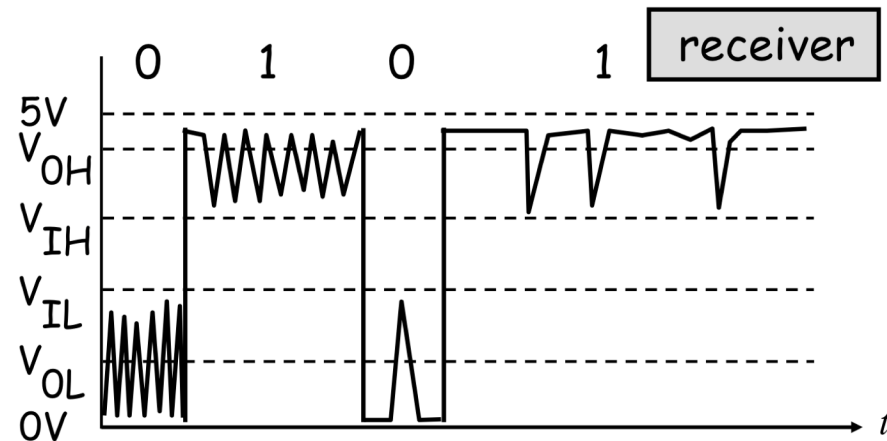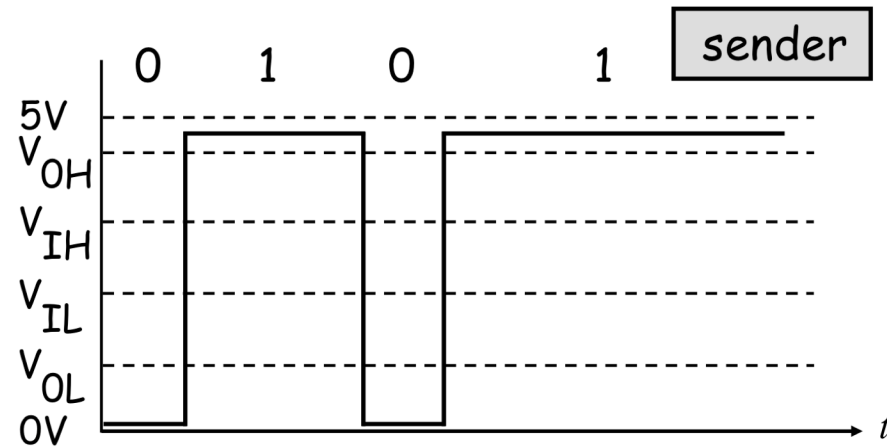

Digital systems follow **static discipline**: if inputs to the digital system meet valid input thresholds, then the system guarantees its outputs will meet valid output thresholds.

Outline

Textbook: Ch. 5.1-5.3

- Voltage Levels and Static Discipline
- **Boolean Logic**
- **Combinational Gates**

Processing digital signals

Recall, we have only two values —

$1, 0 \Rightarrow$ Map naturally to logic: T, F
 \Rightarrow Can also represent numbers


Processing digital signals

■ Boolean Logic

⇒ If X is true and Y is true
Then Z is true else Z is false.

⇒ $Z = X \text{ AND } Y$
 $Z = X \cdot Y$
 Boolean equation

X, Y, Z
are digital signals
"0", "1"

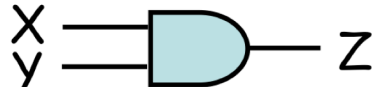⇒  AND gate

⇒ Truth table representation:


X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

Enumerate all input combinations

Combinational gate abstraction


- Adheres to static discipline
- Outputs are a function of inputs alone.

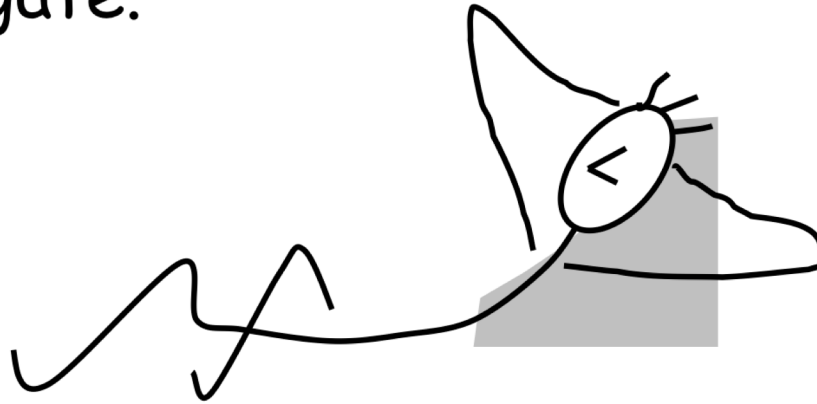Digital logic designers do not have to care about what is inside a gate.



Combinational gate abstraction

- Example:
 $Z = X \bullet Y$ (AND gate)

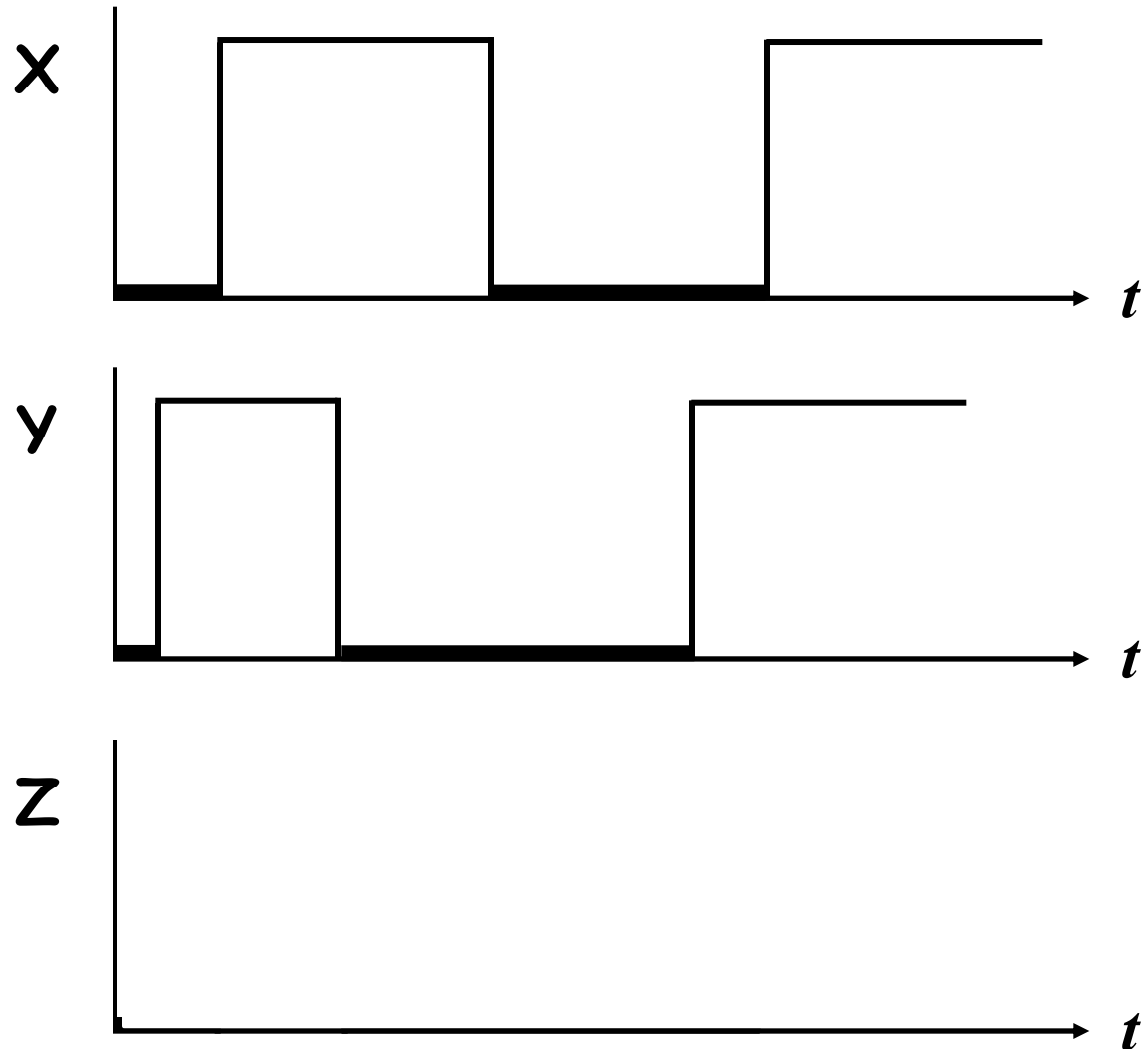


Combinational gate abstraction



■ Another example of gate: OR gate

If (A is true) OR (B is true)
then C is true
else C is false

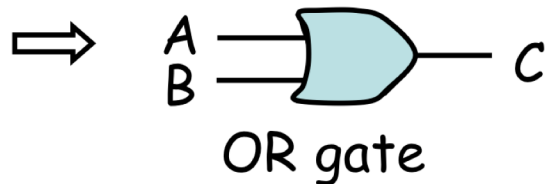$\Rightarrow C = A + B$ Boolean equation
 OR



More gates

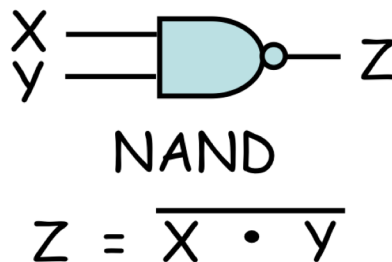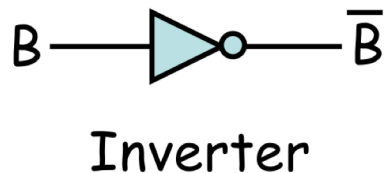

Combinational gate abstraction

■ Boolean identities

$$X \cdot 1 = X$$

$$X \cdot 0 = 0$$

$$X + 1 = 1$$

$$X + 0 = X$$

$$\overline{1} = 0$$

$$\overline{0} = 1$$

$$AB + AC = A \cdot (B + C)$$

■ Digital circuits: $Z = A + \overline{B \cdot C}$

