

4190.309A: Electrical and Electronic Circuits

Exam #2

November 15th, 2018

Professor Jae W. Lee

Student ID #: _____

Name: _____

This is a closed book, closed notes exam.

80 Minutes

16 Pages

Total Score: 200 points

Notes:

- Please turn off all of your electronic devices (phones, tablets, notebooks, netbooks, and so on). A clock is available on the lecture screen.
- Please stay in the classroom until the end of the examination.
- You must not discuss the exam's contents with other students during the exam.
- You must not use any notes on papers, electronic devices, desks, or part of your body.


(This page is intentionally left blank. Feel free to use as you like.)

Part A: Logic Gates (20 points)


Question 1 (20 points)

Draw a schematic of **CMOS logic** for each given Boolean function.


(1) $Z = \overline{A}$

 


(2) $Z = \overline{A + B}$

 

$$(3) Z = \overline{AB}$$

 

 
$$(4) Z = \overline{A + B + \overline{A} \overline{C}}$$



Part B: The MOSFET Amplifier (28 points)

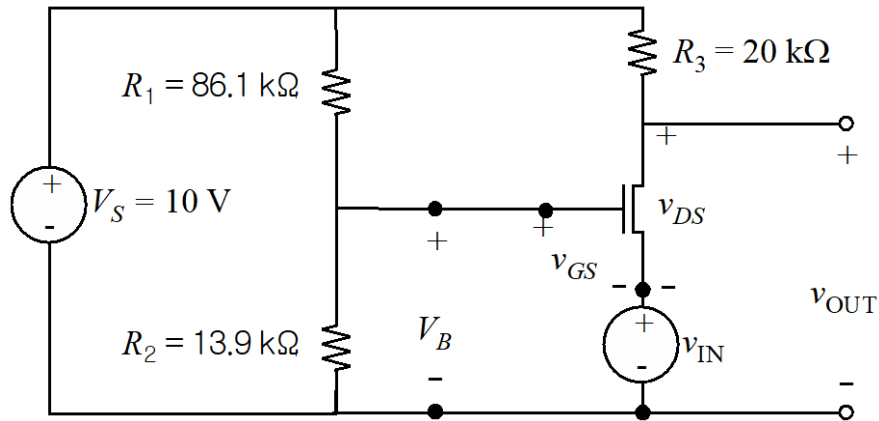Question 2 (28 points)

The circuit shown below is a MOSFET amplifier. Assume that the MOSFET is in the saturation region with $V_T = 1\text{ V}$ and $K = 0.1\text{ mA/V}^2$. (1) Determine the large-signal output (v_{OUT}) as a function of the input voltage (v_{IN}). (2) Determine the valid range of v_{IN} and v_{OUT} over which the MOSFET operation remains in the saturation region.



$$\begin{aligned}
 (1) \quad v_{\text{out}} &= V_S - \frac{R_3 K}{2} (V_B - v_{\text{IN}} - V_T)^2 \\
 &= 10 - (0.39 - v_{\text{IN}})^2 \quad (\because V_B = \frac{13.9}{100} \times 10 = 1.39 \text{ V})
 \end{aligned}$$

(2) To operate on saturation region,

$$\underbrace{v_{\text{out}} - v_{\text{IN}} \geq V_B - v_{\text{IN}} - V_T \geq 0}_{\text{②}} \quad \underbrace{\quad \quad \quad}_{\text{①}}$$

$$\begin{aligned}
 \text{①} \quad V_B - V_T &\geq v_{\text{IN}} \\
 0.39 &\geq v_{\text{IN}}
 \end{aligned}$$

$$\text{②} \quad 10 - (0.39 - v_{\text{IN}})^2 \geq 0.39$$


$$\begin{aligned}
 9.61 &\geq (0.39 - v_{\text{IN}})^2 \\
 -2.71 &\leq v_{\text{IN}} \leq 0.39
 \end{aligned}$$

$$0.39 \leq v_{\text{out}} \leq 10 \text{ V} \quad v_{\text{IN}} \geq -2.71$$

Part C: Small-Signal Models (60 points)

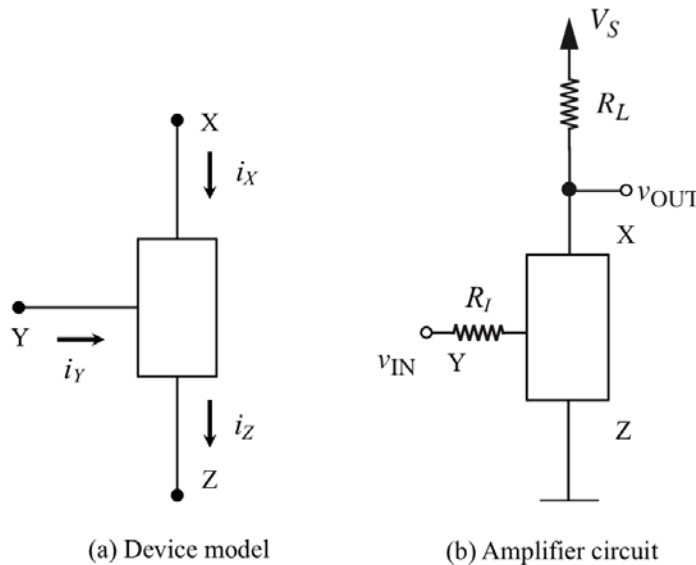Question 3 (28 points)

We have an unknown 3-terminal device (shown as an empty box) whose large-signal current relationship between X, Y, and Z terminals is given as: $i_X = Ki_Y$ and $i_Z = i_X + i_Y$. (Note the reference directions of i_X , i_Y , and i_Z .)



"K is constant"

- (1) Calculate the incremental change in small signal i_x as a function of an incremental change in small signal i_y .


from $i_x = ki_y$, the relationship between the two incremental signal as follows:

$$i_x = \frac{di_x}{di_y} \bigg|_{i_y = I_Y} \cdot i_y$$

$$= \frac{dki_y}{di_y} \bigg|_{i_y = I_Y} \cdot i_y$$

$$= ki_y$$

 - (2) Draw a small-signal circuit diagram of the given amplifier circuit in (b). Also, calculate the small-signal gain ($\frac{v_o}{v_i}$) of this amplifier.



$$v_o = -k i_g R_L$$


$$= -k \frac{v_{in}}{R_I} R_L$$

$$\therefore \frac{v_o}{v_{in}} = -k \frac{R_L}{R_I}$$

(small-signal gain)

 Question 4 (32 points)

Answer the questions about the circuit given below.



- (1) Derive the *small-signal* resistance of M1 from its small signal model.

$$v_{DS} = v_{GS}$$

$$g_{m1} v_{DS} = i_{DS} \quad \therefore \frac{v_{DS}}{i_{DS}} = \frac{1}{g_{m1}} = r_{DS}$$

- (2) Assume that both MOSFETS are operating in the saturation region, determine the small signal gain ($\frac{v_O}{v_I}$) of the given amplifier.

The small-signal equivalent circuit is shown. The input signal v_I is applied to the gate of M2. The source of M2 is connected to ground. The drain of M2 is connected to the source of M1. The gate of M1 is connected to V_{DD} . The drain of M1 is connected to the output v_O . The small-signal model for M1 is represented by a dependent current source $g_{m1}v_{gs}$ in parallel with a resistor $\frac{1}{g_{m1}}$. The small-signal model for M2 is represented by a dependent current source $g_{m2}v_{gs}$ in parallel with a resistor $\frac{1}{g_{m2}}$. The output voltage v_O is taken across the resistor $\frac{1}{g_{m1}}$.


$$v_O = -g_{m2}v_{GS} \times \frac{1}{g_{m1}}$$

$$= -\frac{g_{m2}}{g_{m1}}v_{GS}$$

$$v_O = -\frac{g_{m2}}{g_{m1}}v_I$$

$$\therefore \frac{v_O}{v_I} = -\frac{g_{m2}}{g_{m1}}$$

 - (3) Assuming that two MOSFET transistor are identical, draw the v_O versus v_{IN} curve for the amplifier. Also, draw the output waveform when v_I is a sinusoidal wave with a peak-to-peak voltage of 0.6 V and an DC offset (V_I) of 2 V.



$$V_{T1} = 1$$

We provide an example drawing in the left. Be sure to indicate clearly (1) DC bias point (V_I , V_O), (2) range of swing for both v_I and v_O , and (3) both endpoints of the saturation region in your drawing.

M_2 should operate in saturation

$$V_{T2} \leq V_I \leq V_O + V_{T2}$$


$$I_{D1} = I_{D2}$$

$$\frac{1}{2} k_1 (V_{DD} - V_O - V_{T1})^2 = \frac{1}{2} k_2 (V_I - V_{T2})^2$$

$$K_1 = K_2$$

$$V_{DD} - V_O \approx V_{T1}$$

$$V_O = V_{DD} - V_{T1}$$

 

To determine V_I of triode region

$$V_I = V_O + 1$$


$$V_I = \frac{V_{DD} + 1}{2} = V_{DD} - V_I + 1$$

$$2V_I = V_{DD} + 1$$

Part D: First-order Transients (60 points)


Question 5 (32 points)

 - (1) Write the expression for $i(t)$ ($t > 0$) for the circuit. Assume a zero initial state. Don't forget the unit of the current.




$$i(t) = (1 - e^{-t/\tau}) \text{ mA} \quad \tau = \frac{L}{R} = 10^{-6}$$

 - (2) Write the expression for $v(t)$ ($t > 0$) for the circuit. Assume a zero initial state. Don't forget the unit of the voltage.




$$v(t) = t \text{ kV}$$

 (3) Write the expression for $v_O(t)$ ($t > 0$) for the circuit. Assume a zero initial state.




$$\therefore -\frac{1}{2}(1 - e^{-t/\tau})V$$

$$\tau = 10^{-3}$$

 

 
$$\Rightarrow \frac{1}{2}V \text{ (source)} \Rightarrow \frac{1}{2}(1 - e^{-t/\tau}) \quad \tau = 10^{-3}$$



$$\Rightarrow 1V \text{ (source)} \Rightarrow -(1 - e^{-t/\tau}) \quad \tau = 10^{-3}$$

 (4) Write the expression for $i_O(t)$ ($t > 0$) for the circuit. Assume the switch has been open for a long time before closing at $t = 0$.



$$i_L(0^-) = \frac{8}{50}$$


$$i_O = \frac{9}{40} - \left(\frac{8}{50} e^{-t/\tau} \right) = \frac{9}{40} - \frac{4}{25} e^{-t/\tau}$$

12V에 대한 전류

$$\tau = \frac{1}{200}$$

Question 6 (28 points)

Figure (a) below illustrates an inverter $INV A$ driving n other inverters $INV 1$ through $INV n$. As in Figure (b), each of the inverters is constructed using a MOSFET and a resistor R_L (we only show $INV 1$ in the second stage for brevity), and the inverters satisfy the static discipline.

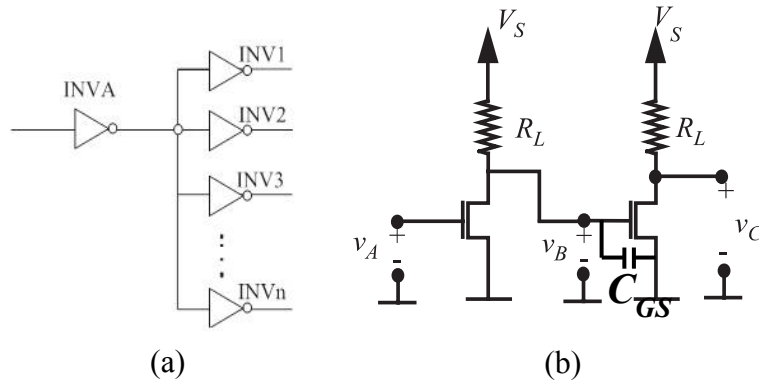

(1) What is the rising delay (t_r) of $INV A$ (i.e., the time for v_B to switch from 0 to V_{OH})?


$$v_B = V_S - V_S e^{-t/\tau} \quad \tau = R_L \cdot n C_{GS}$$

$$\Rightarrow V_{OH} = V_S - V_S e^{-t/\tau}$$


$$e^{-t/\tau} = \frac{V_S - V_{OH}}{V_S}$$

$$-t/\tau = \ln \frac{V_S - V_{OH}}{V_S} \quad \therefore t = -\tau \ln \frac{V_S - V_{OH}}{V_S}$$

 - (2) Assume that each of the wires connecting the output of $INV A$ to each of the inverters $INV 1$ through $INV n$ is non-ideal as depicted in Figure (c). We model each of the wires as shown in Figure (d). Assuming that the input of $INV A$ makes a step transition from 1 to 0, find the rising delay at the input of any of the inverters $INV i$ driven by $INV A$.



(c)

 

(d)


$$T = n(C_{as} + C_w) \left(R_L + \frac{1}{n} R_w \right)$$

나머지 속성은 동일.

Part E: CMOS Circuit (32 points)

 Question 7 (32 points)


The circuit below is an NMOS logic function $Z = \overline{(ABC + D)E}$. Suppose the output of this circuit drives an inverter with a gate capacitance of C_{GS} . Assume that all the MOSFETs in the circuit have the same on-resistance R_{ON} , and same high and low voltage thresholds ($V_{IL} = V_{OL}$ and $V_{IH} = V_{OH}$).



- (1) What is the input (A, B, C, D, E) that results in the worst-case falling delay for the circuit?

$$(A, B, C, D, E) = (1, 1, 1, 0, 1)$$

 - (2) Derive an expression for the worst-case falling delay (i.e., time for v_{OUT} to switch from V_S to V_{OL})?



$$V_L = V_S \frac{4R_{ON}}{R_L + 4R_{ON}} + \left(V_S - V_S \frac{4R_{ON}}{R_L + 4R_{ON}} \right) e^{-t/\tau}$$

$$\tau = C_{GS} \frac{4R_{ON} R_L}{R_L + 4R_{ON}}$$


$$t = -\tau \ln \frac{V_L - V_S \frac{4R_{ON}}{R_L + 4R_{ON}}}{V_S - V_S \frac{4R_{ON}}{R_L + 4R_{ON}}}$$

- (3) What is the maximum power consumption of this circuit? Derive both the worst-case static power and dynamic power. Assume $C_{GS}=1\text{pF}$, $R_L=10\text{k}\Omega$, $f=50\text{MHz}$, $V_s=5\text{V}$, and $R_L \gg R_{ON}$.

$$\text{Static} = \frac{V_s^2}{2R_L (R_L \gg R_{on})} = \frac{25}{20} \text{ mW}$$

$$\begin{aligned} \text{Dynamic} &= C_{GS} V^2 f = 10^{-12} \times 5^2 \times 50 \times 10^6 \\ &= \frac{25}{20} \text{ mW} \quad \therefore 2.5 \text{ mW} \end{aligned}$$

 - (4) Convert this circuit to CMOS logic. How does the power consumption of this circuit differ from that of NMOS logic in (3)? Explain briefly in one paragraph.



(This page is intentionally left blank. Feel free to use as you like.)