

The Small-Signal Model

Lecture 9

October 18th, 2018

Jae W. Lee (jaewlee@snu.ac.kr)


Computer Science and Engineering

Seoul National University

Slide credits: [CS:APP3e] slides from CMU; [COD5e] slides from Elsevier Inc.

Review: MOSFET Amplifier

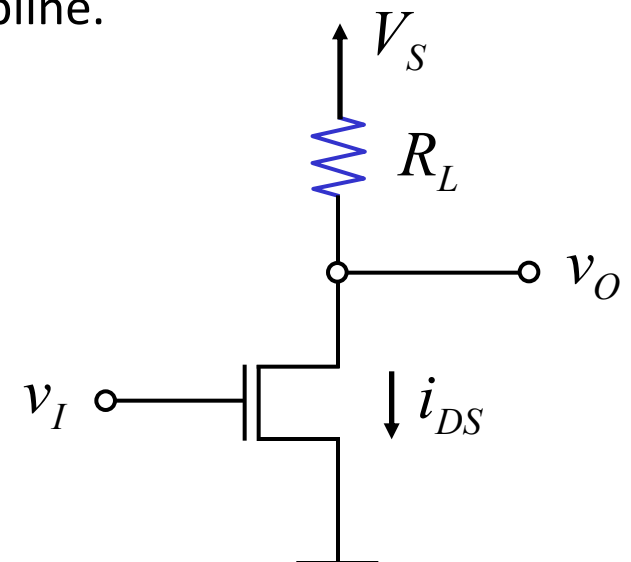- Saturation discipline — operate MOSFET only in saturation region
- Large signal analysis: does two things
 - 1. Find v_O vs v_I under saturation discipline.
 - 2. Valid v_I, v_O ranges under saturation discipline.



Review: Large Signal Analysis

① Find v_O vs v_I

$$v_O = V_S - \frac{K}{2} (v_I - 1)^2 R_L$$

valid for $v_I \geq V_T$


and

$$v_O \geq v_I - V_T$$

(same as $i_{DS} \leq \frac{K}{2} v_O^2$)

Review: Large Signal Analysis


② Valid operating ranges

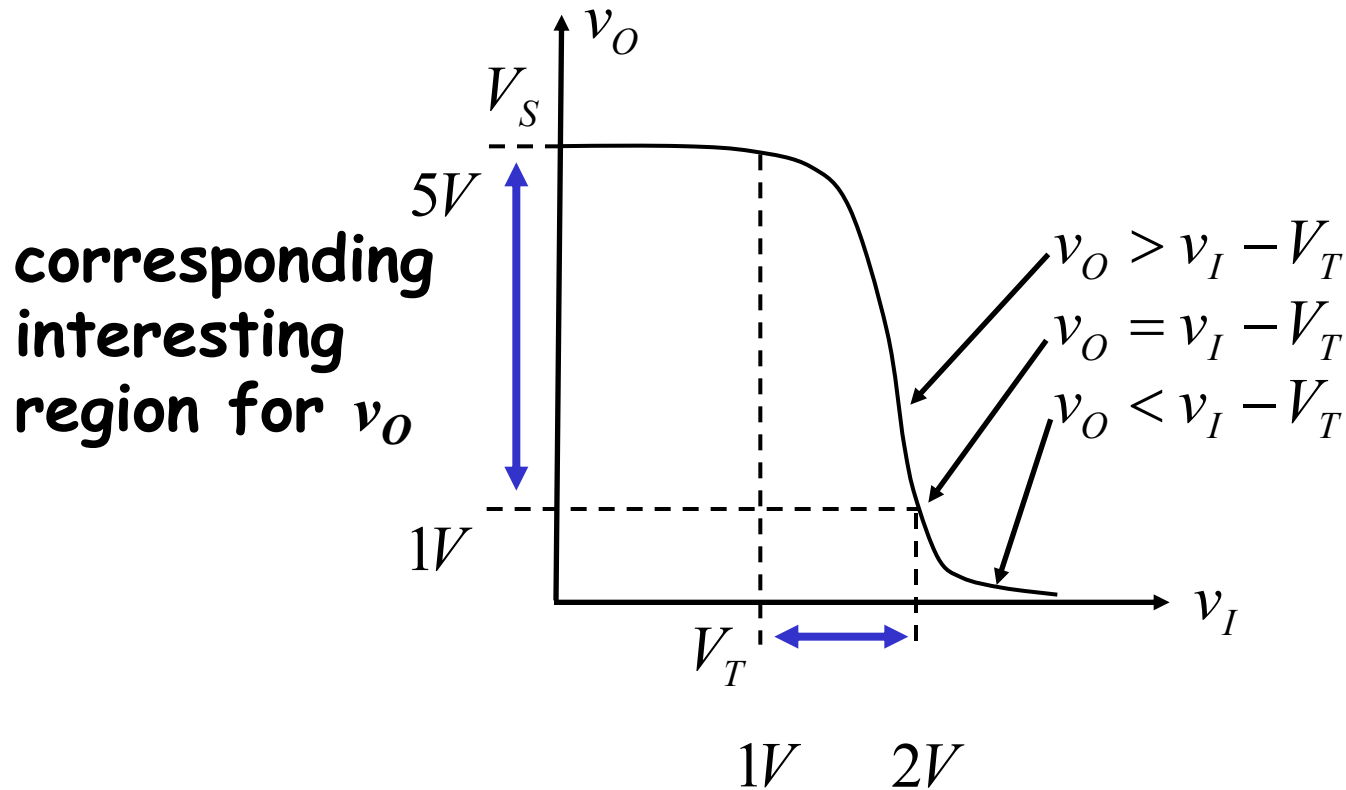


“interesting” region for v_I .
Saturation discipline satisfied.

Review: Large Signal Analysis

■ Non-linearity

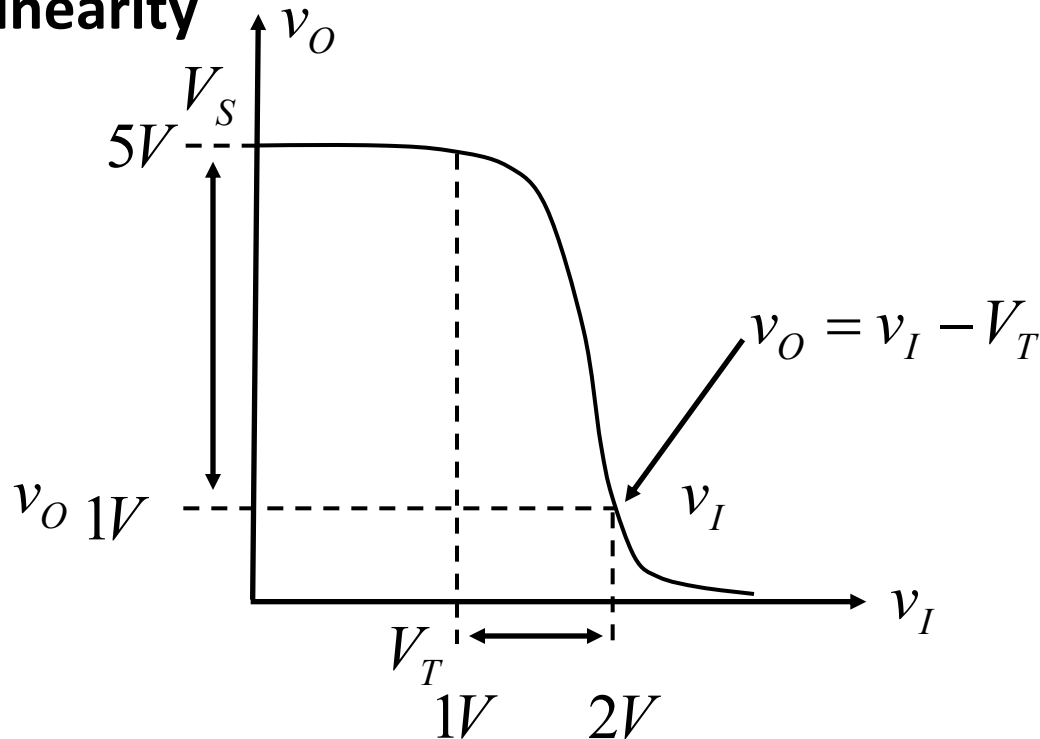

**Amplifies alright,
but distorts**

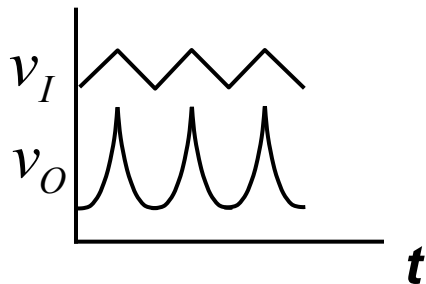

Amp is nonlinear ...



Outline


Textbook: 8.1, 8.2

- **Small-Signal Model**

- Graphical interpretation
- Mathematical interpretation
- Small-signal circuit view

- **Small-Signal Circuit Representation**

Small-Signal Model

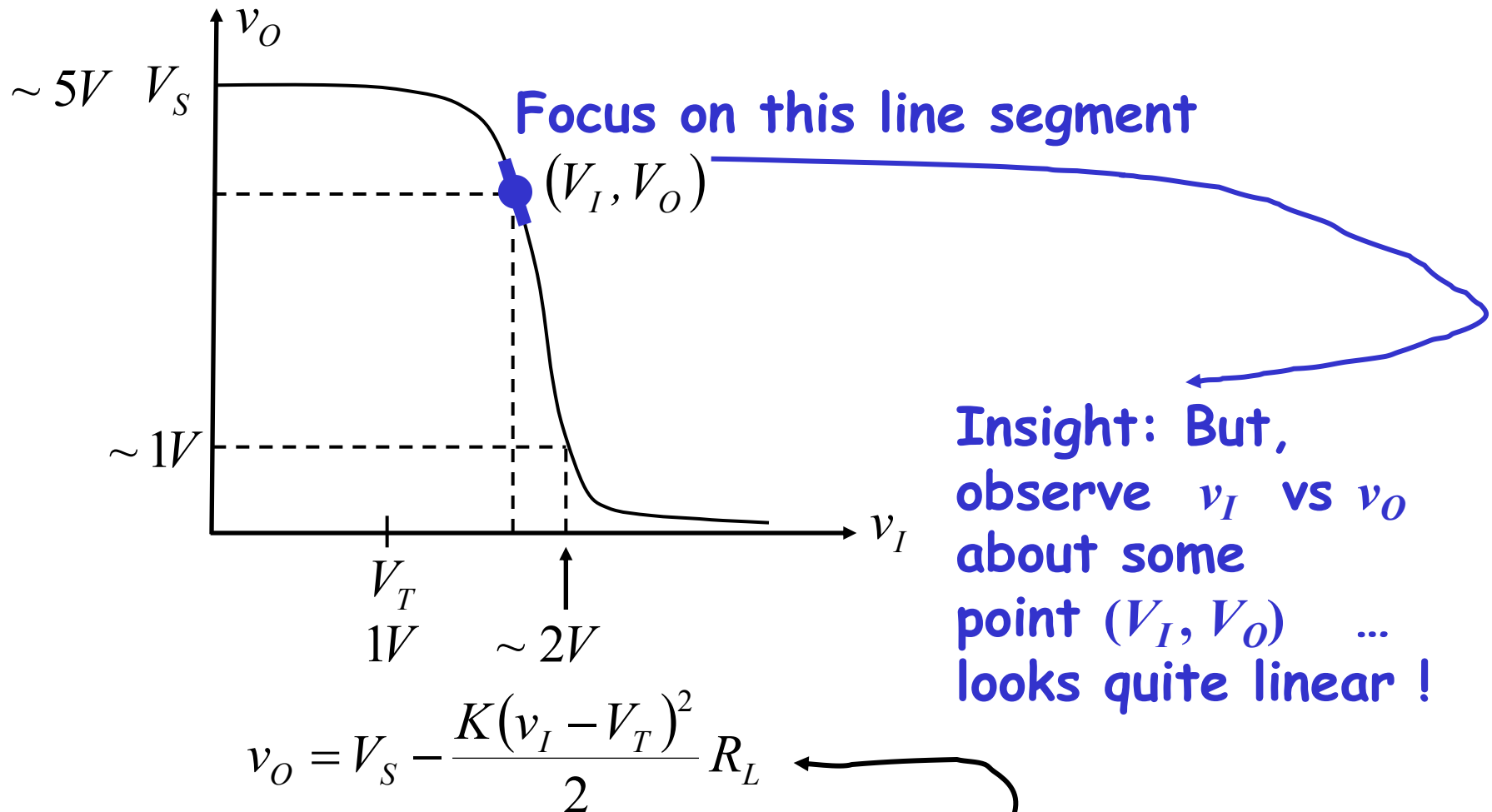


Amp all right, but nonlinear!

Hmmm ... So what about our linear amplifier ???

Small-Signal Model


Trick

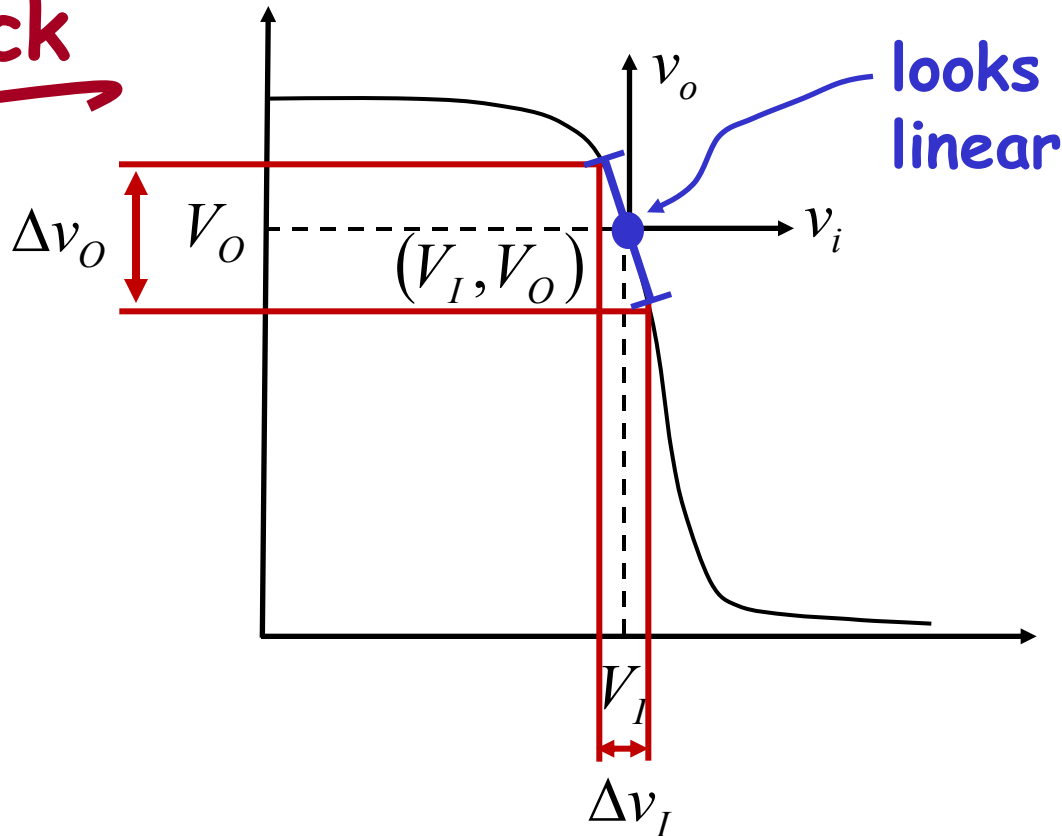

- ❖ Operate amp at V_I, V_O
 → DC "bias" (good choice: midpoint of input operating range)
- ❖ Superimpose small signal on top of V_I
- ❖ Response to small signal seems to be approximately linear

Small-Signal Model

Trick

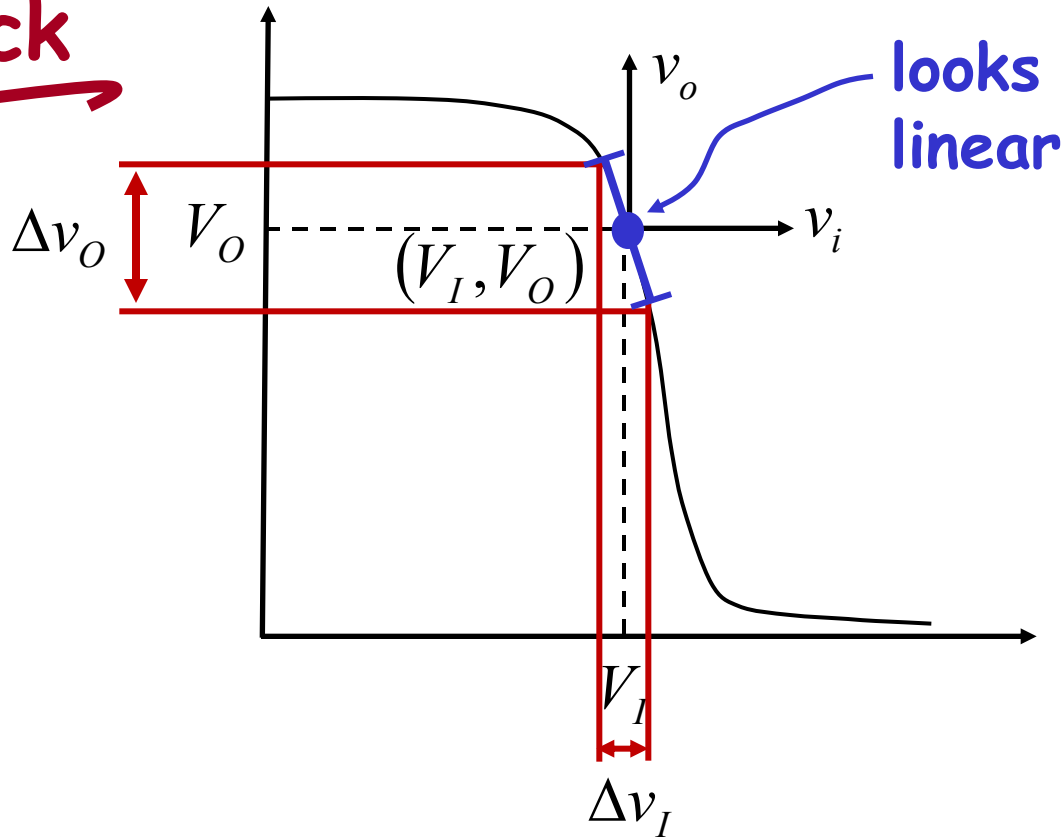

Let's look at this in more detail —


- ❖ Operate amp at V_I, V_O
 - DC "bias" (good choice: midpoint of input operating range)
- ❖ Superimpose small signal on top of V_I
- ❖ Response to small signal seems to be approximately linear

I graphically
 II mathematically
 III from a circuit viewpoint

Small-Signal Model

I Graphically


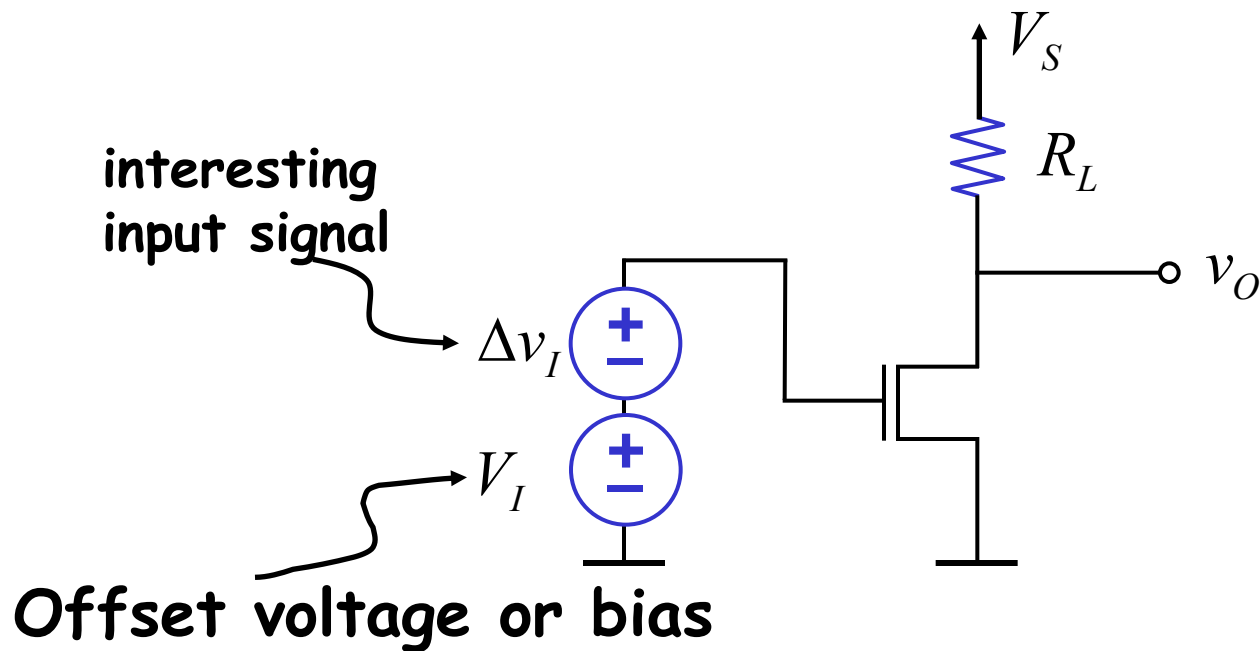
We use a DC bias V_I to “boost” interesting input signal above V_T , and in fact, well above V_T .



Small-Signal Model

I Graphically

interesting
input signal

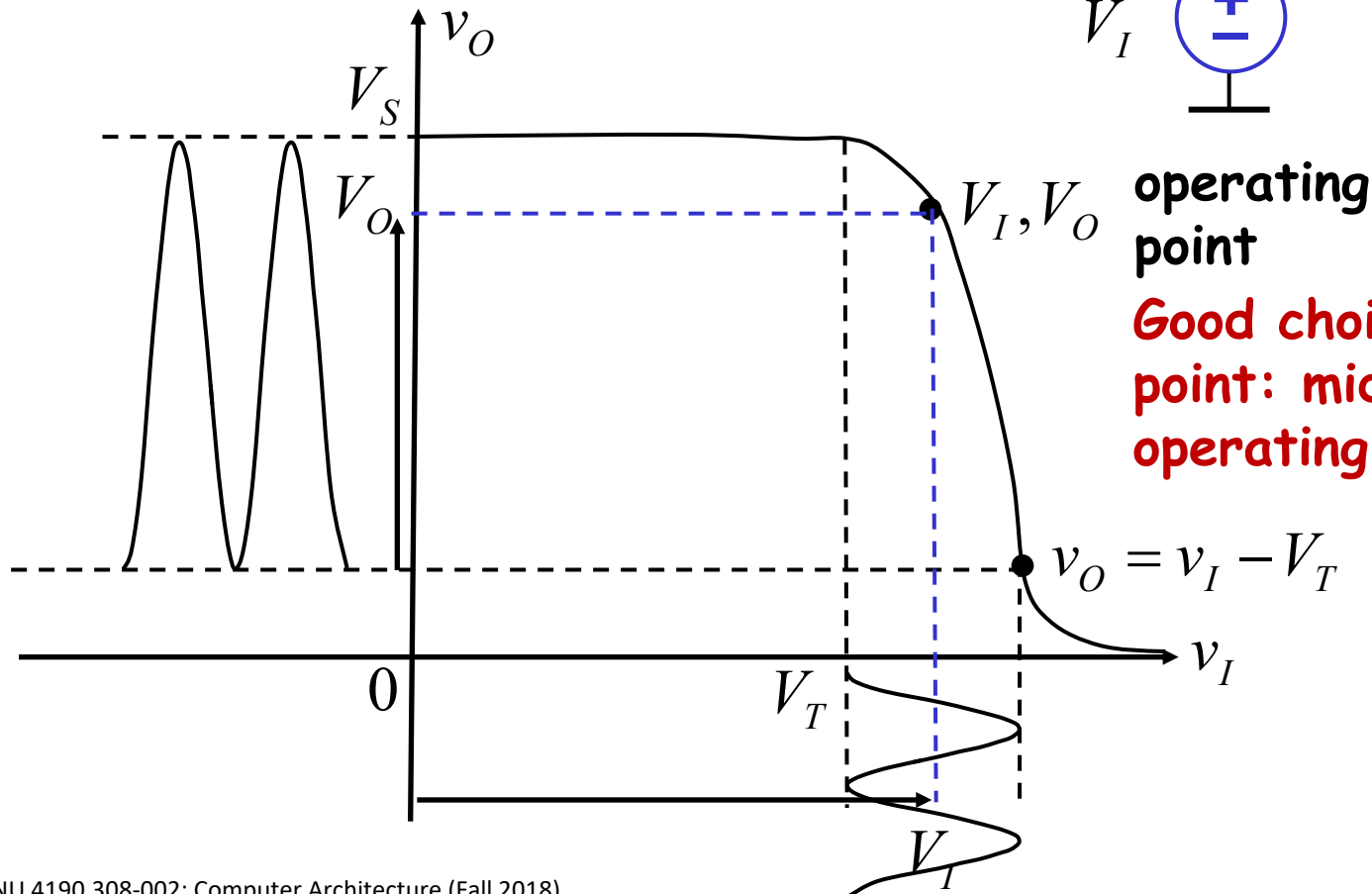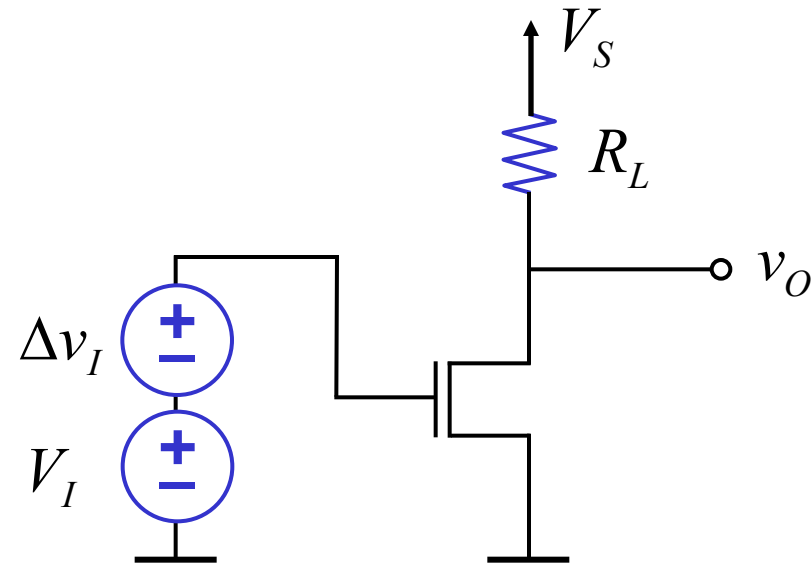

operating
point

Good choice for operating
point: midpoint of input
operating range

Small-Signal Model aka incremental or linearized model

Notation —



Input: $v_I = V_I + v_i$

\nearrow total $\quad \nwarrow$ DC $\quad \nwarrow$ small
 variable bias signal (like Δv_I)

\downarrow
 bias voltage aka operating point voltage

Output: $v_O = V_O + v_o$

Graphically,

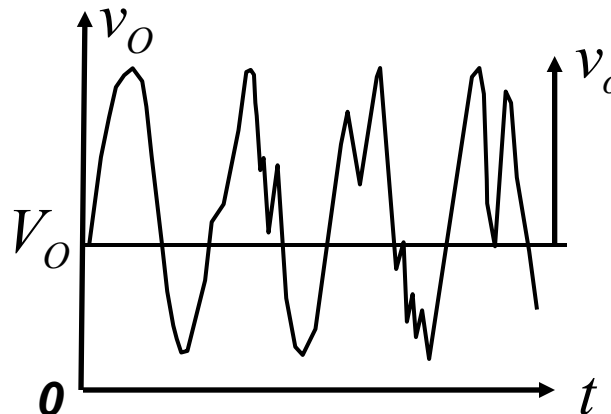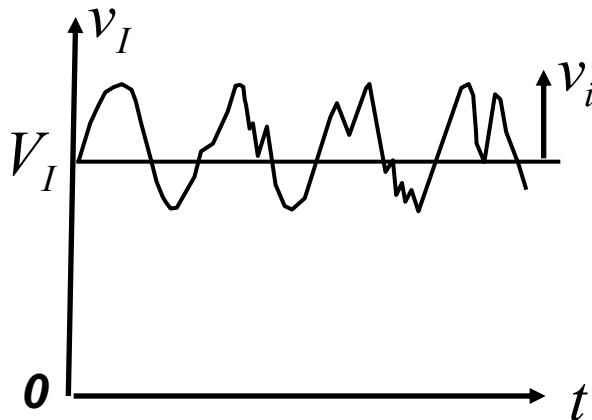

Small-Signal Model

II Mathematically

$$v_O = V_S - \frac{R_L K}{2} (v_I - V_T)^2 \quad \Bigg| \quad V_O = V_S - \frac{R_L K}{2} (V_I - V_T)^2$$

substituting $v_I = V_I + v_i$ $v_i \ll V_I$

$$v_O = V_S - \frac{R_L K}{2} ([V_I + v_i] - v_T)^2$$

$$= V_S - \frac{R_L K}{2} ([V_I - V_T] + v_i)^2$$

$$= V_S - \frac{R_L K}{2} ([V_I - V_T]^2 + 2[V_I - V_T]v_i + v_i^2)$$

$$V_O + v_o = V_S - \frac{R_L K}{2} (V_I - V_T)^2 - R_L K (V_I - V_T) v_i$$

From ,

$$v_o = -R_L K (V_I - V_T) v_i$$

g_m

related to V_I

Small-Signal Model

II Mathematically

(From previous page...)

$$v_o = -R_L \underbrace{K (V_I - V_T)}_{g_m} v_i$$

g_m related to V_I

$$v_o = -g_m R_L v_i$$

For a given DC operating point voltage V_I ,
 $V_I - V_T$ is constant. So,

$$v_o = -A v_i$$


constant w.r.t. v_i

In other words, our circuit behaves like a linear amplifier for small signals

Small-Signal Model

II Mathematically (alternative way)

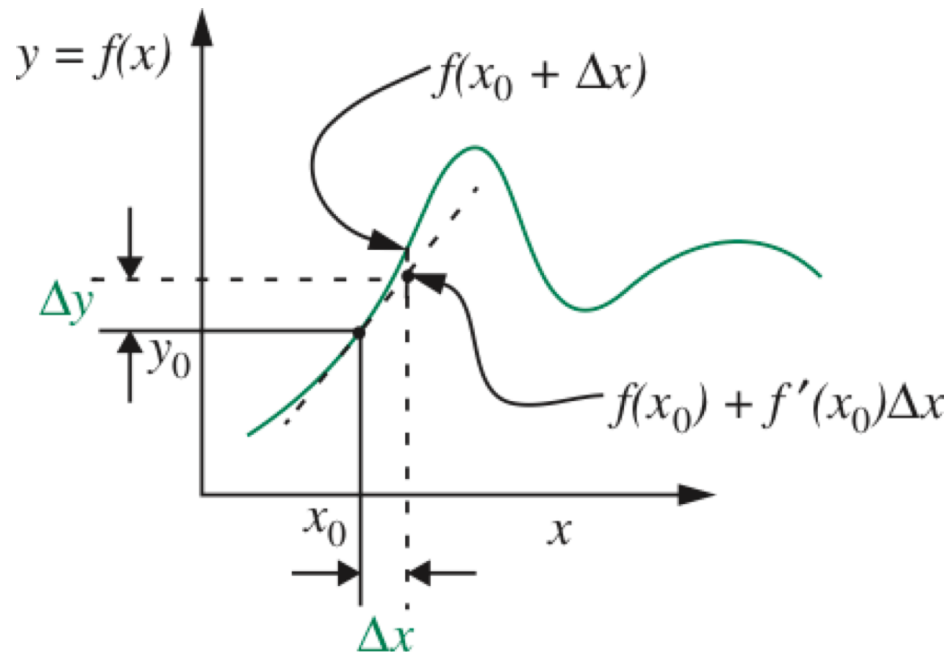For small Δx near x_0 , $f(x_0 + \Delta x) \cong f(x_0) + f'(x_0) \Delta x$



Small-Signal Model

II Mathematically (alternative way)

$$v_o = V_S - \frac{R_L K}{2} (v_I - V_T)^2$$

$$v_o = \underbrace{\frac{d}{dv_I} \left[V_S - \frac{R_L K}{2} (v_I - V_T)^2 \right]}_{\text{slope at } V_I} \bigg|_{v_I = V_I} \cdot v_i$$

$$v_o = -R_L K (V_I - V_T) \cdot v_i$$


$$g_m = K (V_I - V_T)$$

$$A = -g_m R_L \quad \text{amp gain}$$

Small-Signal Model

■ How to choose the bias point?

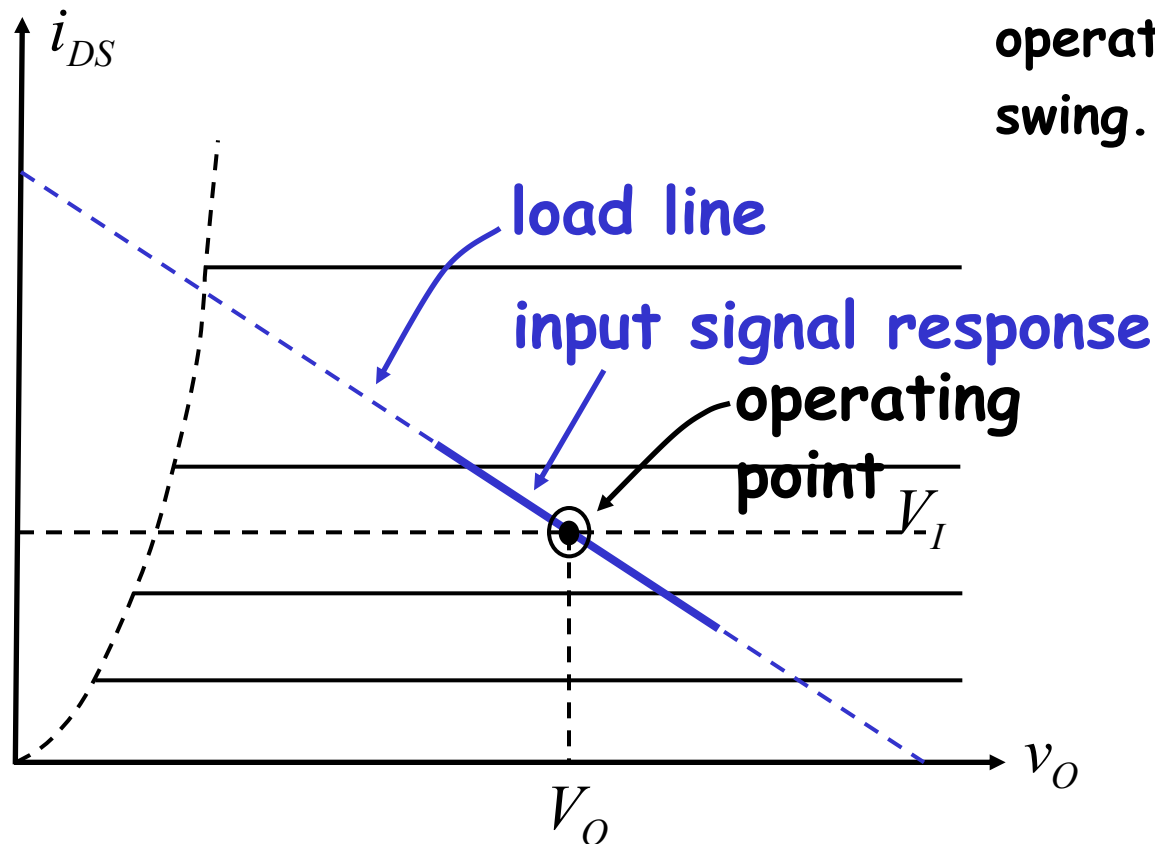1. Gain component $g_m \propto V_I$
2. v_i gets big \rightarrow distortion.
So bias carefully
3. Input valid operating range.
Bias at midpoint of input
operating range for maximum
swing.




Small-Signal Model

III The Small Signal Circuit View

We can derive small circuit equivalent models for our devices, and thereby conduct small signal analysis directly on circuits

e.g. large signal circuit model for amp

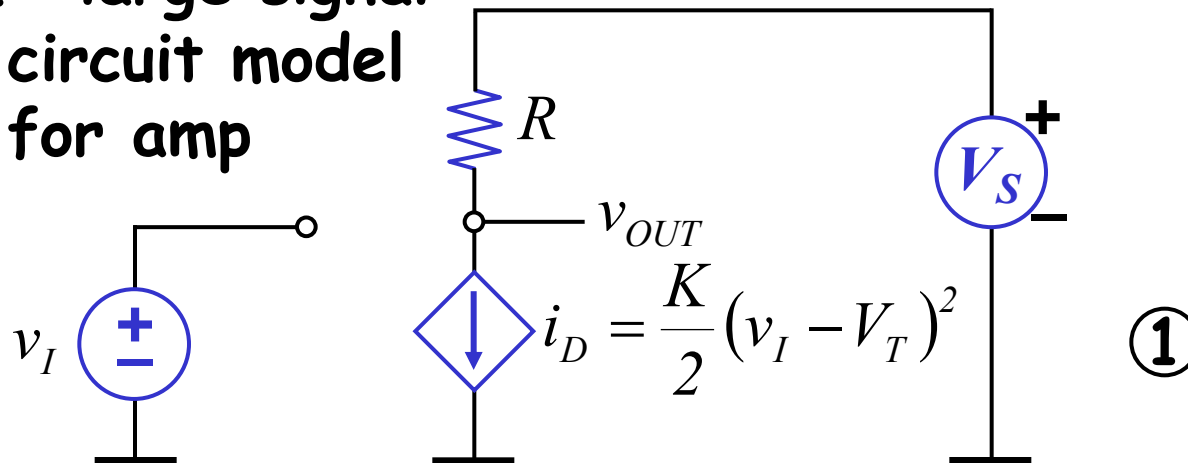

We can replace large signal models with small signal circuit models.

Outline

Textbook: 8.1, 8.2

- **Small-Signal Model**
 - Graphical interpretation
 - Mathematical interpretation
 - Small-signal circuit view
- **Small-Signal Circuit Representation**

Small-Signal Circuit Representation

■ Small-signal circuit analysis


- ① Find operating point using DC bias inputs using large signal model.
- ② Develop small signal (linearized) models for elements.
- ③ Replace original elements with small signal models.

Analyze resulting linearized circuit...

Key: Can use superposition and other linear circuit tools with linearized circuit!

Small-Signal Circuit Representation


Ⓐ MOSFET

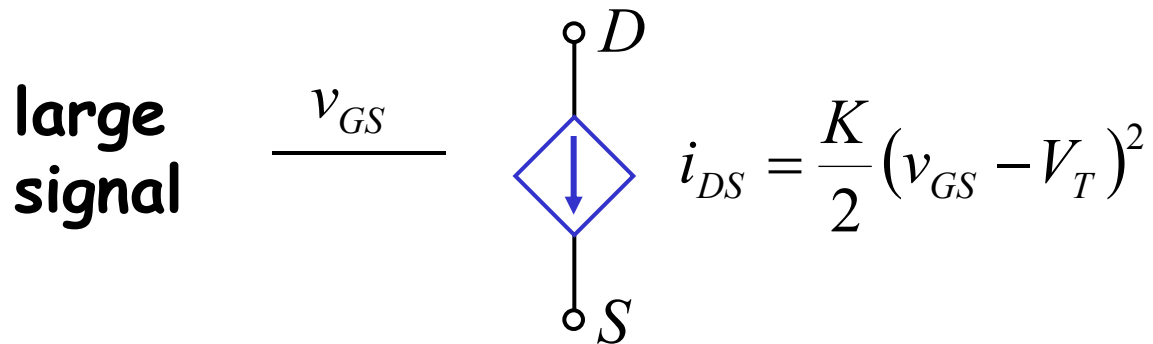

Small signal?

Small-Signal Circuit Representation


Ⓐ MOSFET

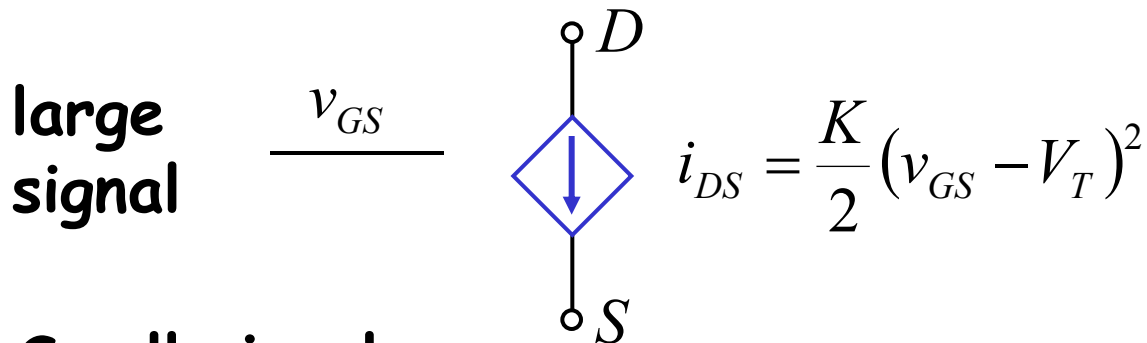

Small signal:

$$i_{DS} = \frac{K}{2} (v_{GS} - V_T)^2$$

small
signal

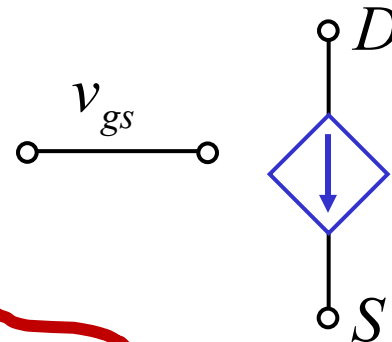

$$i_{ds} = K(V_{GS} - V_T) v_{gs}$$


$$i_{ds} = g_m v_{gs}$$

$$i_{ds} = \frac{\partial}{\partial v_{GS}} \left[\frac{K}{2} (v_{GS} - V_T)^2 \right] \bigg|_{v_{GS}=V_{GS}} \cdot v_{gs}$$

$$i_{ds} = \underbrace{K(V_{GS} - V_T)}_{g_m} \cdot v_{gs} \Rightarrow i_{ds} \text{ is linear in } v_{gs}!$$


Small-Signal Circuit Representation

Ⓑ DC Supply V_S

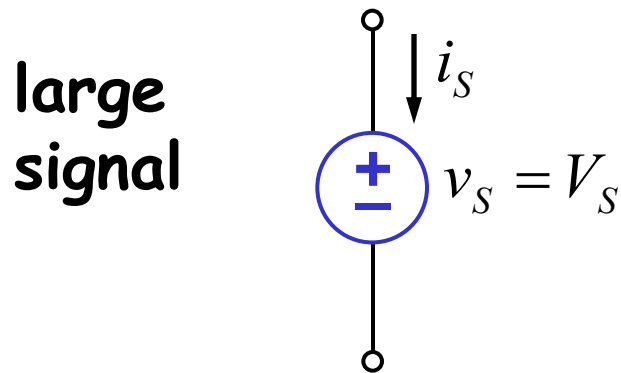

$$v_S = V_S$$

Small signal

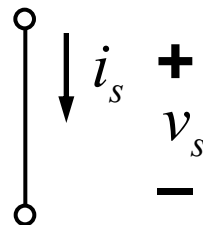

$$v_s = \left. \frac{\partial V_S}{\partial i_S} \right|_{i_S = I_S} \cdot i_s$$


$$v_s = 0$$

DC source behaves as short to small signals.

Small-Signal Circuit Representation

③ Similarly, R

large
signal

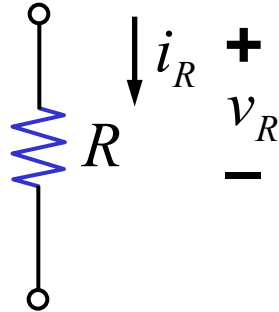


$$v_R = R i_R$$

$$v_r = \left. \frac{\partial(Ri_R)}{\partial i_R} \right|_{i_R=I_R} \cdot i_r$$



$$v_r = R \cdot i_r$$

small
signal

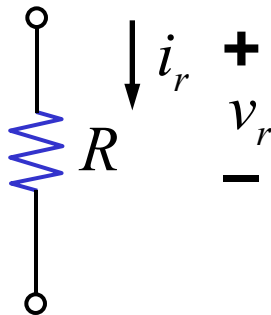

Small-Signal Circuit Representation

■ Amplifier example

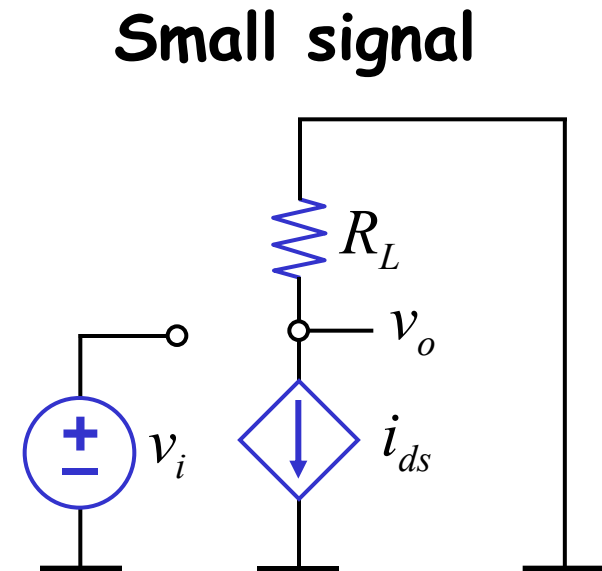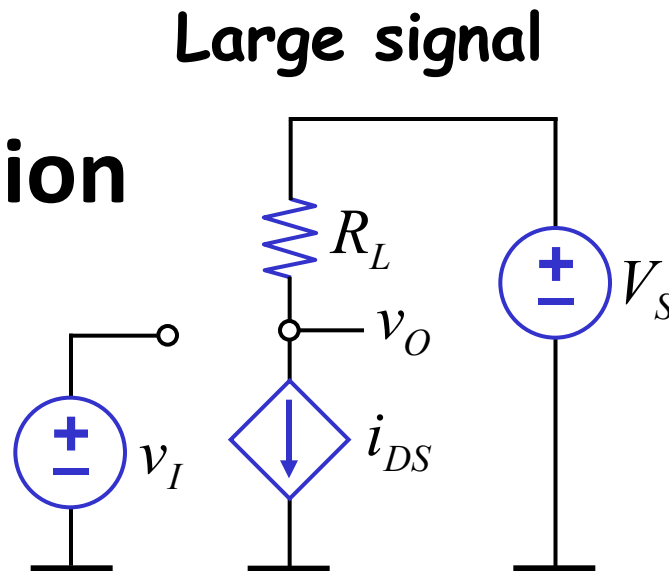

Notice, first we
need to find
operating point
voltages/currents.

Get these from a
large signal analysis.

$$i_{DS} = \frac{K}{2} (v_I - V_T)^2$$

$$v_O = V_S - \frac{K}{2} (v_I - V_T)^2 R_L$$

$$i_{ds} = K(V_I - V_T) \cdot v_i$$

$$i_{ds} R_L + v_o = 0$$

$$v_o = -i_{ds} R_L$$

$$\begin{aligned} v_o &= -K(V_I - V_T) R_L \cdot v_i \\ &= -g_m R_L \cdot v_i \end{aligned}$$

Small-Signal Circuit Representation

■ Example 8.1: Derive a small-signal model

