

# Network Theorems

Lecture 3

September 11<sup>th</sup>, 2018

Jae W. Lee ([jaewlee@snu.ac.kr](mailto:jaewlee@snu.ac.kr))

Computer Science and Engineering  
Seoul National University

*Slide credits: Prof. Anant Agarwal at MIT*





# Review: Circuit Analysis Methods

- Circuit Analysis: Find all element v's and i's for a given circuit
- Method 1: Basic KVL, KCL method

$$\sum_{loop} V_i = 0$$

$$\sum_{node} I_i = 0$$

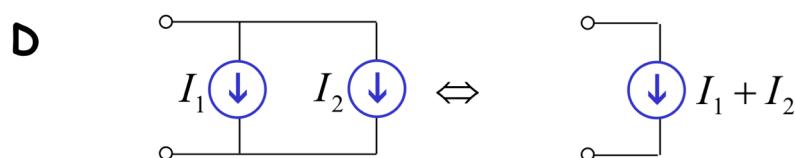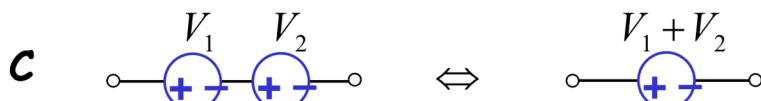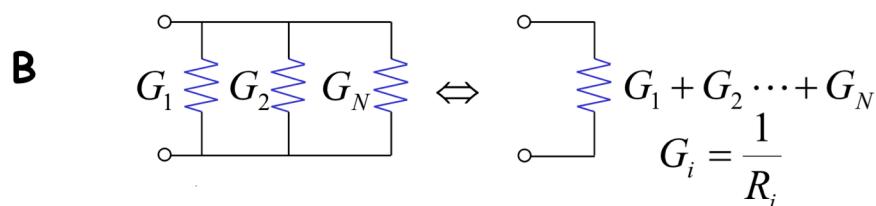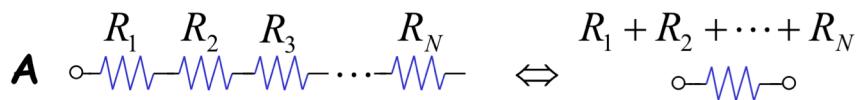- Method 2: Apply element combination rules



# Outline

**Textbook: Ch. 3.1-3.6**

- **Node (Voltage) Analysis**
- Mesh (Loop) Analysis
- Linearity and Superposition Method
- Thevenin's Theorem and Norton's Theorem

# Node Analysis (Method 3)


## ■ Node Analysis = Particular application of KVL, KCL method

- Node voltage: the potential difference between the given node and the reference (ground) node
- Calculating branch current in Node Analysis

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

In the node voltage method, we assign the node voltages  $v_a$  and  $v_b$ ; the branch current flowing from  $a$  to  $b$  is then expressed in terms of these node voltages.


$$i = \frac{v_a - v_b}{R}$$

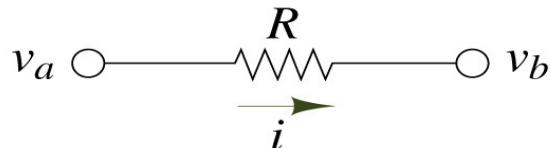


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

By KCL:  $i_1 - i_2 - i_3 = 0$ . In the node voltage method, we express KCL by
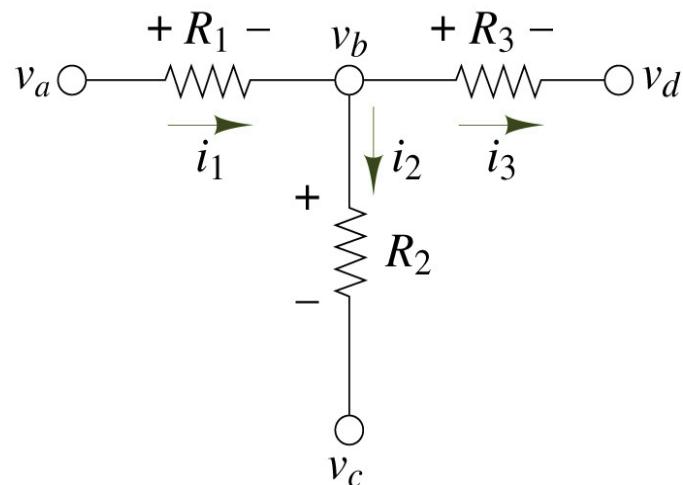
$$\frac{v_a - v_b}{R_1} - \frac{v_b - v_c}{R_2} - \frac{v_b - v_d}{R_3} = 0$$



# Node Analysis: An Illustration


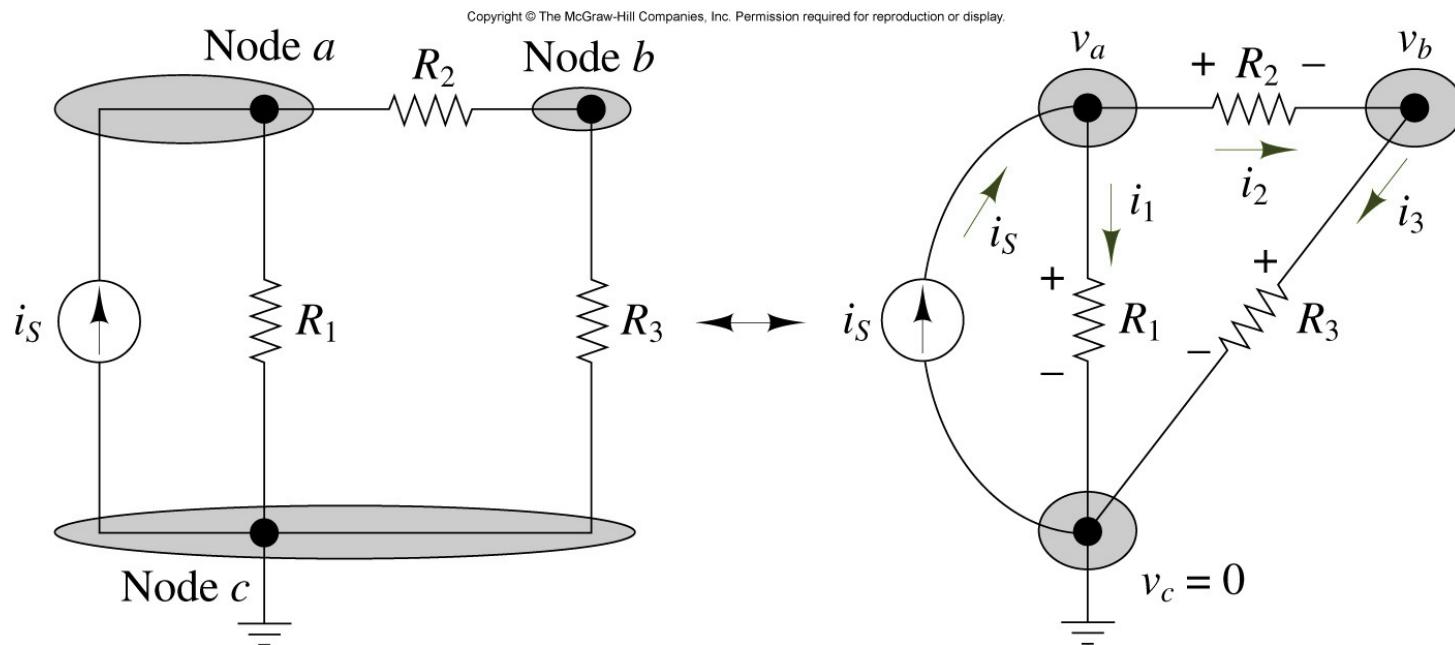


# Node Analysis: Example

$I_1 = 10\text{mA}$ ,  $I_2 = 50\text{mA}$ ,  $R_1 = 1\text{k}\Omega$ ,  $R_2 = 2\text{k}\Omega$

$R_3 = 10\text{k}$ ,  $R_4 = 2\text{k}\Omega$

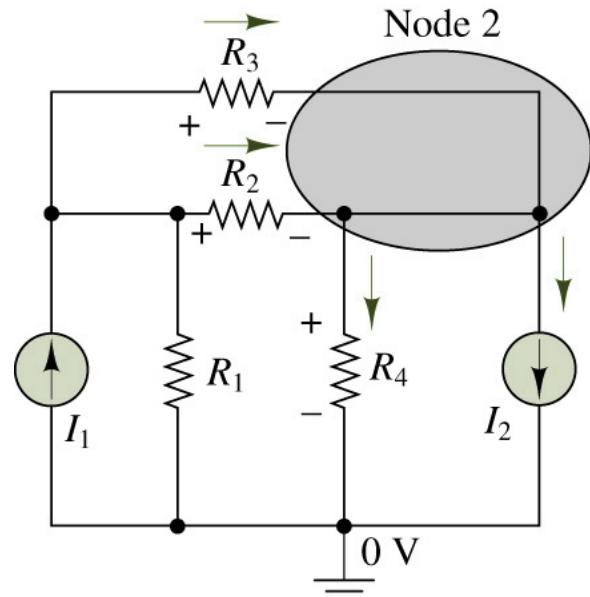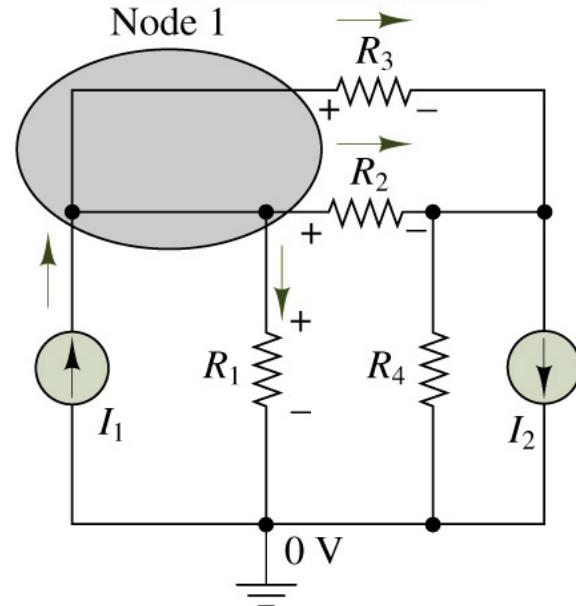Find all node voltages and branch currents




# Node Analysis: Procedure

- 1. Select reference node ( $\perp$  ground) from which voltages are measured.**
- 2. Label voltages of remaining nodes with respect to ground. These are the primary unknowns.**
- 3. Write KCL for all but the ground node, substituting device laws and KVL.**
- 4. Solve for node voltages.**
- 5. Back solve for branch voltages and currents (i.e., the secondary unknowns)**

# Node Analysis

## ■ Example with current source

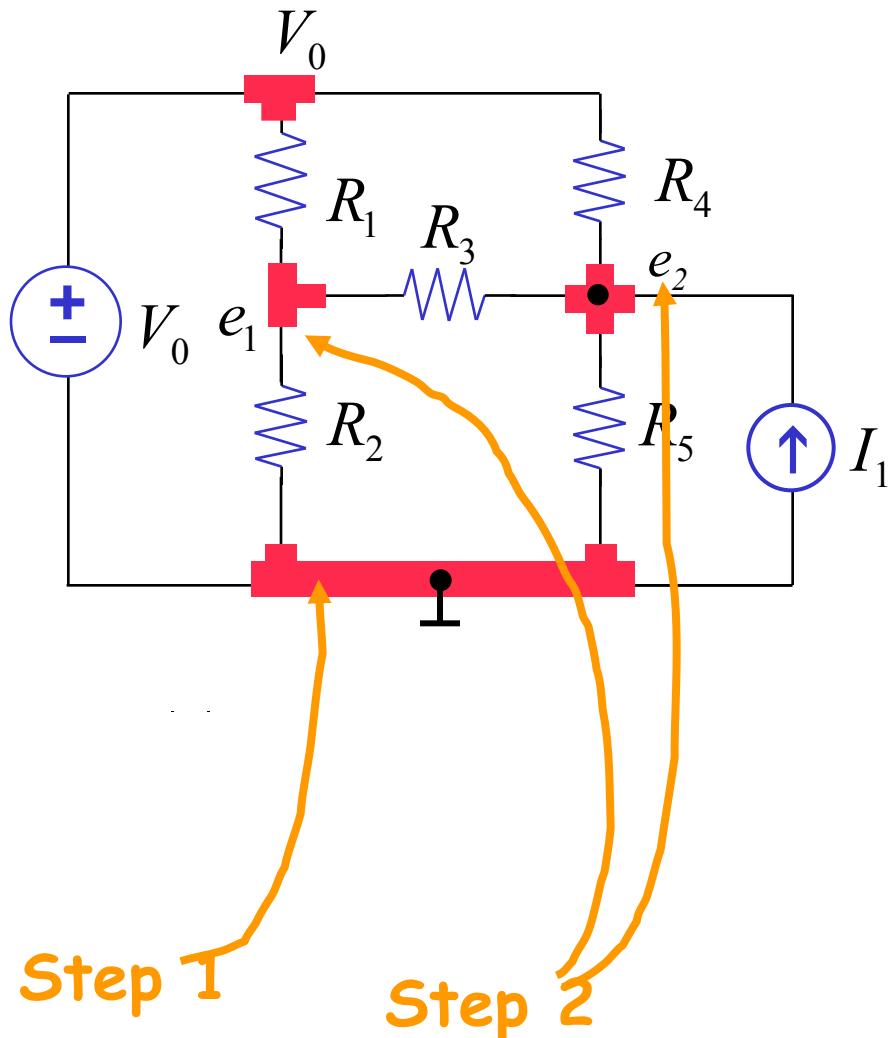


# Node Analysis

## ■ Example with current source

for  
convenience,  
write

$$G_i = \frac{1}{R_i}$$

**Step 3**

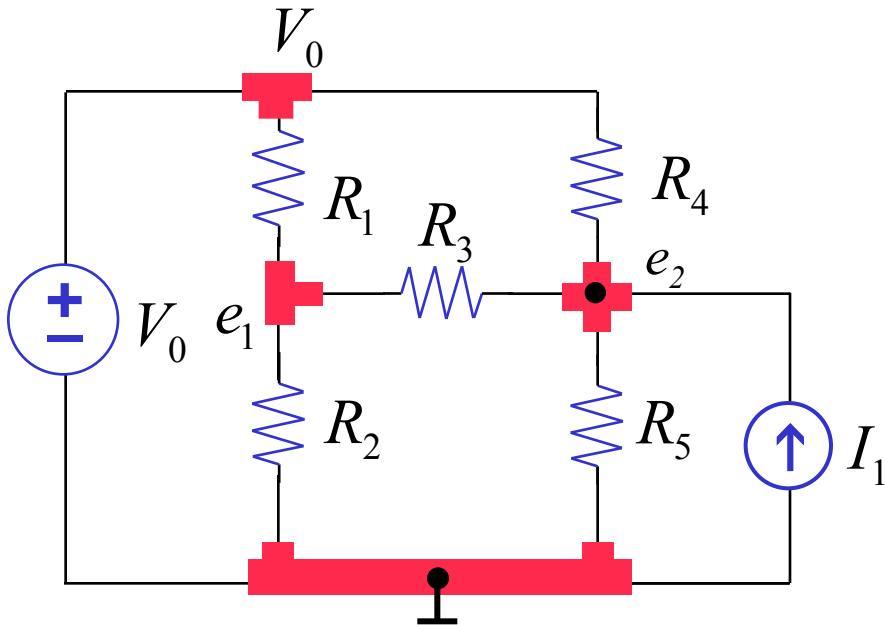

**KCL at  $e_1$**

$$(e_1 - V_0)G_1 + (e_1 - e_2)G_3 + (e_1)G_2 = 0$$

**KCL at  $e_2$**


$$(e_2 - e_1)G_3 + (e_2 - V_0)G_4 + (e_2)G_5 - I_1 = 0$$

# Node Analysis

## ■ Example with current source

for  
convenience,  
write

$$G_i = \frac{1}{R_i}$$

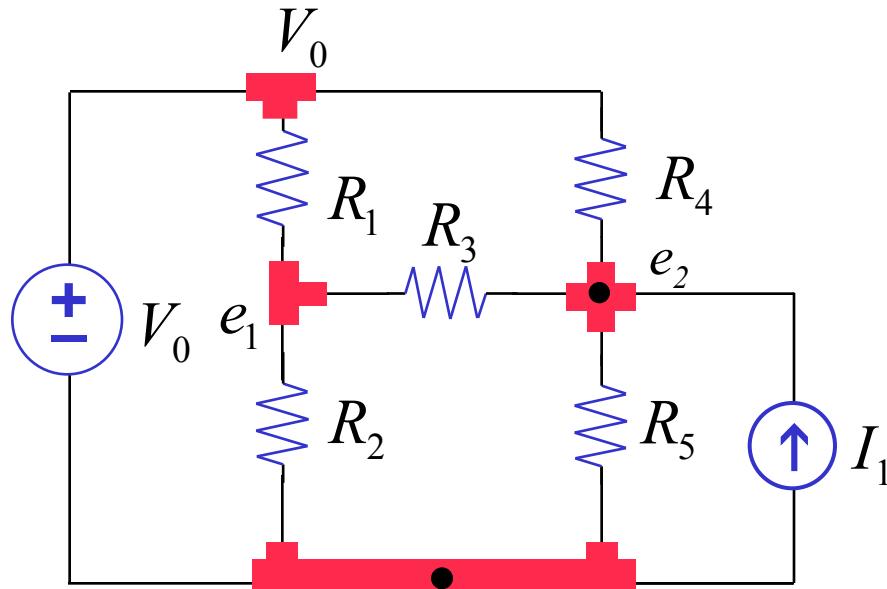

move constant terms to RHS & collect unknowns

$$e_1(G_1 + G_2 + G_3) + e_2(-G_3) = V_0(G_1)$$

$$e_1(-G_3) + e_2(G_3 + G_4 + G_5) = V_0(G_4) + I_1$$

2 equations, 2 unknowns → Solve for e's  
(compare units)

Step 4

# Node Analysis

## ■ Example (cont'd)

$$\begin{bmatrix} a & b \\ c & d \end{bmatrix}^{-1} = \frac{1}{ad-bc} \begin{bmatrix} d & -b \\ -c & a \end{bmatrix}$$

determinant

In matrix form:

$$\left[ \begin{array}{c|c} G_1 + G_2 + G_3 & -G_3 \\ \hline -G_3 & G_3 + G_4 + G_5 \end{array} \right] \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \begin{bmatrix} G_1 V_0 \\ G_4 V_0 + I_1 \end{bmatrix}$$

conductivity matrix      unknown node voltages      sources

Solve

$$\begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \frac{\begin{bmatrix} G_3 + G_4 + G_5 & G_3 \\ \hline G_3 & G_1 + G_2 + G_3 \end{bmatrix}}{(G_1 + G_2 + G_3)(G_3 + G_4 + G_5) - G_3^2} \begin{bmatrix} G_1 V_0 \\ G_4 V_0 + I_1 \end{bmatrix}$$

Notice: linear in  $V_0, I_1$   
no negatives  
in denominator

$$e_1 = \frac{(G_3 + G_4 + G_5)G_1 V_0 + (G_3)G_4 V_0 + I_1}{G_1 G_3 + G_1 G_4 + G_1 G_5 + G_2 G_3 + G_2 G_4 + G_2 G_5 + G_3^2 + G_3 G_4 + G_3 G_5}$$

$$e_2 = \frac{(G_3)(G_1 V_0) + (G_1 + G_2 + G_3)(G_4 V_0 + I_1)}{G_1 G_3 + G_1 G_4 + G_1 G_5 + G_2 G_3 + G_2 G_4 + G_2 G_5 + G_3^2 + G_3 G_4 + G_3 G_5}$$

(same denominator)

# Node Analysis

## ■ Example (cont'd)

Solve, given

$$\left. \begin{array}{l} G_1 \\ G_5 \end{array} \right\} = \frac{1}{8.2K} \quad \left. \begin{array}{l} G_2 \\ G_4 \end{array} \right\} = \frac{1}{3.9K} \quad G_3 = \frac{1}{1.5K}$$

$$I_1 = 0$$

$$e_2 = \frac{G_3 G_1 V_0 + (G_1 + G_2 + G_3) G_4 V_0 + I_1}{(G_1 + G_2 + G_3) + (G_3 + G_4 + G_5) - G_3^2}$$

$$G_1 + G_2 + G_3 = \frac{1}{8.2} + \frac{1}{3.9} + \frac{1}{1.5} = 1$$

$$G_3 + G_4 + G_5 = \frac{1}{1.5} + \frac{1}{3.9} + \frac{1}{8.2} = 1$$



$$e_2 = \frac{\frac{1}{8.2} \times \frac{1}{1.5} + 1 \times \frac{1}{3.9}}{1 - \frac{1}{1.5^2}} V_0$$

$$e_2 = 0.6V_0$$

If  $V_0 = 3V$ , then  $e_2 = 1.8V_0$

# Node Analysis

## ■ Example with Voltage Source

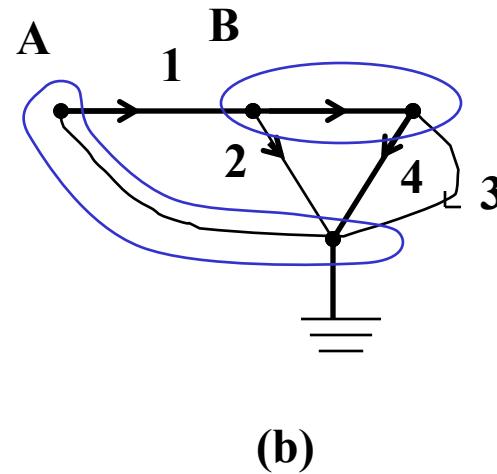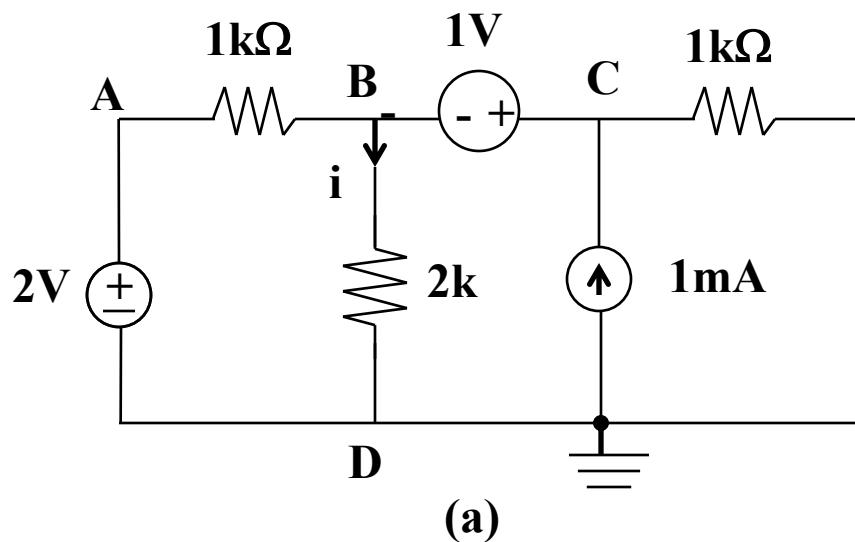


$$\frac{e_B - e_A}{1} + \frac{e_B}{2} + \frac{e_C}{1} = 1 \Rightarrow \frac{e_B - 2}{1} + \frac{e_B}{2} + \frac{e_B + 1}{1} = 1$$

$$e_B = 0.8, \quad i = 0.4(mA)$$

# Node Analysis

## ■ Example with controlled sources

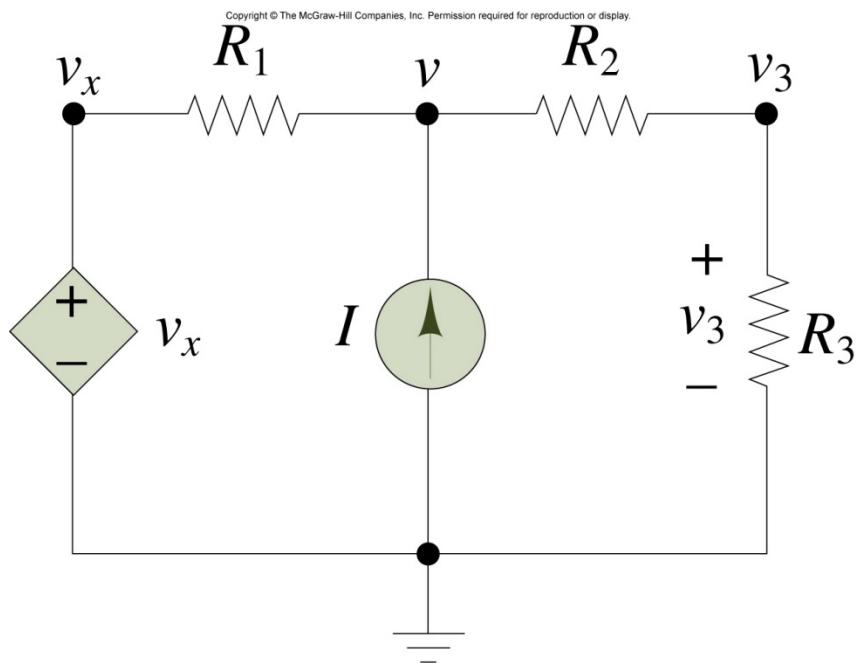

$$I = 0.5\text{mA}, V_x = 2 \times v_3$$


$$R_1 = 5\text{k}\Omega, R_2 = 2\text{k}\Omega, R_3 = 4\text{k}\Omega$$

Find  $v$
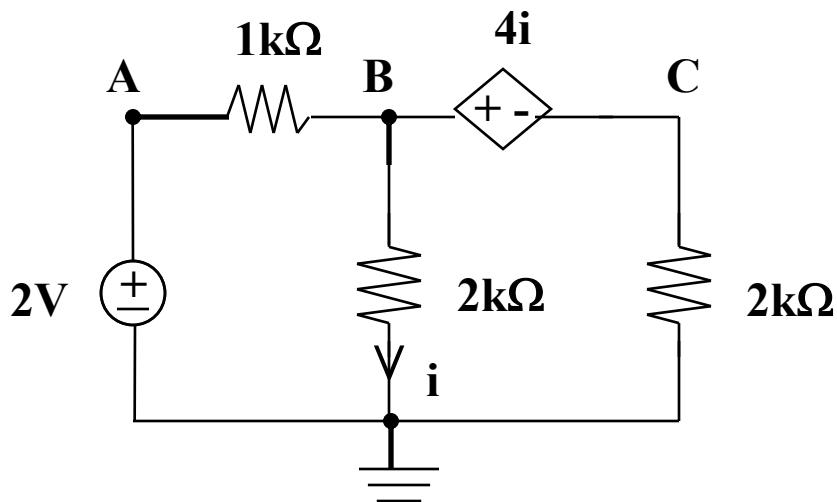
# Exercise



Find  $i$  using the node analysis technique



# Outline

## Textbook: Ch. 3.1-3.6


- Node (Voltage) Analysis
- Mesh (Loop) Analysis
- Linearity and Superposition Method
- Thevenin's Theorem and Norton's Theorem

# Mesh (Loop) Analysis

- Simplified analysis method based on an astute choice of current variables that parallel Node Analysis
- Basic principle


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

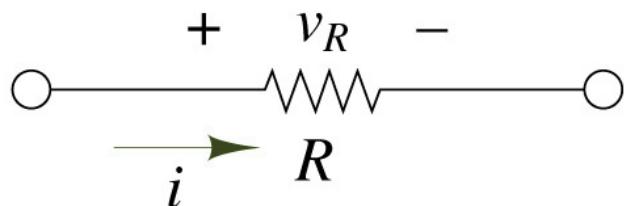The current  $i$ , defined as flowing from left to right, establishes the polarity of the voltage across  $R$ .



Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

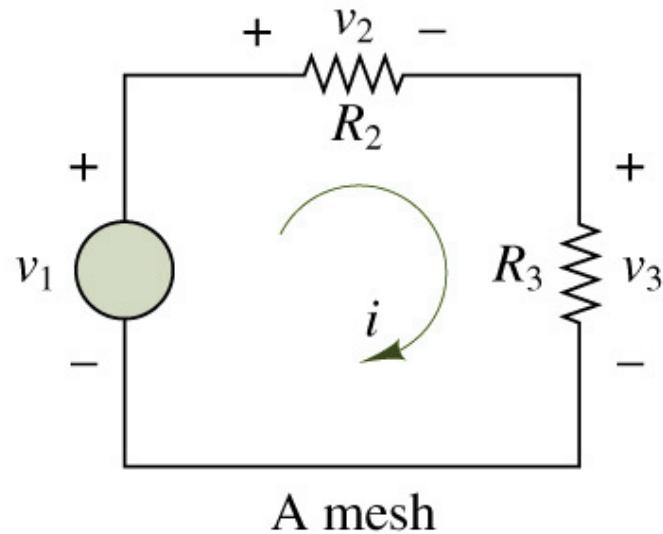Once the direction of current flow has been selected, KVL requires that  $v_1 - v_2 - v_3 = 0$ .




# Mesh (Loop) Analysis

## ■ Two-mesh circuit

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

Mesh 1: KVL requires that
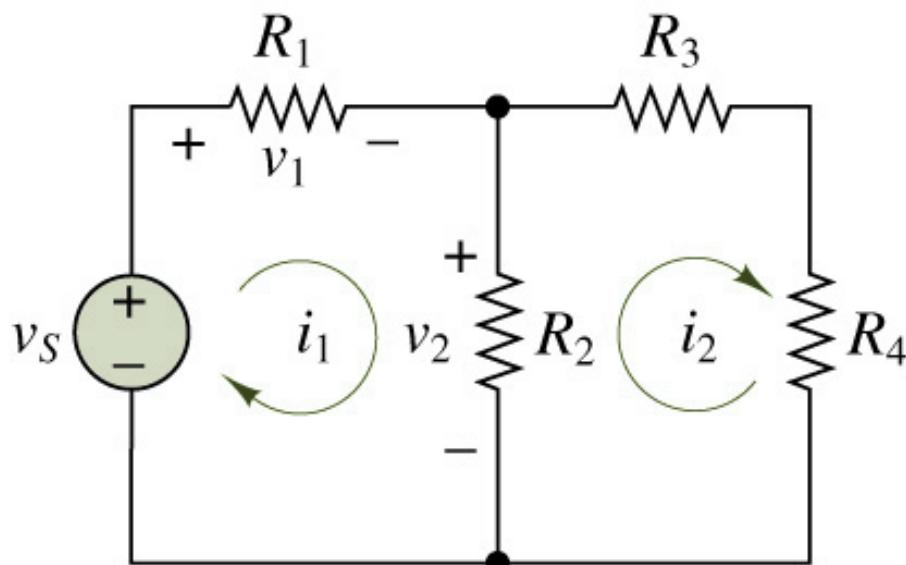
$$v_S - v_1 - v_2 = 0, \text{ where } v_1 = i_1 R_1,$$
$$v_2 = (i_1 - i_2) R_1.$$



# Mesh (Loop) Analysis


## ■ Example

$V_1 = 10V, V_2 = 9V, V_3 = 1V,$

$R_1 = 5k\Omega, R_2 = 10k\Omega,$   
 $R_3 = 5k\Omega, R_4 = 5k\Omega$


Find  $i$

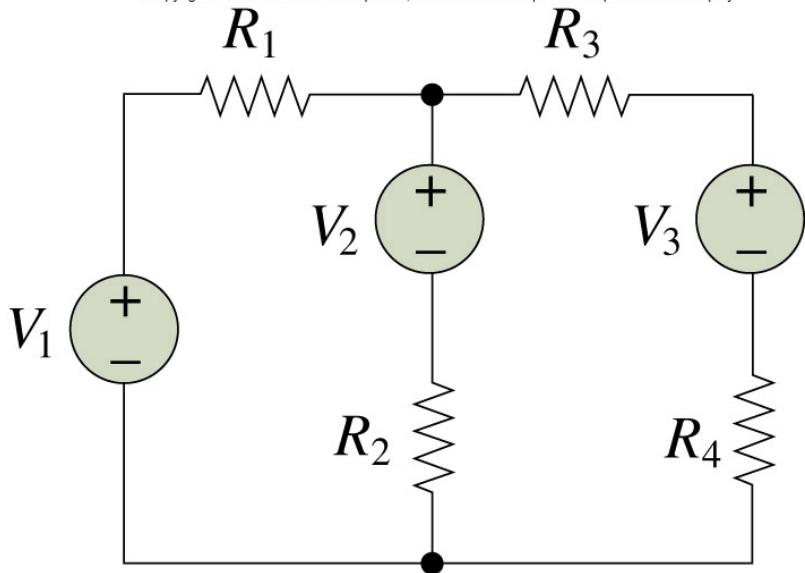Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



# Mesh (Loop) Analysis


## ■ Example with current sources

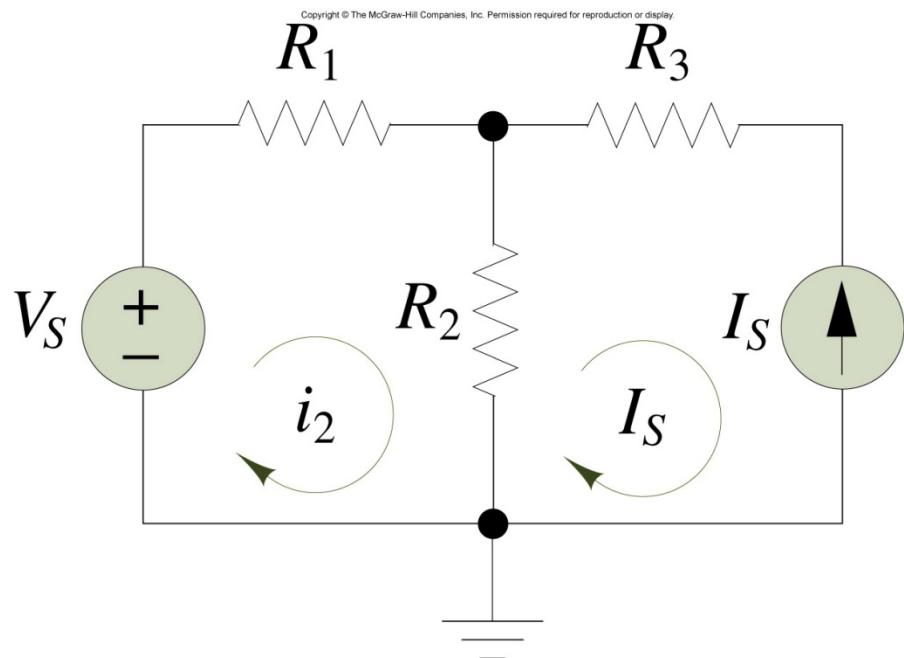

# Mesh (Loop) Analysis
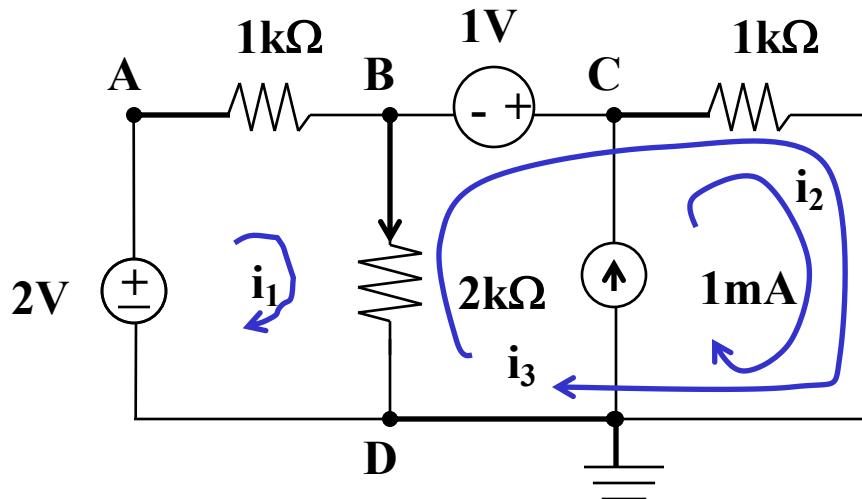
## ■ (Another) Example

- Every element must be traversed by at least one loop current.




$$\{A, B, D, A\} \quad i_1 + 2(i_1 - i_3) = 2$$

$$\{B, C, D, B\} \quad (i_3 + i_2) + 2(i_3 - i_1) = 1, \quad i_2 = 1$$
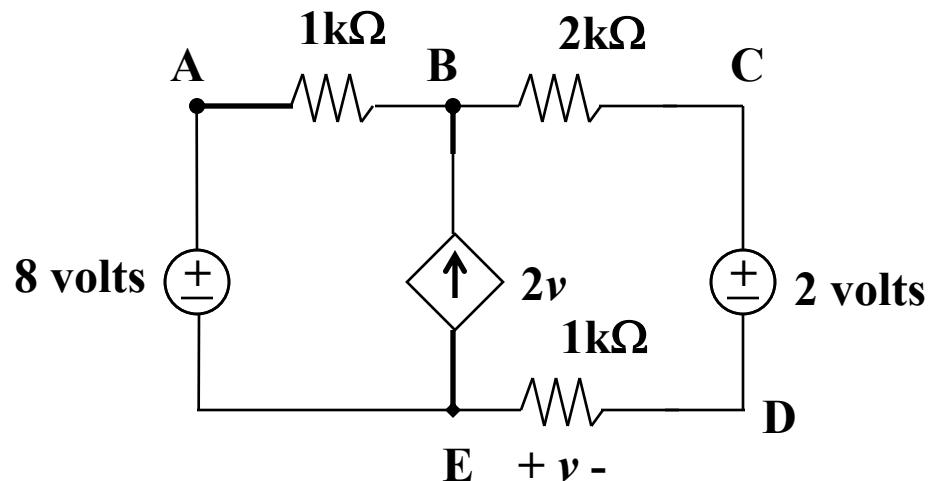
# Exercise



Find  $v$  using the loop analysis technique.




# Outline

## Textbook: Ch. 3.1-3.6

- Node (Voltage) Analysis
- Mesh (Loop) Analysis
- Linearity and Superposition Method
- Thevenin's Theorem and Norton's Theorem


# Linearity

Consider

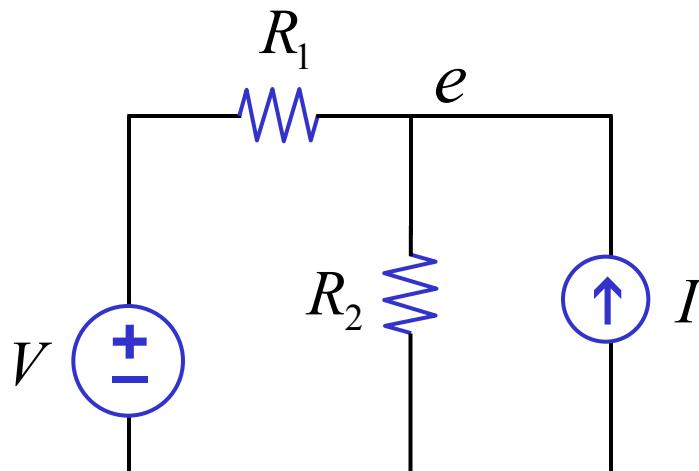

Write node equations -

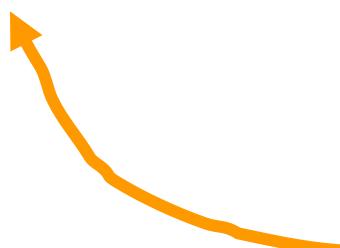
$$\frac{e-V}{R_1} + \frac{e}{R_2} - I = 0$$



Notice:  
linear in  $e, V, I$   
No  $eV, VI$   
terms

# Linearity

Consider

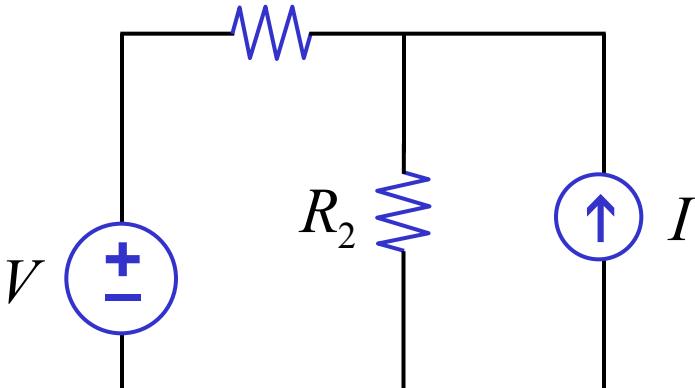

Write node equations --

$$\frac{e - V}{R_1} + \frac{e}{R_2} - I = 0 \quad \text{linear in } e, V, I$$

Rearrange --

$$\left[ \frac{1}{R_1} + \frac{1}{R_2} \right] e = \frac{V}{R_1} + I$$

conductance matrix      node voltages of sources      linear sum of sources

$$G e = S$$

Write node equations --

# Linearity

$$\frac{e-V}{R_1} + \frac{e}{R_2} - I = 0 \quad \text{linear in } e, V, I$$

Rearrange --

$$\left[ \frac{1}{R_1} + \frac{1}{R_2} \right] e = \frac{V}{R_1} + I$$

conductance matrix      node linear sum  
 voltages of sources

or

$$e = \frac{R_2}{R_1 + R_2} V + \frac{R_1 R_2}{R_1 + R_2} I$$

$$e = a_1 V_1 + a_2 V_2 + \dots + b_1 I_1 + b_2 I_2 + \dots$$

Linear!

# Linearity

Linearity  $\Rightarrow$  Homogeneity  
Superposition


Linearity  $\Rightarrow$  Homogeneity  
Superposition

■ Homogeneity




Linearity  $\Rightarrow$  Homogeneity  
Superposition

■ Superposition

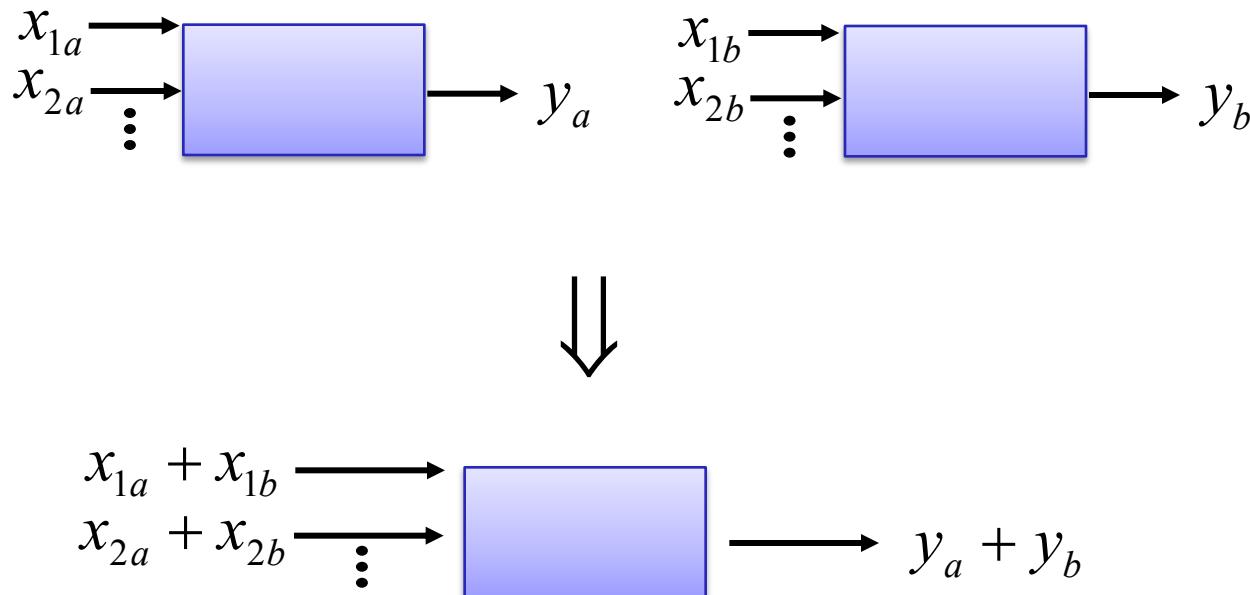

Linearity  $\Rightarrow$  Homogeneity  
Superposition

■ Specific superposition example

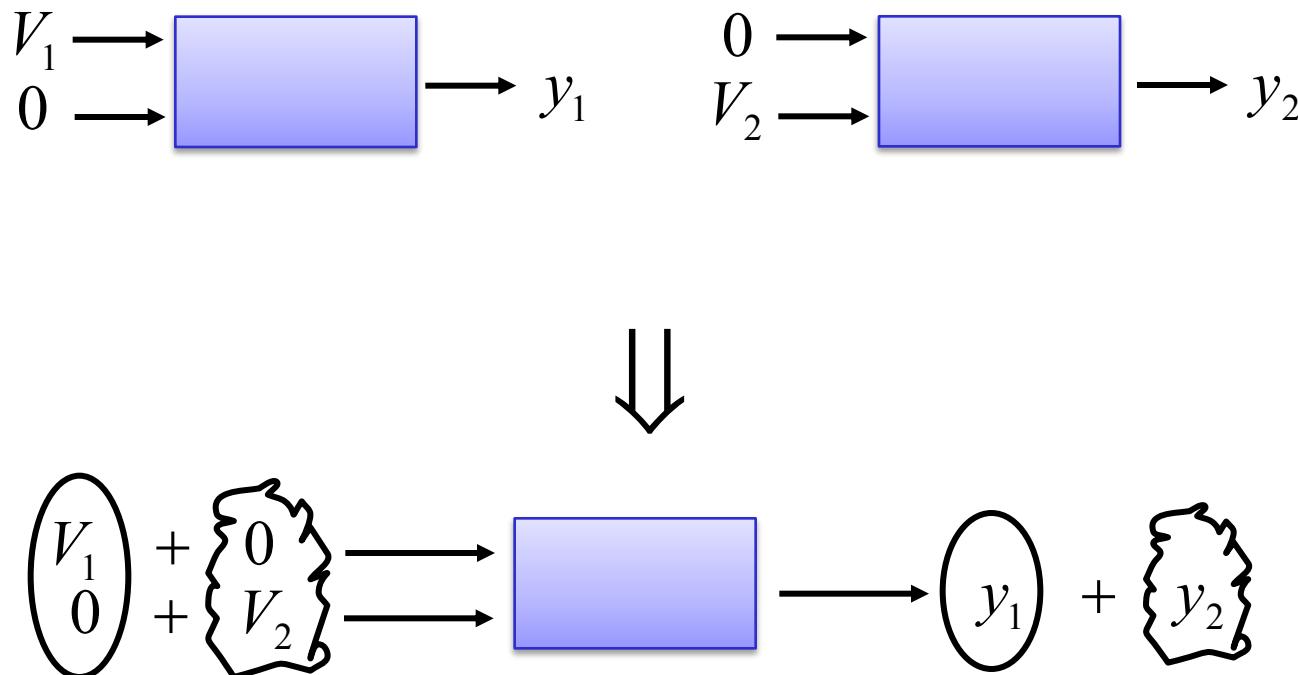

# Superposition Method (Method 4)


The output of a circuit is determined by summing the responses to each source acting alone.



independent sources  
only


# Superposition Method

## ■ Zeroing voltage and current sources

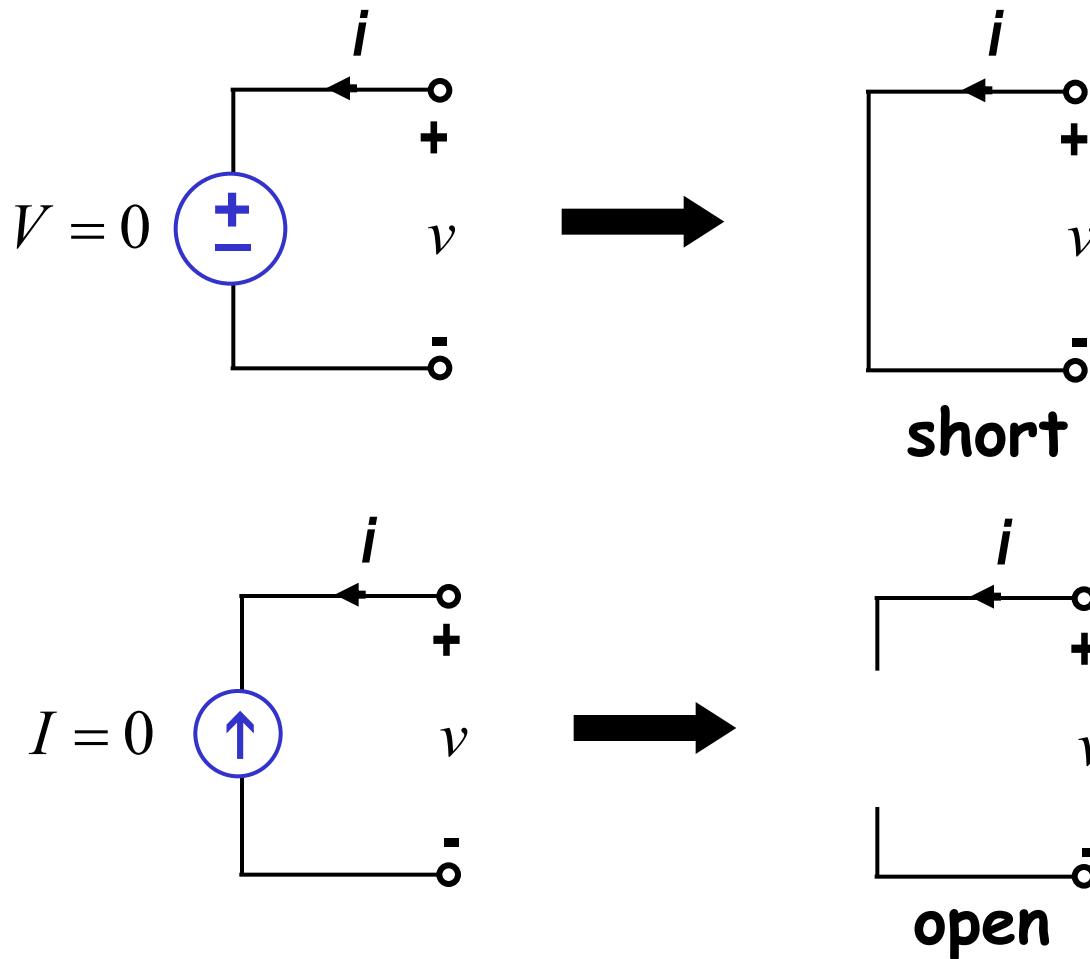

# Superposition Method


## ■ Back to the example

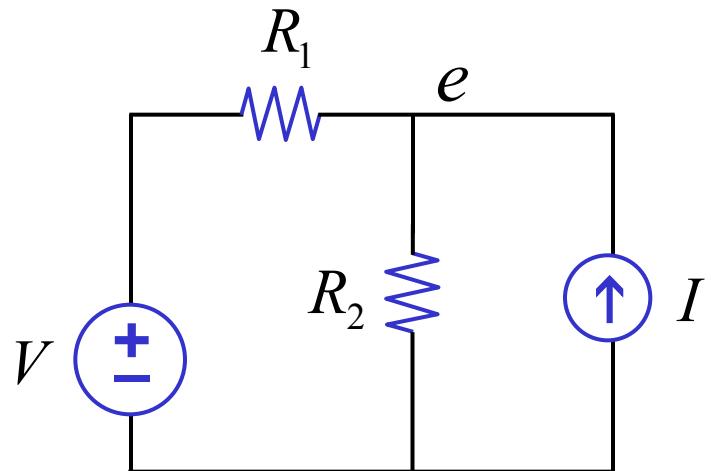


# Superposition

## Method

- Back to the example

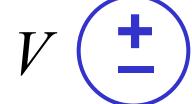
 $V$ 

*V acting alone*

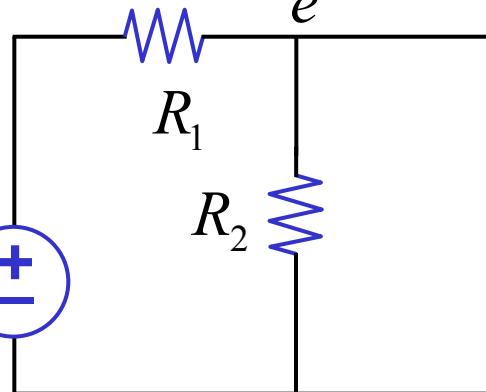

$$I = 0 \quad e_V = \frac{R_2}{R_1 + R_2} V$$

*I acting alone*

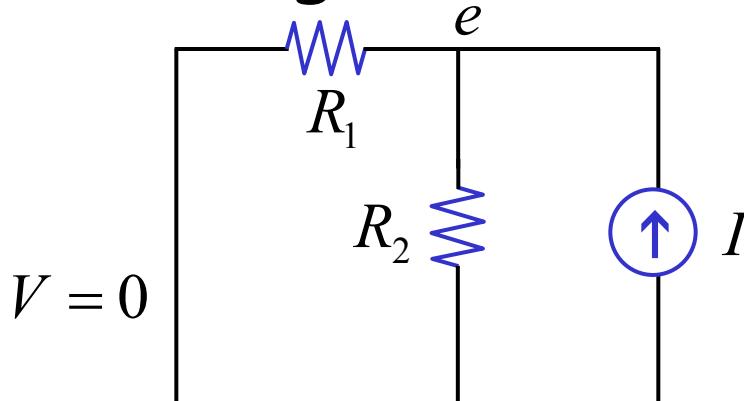


$$e_I = \frac{R_1 R_2}{R_1 + R_2} I$$


sum → superposition

$$e = e_V + e_I = \frac{R_2}{R_1 + R_2} V + \frac{R_1 R_2}{R_1 + R_2} I$$


# Exercise

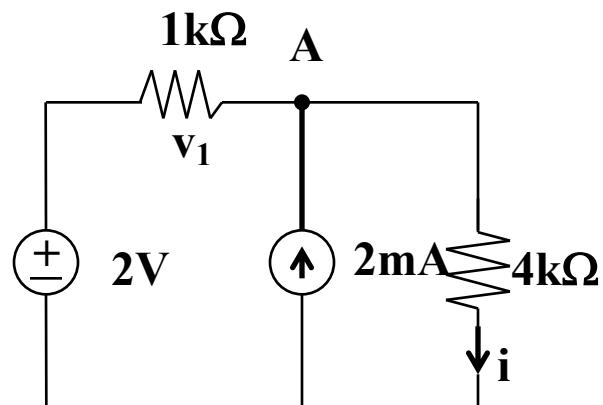

(a)

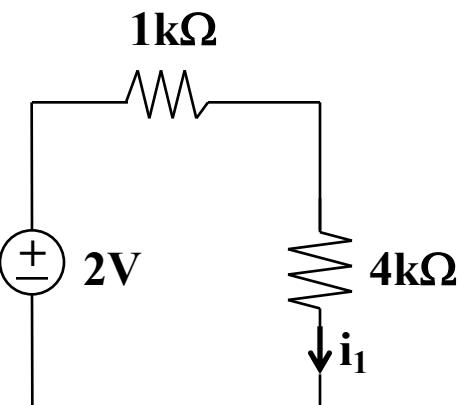


(b)

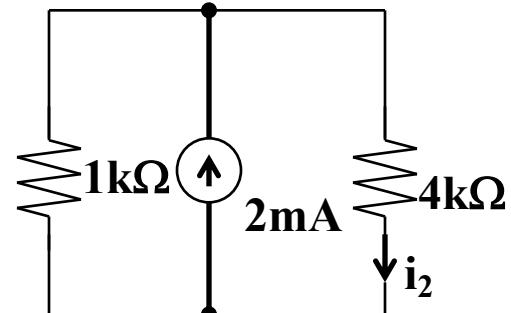


(c)

# Superposition Method


## ■ Example with controlled sources

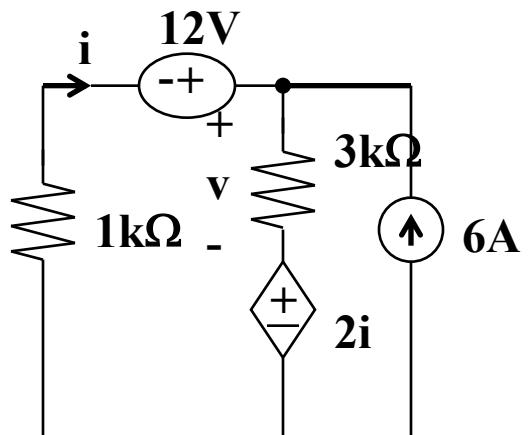

(a)

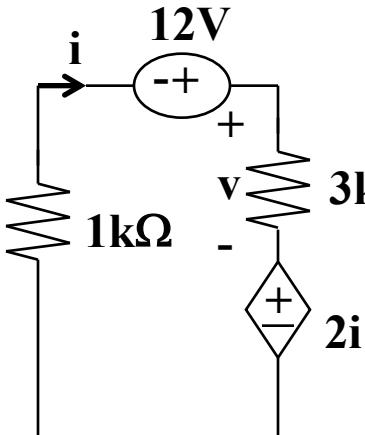

(b)

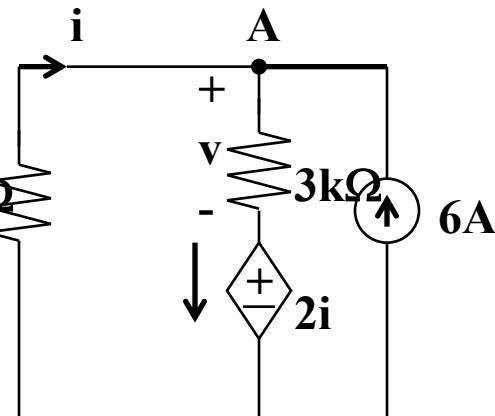

(c)

$$v = v_{(b)} + v_{(c)}$$

$$(b): 12 = 3i + 2i + i \rightarrow i = 2, v = 6$$

$$(c): i + 3(i + 6) + 2i = 0 \rightarrow i = -3, v = 9$$

# Outline


## Textbook: Ch. 3.1-3.6

- Node (Voltage) Analysis
- Mesh (Loop) Analysis
- Linearity and Superposition Method
- Thevenin's Theorem and Norton's Theorem

# Thevenin's Theorem
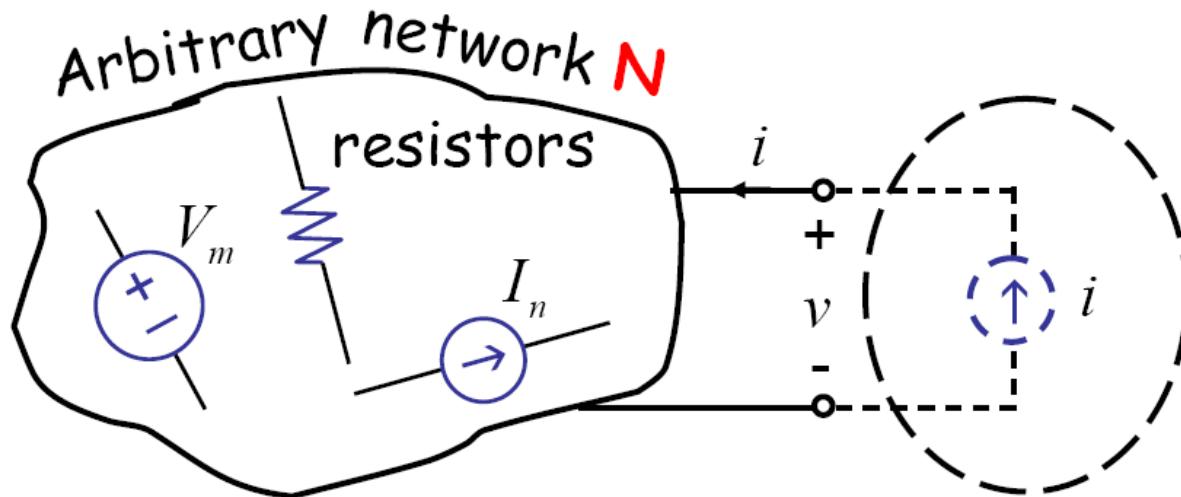
## ■ Derivation of Thevenin's network

- Thevenin's network abstracts the behavior of a linear network at a given pair of terminals as a voltage source in series with a resistor
- Consider



# Thevenin's Theorem

- Derivation of Thevenin's network

By superposition

$$v = \sum_m \alpha_m V_m + \sum_n \beta_n I_n + Ri$$


no units      resistance units      All

also independent of external excitement & behaves like a resistor

By setting

$$\begin{cases} \forall_n I_n = 0, \\ i = 0 \end{cases} \quad \begin{cases} \forall_m V_m = 0, \\ i = 0 \end{cases} \quad \begin{cases} \forall_n I_n = 0, \\ \forall_m V_m = 0 \end{cases}$$

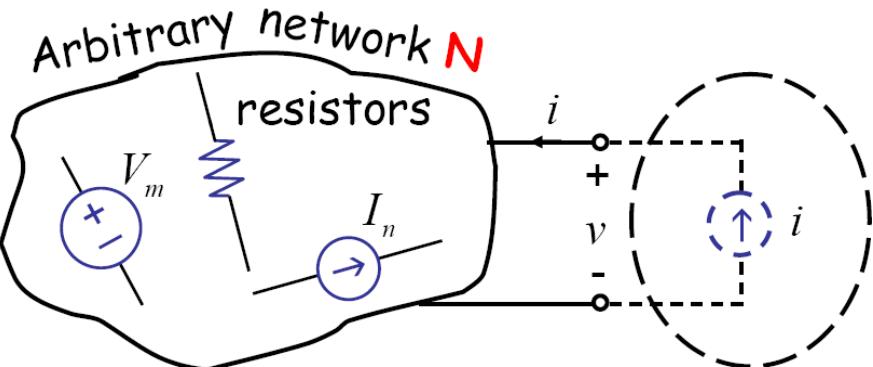independent of external excitation and behaves like a voltage " $v_{TH}$ "




# Thevenin's Theorem
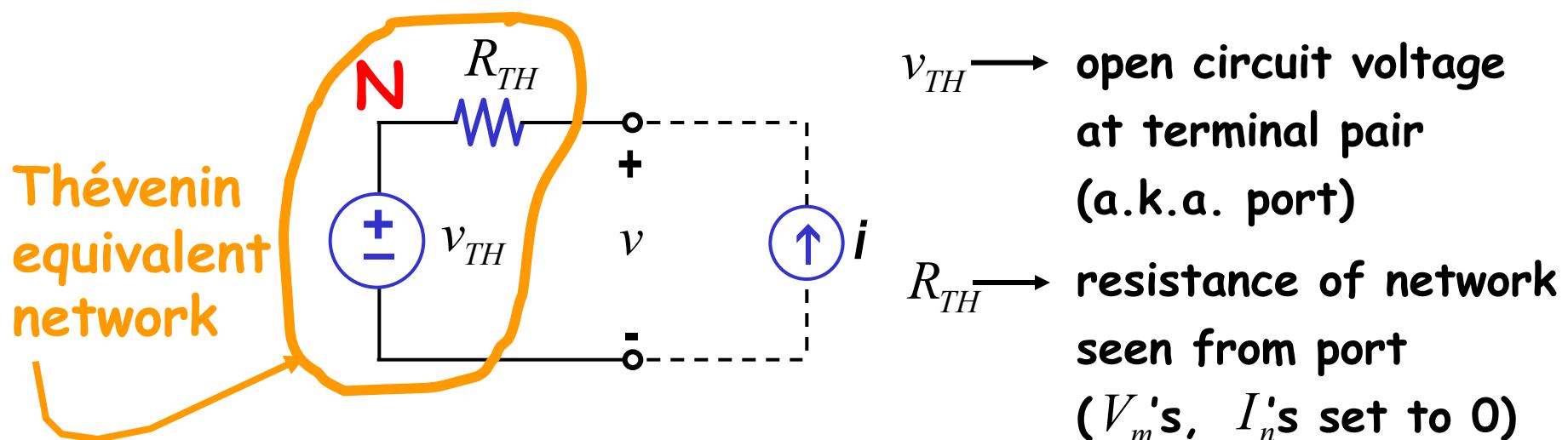
## ■ Derivation of Thevenin's network

$$v = v_{TH} + R_{TH}i$$


- As far as the external world is concerned (for the purpose of I-V relation), “Arbitrary network **N**” is indistinguishable from:


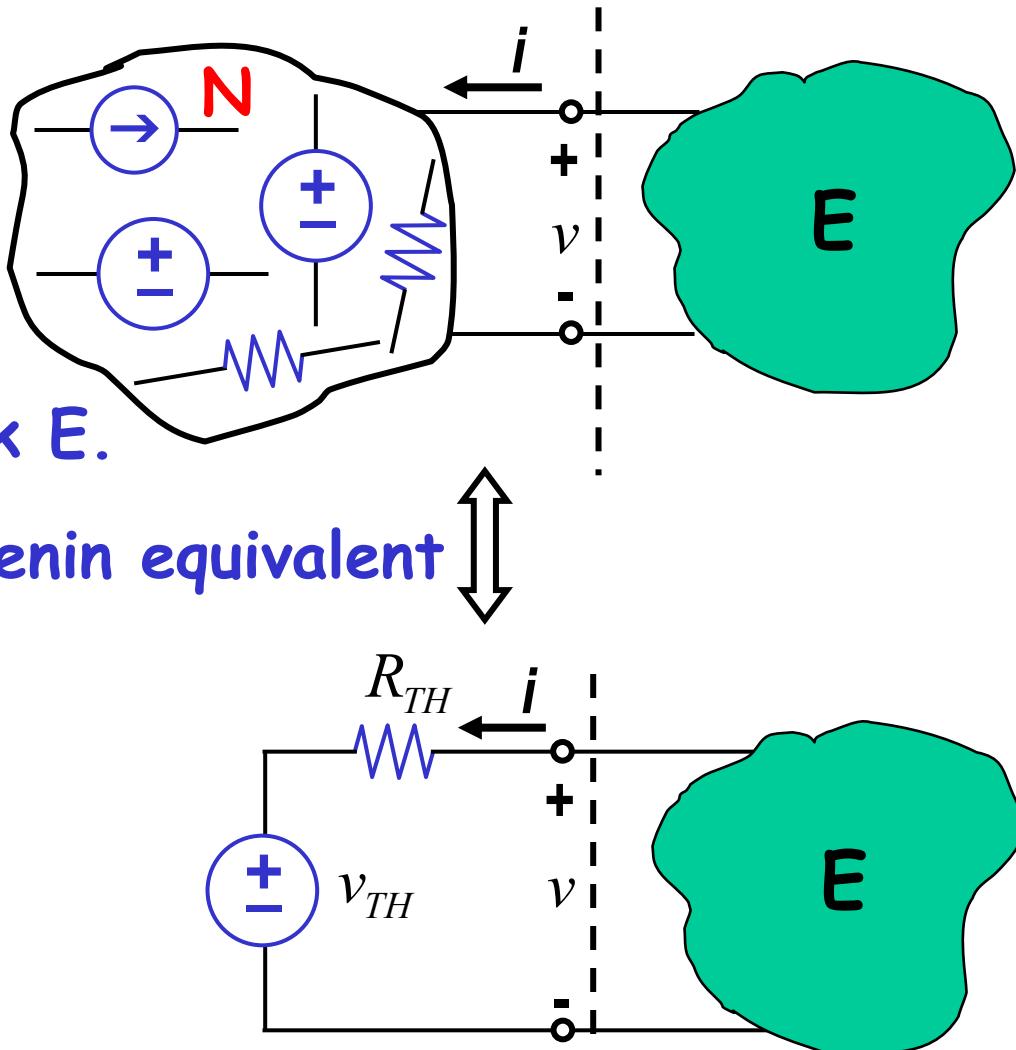
# Thevenin's Theorem



- The Thévenin Method  
(Method 5-1)

Replace network  $N$  with  
its Thévenin equivalent,  
then solve external network  $E$ .



# Thevenin's Theorem

## ■ Example

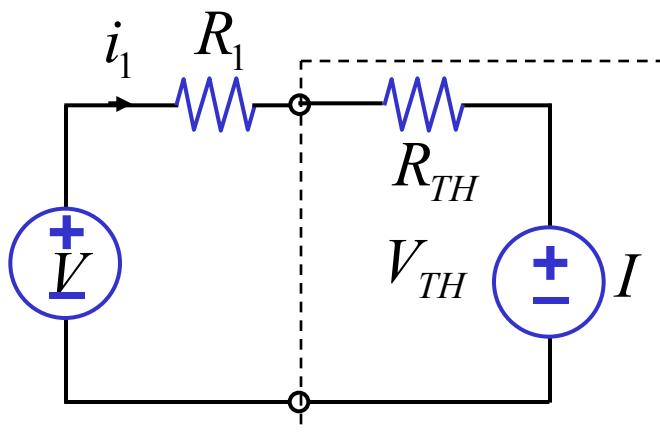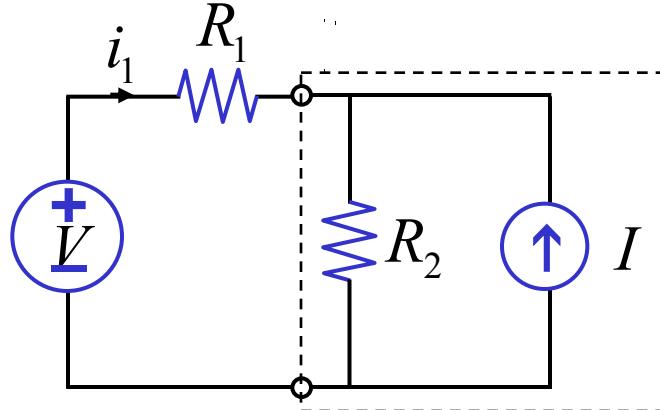


$$i_1 = \frac{V - V_{TH}}{R_1 + R_{TH}}$$

# Thevenin's Theorem

## ■ Example (Cont'd)


$V_{TH}$  :

$$V_{TH} = IR_2$$

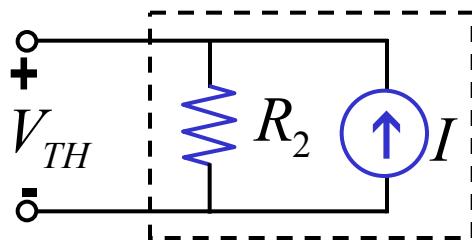

$R_{TH}$  :


$$R_{TH} = R_2$$

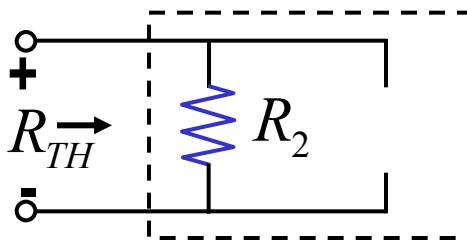

# Thevenin's Theorem

## ■ Graphical interpretation

$$v = v_{TH} + R_{TH}i$$

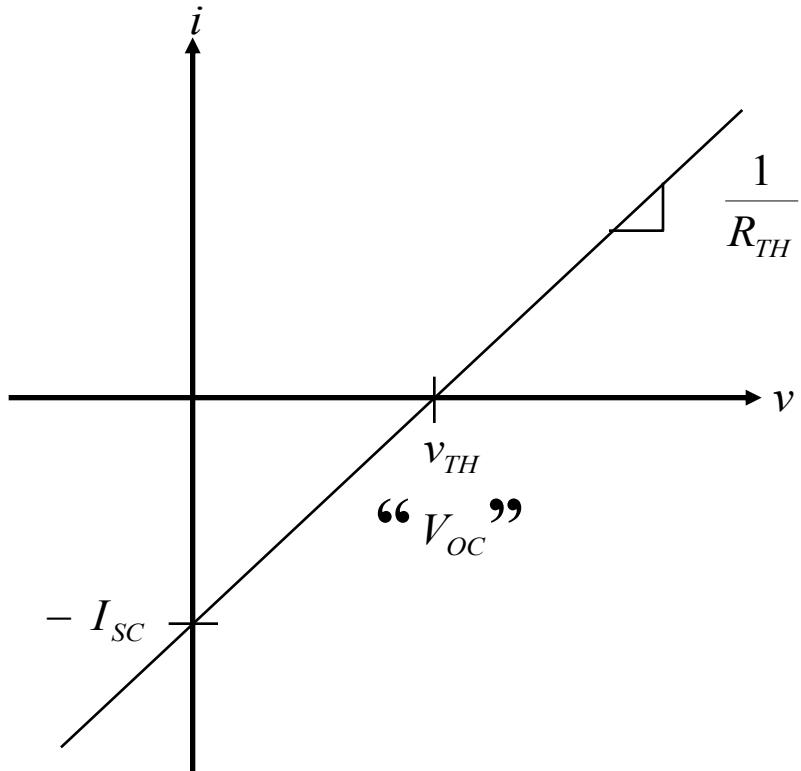

**Open circuit**  
 $(i \equiv 0)$


$$v = v_{TH} \xleftarrow{V_{OC}}$$

**Short circuit**  
 $(v \equiv 0)$

$$i = \frac{-v_{TH}}{R_{TH}} \xleftarrow{-I_{SC}}$$

# Norton's Theorem (Method 5-2)


## ■ Norton equivalent circuit

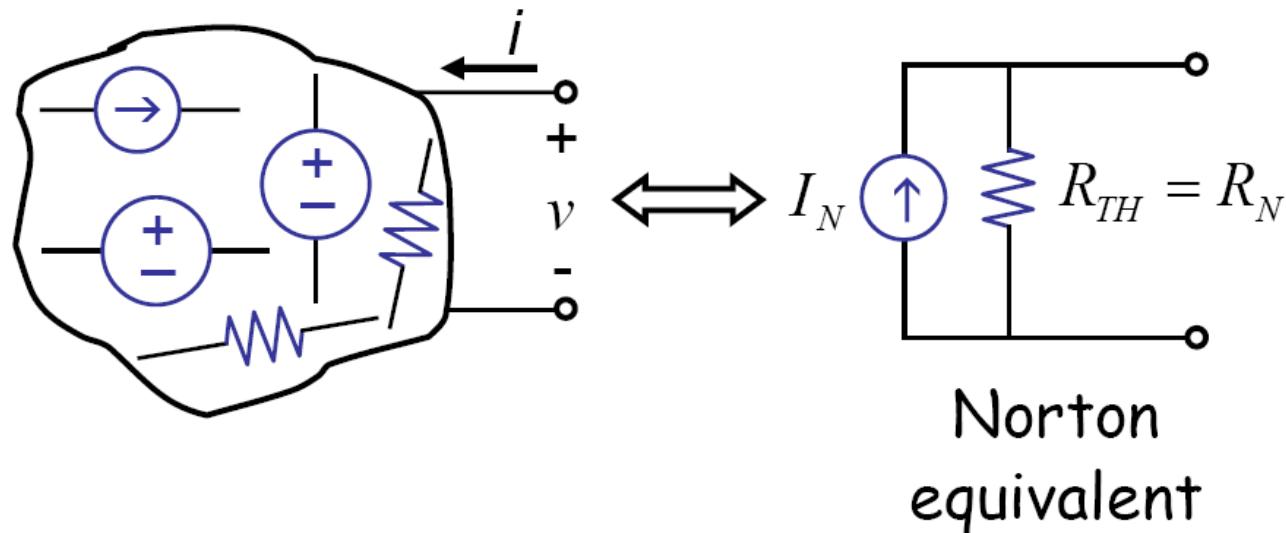

$$I_N = \frac{V_{TH}}{R_{TH}}$$

# Norton's Theorem

## ■ Illustration of Norton's Theorem

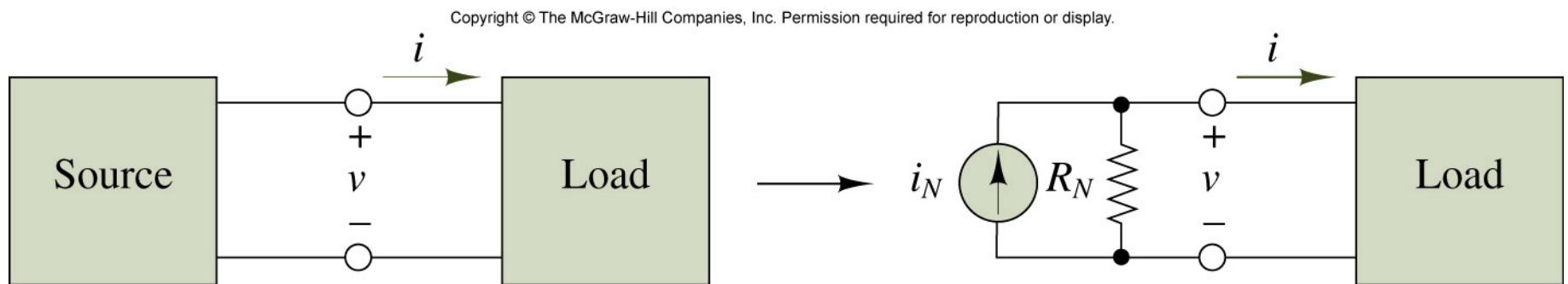


# Norton's Theorem

## ■ Computation of Norton current


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Short circuit  
replacing the load


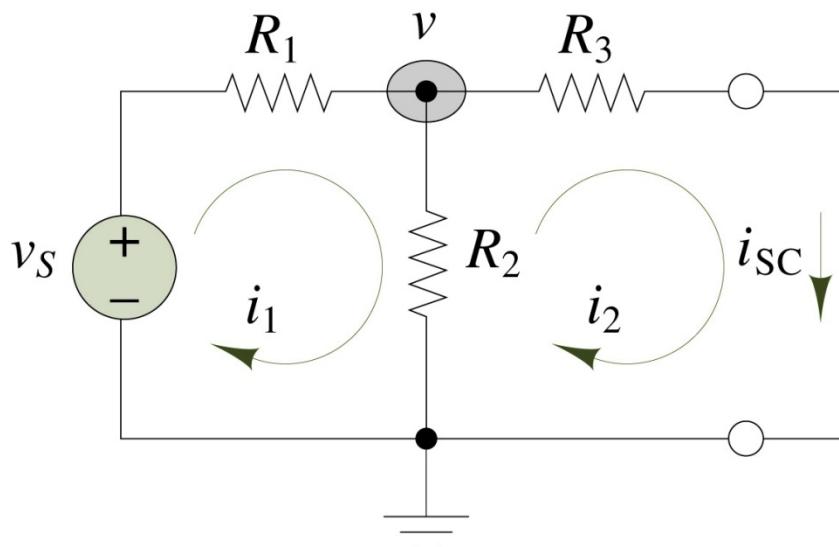


# Norton's Theorem


## ■ Example

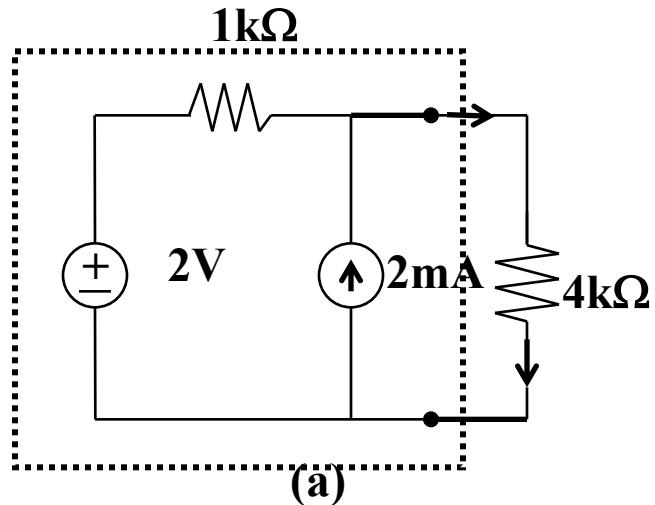

# Source Transformation

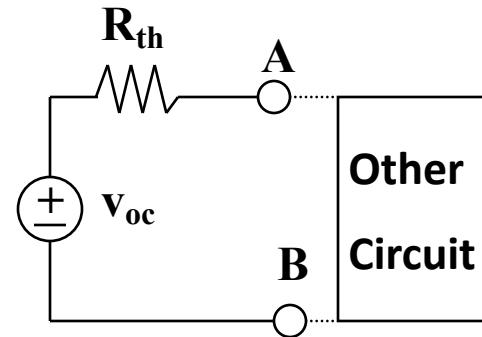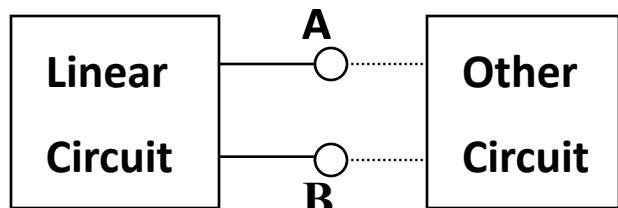


(b) Thevenin

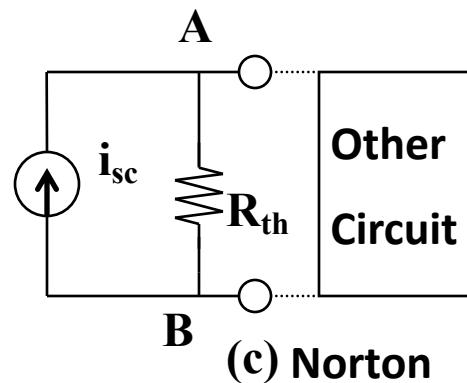


# Source Transformation
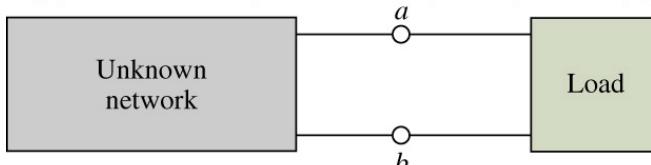
## ■ Measurement of open-circuit voltage and short-circuit current


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



An unknown network connected to a load

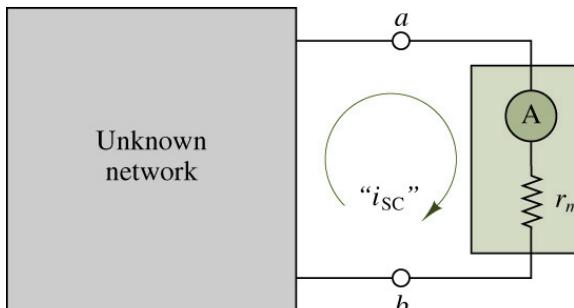

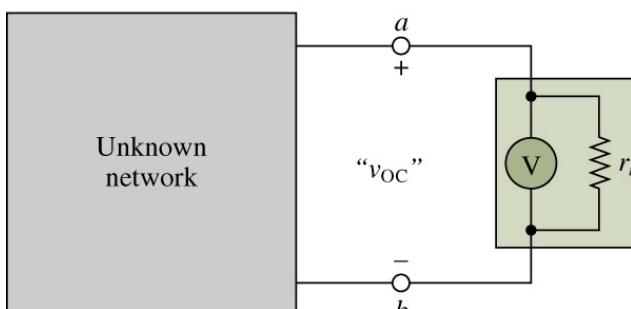Network connected for measurement of short-circuit current



Network connected for measurement of open-circuit voltage