

**V-code: ???**

# Sinusoidal Steady State: Impedance, Frequency Response, and Resonance

Lecture 16

November 22<sup>nd</sup>, 2018

Jae W. Lee ([jaewlee@snu.ac.kr](mailto:jaewlee@snu.ac.kr))


Computer Science and Engineering  
Seoul National University

*Slide credits: Prof. Anant Agarwal at MIT*

V-code: ???

# Review: Second-Order Transient

- We now understand the why of:

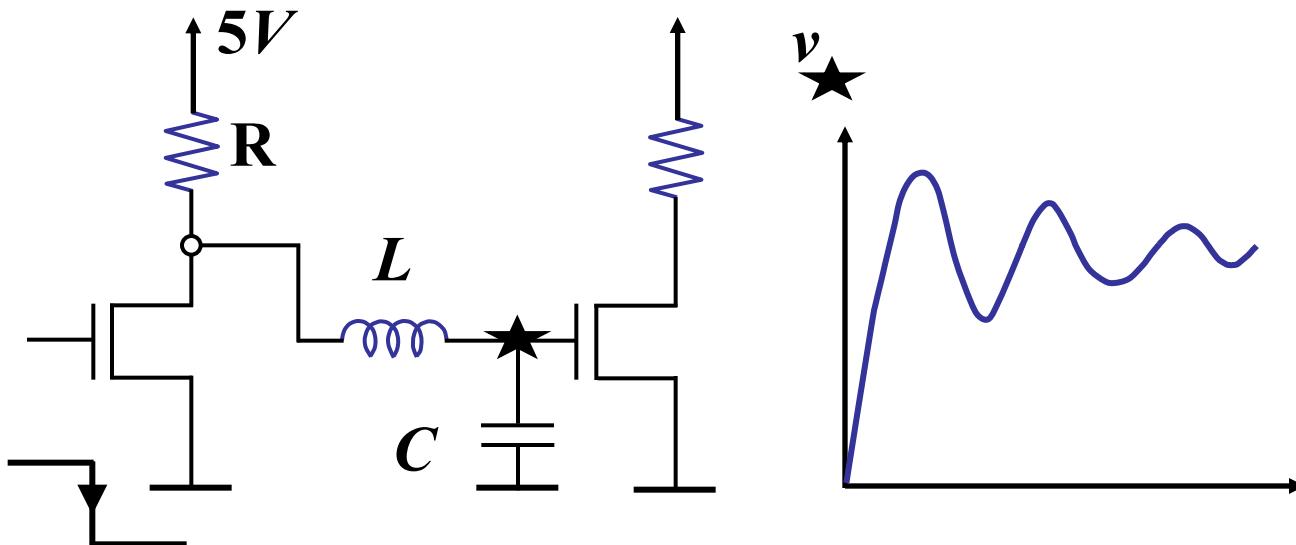

- Today, look at response of networks to sinusoidal drive.


Sinusoids important because signals can be represented as a sum of sinusoids. Response to sinusoids of various frequencies -- aka frequency response -- tells us a lot about the system

V-code: ???

# Introduction
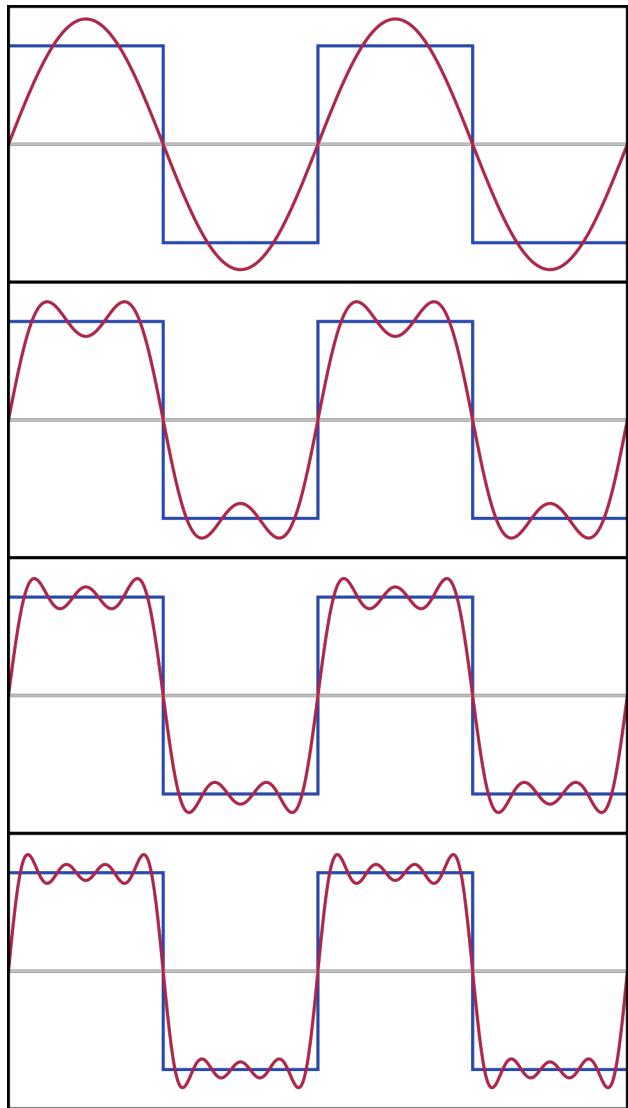
## ■ Fourier synthesis of periodic function

- Any periodic signal is a sum of discrete sinusoidal components.
- Example: Square wave
- Demo: [http://195.134.76.37/applets/  
AppletFourier/App\\_Fourier2.html](http://195.134.76.37/applets/AppletFourier/App_Fourier2.html)



Source: [https://upload.wikimedia.org/wikipedia/commons/2/2c/Fourier\\_Series.svg](https://upload.wikimedia.org/wikipedia/commons/2/2c/Fourier_Series.svg)

**V-code: ???**

# Outline


**Textbook: 13.1, 13.2, 13.3, 13.4, 13.5, 14.2, 14.3**

- **Sinusoidal Response of RC Network: Three Approaches**
- Impedance Model
- Frequency Response and Filters
- Frequency Response for Resonance Systems

V-code: ???


# Sinusoidal Response of RC Network

Example:

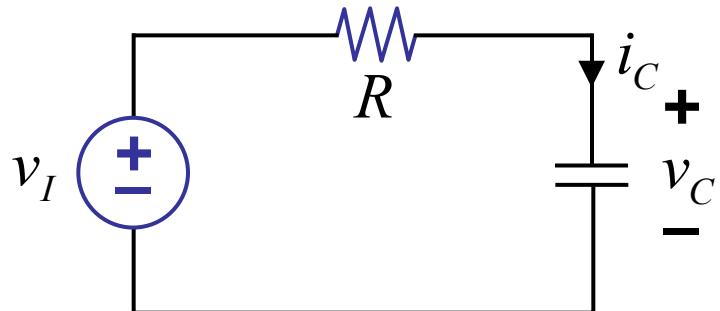



$$\begin{aligned} v_I(t) &= V_i \cos \omega t && \text{for } t \geq 0 && (V_i \text{ real}) \\ &= 0 && \text{for } t < 0 \end{aligned}$$

$$v_C(0) = 0 \quad \text{for } t = 0$$

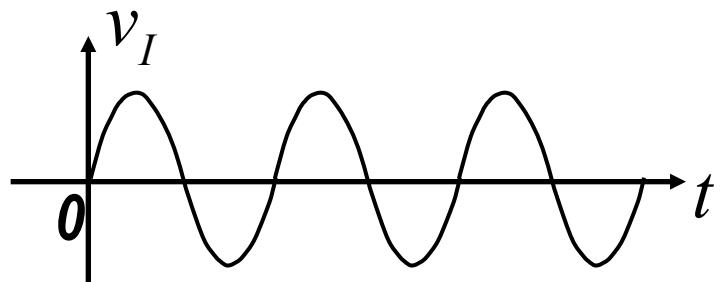
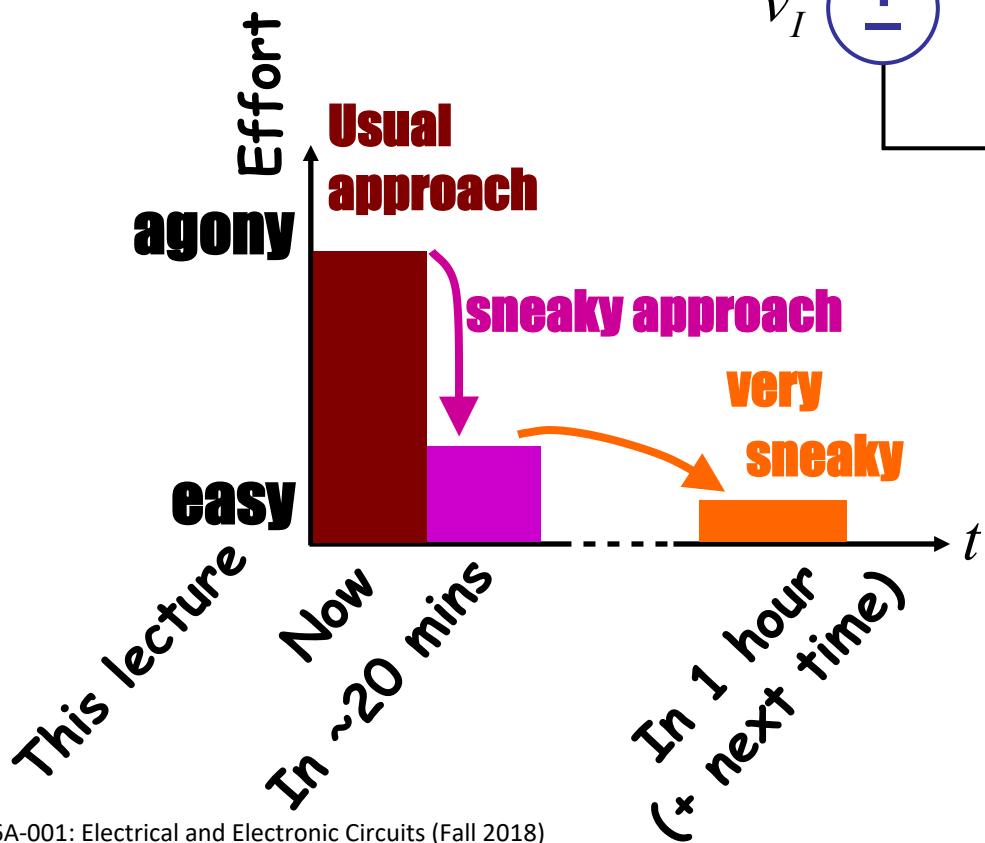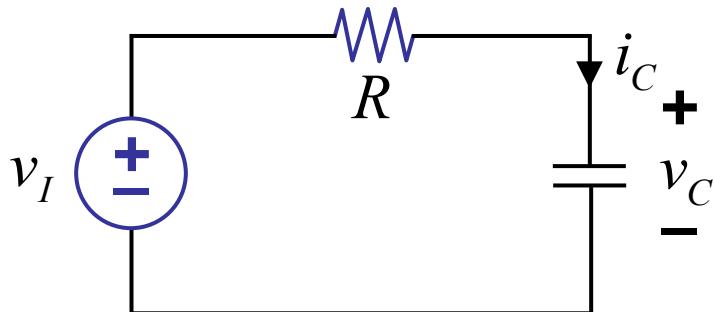
# Sinusoidal Response of RC Network

- Three approaches to determine  $v_C(t)$



# Approach 1: Usual Approach

Let's use the usual approach...

- ① Set up DE.
- ② Find  $v_p$ .
- ③ Find  $v_H$ .
- ④  $v_C = v_P + v_H$ , solve for unknowns using initial conditions

V-code: ???

# Approach 1: Usual Approach

## ① Set up DE

$$RC \frac{dv_C}{dt} + v_C = v_I \\ = V_i \cos \omega t$$

That was easy!

V-code: ???

# Approach 1: Usual Approach

② Find  $v_p$      $RC \frac{dv_P}{dt} + v_P = V_i \cos \omega t$

First try:  $v_P = A \rightarrow \text{nope}$

Second try:  $v_P = A \cos \omega t \rightarrow \text{nope}$

Third try:  $v_P = A \cos(\omega t + \phi)$

$$-RCA\omega \sin(\omega t + \phi) + A \cos(\omega t + \phi) = V_i \cos \omega t$$


$$\begin{aligned} -RCA\omega \sin \omega t \cos \phi - RCA\omega \cos \omega t \sin \phi + \\ A \cos \omega t \cos \phi - A \sin \omega t \sin \phi &= V_i \cos \omega t \end{aligned}$$

⋮    **gasp !**

**works, but trig nightmare!**

V-code: ???

# Approach 2: Sneaky Approach

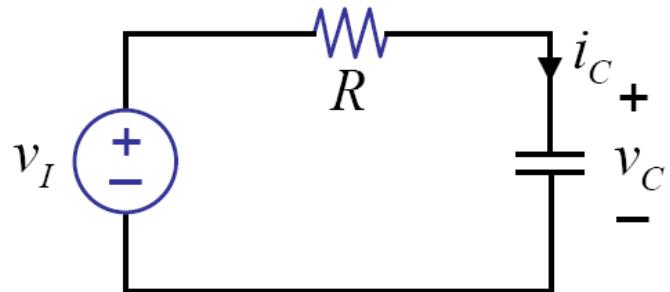

$$v_I(t) = \begin{cases} V_i \cos \omega t & \text{for } t \geq 0 \\ 0 & \text{for } t < 0 \end{cases} \quad (V_i \text{ real})$$

$$v_C(0) = 0 \quad \text{for } t = 0$$

$$v_I(t) = V_i \frac{e^{j\omega t} + e^{-j\omega t}}{2}$$

Find the particular solution to (fake input)  $V_i e^{j\omega t}$

V-code: ???

# Approach 2: Sneaky Approach

Let's get sneaky!

Find particular solution to another input...

$$RC \frac{dv_{PS}}{dt} + v_{PS} = v_{IS}$$

(s: sneaky :-))

$$= V_i e^{st}$$

Try solution  $v_{PS} = V_p e^{st}$

$$RC \frac{dV_p e^{st}}{dt} + V_p e^{st} = V_i e^{st}$$

$$\cancel{sRCV_p e^{st}} + V_p e^{st} = V_i e^{st}$$

$$(sRC + 1)V_p = V_i$$

Nice  
property  
of  
exponentials

$$V_p = \frac{V_i}{1 + sRC}$$

V-code: ???

# Approach 2: Sneaky Approach

Let's get sneaky! (Cont'd)

Thus,  $v_{PS} = \frac{V_i}{1 + sRC} \cdot e^{st}$



is particular solution to  $V_i e^{st}$

Similarly

$$\frac{V_i}{1 + j\omega RC} \cdot e^{j\omega t} \rightarrow \text{solution for } V_i e^{j\omega t}$$

where we replace  $s = j\omega$



$V_p$  → complex amplitude

V-code: ???

# Approach 2: Sneaky Approach

② Fourth try to find  $v_P$ ...

using the sneaky approach

Fact 1: Finding the response to

$$V_i e^{j\omega t}$$

was easy.

Fact 2:  $v_I = V_i \cos \omega t$

$$= \text{real}[V_i e^{j\omega t}] = \text{real}[v_{IS}]$$


from Euler relation,

$$e^{j\omega t} = \cos \omega t + j \sin \omega t$$

# Approach 2: Sneaky Approach

② Fourth try to find  $v_P$ ...

using the sneaky approach (cont'd)

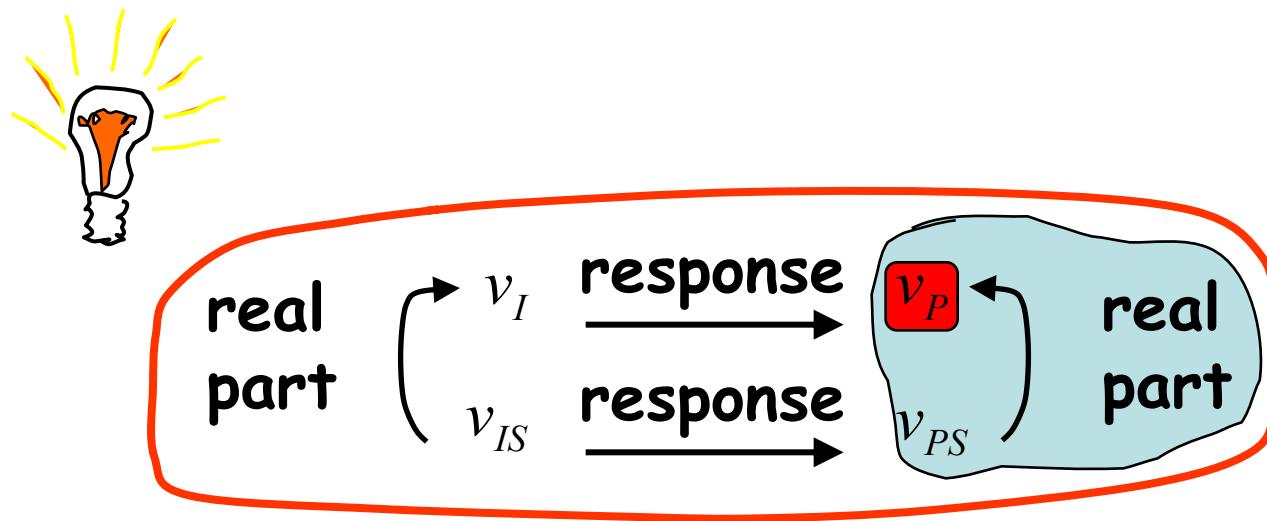

an inverse superposition argument,  
assuming system is real, linear.

V-code: ???

# Approach 2: Sneaky Approach

② Fourth try to find  $v_P$ ...

so,

 complex

$$\begin{aligned}
 v_P &= \operatorname{Re}[v_{PS}] = \operatorname{Re}[V_p e^{j\omega t}] \\
 &= \operatorname{Re}\left[\frac{V_i}{1 + j\omega RC} \cdot e^{j\omega t}\right] \\
 &= \operatorname{Re}\left[\frac{V_i(1 - j\omega RC)}{1 + \omega^2 R^2 C^2} \cdot e^{j\omega t}\right] \\
 &= \operatorname{Re}\left[\frac{V_i}{\sqrt{1 + \omega^2 R^2 C^2}} \cdot e^{j\phi} e^{j\omega t}\right], \tan \phi = -\omega RC \\
 &= \operatorname{Re}\left[\frac{V_i}{\sqrt{1 + \omega^2 R^2 C^2}} \cdot e^{j(\omega t + \phi)}\right]
 \end{aligned}$$

$$v_P = \frac{V_i}{\sqrt{1 + \omega^2 R^2 C^2}} \cdot \cos(\omega t + \phi)$$

Recall,  $v_P$  is particular response to  $V_i \cos \omega t$ .

**V-code: ???**

# Approach 2: Sneaky Approach

③ Find  $v_H$

Recall,  $v_H = Ae^{\frac{-t}{RC}}$

V-code: ???

# Approach 2: Sneaky Approach

## ④ Find total solution

$$v_C = v_P + v_H$$

$$v_C = \frac{V_i}{\sqrt{1 + \omega^2 R^2 C^2}} \cos(\omega t + \phi) + A e^{-\frac{t}{RC}}$$

where  $\phi = \tan^{-1}(-\omega RC)$

**Given**  $v_C(0) = 0$  for  $t = 0$

so,

$$A = -\frac{V_i}{\sqrt{1 + \omega^2 R^2 C^2}} \cos(\phi)$$

**Done!** *Phew!*

V-code: ???

# Sinusoidal Steady State

We are usually interested only in the particular solution for sinusoids,  
i.e. after transients have died.

Notice when  $t \rightarrow \infty$ ,  $v_C \rightarrow v_P$  as  $e^{-\frac{t}{RC}} \rightarrow 0$

$$v_C = \frac{V_i}{\sqrt{1 + \omega^2 R^2 C^2}} \cos(\omega t + \phi) + A e^{-\frac{t}{RC}}$$

where  $\phi = \tan^{-1}(-\omega RC)$

$$A = -\frac{V_i}{\sqrt{1 + \omega^2 R^2 C^2}} \cos(\phi)$$

Described as

**SSS: Sinusoidal Steady State**



V-code: ???

# Sinusoidal Steady State

All information about SSS is contained in  , the complex amplitude!

Recall

$$\begin{array}{c} \textcolor{red}{\triangle} \\ V_p \end{array} = \frac{V_i}{1 + j\omega RC}$$

Steps ③ ④  
were a waste of time!

$$\frac{V_p}{V_i} = \frac{1}{1 + j\omega RC}$$

$$\frac{V_p}{V_i} = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}} e^{j\phi}$$

where

$$\phi = \tan^{-1} - \omega RC$$


**magnitude**  $\left| \frac{V_p}{V_i} \right| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$

phase  $\phi$ :  $\angle \frac{V_p}{V_i} = -\tan^{-1} \omega RC$

V-code: ???
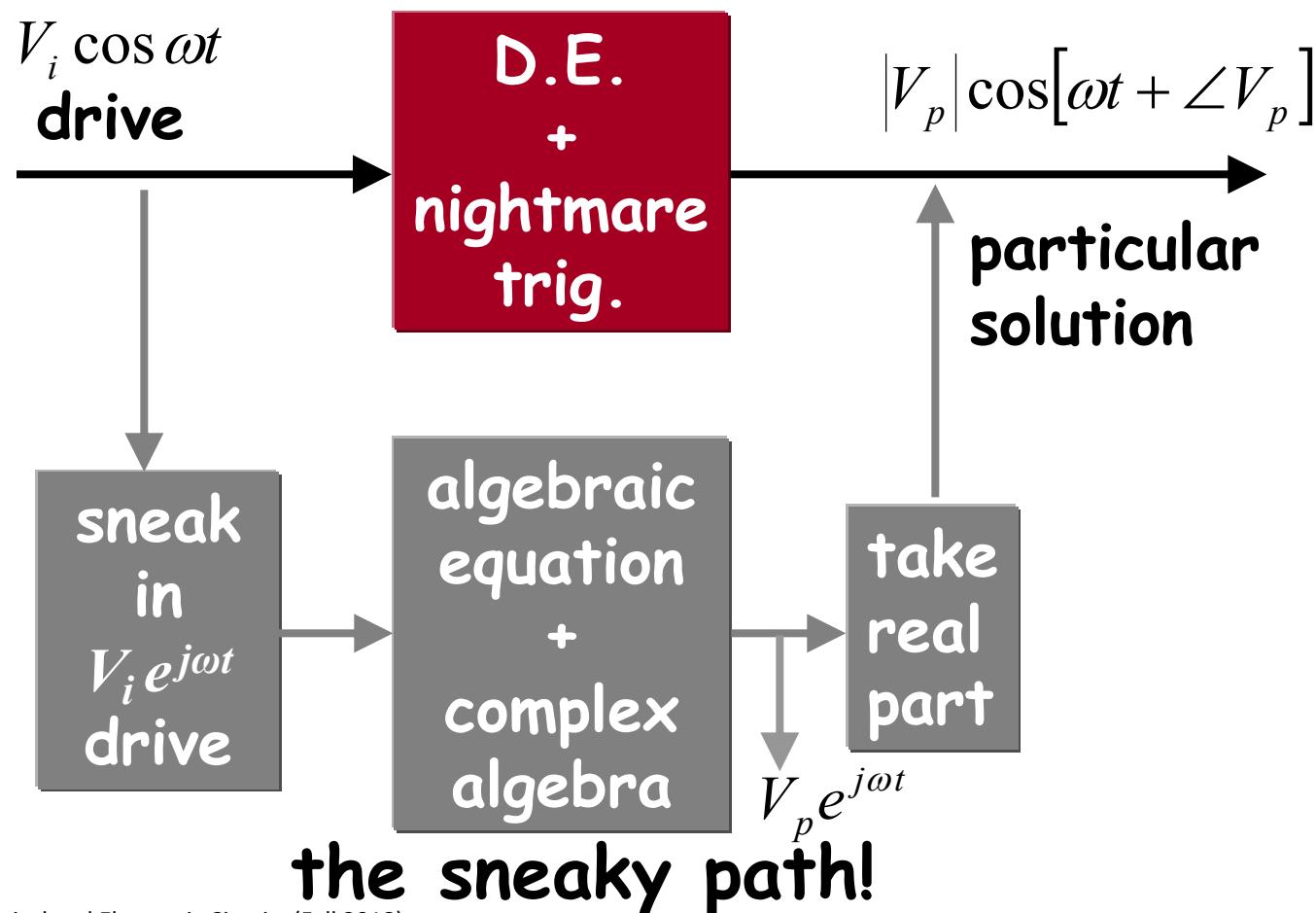
# Sinusoidal Steady State

Visualizing the process of finding the particular solution  $v_P$



V-code: ???


# Sinusoidal Steady State

## Magnitude Plot

transfer function

$$H(j\omega) = \frac{V_p}{V_i}$$


$$\left| \frac{V_p}{V_i} \right| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

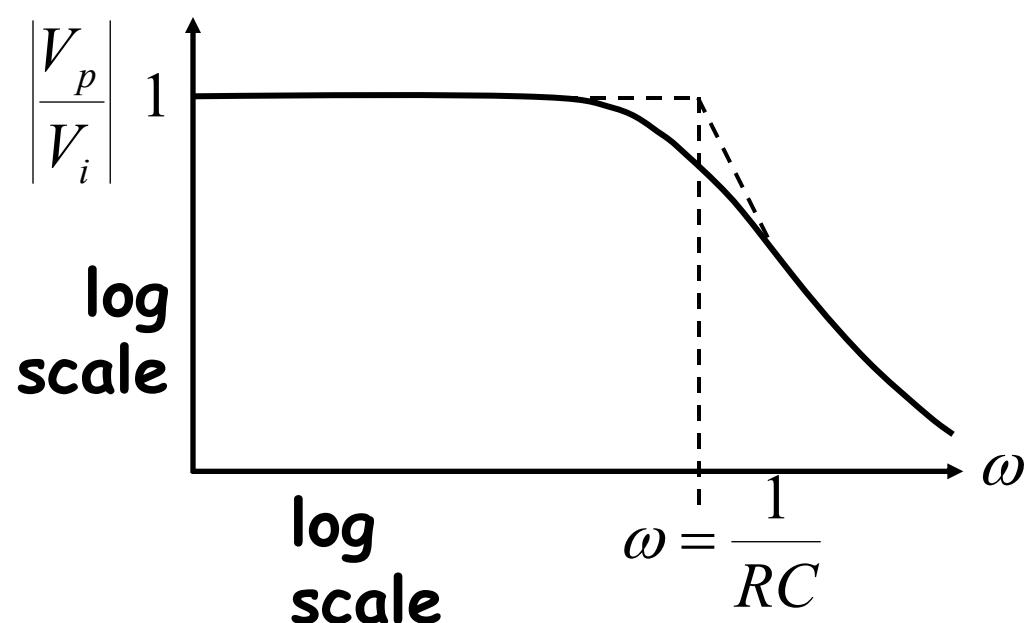

# Sinusoidal Steady State

## Phase Plot

$$\phi = \tan^{-1} - \omega RC$$

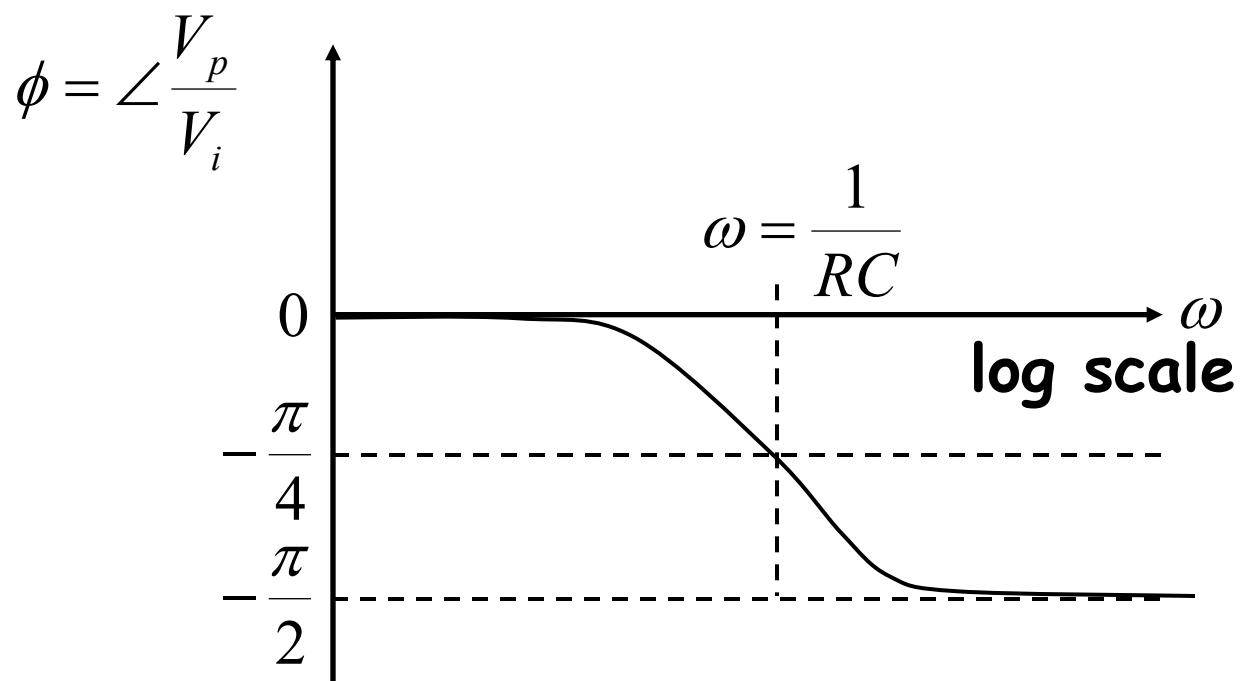

**V-code: ???**


# Outline

**Textbook: 13.1, 13.2, 13.3, 13.4, 13.5, 14.2, 14.3**

- Sinusoidal Response of RC Network: Three Approaches
- Impedance Model
- Frequency Response and Filters
- Frequency Response for Resonance Systems

# Review

## ■ Sinusoidal Steady State (SSS)

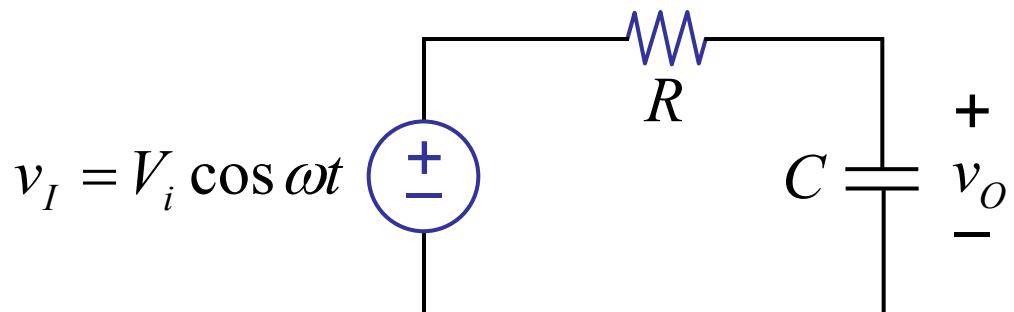


SSS

- Focus on steady state, only care about  $v_P$  as  $v_H$  dies away.
- Focus on sinusoids.

# Review

# V-code: ???

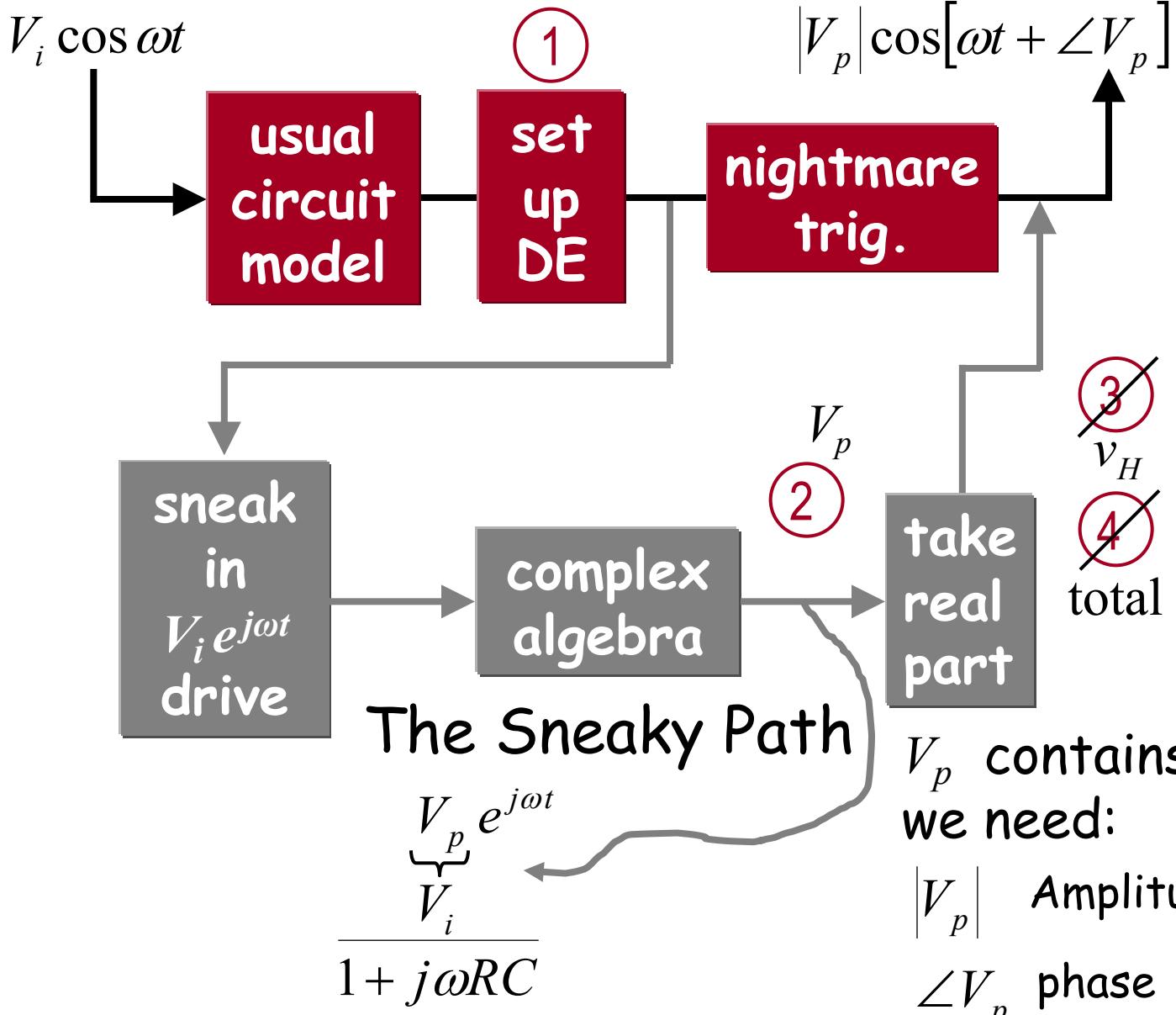

$V_p$  contains all the info we need:

$|V_p|$  Amplitude of output cosine  
 $\angle V_p$  phase


# Review

V-code: ???

$$v_o = |V_p| \cos(\omega t + \angle V_p)$$

$$\frac{V_p}{V_i} = \frac{1}{1 + j\omega RC} = H(j\omega)$$

transfer  
function

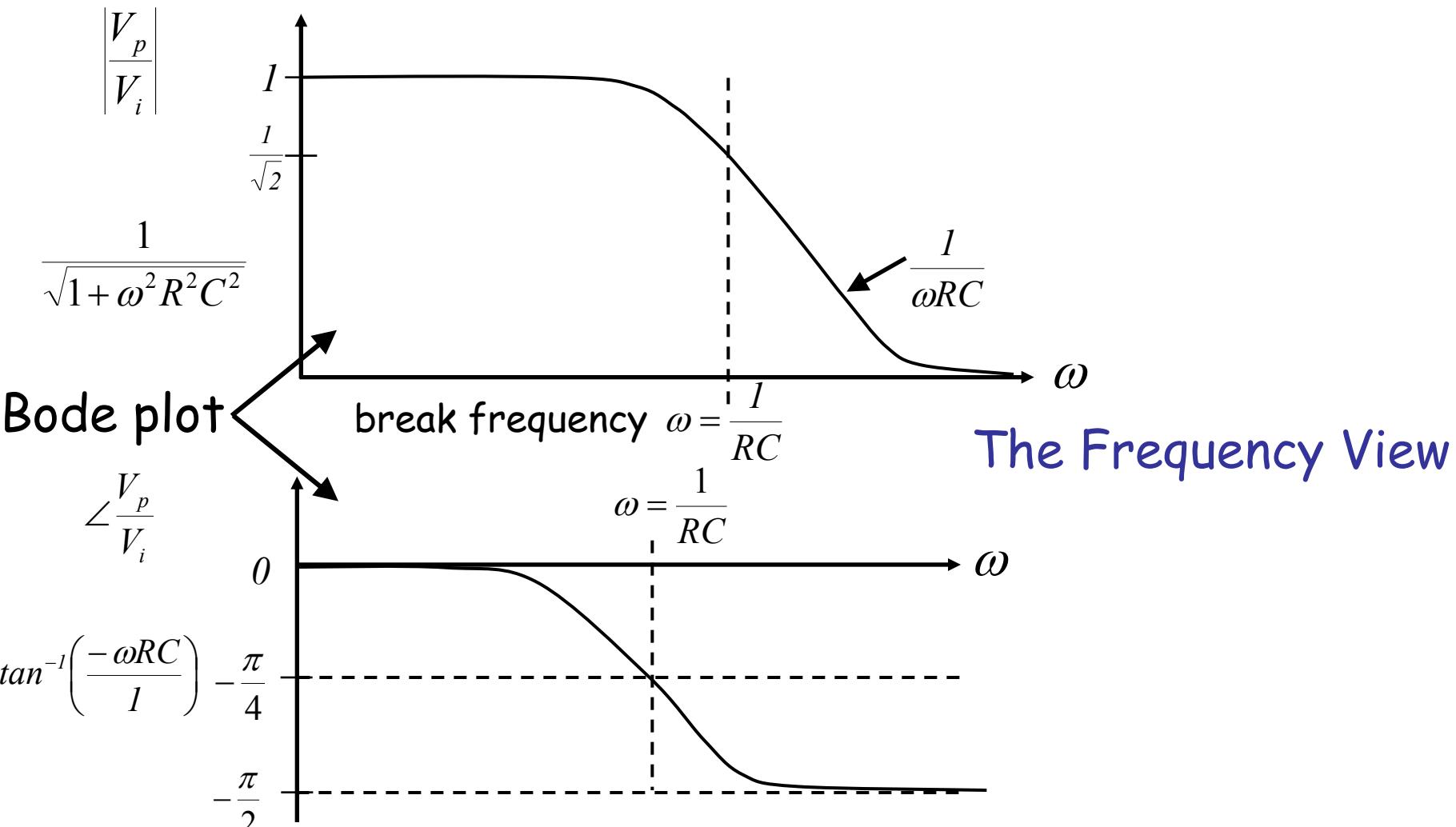

V-code: ???

# Approach 3: Impedance Model

Is there an even simpler way to get  $V_p$ ?

$$V_p = \frac{V_i}{1 + j\omega RC}$$

Divide numerator and denominator by  $j\omega C$ .

$$V_p = V_i \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R}$$

Hmmm... looks like a voltage divider relationship.


$$V_p = V_i \frac{Z_C}{Z_C + R}$$

Let's explore further...

# Approach 3: Impedance Model

V-code: ???

Consider:

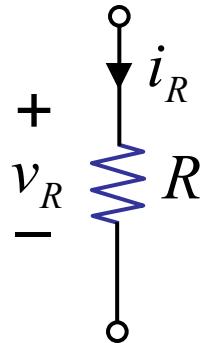

$$i_R = I_r e^{j\omega t}$$


$$v_R = V_r e^{j\omega t}$$

$$v_R = R i_R$$

$$V_r e^{j\omega t} = R I_r e^{j\omega t}$$

$$V_r = R I_r$$

**Resistor**

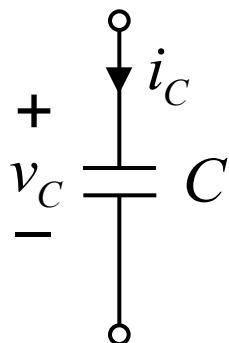

$$i_C = I_C e^{j\omega t}$$


$$v_C = V_C e^{j\omega t}$$

$$i_C = C \frac{dv_C}{dt}$$

$$I_C e^{j\omega t} = C V_C j \omega e^{j\omega t}$$

$$V_C = \frac{1}{j \omega C} I_C$$

**Capacitor**

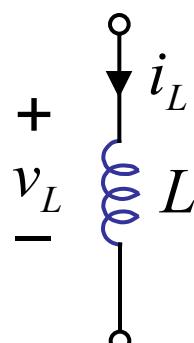

$$i_L = I_l e^{j\omega t}$$

$$v_L = V_l e^{j\omega t}$$

$$v_L = L \frac{di_L}{dt}$$

$$V_l e^{j\omega t} = L I_l j \omega e^{j\omega t}$$

**Inductor**


$$V_l = j \omega L I_l$$

# Approach 3: Impedance Model

V-code: ???

In other words,

capacitor

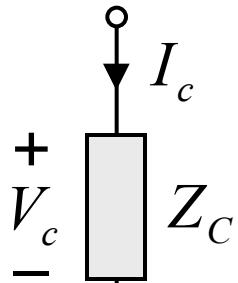


$$V_c = Z_C I_c$$

$$Z_C = \frac{1}{j\omega C}$$

impedance


inductor

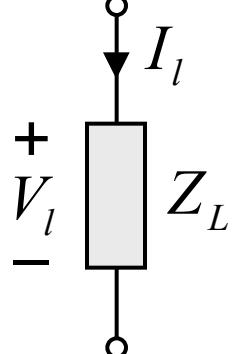

$$V_l = Z_l I_l$$

$$Z_l = j\omega L$$

resistor

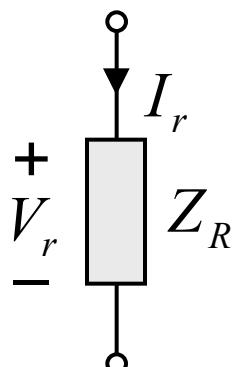

$$V_r = Z_r I_r$$

$$Z_r = R$$



For a drive of the form  $V_c e^{j\omega t}$ , complex amplitude  $V_c$  is related to the complex amplitude  $I_c$  algebraically, by a generalization of Ohm's Law.

V-code: ???

# Approach 3: Impedance Model

**Back to RC example...**

Impedance model:

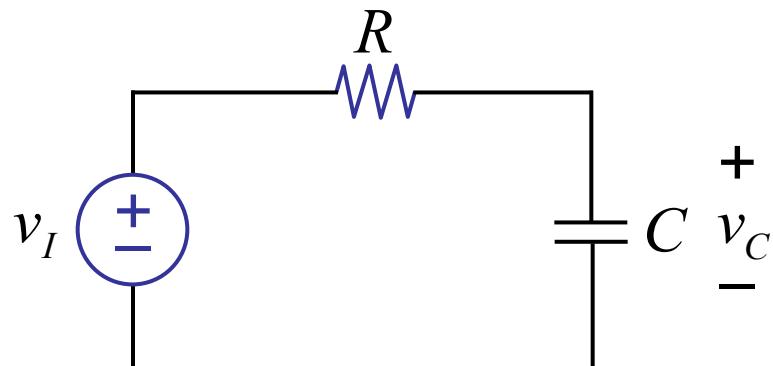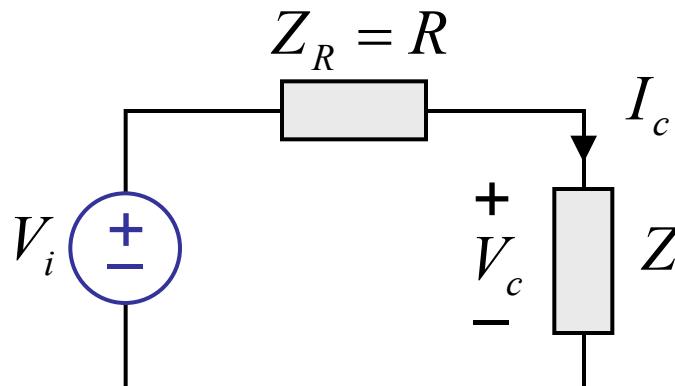

$$Z_C = \frac{1}{j\omega C}$$

$$V_c = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} V_i = \frac{Z_C}{Z_C + Z_R} V_i$$

$$V_c = \frac{1}{1 + j\omega RC} V_i$$

**Done!**


All our old friends apply!  
KVL, KCL, superposition...

V-code: ???

# Approach 3: Impedance Model

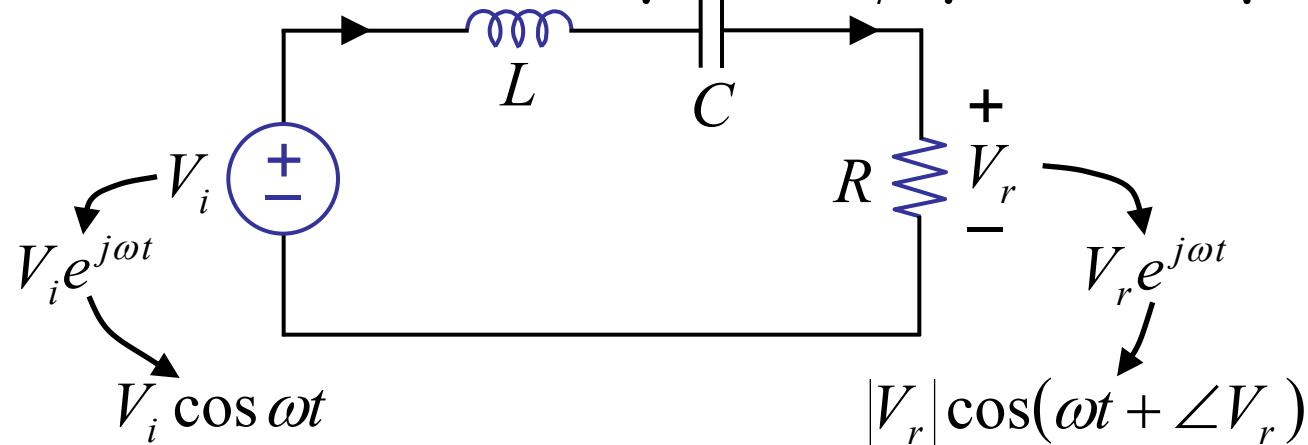**Another example, recall series RLC:**

Remember, we want only the steady-state response to sinusoid



$$V_r = \frac{V_i Z_R}{Z_L + Z_C + Z_R}$$


$$V_r = \frac{V_i R}{j\omega L + \frac{1}{j\omega C} + R} \quad \rightarrow \quad V_r = \frac{V_i j\omega CR}{-\omega^2 LC + 1 + j\omega CR}$$

We will study this and other functions in more detail in the next lecture.

V-code: ???

# Approach 3: Impedance Model

## ■ Exercise 1

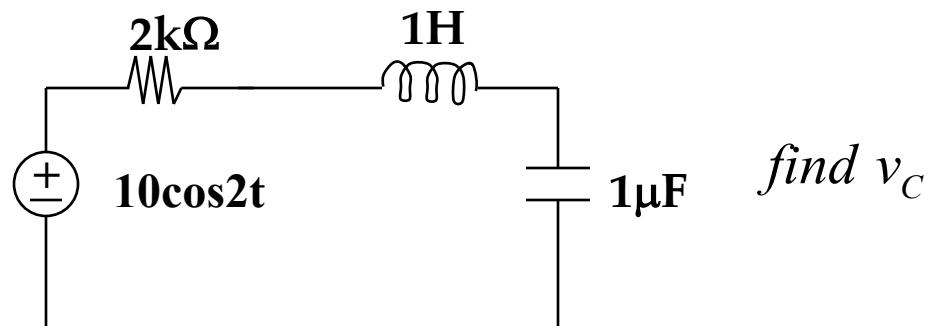


# Notation for Voltages and Currents

## ■ We abide by the international standard!

- ▶ DC or operating-point variables: uppercase symbols with uppercase subscripts (for example,  $V_A$ )
- ▶ Total instantaneous variables: lowercase symbols with uppercase subscripts (for example,  $v_A$ )
- ▶ Incremental instantaneous variables: lowercase symbols with lowercase subscripts (for example,  $v_a$ )
- ▶ Complex amplitudes or complex amplitudes of incremental components, and real amplitudes of sinusoidal input sources: uppercase symbols with lowercase subscripts (for example,  $V_a$ )

# Approach 3: Impedance Model

## The Big Picture...

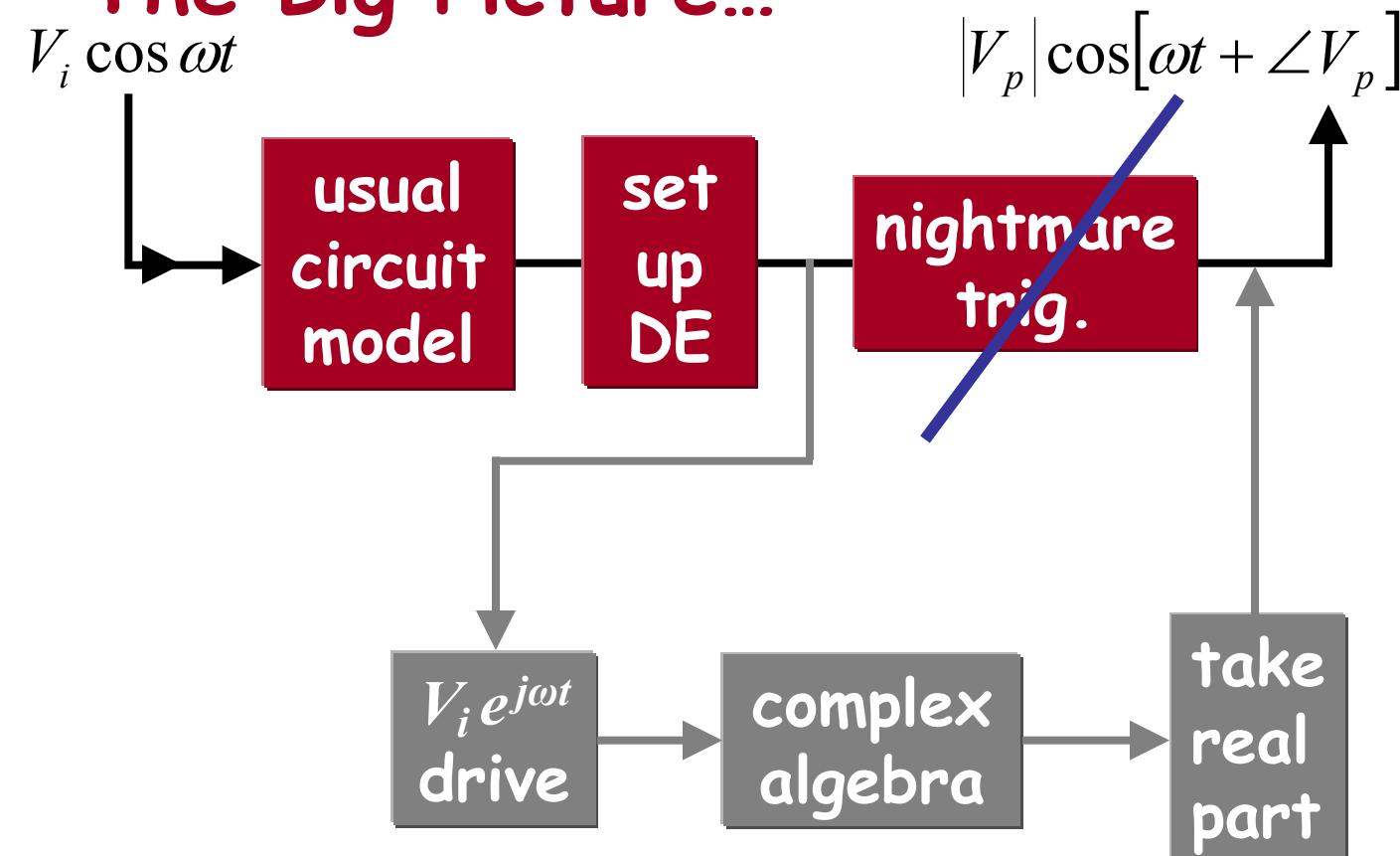


V-code: ???

# Approach 3: Impedance Model

## The Big Picture...

V-code: ???

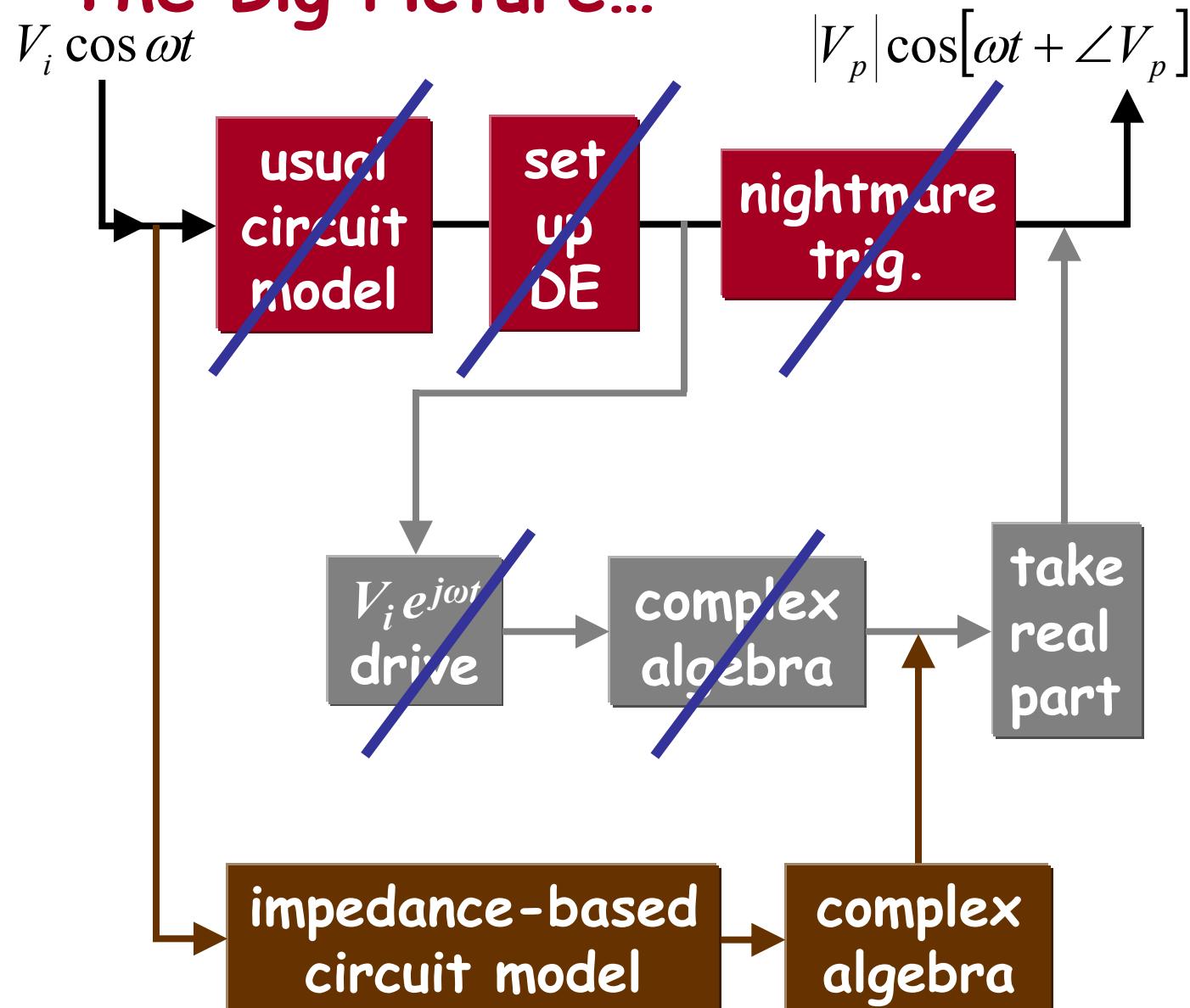

**V-code: ???**

# Approach 3: Impedance Model


**Back to**

$$\frac{V_r}{V_i} = \frac{j\omega RC}{1 + j\omega RC - \omega^2 LC}$$

**Let's study this transfer function**

$$\begin{aligned}\frac{V_r}{V_i} &= \frac{j\omega RC}{1 + j\omega RC - \omega^2 LC} \\ &= \frac{j\omega RC}{(1 - \omega^2 LC) + j\omega RC} \cdot \frac{(1 - \omega^2 LC) - j\omega RC}{(1 - \omega^2 LC) - j\omega RC}\end{aligned}$$


$$\left| \frac{V_r}{V_i} \right| = \frac{\omega RC}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}}$$

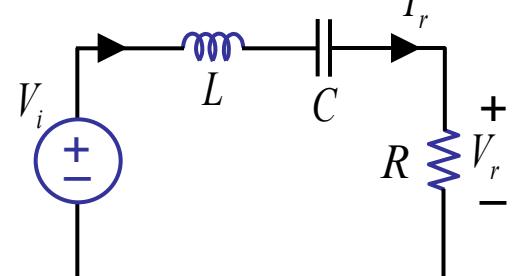**Observe**Low  $\omega$ :  $\approx \omega RC$ High  $\omega$ :  $\approx \frac{R}{\omega L}$  $\omega\sqrt{LC} = 1$ :  $\approx 1$ 

**V-code: ???**

# Approach 3: Impedance Model

$$\left| \frac{V_r}{V_i} \right| = \frac{\omega RC}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}}$$

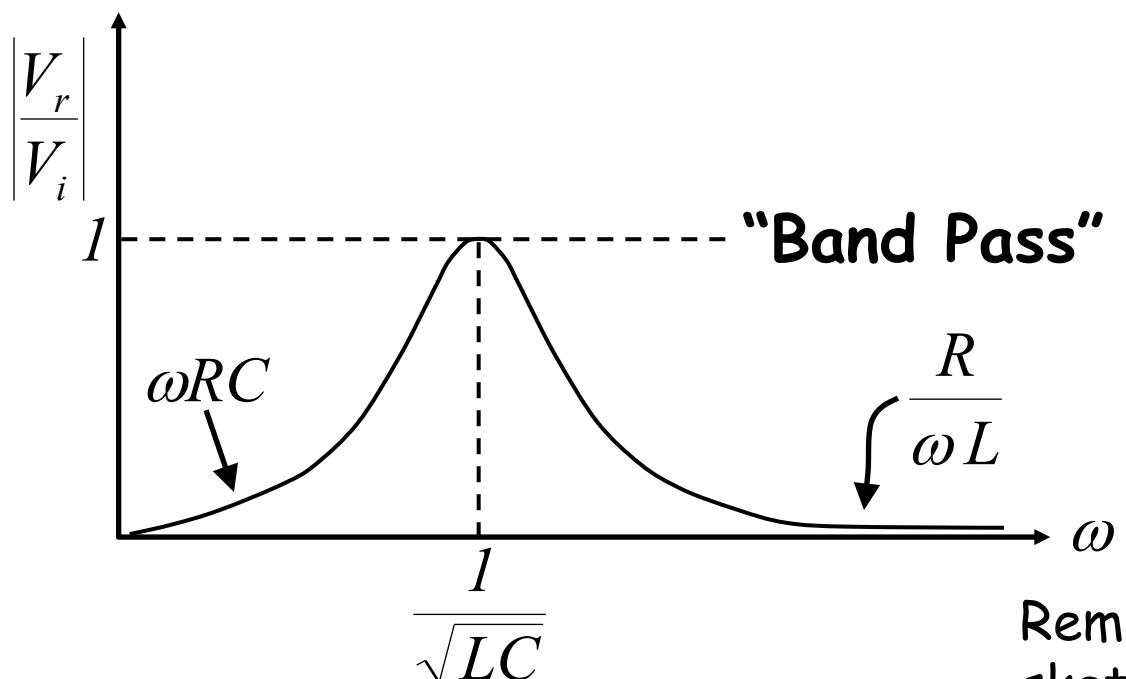


$$\text{Low } \omega : \approx \omega RC$$

$$\text{High } \omega : \approx \frac{R}{\omega L}$$

$$\omega \sqrt{LC} = 1 : \approx 1$$

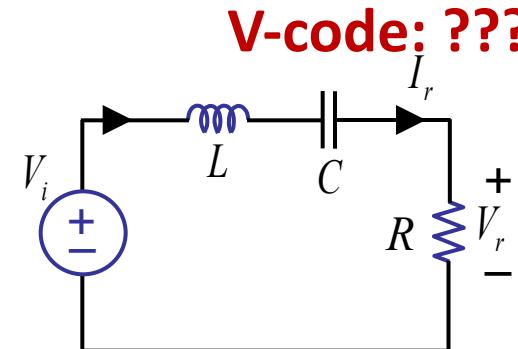Remember this trick to sketch the form of transfer functions quickly.



**V-code: ???**


# Outline

**Textbook: 13.1, 13.2, 13.3, 13.4, 13.5, 14.2, 14.3**

- Sinusoidal Response of RC Network: Three Approaches
- Impedance Model
- Frequency Response and Filters
- Frequency Response for Resonance Systems

# Review

V-code: ???

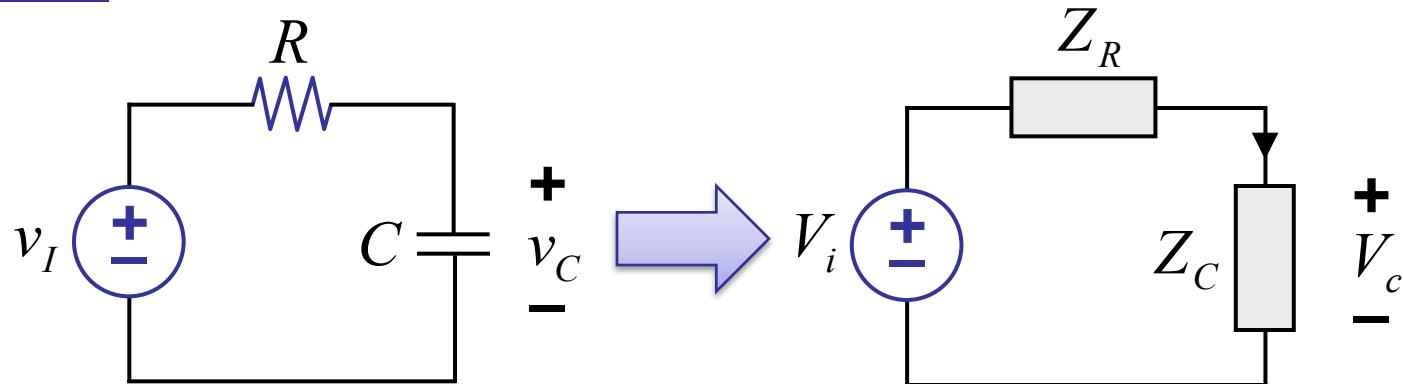


$$V_c = \frac{Z_C}{Z_C + Z_R} \cdot V_i$$

$$\frac{V_c}{V_i} = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} = \frac{1}{1 + j\omega RC}$$

# Review


V-code: ???

## A Filter

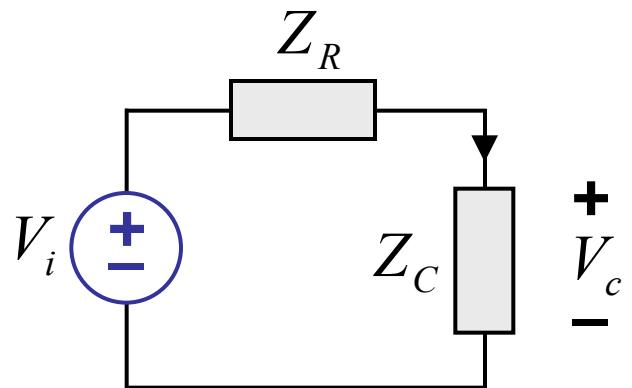

$$V_c = \frac{Z_C}{Z_C + Z_R} \cdot V_i = \frac{I}{1 + j\omega RC}$$

$$|H(\omega)| = \left| \frac{V_c}{V_i} \right|$$


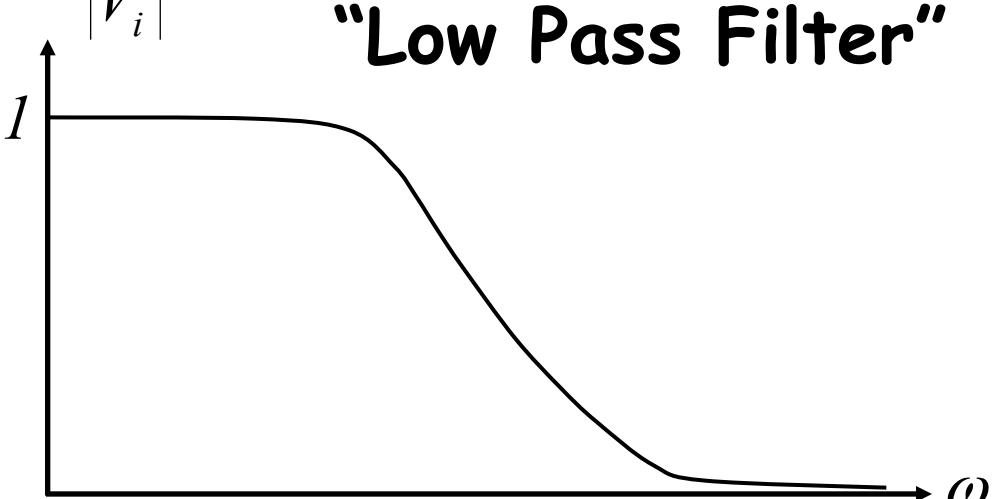


“Low Pass Filter”

# Review

V-code: ???

## Quick Review of Impedances - Just as

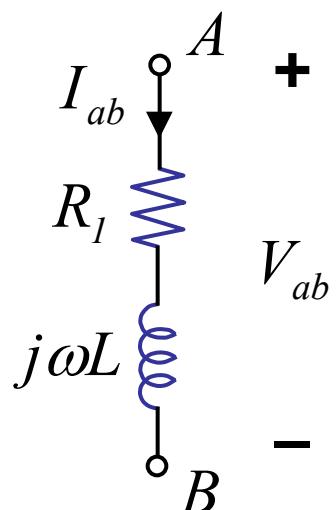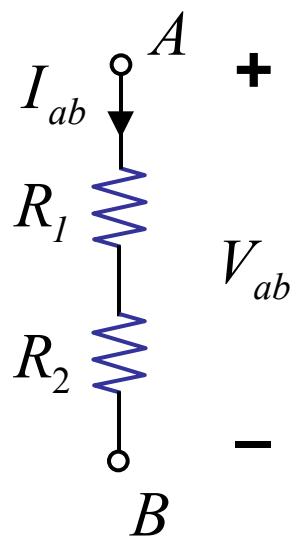

$$R_{AB} = \frac{V_{ab}}{I_{ab}} = R_1 + R_2$$


$$Z_{AB} = \frac{V_{ab}}{I_{ab}} = R_l + j\omega L$$

# Review

V-code: ???

## Quick Review of Impedances

Similarly

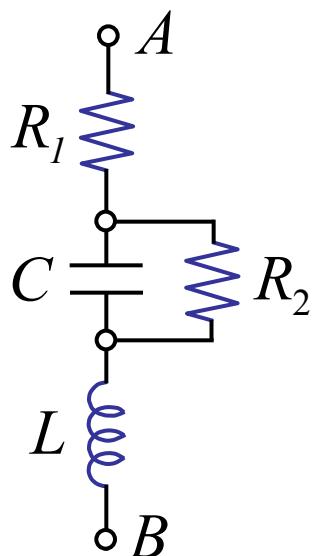


$$\begin{aligned} Z_{AB} &= R_1 + Z_C \parallel R_2 + Z_L \\ &= R_1 + \frac{Z_C R_2}{Z_C + R_2} + Z_L \\ &= R_1 + \frac{R_2}{1 + j\omega C R_2} + j\omega L \end{aligned}$$
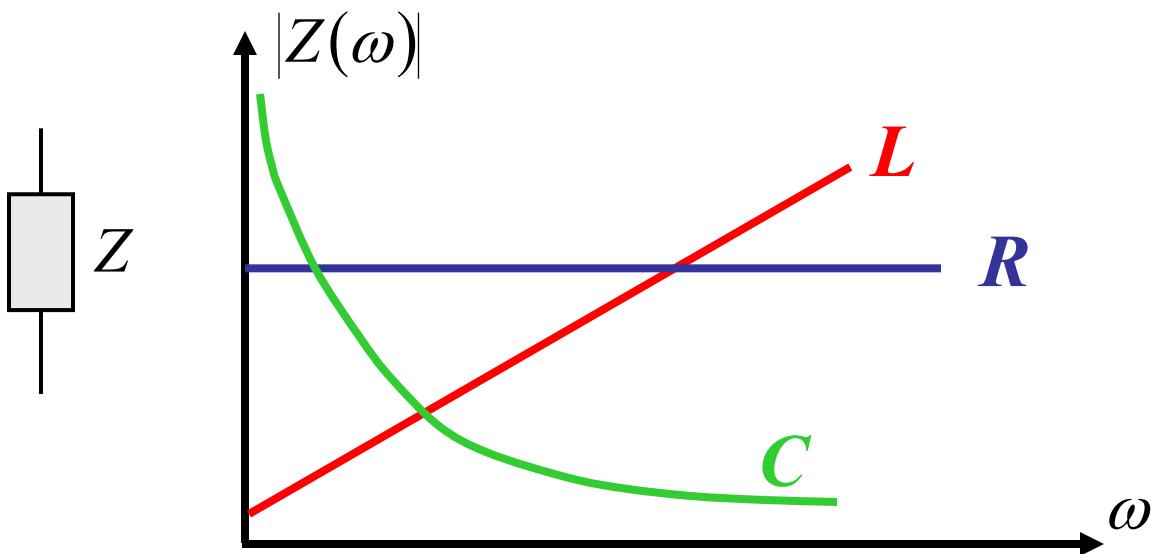
# Filters








We can build other filters by combining impedances.

Filter = only passing signals within a specific range of frequency while rejecting ones outside the range.


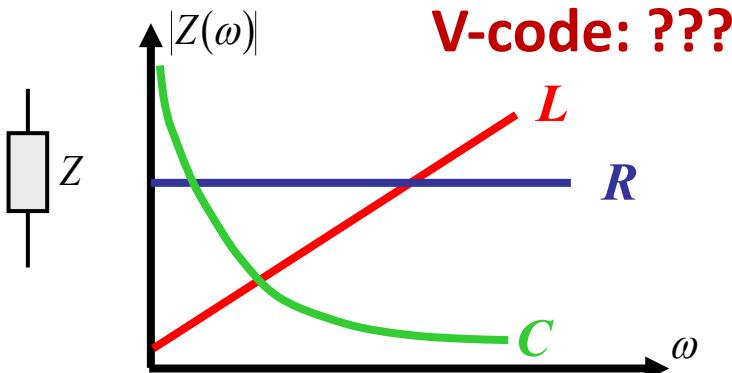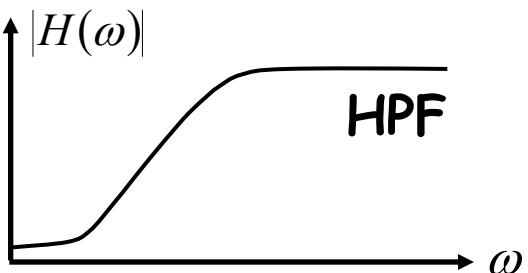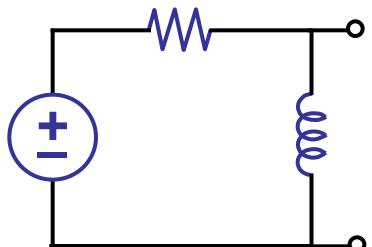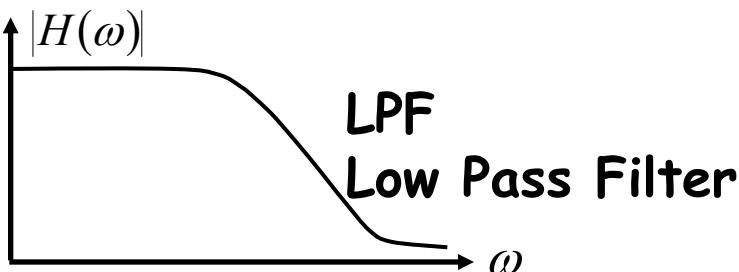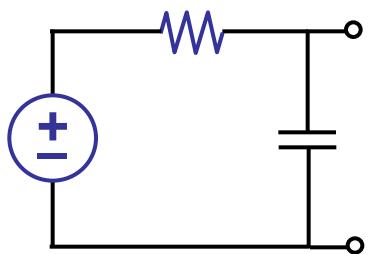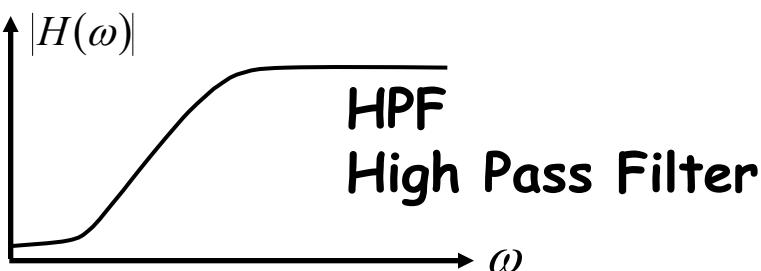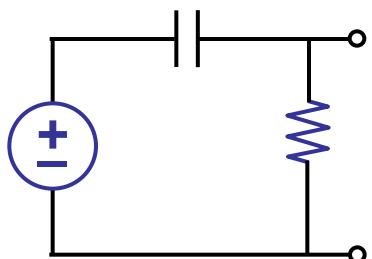
# Filters

We can build other filters by combining impedances.





V-code: ???

V-code: ???

# Filters

**Check out:**

**Intuitively:**

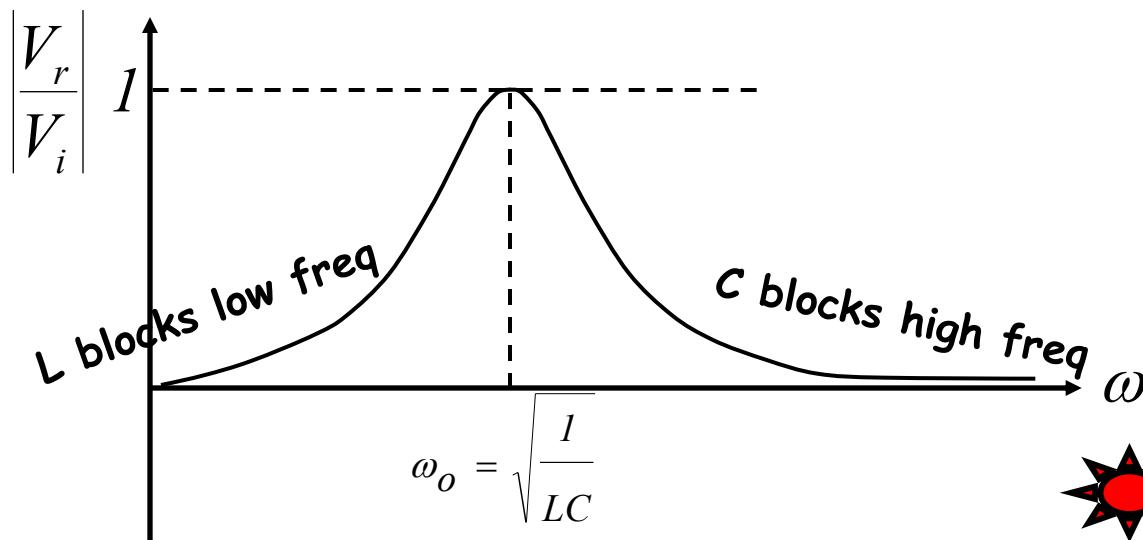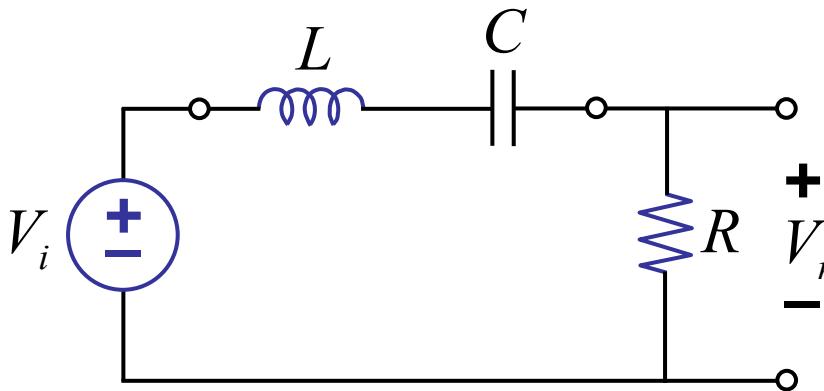

$$\frac{V_r}{V_i} = \frac{R}{j\omega L + \frac{1}{j\omega C} + R} = \frac{j\omega RC}{1 - \omega^2 LC + j\omega RC}$$



$$\left| \frac{V_r}{V_i} \right| = \frac{\omega RC}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}}$$

**At resonance,**  
 $\omega = \omega_0$   
**and**  
 $Z_L + Z_C = 0,$   
**so**  $V_i$  **sees**  
**only**  $R!$   
**→ Maximum Response**

**V-code: ???**

# Filters



What about:

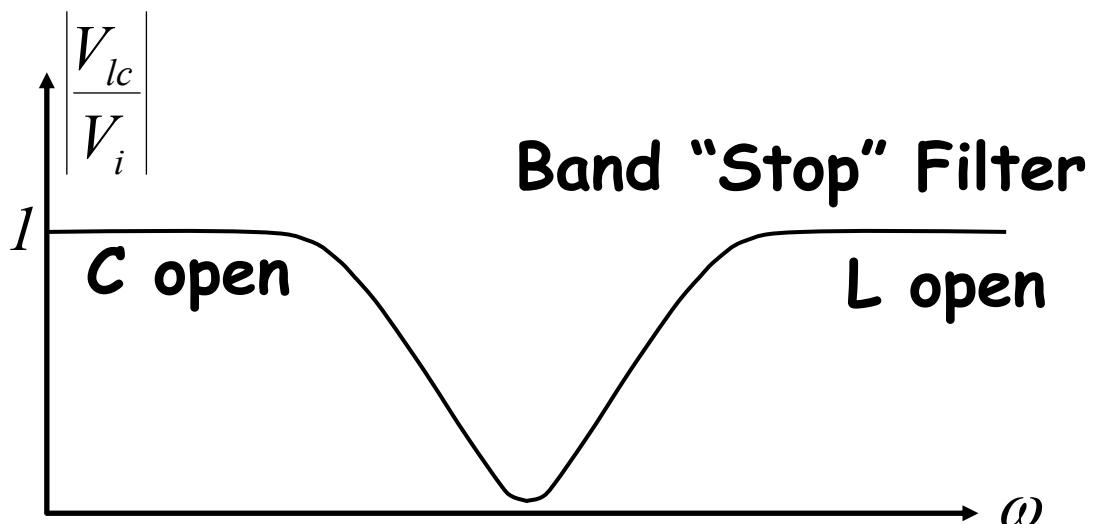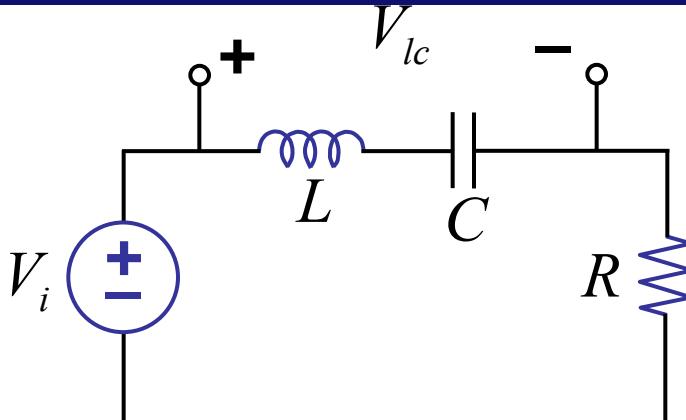

V-code: ???

# Filters

Another example:

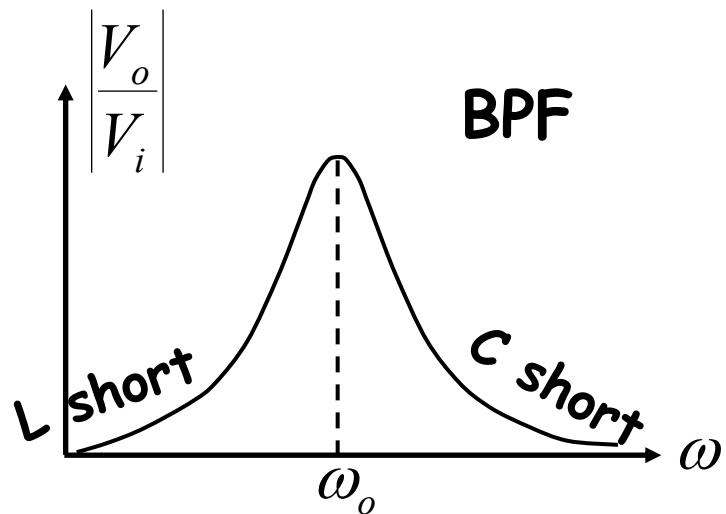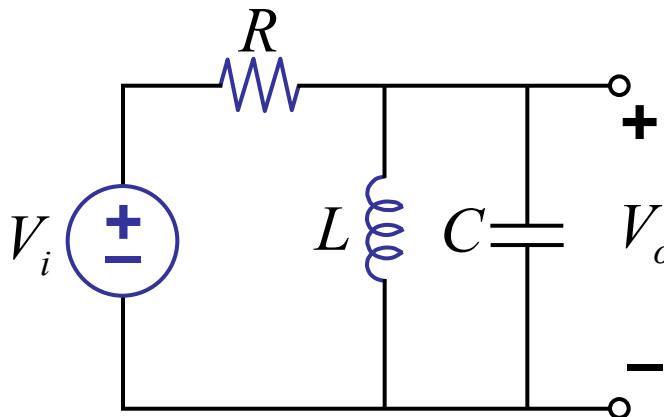

Application: see AM radio coming up shortly

**V-code: ???**

# Outline


**Textbook: 13.1, 13.2, 13.3, 13.4, 13.5, 14.2, 14.3**

- Sinusoidal Response of RC Network: Three Approaches
- Impedance Model
- Frequency Response and Filters
- **Frequency Response for Resonance Systems**

V-code: ???

# Filters

## AM Radio Receiver

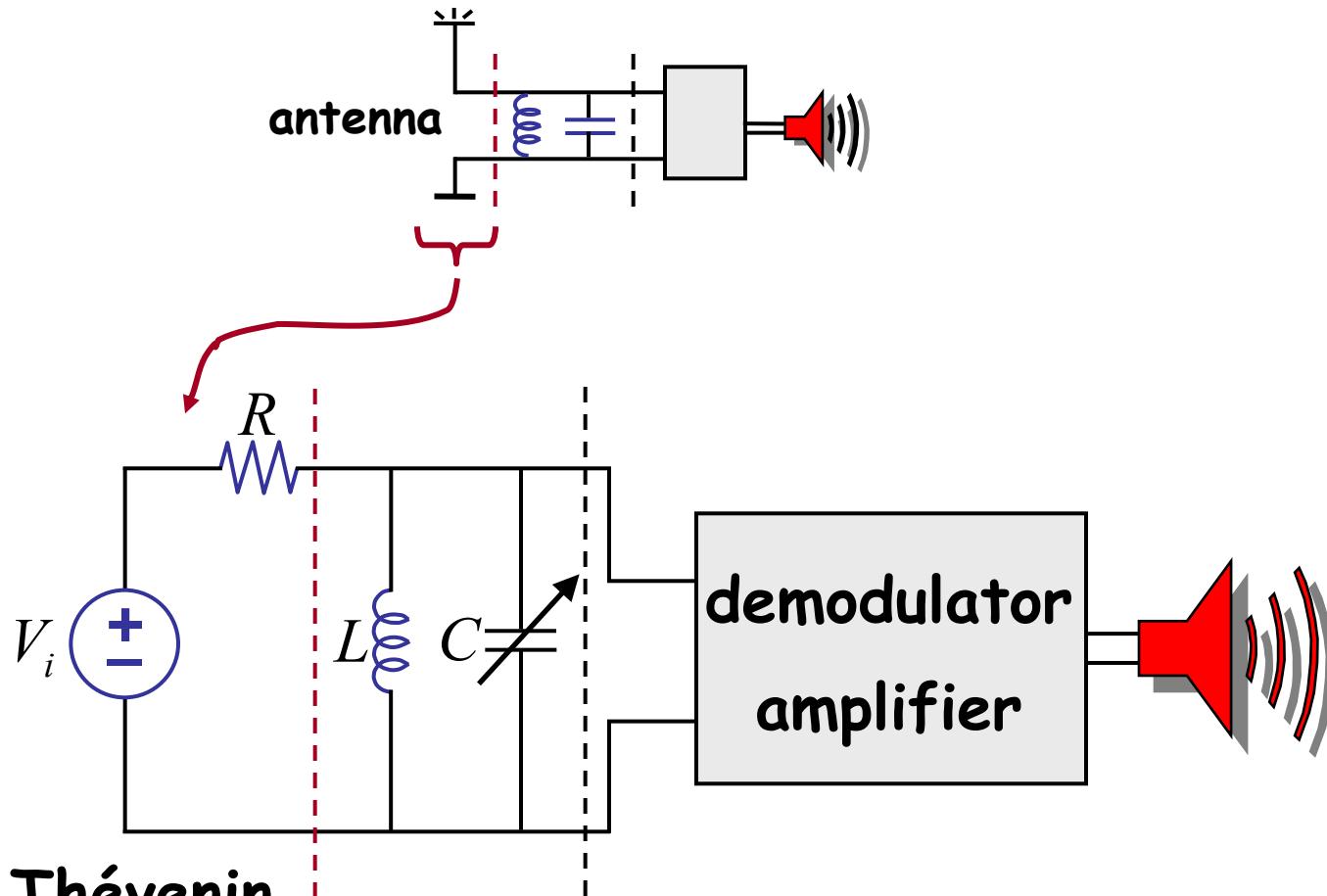


Thévenin  
antenna  
model

V-code: ???

# Filters

## AM Receiver


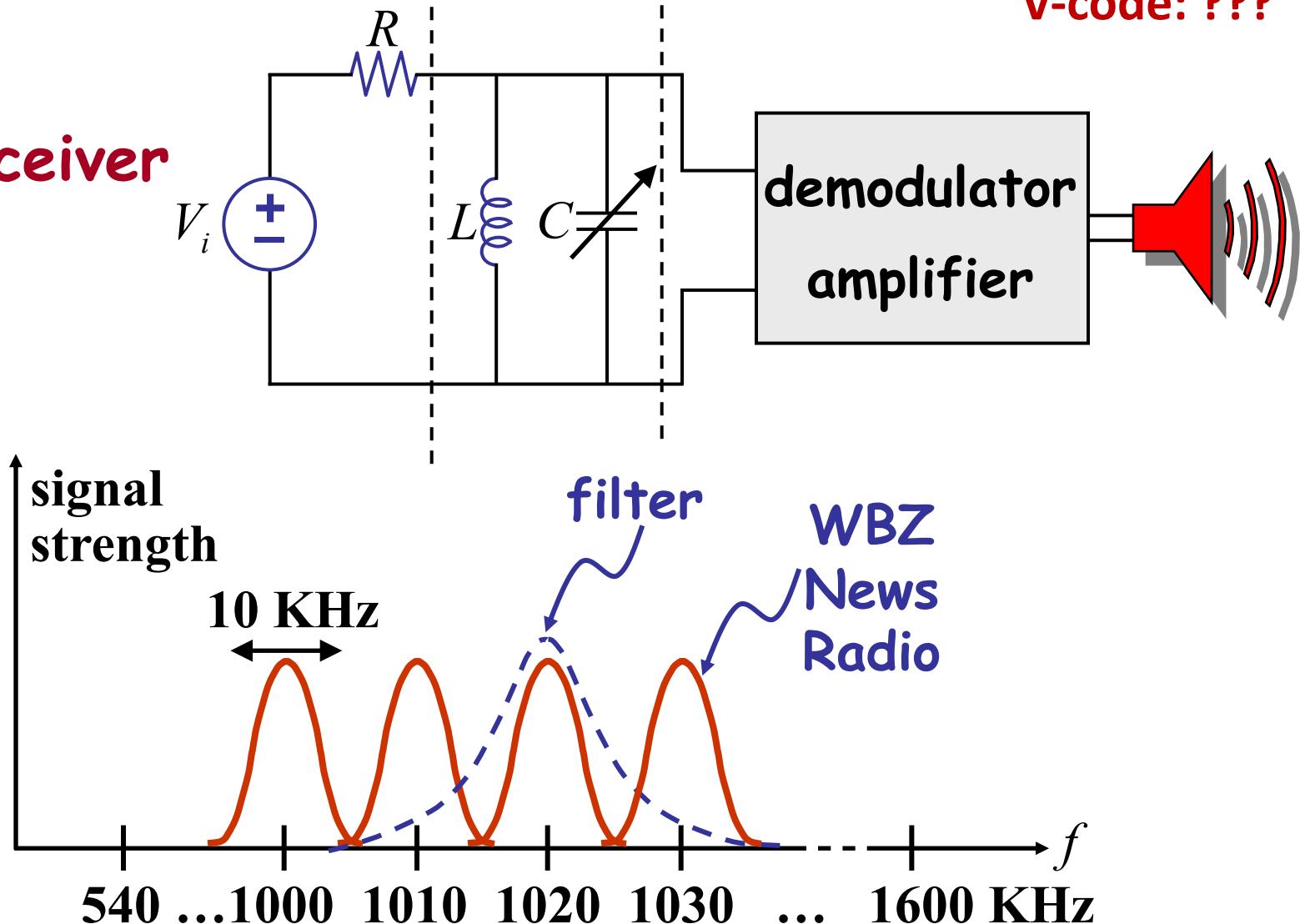


“Selectivity” important –  
relates to a parameter “ $Q$ ” for the filter. Next...

# Filters

Selectivity:

Look at series RLC  
in more detail

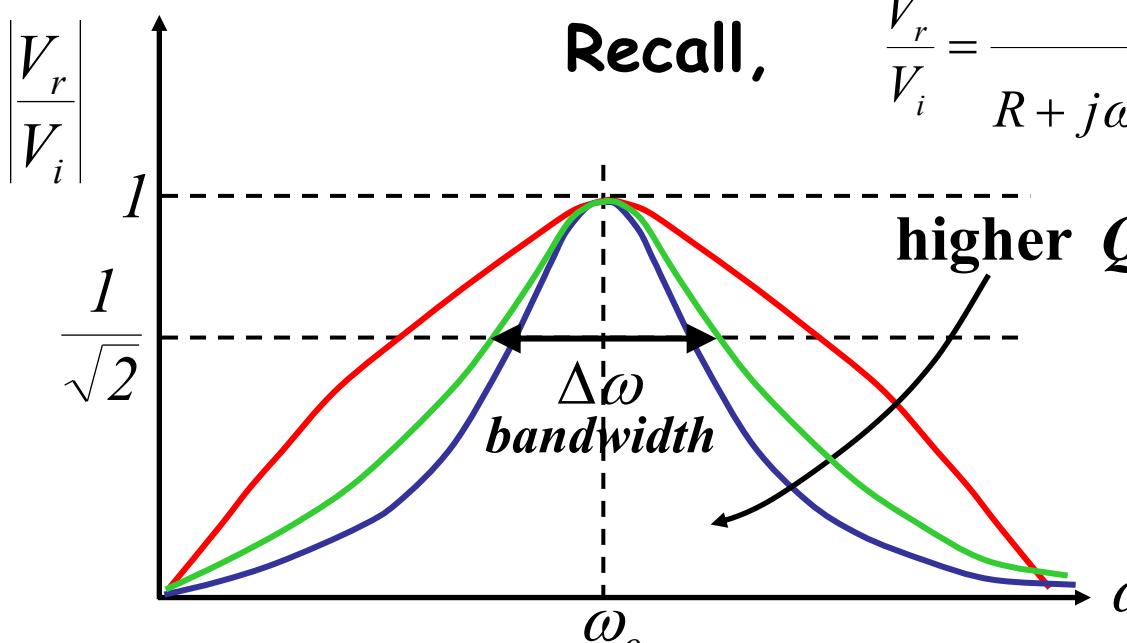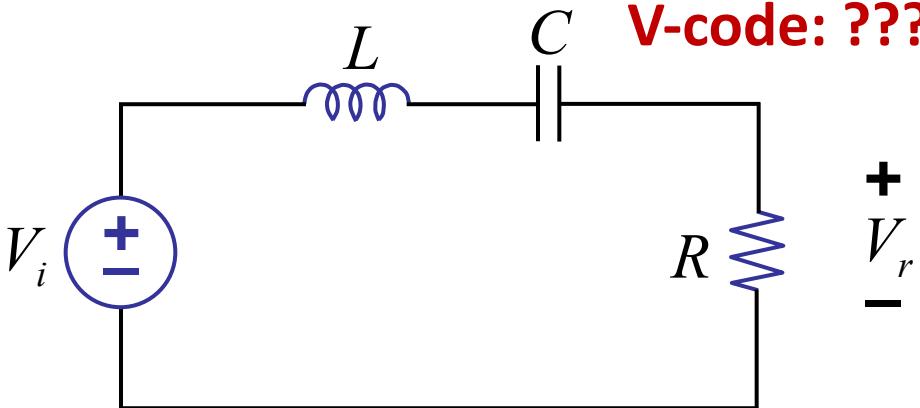

Recall,

$$\frac{V_r}{V_i} = \frac{R}{R + j\omega L + \frac{1}{j\omega C}}$$

higher  $Q$

Define  $Q = \frac{\omega_o}{\Delta\omega}$       *quality factor*  
 high  $Q$      $\Rightarrow$     more selective

**V-code: ???**

# Quality Factor Q

$$Q = \frac{\omega_o}{\Delta\omega}$$

$\omega_o$ :

$$\frac{V_r}{V_i} = \frac{R}{R + j\omega L + \frac{1}{j\omega C}} = \frac{1}{1 + j\left(\omega \frac{L}{R} - \frac{1}{\omega CR}\right)}$$

$\underbrace{\qquad\qquad\qquad}_{\text{at } \omega_o = 0}$

$$\omega_o = \frac{1}{\sqrt{LC}}$$

$\Delta\omega$  ?

V-code: ???

# Quality Factor Q

$$Q = \frac{\omega_o}{\Delta\omega}$$

$\Delta\omega$ :

Note that abs magnitude is  $\frac{I}{\sqrt{2}}$

when  $\frac{V_r}{V_i} = \frac{I}{I + j\left(\omega\frac{L}{R} - \frac{1}{\omega CR}\right)} = \frac{I}{I \pm jI}$

i.e. when  $\frac{\omega L}{R} - \frac{1}{\omega CR} = \pm I$

$$\omega^2 \mp \frac{\omega R}{L} - \frac{1}{LC} = 0$$

Looking at the roots of both equations,

$$\omega_1 = \frac{R}{2L} + \frac{1}{2} \sqrt{\frac{R^2}{L^2} + \frac{4}{LC}} \quad \omega_2 = -\frac{R}{2L} + \frac{1}{2} \sqrt{\frac{R^2}{L^2} + \frac{4}{LC}}$$

$$\Delta\omega = \omega_1 - \omega_2 = \frac{R}{L}$$

**V-code: ???**

# Quality Factor Q

$$Q = \frac{\omega_o}{\Delta\omega}$$

$$Q = \frac{\omega_o}{R} = \frac{\omega_o L}{R}$$

$$\omega_o = \frac{1}{\sqrt{LC}}$$

The lower the  $R$  (for series  $R$ ), the sharper the peak

**V-code: ???**

# Quality Factor Q

Another way of looking at  $Q$ :

$$Q = 2\pi \frac{\text{energy stored}}{\text{energy lost per cycle}}$$

$$= 2\pi \frac{\frac{1}{2}L|I_r|^2}{\frac{1}{2}|I_r|^2 R \frac{2\pi}{\omega_0}}$$

$$Q = \frac{\omega_o L}{R}$$

V-code: ???

# Exercise



Find the resonance frequency and the equivalent impedance at resonance.

