

# First-Order Transients in Linear Electrical Networks (1)

Lecture 12

October 30<sup>th</sup>, 2018

Jae W. Lee ([jaewlee@snu.ac.kr](mailto:jaewlee@snu.ac.kr))

Computer Science and Engineering

Seoul National University

*Slide credits: Prof. Anant Agarwal at MIT*

# Outline


**Textbook: 10.1, 10.3**

- **Analysis of RC Circuits**
- **Intuitive Analysis**

# Analysis of RC Circuits

- What is  $v_C(t)$ ?

Thévenin Equivalent: ←

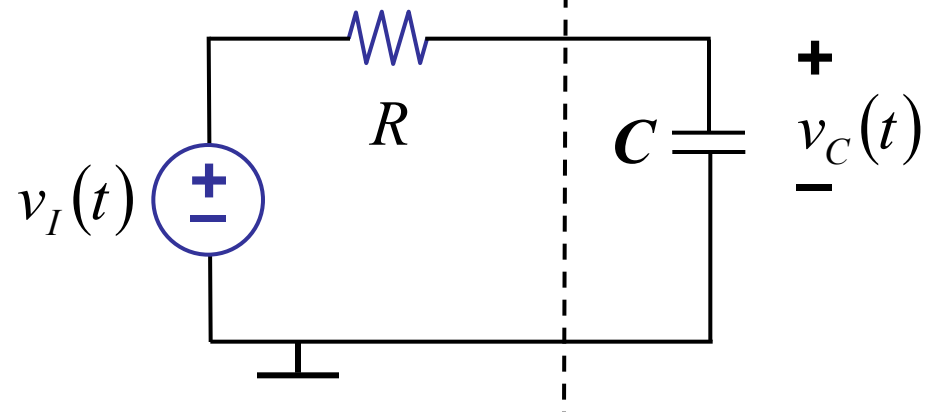


Apply node method:

$$\frac{v_C - v_I}{R} + C \frac{dv_C}{dt} = 0$$

$$\underbrace{(RC)}_{\substack{\uparrow \\ \text{units} \\ \text{of time}}} \frac{dv_C}{dt} + v_C = v_I \quad \begin{cases} t \geq t_0 \\ v_C(t_0) \text{ given} \end{cases}$$

# Analysis of RC Circuits

Let's do an example:

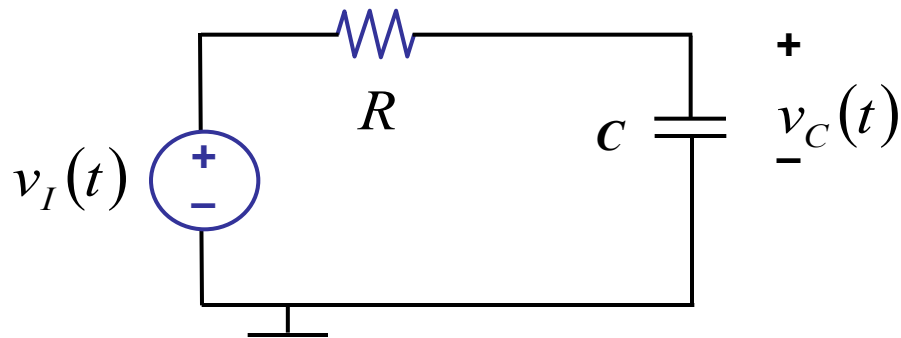

$$v_I(t) = V_I$$

$$v_C(0) = V_0 \quad \text{given}$$

$$RC \frac{dv_C}{dt} + v_C = V_I \quad \text{—————} \otimes$$

# Analysis of RC Circuits

Let's do an example:

$$v_I(t) = V_I$$

$$v_C(0) = V_0 \quad \text{given}$$

$$RC \frac{dv_C}{dt} + v_C = V_I \quad \text{—————} \quad \textcircled{\times}$$

$$v_C(t) = v_{CH}(t) + v_{CP}(t)$$

**total    homogeneous    particular**

# Analysis of RC Circuits

## Example...

$$v_C(t) = v_{CH}(t) + v_{CP}(t)$$

total   homogeneous   particular

## Method of homogeneous and particular solutions:

- ① Find the particular solution.
- ② Find the homogeneous solution.
- ③ The total solution is the sum of the particular and homogeneous solutions.

Use the initial conditions to solve for the remaining constants.

# Analysis of RC Circuits

## ① Particular solution

$$RC \frac{dv_{CP}}{dt} + v_{CP} = V_I$$

$$v_{CP} = V_I \quad \text{works}$$

$$RC \frac{dV_I}{dt} + V_I = V_I$$

0

In general, use trial and error.

$v_{CP}$  : any solution that satisfies the original equation (X)

# Analysis of RC Circuits

## ② Homogeneous solution

$$RC \frac{dv_{CH}}{dt} + v_{CH} = 0 \quad \text{—————} \quad \textcircled{y}$$

$v_{CH}$ : solution to the homogeneous equation  $\textcircled{y}$   
(set drive to zero)

$v_{CH} = Ae^{st}$       assume solution  
of this form.  $A, s$  ?

$$RC \frac{dAe^{st}}{dt} + Ae^{st} = 0$$

$$RCAs\cancel{e^{st}} + A\cancel{e^{st}} = 0$$



# Analysis of RC Circuits

## ② Homogeneous solution (cont...)

Discard trivial  $A = 0$  solution,

$$RCs + 1 = 0 \quad \text{Characteristic equation}$$

$$\longrightarrow s = -\frac{1}{RC}$$

or  $v_{CH} = Ae^{\frac{-t}{RC}}$

$RC$  called time constant  $\tau$

# Analysis of RC Circuits

## ③ Total solution

$$v_C = v_{CP} + v_{CH}$$

$$v_C = V_I + A e^{\frac{-t}{RC}}$$

Find remaining unknown from initial conditions:

Given,  $v_C = V_0$  at  $t = 0$

so,  $V_0 = V_I + A$

or  $A = V_0 - V_I$

thus

$$v_C = V_I + (V_0 - V_I) e^{\frac{-t}{RC}}$$


also

$$i_C = C \frac{dv_C}{dt} = -\frac{(V_0 - V_I)}{R} e^{\frac{-t}{RC}}$$

# Analysis of RC Circuits

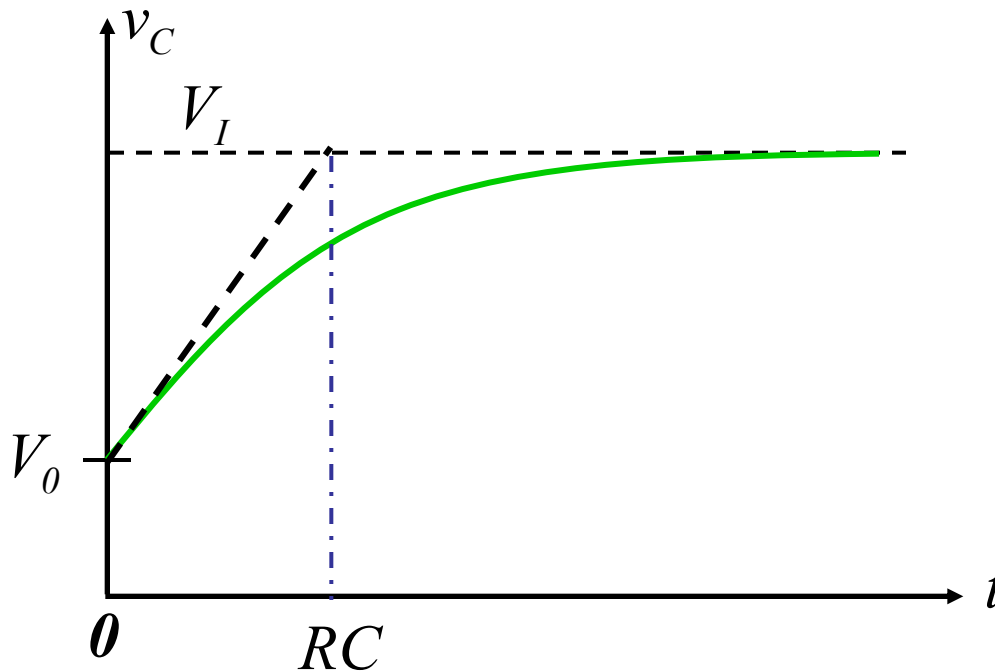
## ③ Total solution

$$v_C = V_I + (V_0 - V_I) e^{\frac{-t}{RC}}$$




# Analysis of RC Circuits

## ■ Examples

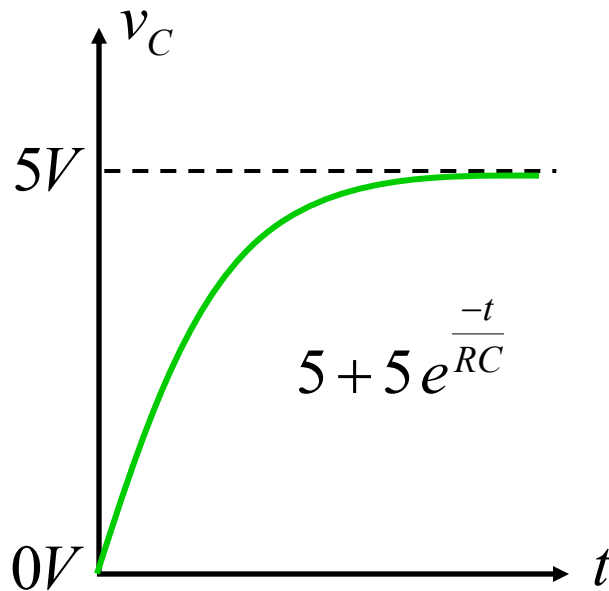

$$V_O = 0V$$

$$V_I = 5V$$

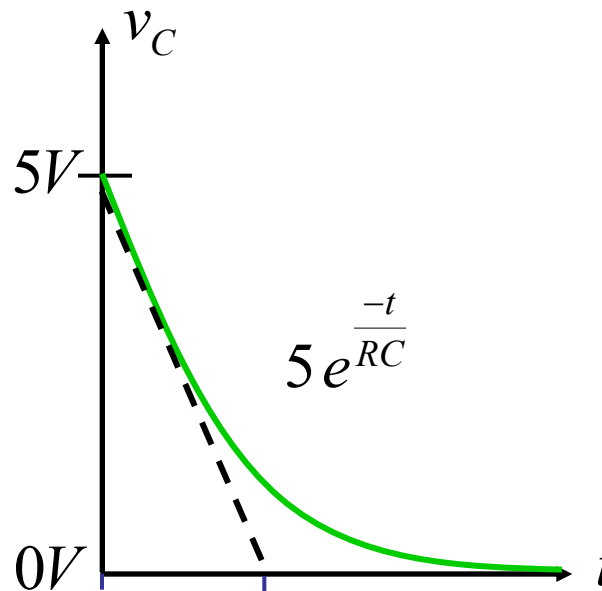

$$V_O = 5V$$

$$V_I = 0V$$

Time constant  $\tau = RC$

# Outline





**Textbook: 10.1, 10.3**

- Analysis of RC Circuits
- **Intuitive Analysis**

# Intuitive Analysis
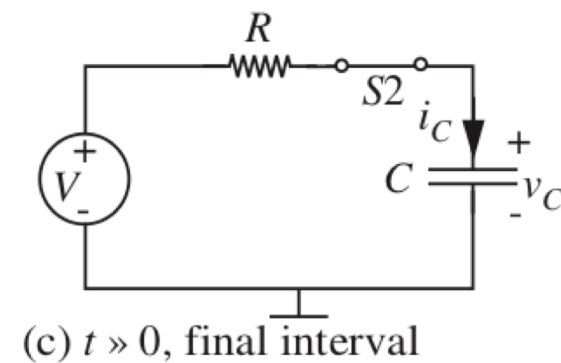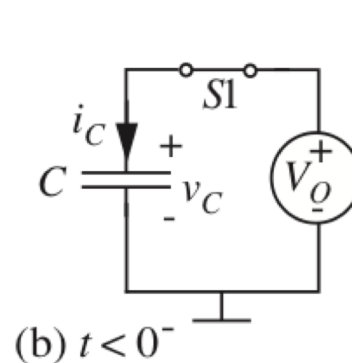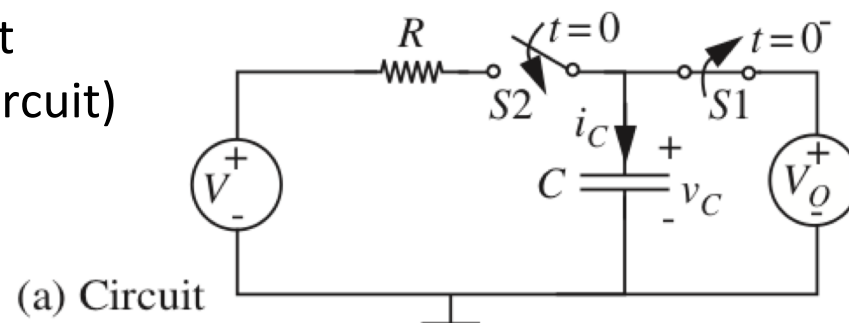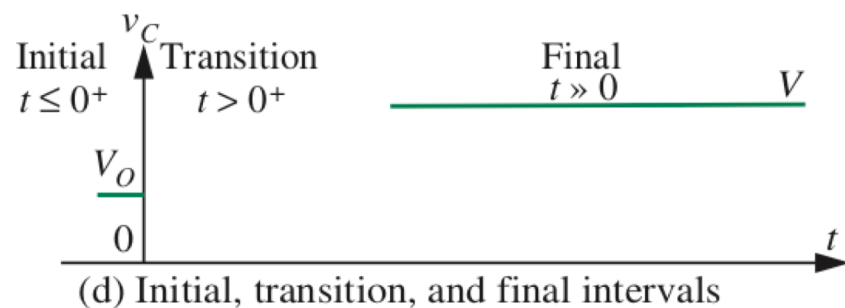
## ■ How to calculate $v_C(t)$ (without solving differential eq.)?

- For simple excitations (like step functions), the response of the first order-systems can be sketched easily using some intuition.
- DC steady state with DC voltage or current source
  - After a long time:  $t \rightarrow \infty$ 
    - Capacitor: **open** circuit  
(cf. Inductor: **closed** circuit)



# Intuitive Analysis


## ■ How to calculate $v_C(t)$ (without solving differential eq.)?

- Transition interval ( $t > 0^+$ ): General form

$$v_C = \text{initial value } e^{-t/\text{time constant}} + \text{final value}(1 - e^{-t/\text{time constant}}) \quad (10.62)$$

**Time constant ( $\tau$ ) = RC**

- Complete response form

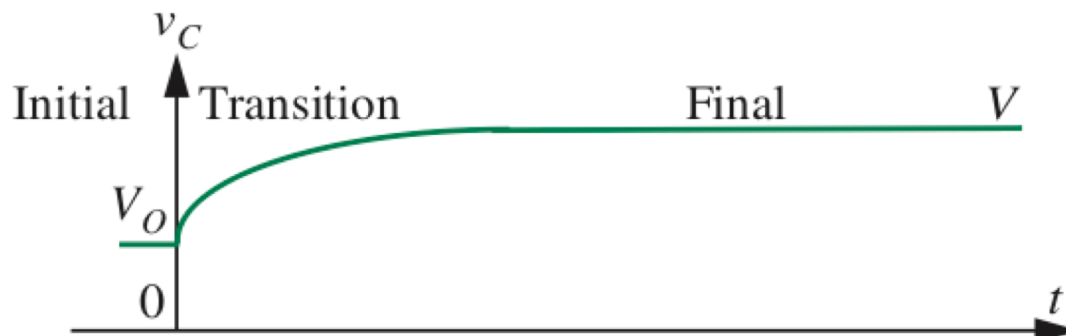

- Can be applied to obtain capacitor current ( $i_C(t)$ ) as well!