

---

**EXAMPLE 2.28 BASIC CIRCUIT ANALYSIS METHOD** Solve the circuit in Figure 2.58 using the basic method.

Step 1 is to assign the branch variables. Figure 2.59 shows the circuit with the variables properly assigned.

In Step 2, we write the constituent relations:

$$v_S = -V \quad (2.153)$$

$$v_1 = i_1 R_1 \quad (2.154)$$

$$v_2 = i_2 R_2 \quad (2.155)$$

$$v_3 = i_3 R_3 \quad (2.156)$$

$$v_4 = i_4 R_4 \quad (2.157)$$

$$v_5 = i_5 R_5. \quad (2.158)$$

In Step 3, we write the KVL and KCL equations. The KVL equations with respect to the loop choice shown in Figure 2.60, are

$$v_S + v_1 + v_2 + v_4 = 0 \quad (2.159)$$

$$-v_2 + v_3 = 0 \quad (2.160)$$

$$-v_4 + v_5 = 0 \quad (2.161)$$

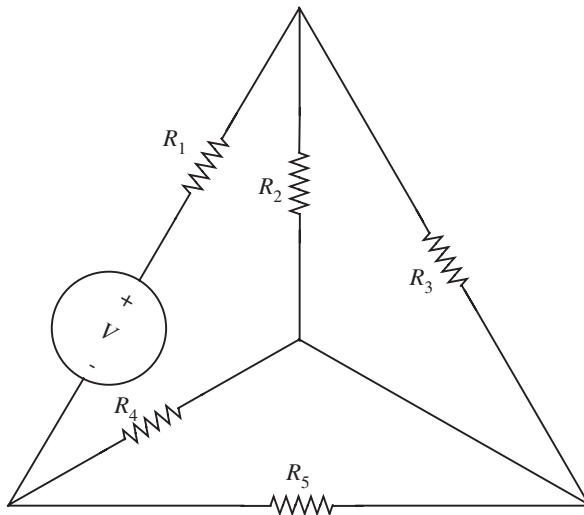


FIGURE 2.58 Circuit example.

FIGURE 2.59 Circuit with properly assigned variables.


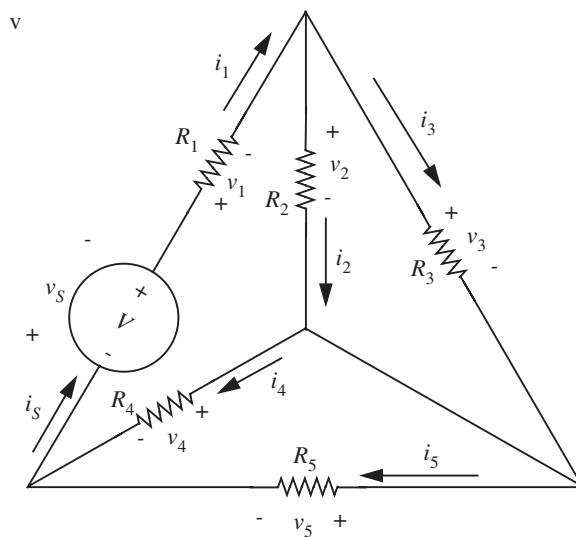


FIGURE 2.60 Loop and node choice.

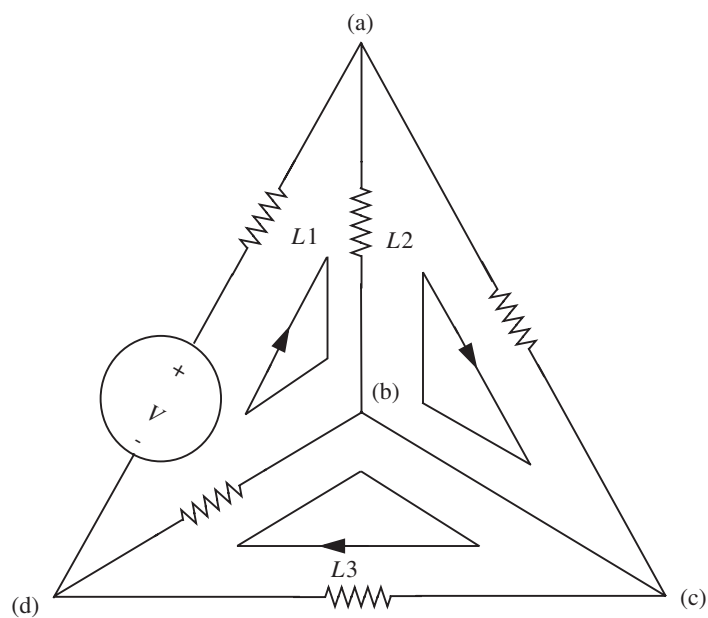

At node (a), the KCL equation is

$$i_1 - i_2 - i_3 = 0. \quad (2.162)$$

Notice that nodes (b) and (c) are connected by a wire, so they yield only one KCL equation

$$i_2 + i_3 - i_4 - i_5 = 0. \quad (2.163)$$

Lastly, at node (d), we have

$$i_4 + i_5 - i_S = 0. \quad (2.164)$$

Combining the constituent relations with KVL equations, we obtain

$$-V + i_1 R_1 + i_2 R_2 + i_4 R_4 = 0 \quad (2.165)$$

$$-i_2 R_2 + i_3 R_3 = 0 \quad (2.166)$$

$$-i_4 R_4 + i_5 R_5 = 0. \quad (2.167)$$

By adding Equations 2.162–2.164, we have

$$i_S = i_1. \quad (2.168)$$

Eliminating  $i_2$  and  $i_4$  and substituting back into Equations 2.166–2.167 gives us

$$i_3 = i_S \frac{R_2}{R_2 + R_3} \quad (2.169)$$

$$i_5 = i_S \frac{R_4}{R_4 + R_5} \quad (2.170)$$

$$V = i_S \left( R_1 + R_2 + R_4 - \frac{R_2^2}{R_2 + R_3} - \frac{R_4^2}{R_4 + R_5} \right) \quad (2.171)$$

$$= i_S \left( R_1 + \frac{R_2 R_3}{R_2 + R_3} + \frac{R_4 R_5}{R_4 + R_5} \right). \quad (2.172)$$

As a quick sanity check of the solution, one might notice that the equivalent resistance of the network around the voltage source is  $R_1 + R_2 \parallel R_3 + R_4 \parallel R_5$ , which is correctly shown by Equation 2.172.

---