

# Analysis of Nonlinear Circuits

Lecture 6

September 27<sup>th</sup>, 2018

Jae W. Lee ([jaewlee@snu.ac.kr](mailto:jaewlee@snu.ac.kr))

Computer Science and Engineering

Seoul National University

***Slide credits: Prof. Anant Agarwal at MIT***

# Review: Discretize Matters


- Lumped Matter Discipline (LMD) simplifies circuit analysis.

m1	▶	KVL, KCL, $i$ - $v$	}	any circuit
m2	▶	Composition rules		
m3	▶	Node method		
m4	▶	Superposition	}	linear circuits
m5	▶	Thévenin, Norton		

# Review: Discretize Value
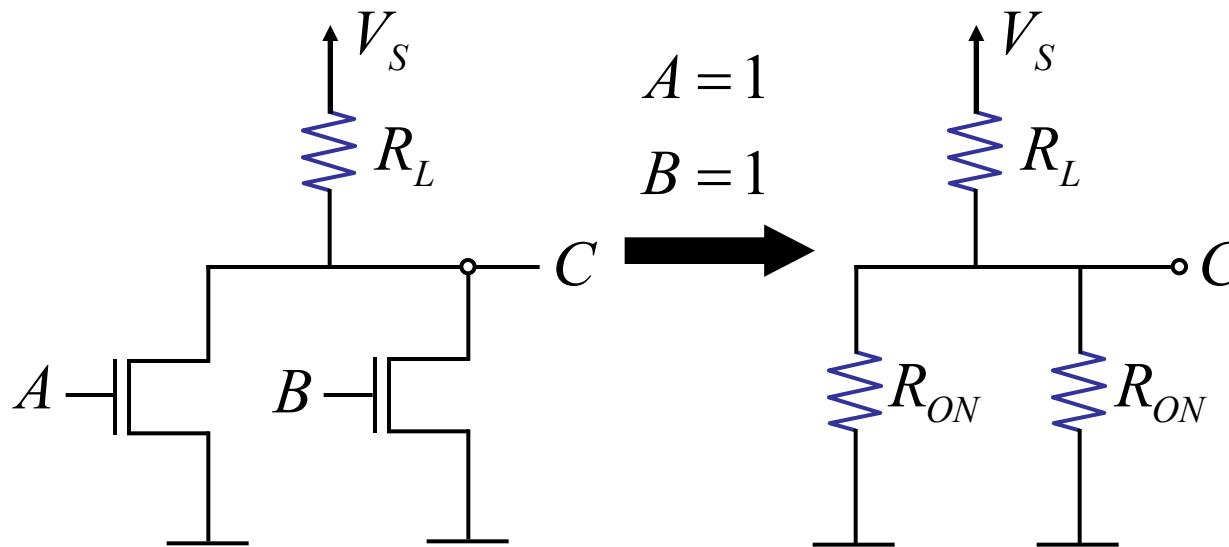
## ■ Digital abstraction

► Subcircuits for given “switch” setting are linear! So, all 5 methods (**m1 - m5**) can be applied



**SR MOSFET Model**


# Outline

**Textbook: Ch. 4.1, 4.2, 4.3, 4.5**

- **Analytical Method (based on  $m_1$ ,  $m_2$ ,  $m_3$ )**
- **Graphical Method**
- **Incremental Analysis**
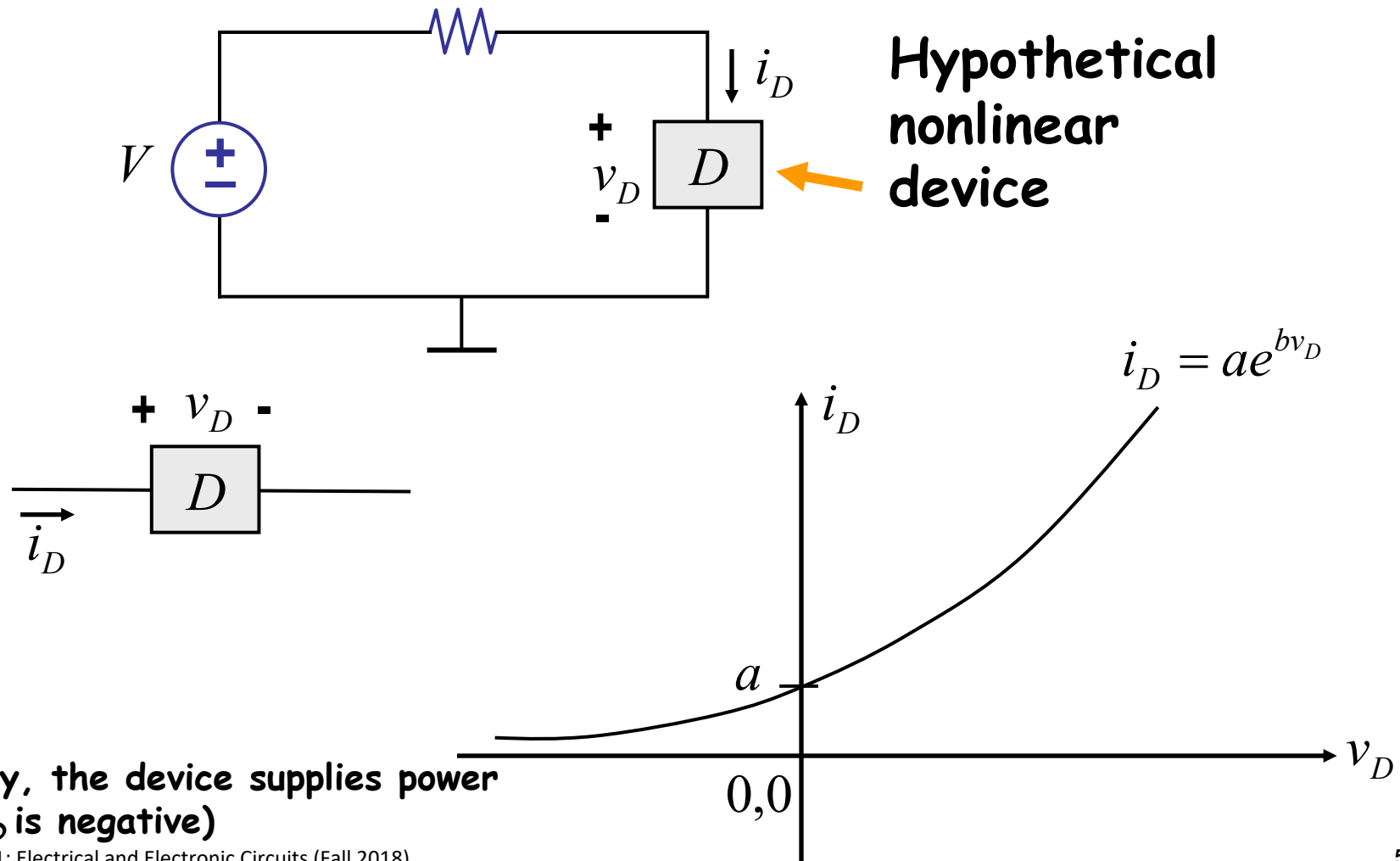
# Analytical Method

- How do we analyze nonlinear circuits, for example:



# Analytical Method

- Using the node method!

(remember the node method applies for linear or nonlinear circuits)

$$\frac{v_D - V}{R} + i_D = 0 \quad \textcircled{1}$$

$$i_D = ae^{bv_D} \quad \textcircled{2}$$

2 unknowns

2 equations


Solve the equation by

- trial and error
- numerical methods

# Graphical Method


Note: the solution satisfies equations

① and ②

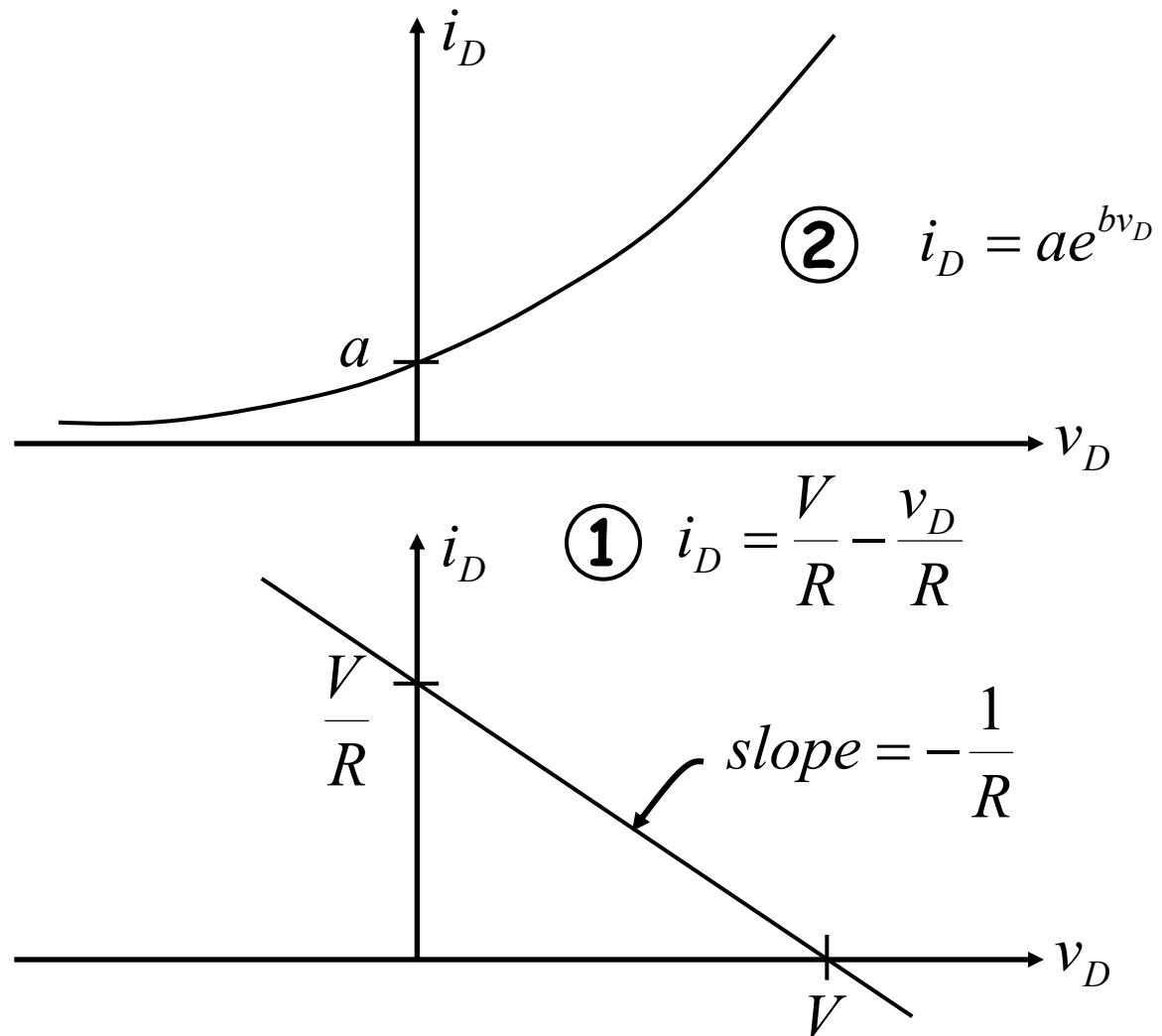

# Graphical Method

Combine the two constraints

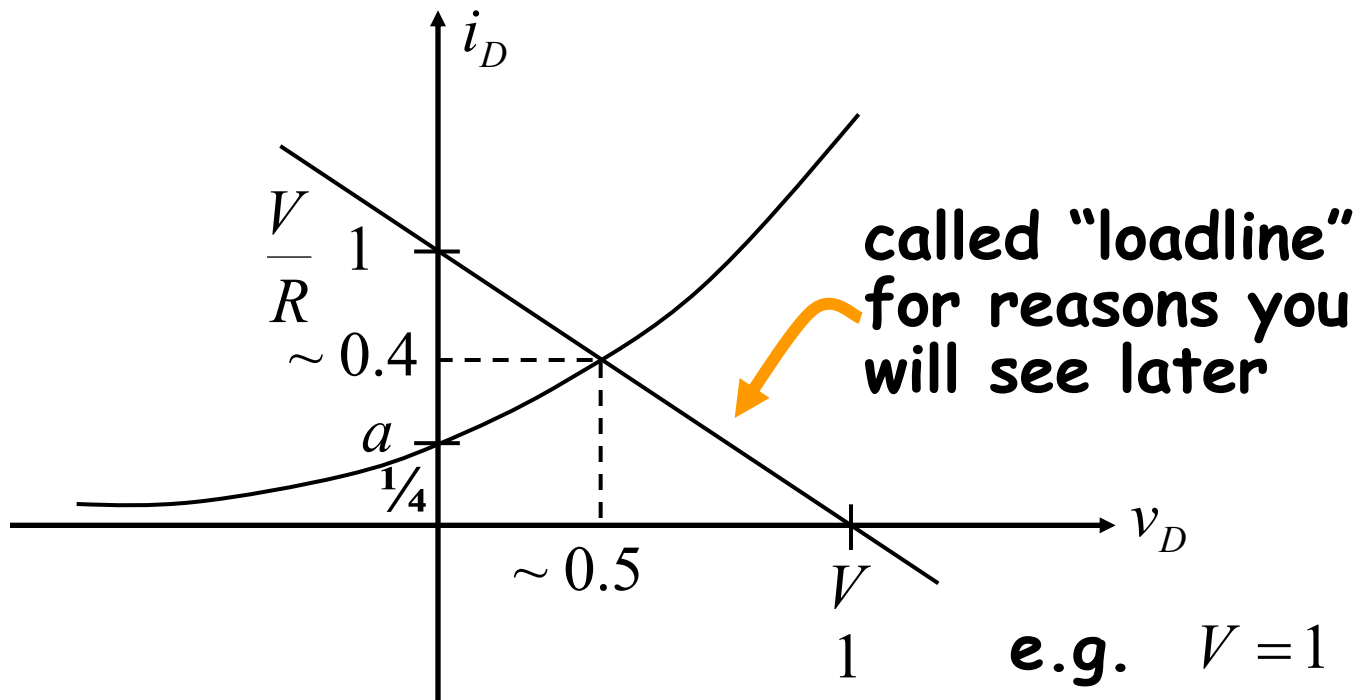

e.g.  $V = 1$

$R = 1$

$a = \frac{1}{4}$

$b = 1$

$v_D = 0.5V$

$i_D = 0.4A$





# Outline

**Textbook: Ch. 4.1, 4.2, 4.3, 4.5**

- Analytical Method (based on  $m_1$ ,  $m_2$ ,  $m_3$ )
- Graphical Method
- **Incremental Analysis**

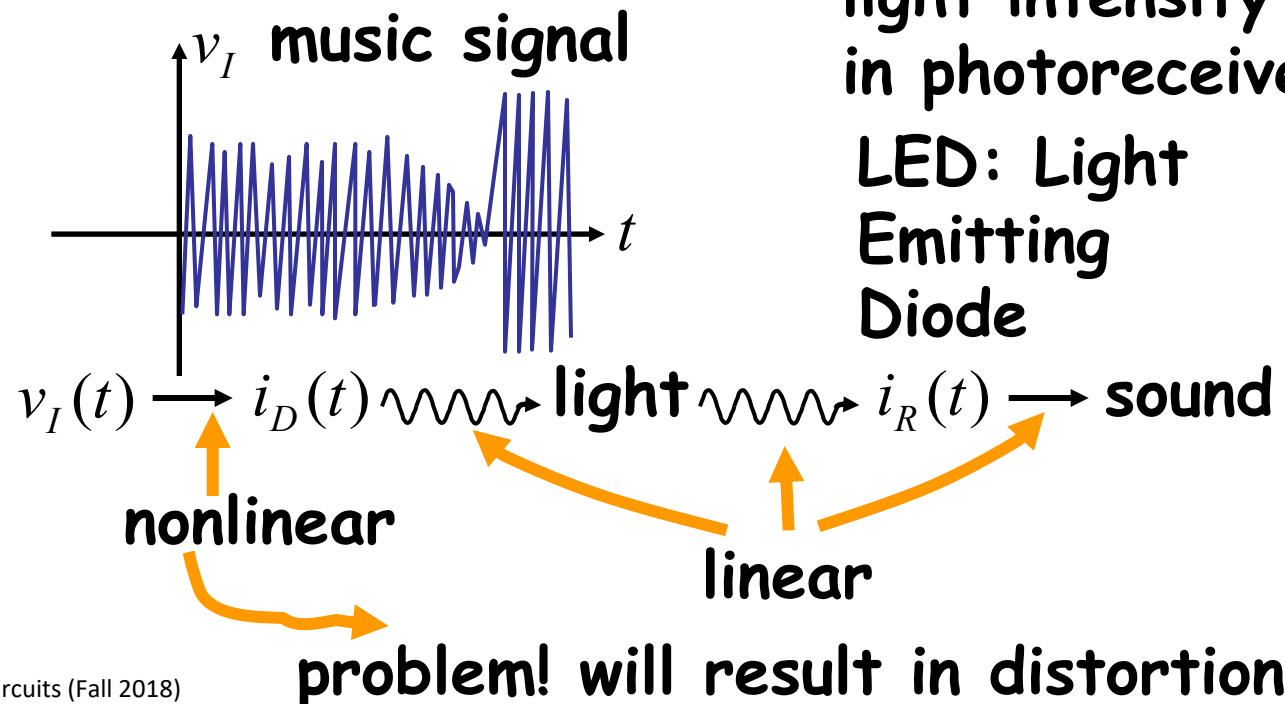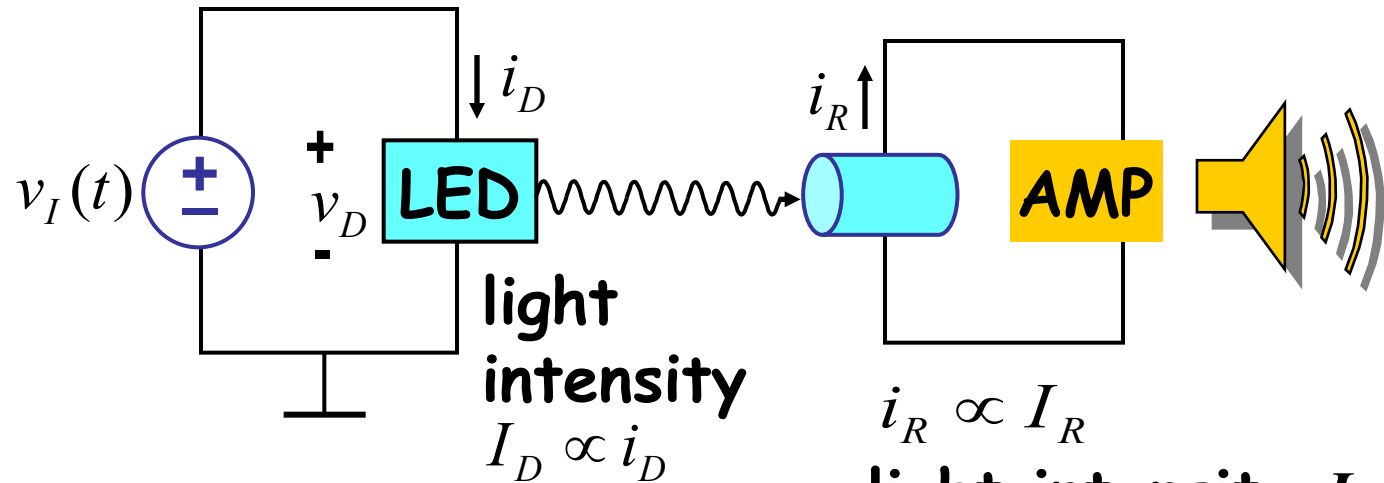
# Incremental Analysis

- **Motivation:**  
music over  
a light beam



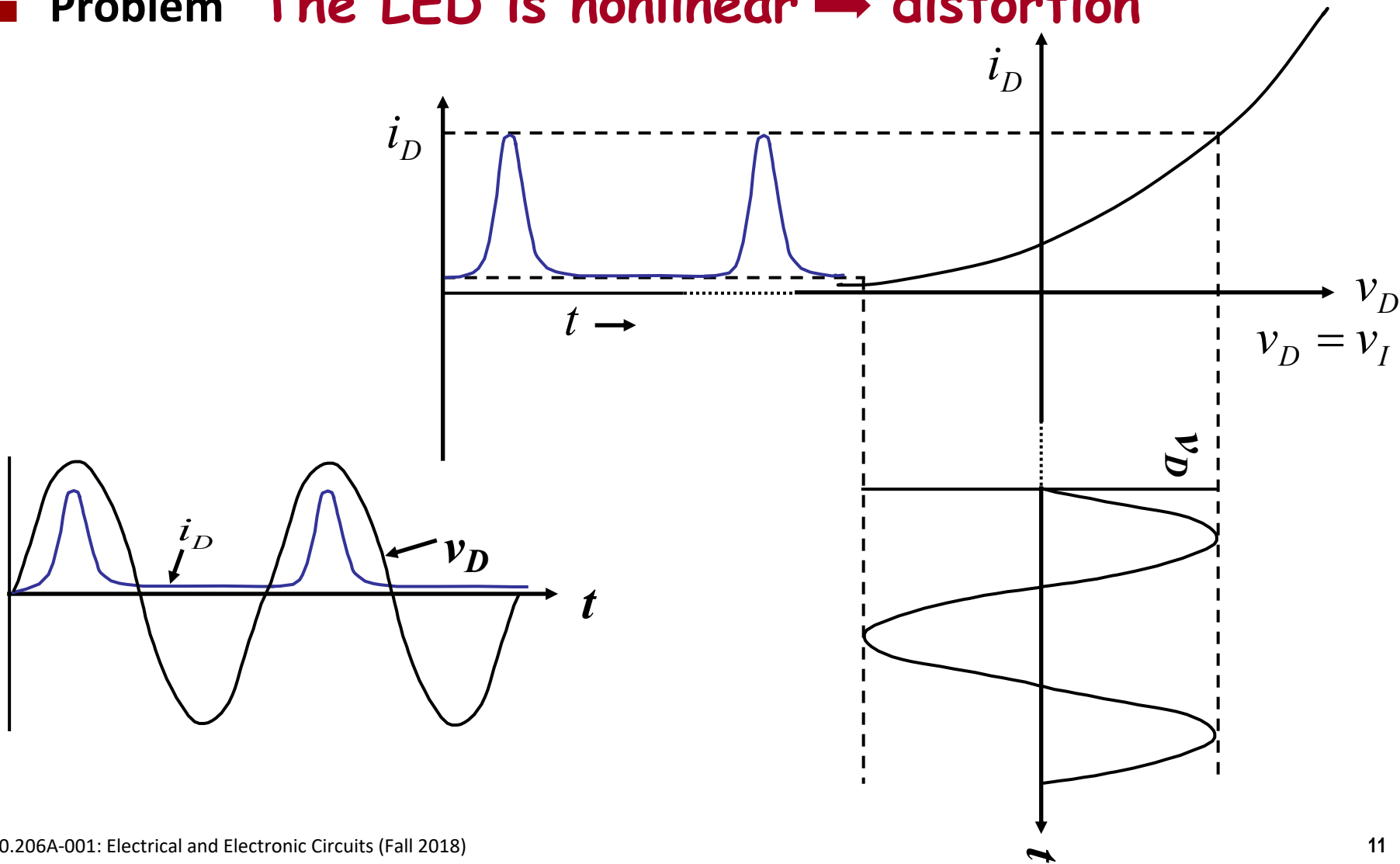
# Incremental Analysis

■ Problem **The LED is nonlinear  $\rightarrow$  distortion**



# Incremental Analysis

- If only it were linear ...  $i_D$

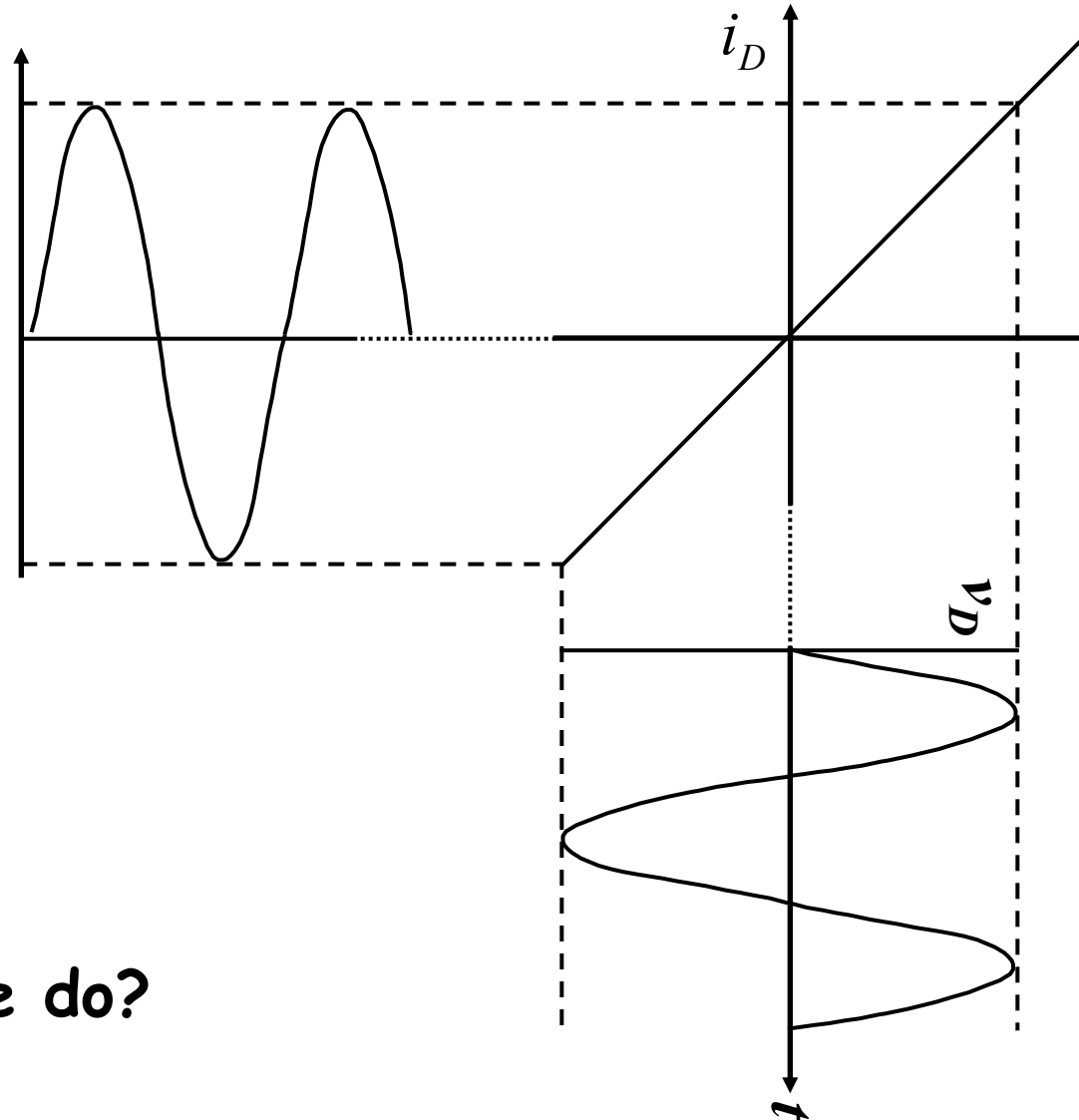


it would've been ok.


What do we do?

# Incremental Analysis

**Insight:**

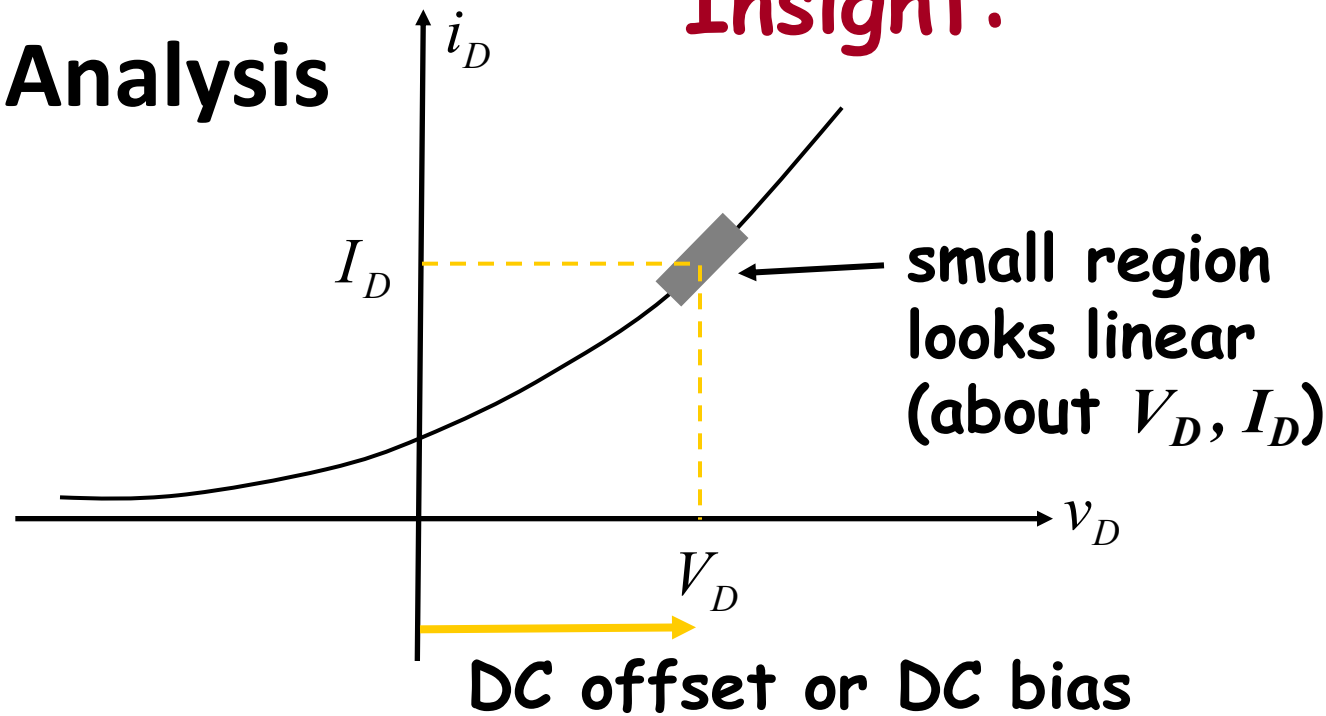


**Trick:**

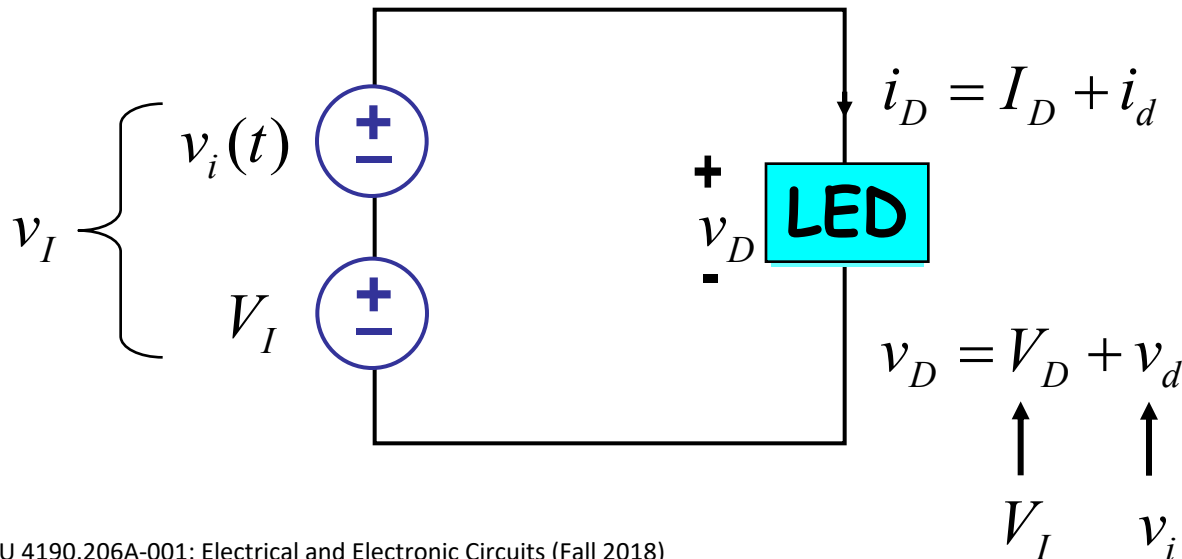



# Incremental Analysis

## Result

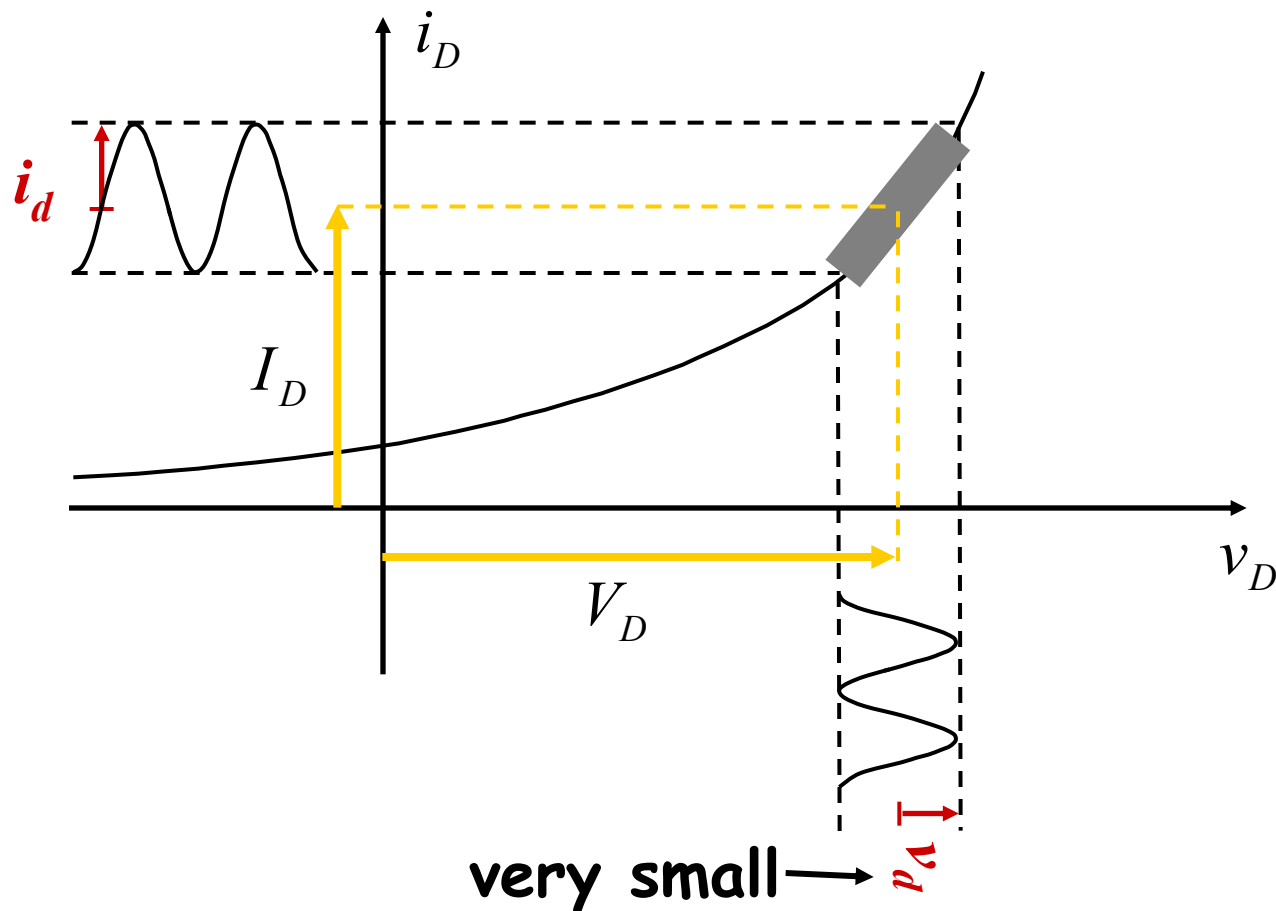

# Incremental Analysis

Result

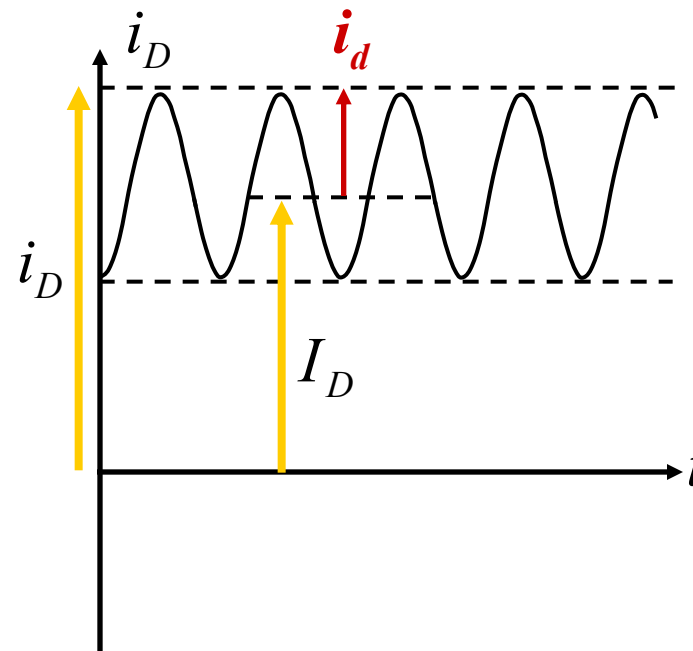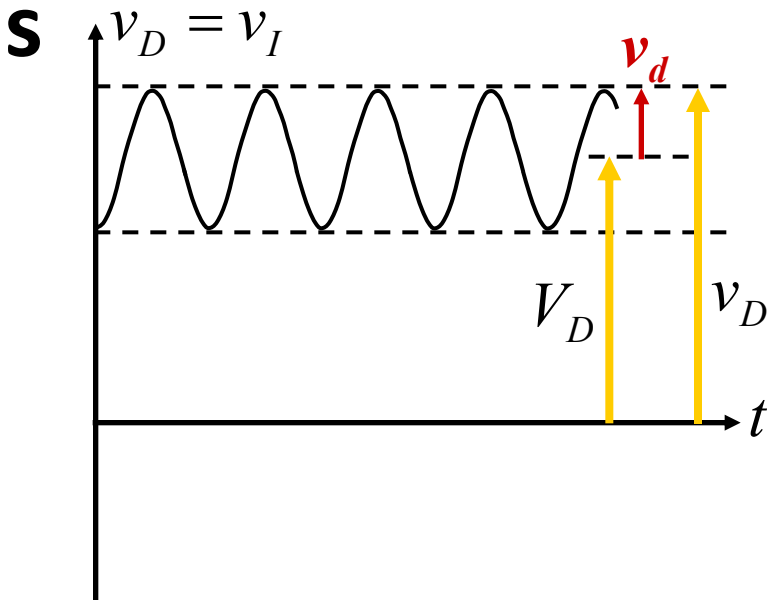

~linear!

# Incremental Analysis

## ■ The incremental method (or small signal method)

1. Operate at some DC offset or bias point  $V_D, I_D$ .
2. Superimpose small signal (music) on top of  $V_D$ .  $v_d$
3. Response  $i_d$  to small signal  $v_d$  is approximately linear.

Notation:  $i_D = I_D + i_d$

total DC small  
variable offset superimposed signal



# Incremental Analysis

## ■ What does this mean mathematically?

- Or, why is the small signal response linear?

**nonlinear**

$$i_D = f(v_D)$$

**We replaced**

$$v_D = V_D + \Delta v_D$$

**large DC**

**increment from  $V_D$**

**using Taylor's Expansion to expand  $f(v_D)$  near  $v_D = V_D$  :**

$$i_D = f(V_D) + \left. \frac{df(v_D)}{dv_D} \right|_{v_D=V_D} \cdot \Delta v_D$$

**neglect higher order terms**  
**because  $\Delta v_D$  is small**

$$+ \frac{1}{2!} \left. \frac{d^2 f(v_D)}{dv_D^2} \right|_{v_D=V_D} \cdot \Delta v_D^2 + \dots$$

# Incremental Analysis

## ■ What does this mean mathematically? (Cont'd)

$$i_D \approx \underbrace{f(V_D)}_{\text{constant w.r.t. } \Delta v_D} + \underbrace{\left. \frac{df(v_D)}{dv_D} \right|_{v_D=V_D}}_{\text{constant w.r.t. } \Delta v_D, \text{ slope at } V_D, I_D} \cdot \Delta v_D$$

We can write

$$\textcircled{\times} : I_D + \Delta i_D \approx f(V_D) + \left. \frac{df(v_D)}{dv_D} \right|_{v_D=V_D} \cdot \Delta v_D$$

# Incremental Analysis

- What does this mean mathematically? (Cont'd)

equating DC and time-varying parts,

$$I_D = f(V_D) \longrightarrow \text{operating point}$$

$$\Delta i_D = \underbrace{\left. \frac{df(v_D)}{dv_D} \right|_{v_D=V_D}}_{\text{constant w.r.t. } \Delta v_D} \cdot \Delta v_D$$

**so,  $\Delta i_D \propto \Delta v_D$**

**By notation,**


$$\begin{aligned} \Delta i_D &= i_d \\ \Delta v_D &= v_d \end{aligned}$$

# Incremental Analysis

- What does this mean mathematically? (Cont'd)

In our example,

$$i_D = a e^{b v_D}$$

From  :  $I_D + i_d \approx a e^{b V_D} + a e^{b V_D} \cdot b \cdot v_d$

Equate DC and incremental terms,

$$\boxed{I_D = a e^{b V_D}} \longrightarrow \text{operating point}$$

[ aka bias pt.  
aka DC offset

$$i_d = \underbrace{a e^{b V_D}}_{\text{constant}} b \cdot v_d$$

$$i_d = \underbrace{I_D \cdot b}_{\text{constant}} \cdot v_d \longrightarrow \text{small signal behavior}$$


**constant**  $\longrightarrow$  **linear!**

# Incremental Analysis

## ■ Graphical interpretation

$$I_D = a e^{bV_D} \quad \longrightarrow \text{operating point}$$

$$i_d = I_D \cdot b \cdot v_d$$

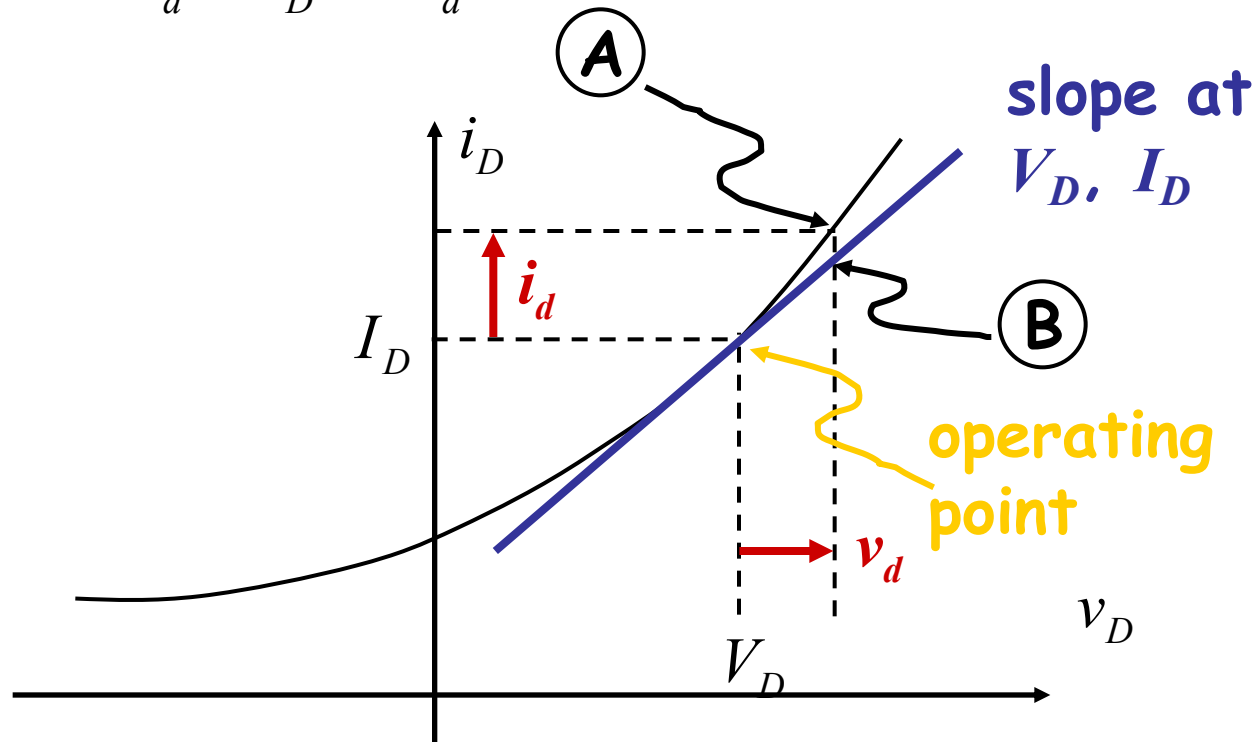


We are approximating (A) with (B)!

# Incremental Analysis


We saw the small signal 
 $\swarrow$  graphically  
 $\rightarrow$  mathematically  
 $\searrow$  **now, circuit**

Large signal circuit:

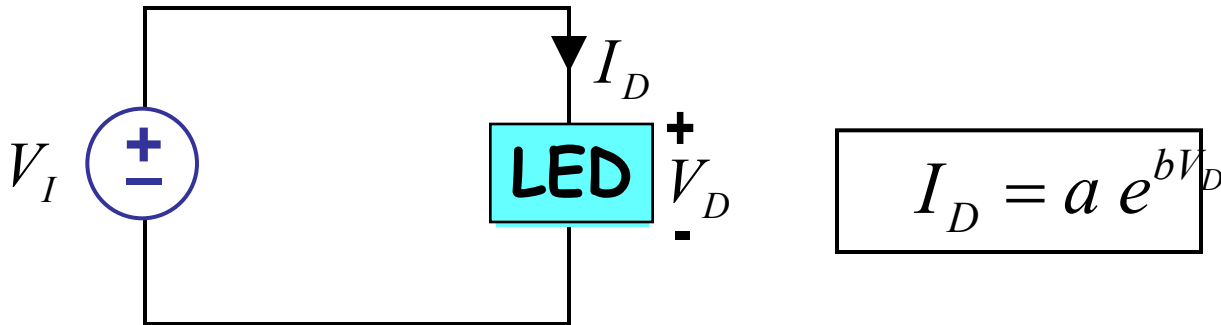


Small signal response:  $i_d = I_D b v_d$

behaves like:

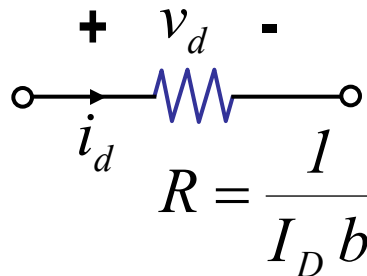


small signal circuit:

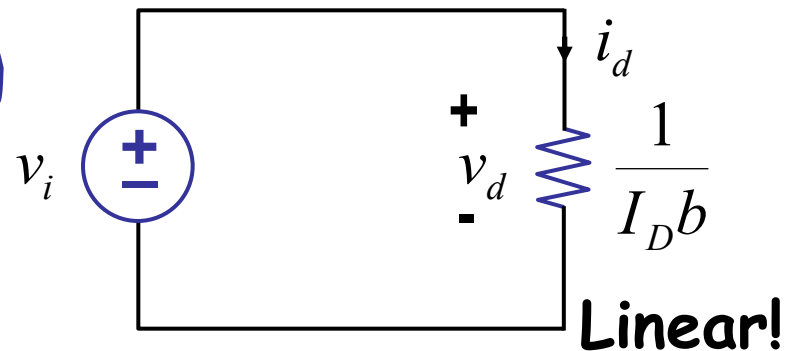

# Incremental Analysis
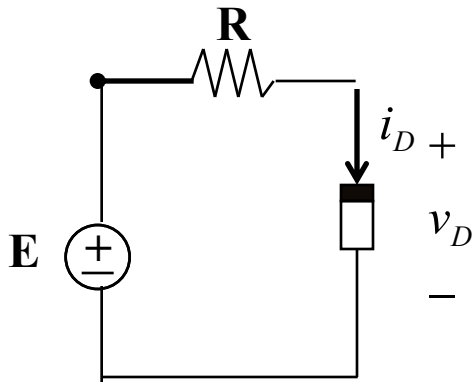
## ■ Example: Draw the small signal circuit



$$i_D = \begin{cases} Kv_D^2 & \text{for } v_D > 0 \\ 0 & \text{for } v_D \leq 0 \end{cases}$$

$$K = 1 \text{ mA/V}^2$$

$$V_D = 1 \text{ V}$$

# Conclusion

## ■ Nonlinear elements

- e.g., (light emitting) diodes

## ■ Solution methods

- Analytical method
- Graphical method
- Piecewise linear method (not covered, Chapter 4.4)
- Incremental analysis

## ■ Two types of non-linear circuits

- Digital circuit: assume the operating mode of the device
  - e.g., logic gates
- Analog circuit: bias + incremental analysis (small signal analysis)
  - e.g., amplifiers