

V-code: ???

Transients in Second-Order Circuits

Lecture 15

November 13th, 2018


Jae W. Lee (jaewlee@snu.ac.kr)

Computer Science and Engineering
Seoul National University

Slide credits: Prof. Anant Agarwal at MIT

V-code: ???


Second-Order Systems

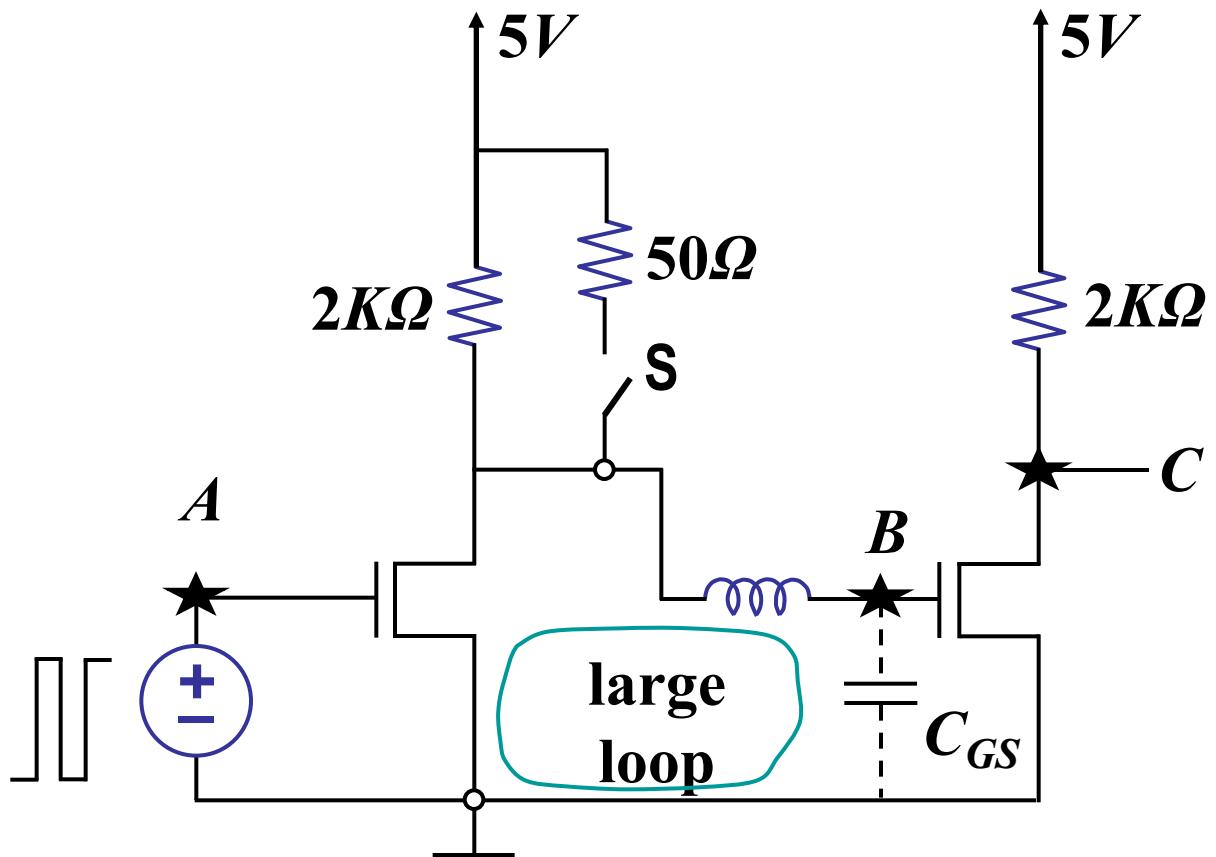

Our old friend, the inverter, driving another.
The parasitic inductance of the wire and the gate-to-source capacitance of the MOSFET are shown

V-code: ???

Second-Order Systems

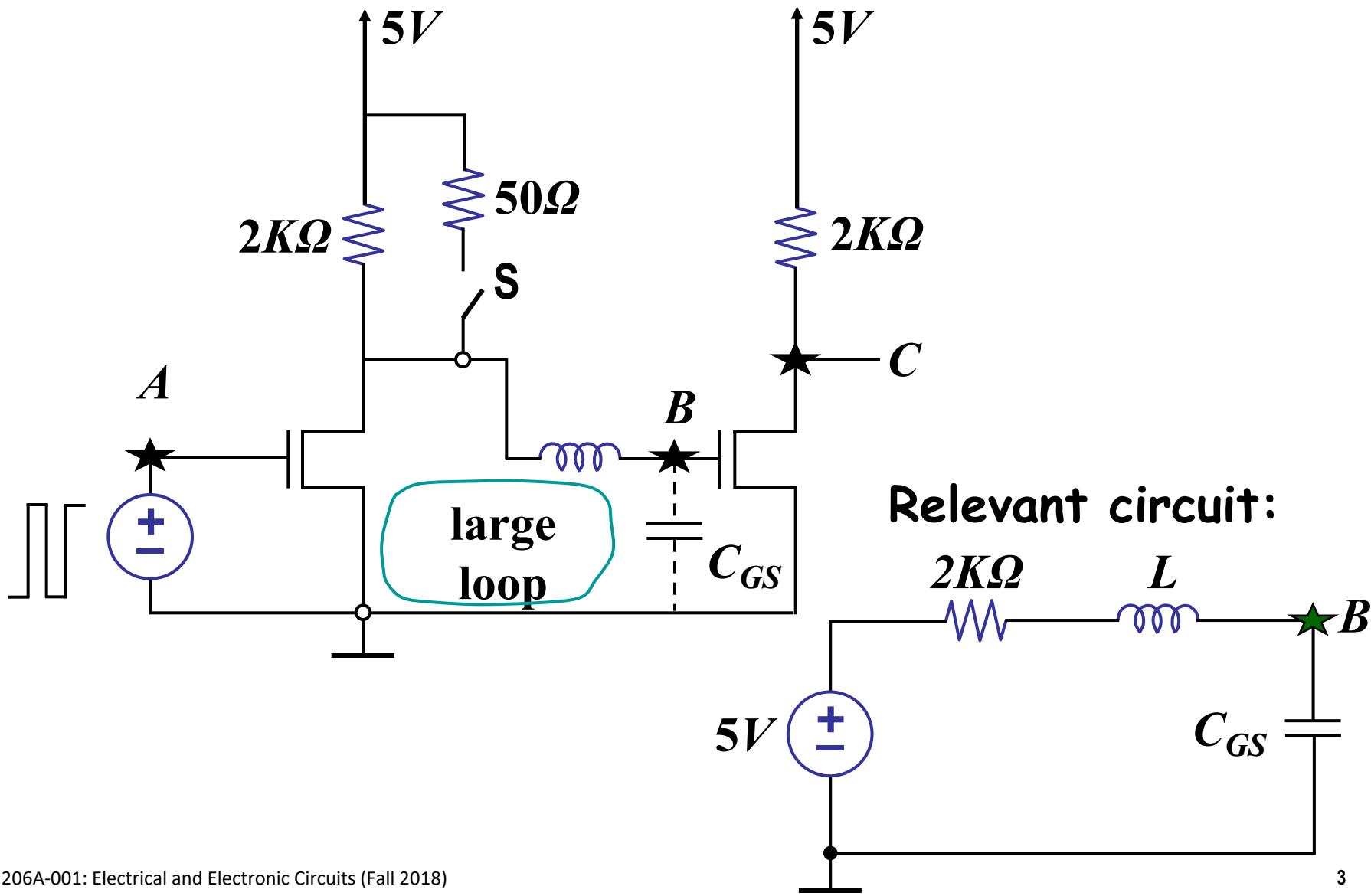


Second-Order Systems

V-code: ???

Observed Output

$2k\Omega$

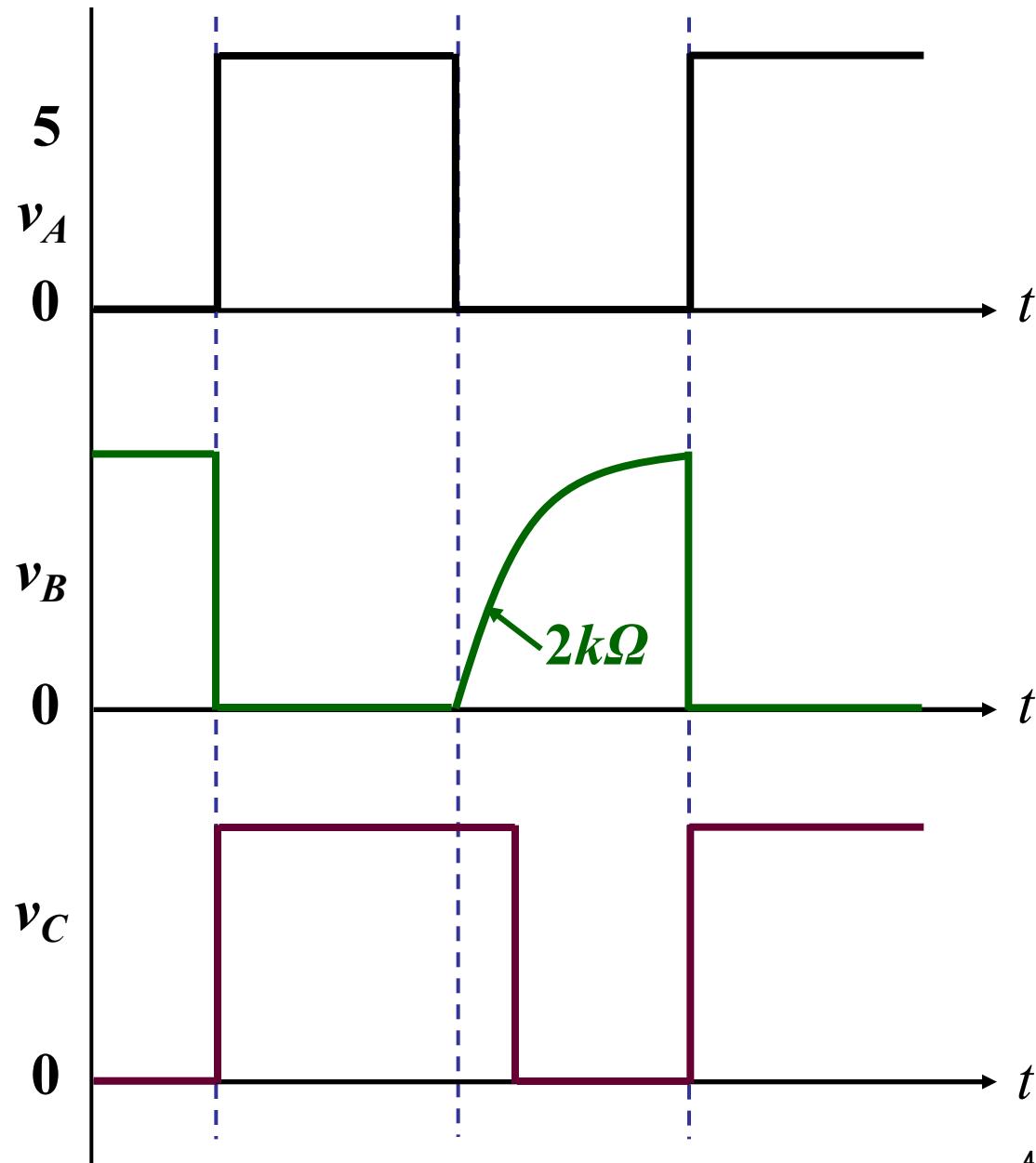Now, let's try to speed up our inverter by closing the switch S to lower the effective resistance




Second-Order Systems

V-code: ???

Observed Output

$\sim 50\Omega$

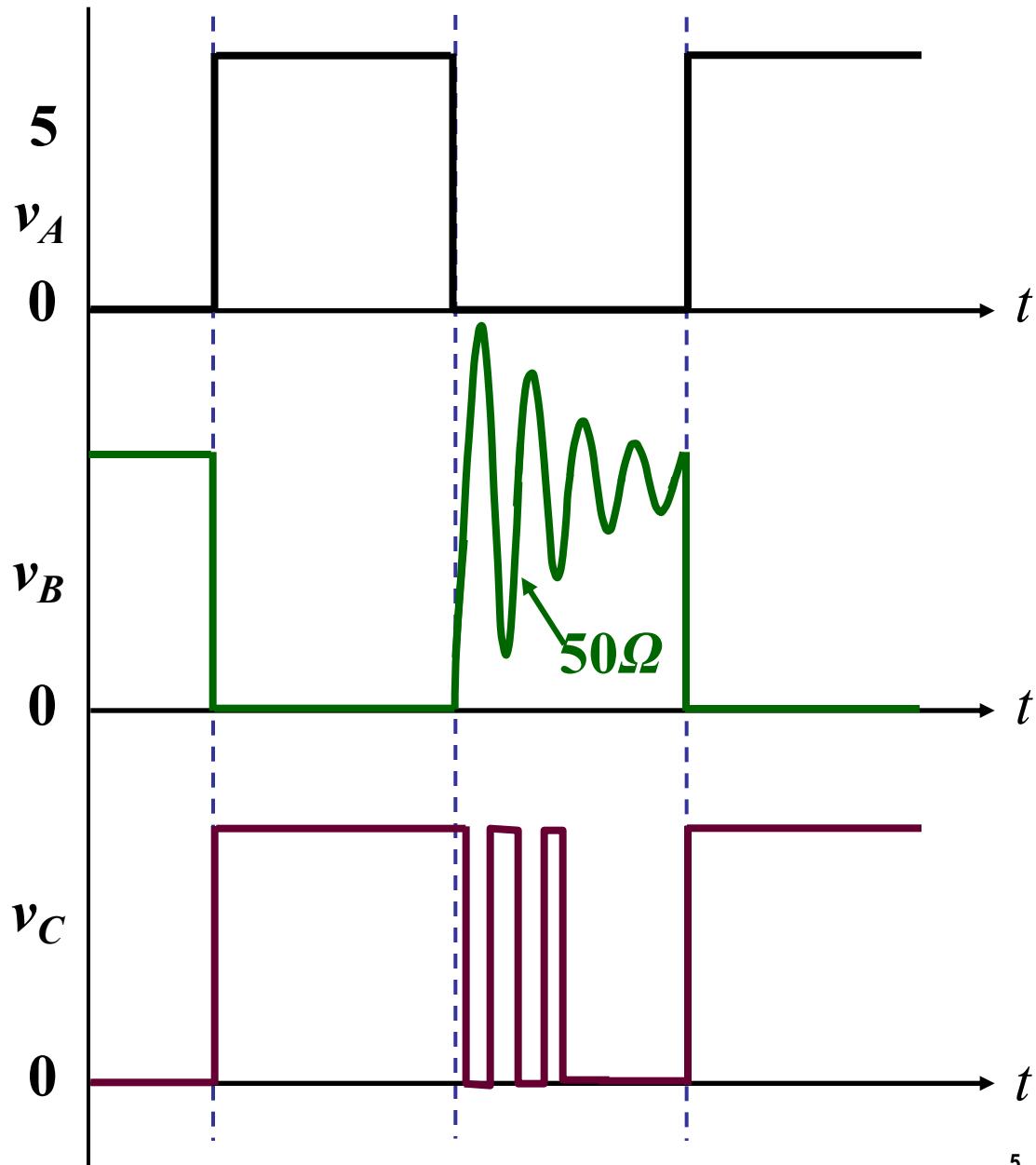

V-code: ???

Outline

Textbook: 12.1, 12.2, 12.3, 12.5, 12.7

- LC Circuits
- RLC Circuits
- Idealized Analysis

Series LC Circuits

First, let's analyze
the LC network


Node method: $i(t) = C \frac{dv}{dt}$

$$\frac{1}{L} \int_{-\infty}^t (v_I - v) dt = C \frac{dv}{dt}$$

$$\frac{1}{L} (v_I - v) = C \frac{d^2v}{dt^2}$$

$$LC \frac{d^2v}{dt^2} + v = v_I$$

$\underbrace{}$
time²

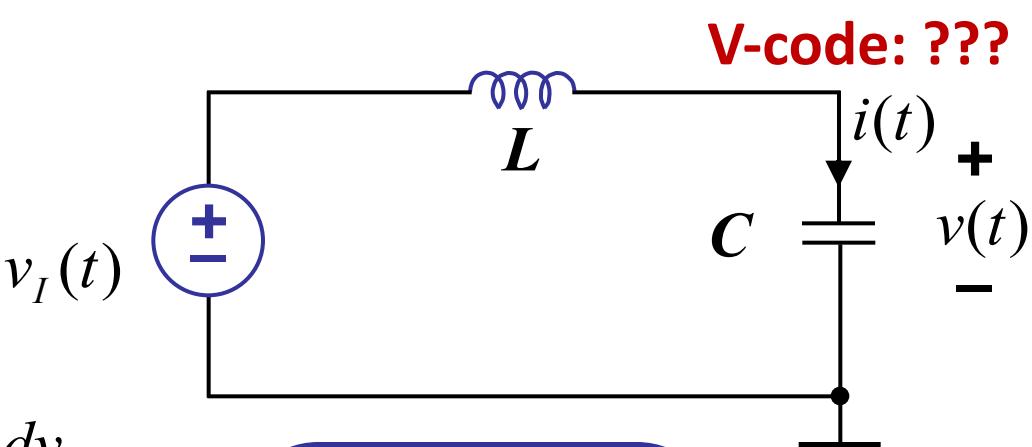

Recall

$$v_I - v = L \frac{di}{dt}$$

$$\frac{1}{L} \int_{-\infty}^t (v_I - v) dt = i$$

v, i state variables

Series LC Circuits

Solving

Recall, the method of homogeneous and particular solutions:

- ① Find the particular solution.
- ② Find the homogeneous solution.
↓
4 steps
- ③ The total solution is the sum of the particular and homogeneous.
Use initial conditions to solve for the remaining constants.

$$\nu = \nu_P(t) + \nu_H(t)$$


V-code: ???

Series LC Circuits

Let's solve

$$LC \frac{d^2v}{dt^2} + v = v_I$$

For input

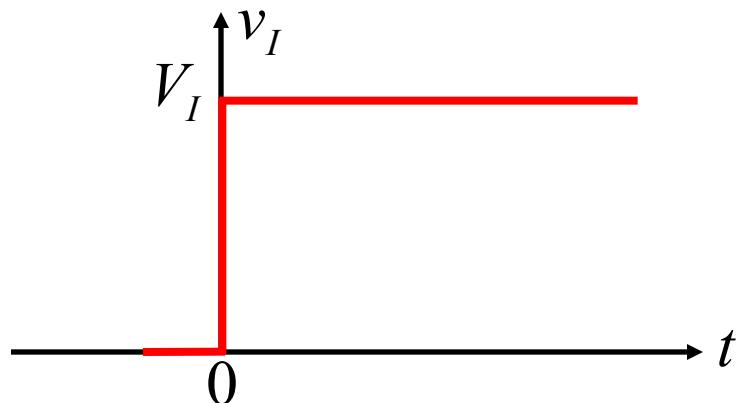

And for initial conditions

$$v(0) = 0 \quad i(0) = 0 \quad [\text{ZSR}]$$

Series LC Circuits

① Particular solution

$$LC \frac{d^2v_P}{dt^2} + v_P = V_0$$

$v_P = V_0$ is a solution.

Series LC Circuits

② Homogeneous solution

Solution to

$$LC \frac{d^2v_H}{dt^2} + v_H = 0$$

Recall, v_H : solution to homogeneous
equation (drive set to zero)

Four-step method:

Ⓐ Assume solution of the form*

$$v_H = A e^{st}, \quad A, s = ?$$

*Differential equations are commonly solved by guessing solutions

so, $LC \cancel{A} s^2 e^{st} + \cancel{A} e^{st} = 0$

Ⓑ $s^2 = -\frac{1}{LC}$ **characteristic equation**

$$s = \pm j \sqrt{\frac{1}{LC}}$$

$$j = \sqrt{-1}$$

Series LC Circuits

② Homogeneous solution

Solution to

$$LC \frac{d^2v_H}{dt^2} + v_H = 0$$

Four-step method: (cont'd)

③ Roots $s = \pm j\omega_o$

$$\omega_o = \sqrt{\frac{1}{LC}}$$

General solution,

④ $v_H = A_1 e^{j\omega_o t} + A_2 e^{-j\omega_o t}$

Series LC Circuits

③ Total solution

$$v(t) = v_P(t) + v_H(t)$$

$$v(t) = V_0 + A_1 e^{j\omega_o t} + A_2 e^{-j\omega_o t}$$

Find unknowns from initial conditions.

$$v(0) = 0$$

$$0 = V_0 + A_1 + A_2$$

$$i(0) = 0$$

$$i(t) = C \frac{dv}{dt}$$

$$i(t) = CA_1 j\omega_o e^{j\omega_o t} - CA_2 j\omega_o e^{-j\omega_o t}$$

so, $0 = CA_1 j\omega_o - CA_2 j\omega_o$

or, $A_1 = A_2$

$$-V_0 = 2A$$

$$A_1 = -\frac{V_0}{2}$$

so, $v(t) = V_0 - \frac{V_0}{2} (e^{j\omega_o t} + e^{-j\omega_o t})$

Series LC Circuits

③ Total solution

Remember Euler relation

$$e^{jx} = \cos x + j \sin x$$

(verify using Taylor's expansion)

$$\frac{e^{jx} + e^{-jx}}{2} = \cos x$$

so,

$$v(t) = V_0 - V_0 \cos \omega_o t$$

where

$$\omega_o = \frac{1}{\sqrt{LC}}$$



$$i(t) = CV_0 \omega_o \sin \omega_o t$$

The output looks sinusoidal

V-code: ???

Series LC Circuits

③ Total solution:
Plotting it

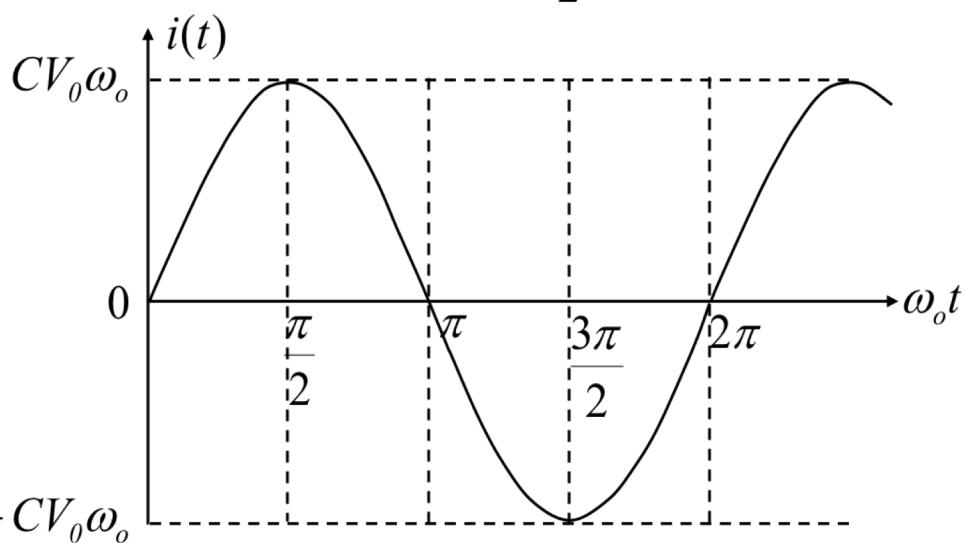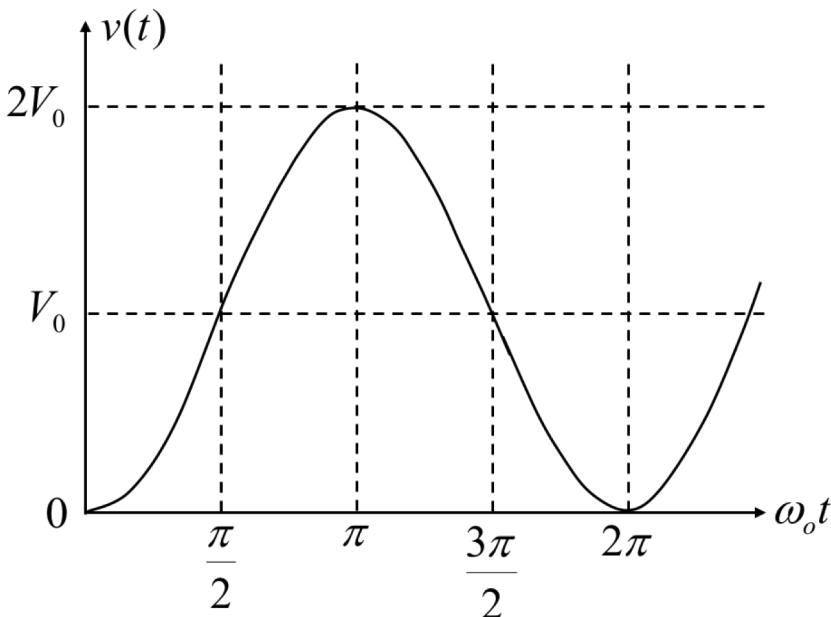

Series LC Circuits


Summary of Method

- ① Write DE for circuit by applying node method.
- ② Find particular solution v_P by guessing and trial & error.
- ③ Find homogeneous solution v_H
 - A Assume solution of the form Ae^{st} .
 - B Obtain characteristic equation.
 - C Solve characteristic equation for roots s_i .
 - D Form v_H by summing $A_i e^{s_i t}$ terms.
- ④ Total solution is $v_P + v_H$, solve for remaining constants using initial conditions.

Undriven LC Circuits

Example


What if we have:

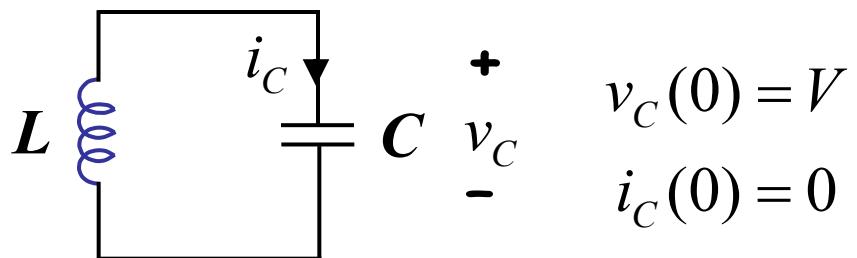

We can obtain the answer directly from the homogeneous solution ($V_0 = 0$).

Undriven LC Circuits

Example

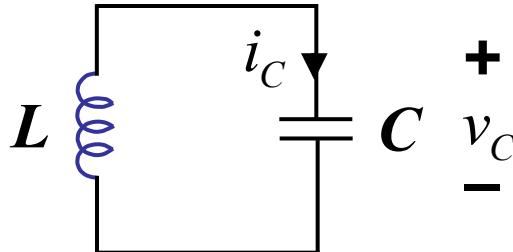

V-code: ???

$$v_C(0) = V$$

$$i_C(0) = 0$$

We can obtain the answer directly from the homogeneous solution ($V_0 = 0$).

$$v_C(t) = A_1 e^{j\omega_o t} + A_2 e^{-j\omega_o t}$$

$$v_C(0) = V$$

$$V = A_1 + A_2$$

$$i_C(0) = 0$$

$$0 = CA_1 j\omega_o - CA_2 j\omega_o$$

or $A_1 = A_2 = \frac{V}{2}$



or $v_C = \frac{V}{2} (e^{j\omega_o t} + e^{-j\omega_o t})$

$$v_C = V \cos \omega_o t$$

$$i_C = -CV \omega_o \sin \omega_o t$$

Undriven LC Circuits

Example

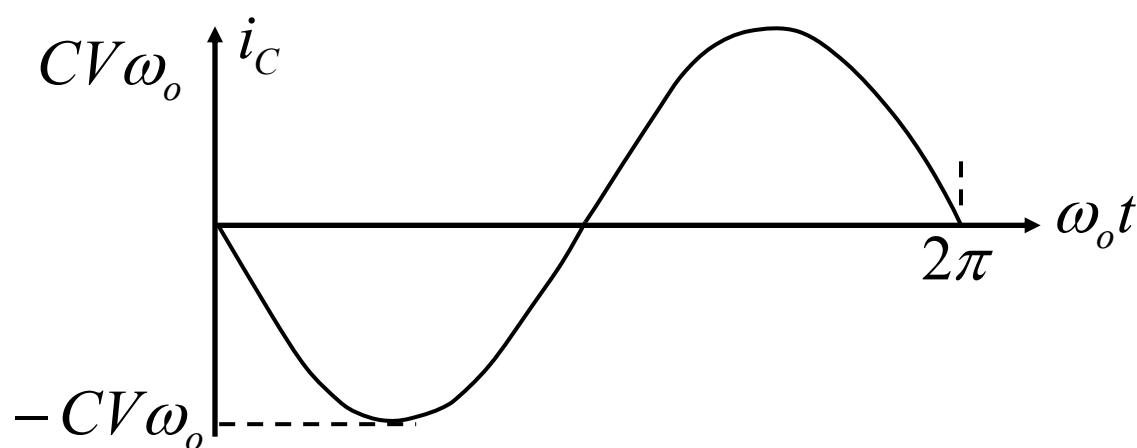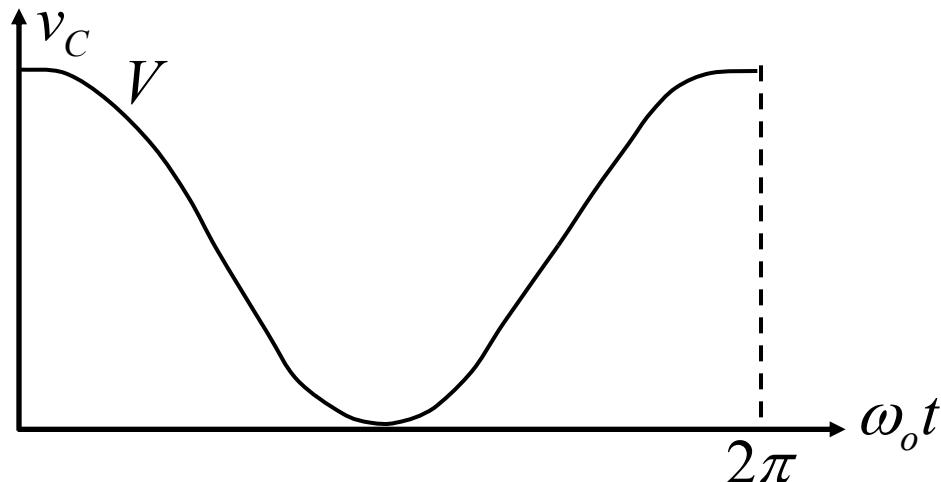


V-code: ???

Undriven LC Circuits

Energy

$$C: \frac{1}{2} Cv_C^2$$

$$L: \frac{1}{2} Li_C^2$$

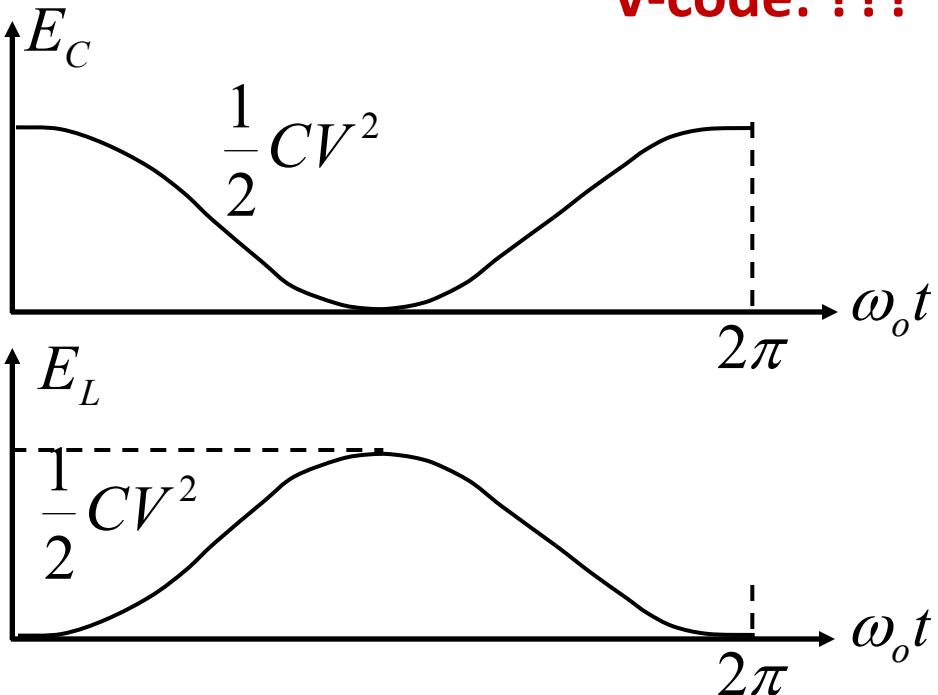

Notice $\frac{1}{2} Cv_C^2 + \frac{1}{2} Li_C^2 = \frac{1}{2} CV^2$

Total energy in the system is a constant, but it sloshes back and forth between the Capacitor and the inductor

V-code: ???

Undriven LC Circuits

- **Example 12.1: Oscillation frequency of i_L and v_C ? Peak values?**

$C = 1\mu F, L = 100\mu H, (i_L = 0.5A, v_C = 10V \text{ at some } t)$

V-code: ???

Outline

Textbook: 12.1, 12.2, 12.3, 12.5, 12.7


- LC Circuits
- RLC Circuits
- Idealized Analysis

V-code: ???

Review: LC Circuit


Total solution

$$v(t) = V_I - V_I \cos \omega_o t$$

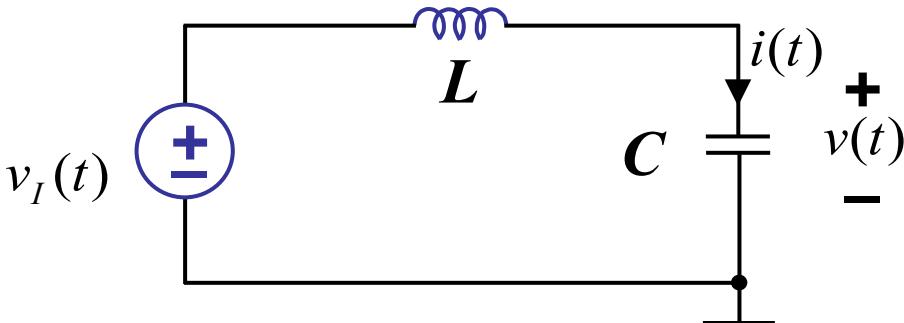



where

$$\omega_o = \frac{1}{\sqrt{LC}}$$

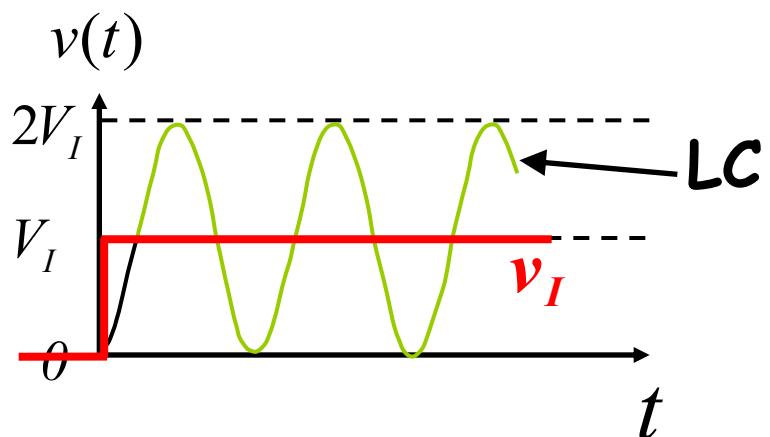

V-code: ???

Series RLC Circuits

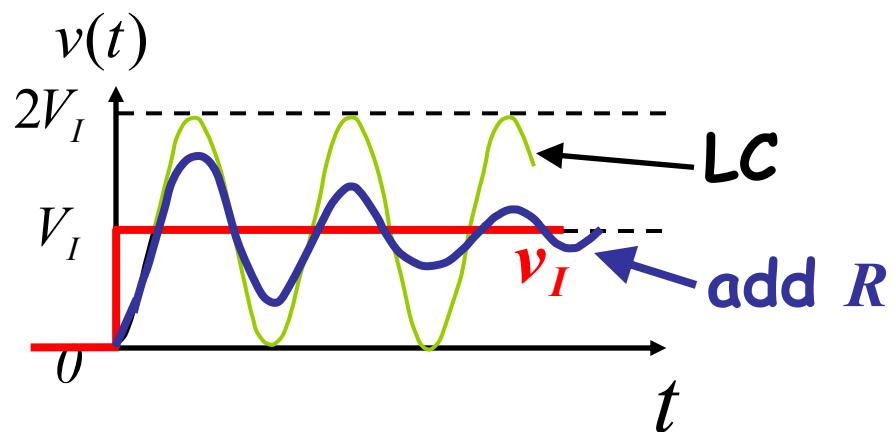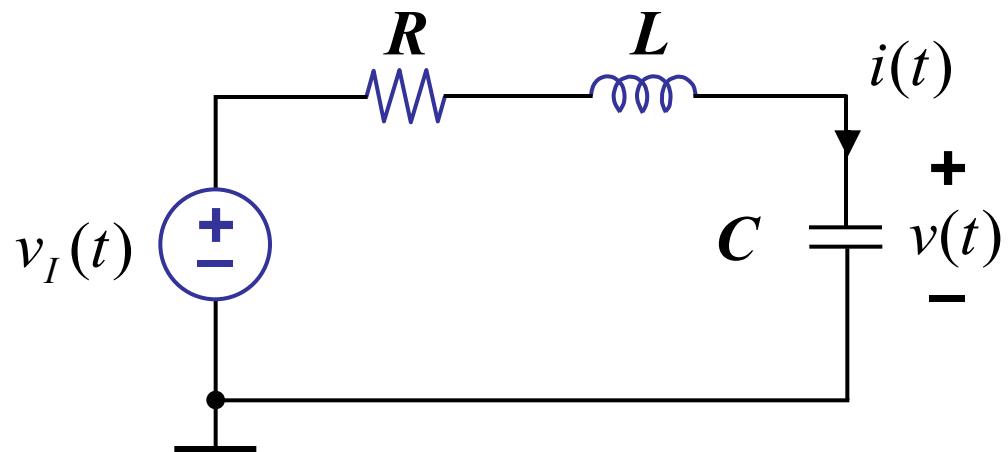

Damped sinusoids with R!

Series RLC Circuits

Let's analyze the RLC network


Node method:

$$v_A : \frac{1}{L} \int_{-\infty}^t (v_I - v_A) dt = \frac{v_A - v}{R}$$

$$v : \frac{v_A - v}{R} = C \frac{dv}{dt}$$

$$\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{1}{LC} v = \frac{1}{LC} v_I$$

$v_I(t)$

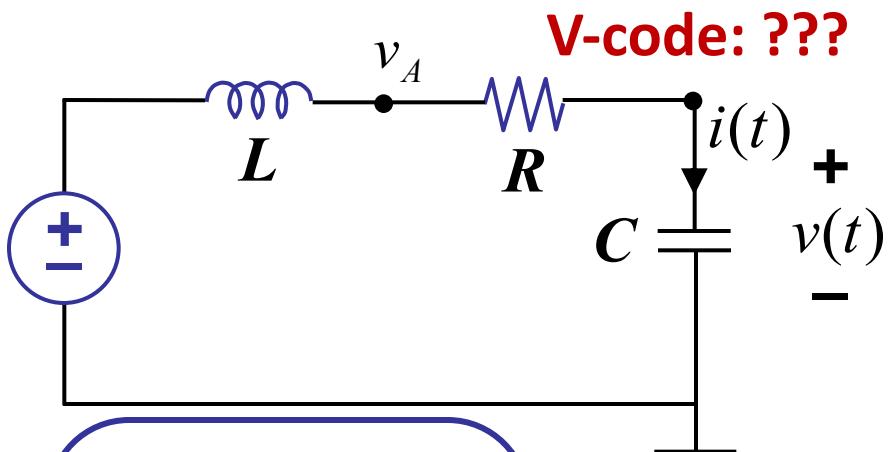

Recall
element rules

L:

$$v_L = L \frac{di}{dt}$$

$$\frac{1}{L} \int_{-\infty}^t v_L dt = i$$


C:

$$i_C = C \frac{dv_C}{dt}$$

v, i state variables

Series RLC Circuits

Let's analyze the RLC network

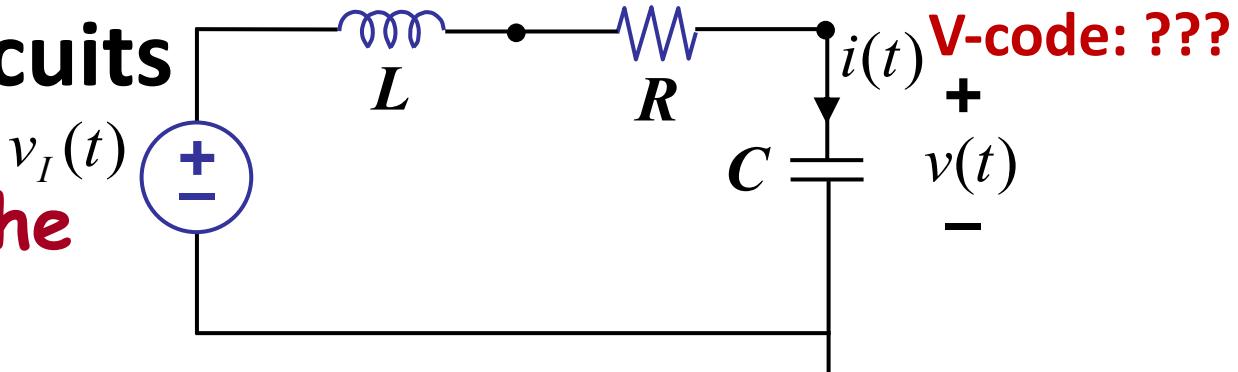

Node method:

$$v_A : \quad \frac{1}{L} \int_{-\infty}^t (v_I - v_A) dt = \frac{v_A - v}{R}$$

$$v : \quad \frac{v_A - v}{R} = C \frac{dv}{dt}$$

$$\frac{1}{L} (v_I - v_A) = C \frac{d^2 v}{dt^2}$$

$$\frac{1}{LC} (v_I - v_A) = \frac{d^2 v}{dt^2}$$

$$v_A = RC \frac{dv}{dt} + v$$

$$\frac{1}{LC} (v_I - RC \frac{dv}{dt} - v) = \frac{d^2 v}{dt^2}$$

$$\frac{d^2 v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{1}{LC} v = \frac{1}{LC} v_I$$

V-code: ???

Series RLC Circuits

Solving

Recall, the method of homogeneous and particular solutions:

- ① Find the particular solution.
- ② Find the homogeneous solution.
↓
4 steps
- ③ The total solution is the sum of the particular and homogeneous.
Use initial conditions to solve for the remaining constants.

$$\nu = \nu_P(t) + \nu_H(t)$$


V-code: ???

Series RLC Circuits

Let's solve

$$\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{1}{LC} v = \frac{1}{LC} v_I$$

For input

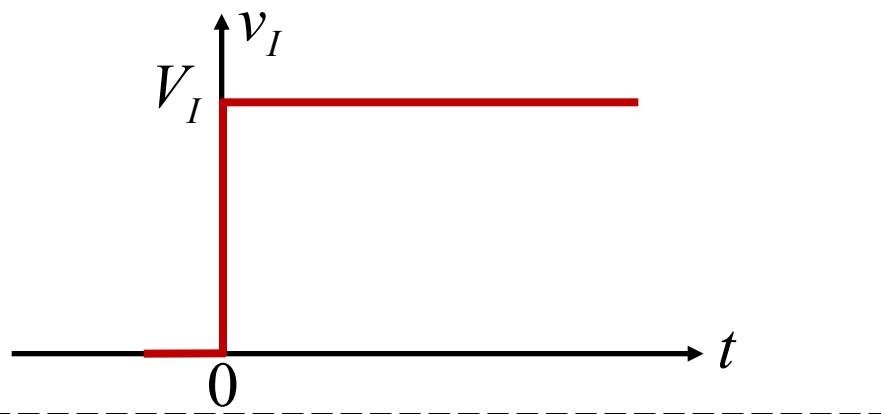

And for initial conditions

$$v(0) = 0 \quad i(0) = 0 \quad [\text{ZSR}]$$

V-code: ???

Series RLC Circuits

① Particular solution

$$\frac{d^2v_P}{dt^2} + \frac{R}{L} \frac{dv_P}{dt} + \frac{1}{LC} v_P = \frac{1}{LC} V_I$$

$v_P = V_I$ **is a solution.**

Series RLC Circuits

② Homogeneous solution

Solution to $\frac{d^2v_H}{dt^2} + \frac{R}{L} \frac{dv_H}{dt} + \frac{1}{LC} v_H = 0$

Recall, v_H : solution to homogeneous
equation (drive set to zero)

Four-step method:

Ⓐ Assume solution of the form

$$v_H = A e^{st}, \quad A, s = ?$$

Ⓑ Form the characteristic equation $f(s)$

Ⓒ Find the roots of the characteristic equation s_1, s_2

Ⓓ General solution $v_H = A_1 e^{s_1 t} + A_2 e^{s_2 t}$

Series RLC Circuits

② Homogeneous solution

Solution to $\frac{d^2v_H}{dt^2} + \frac{R}{L} \frac{dv_H}{dt} + \frac{1}{LC} v_H = 0$

Ⓐ Assume solution of the form

$$v_H = A e^{st}, \quad A, s = ?$$

so, $\cancel{A}s^2 e^{st} + \frac{R}{L} \cancel{A} s e^{st} + \frac{1}{LC} \cancel{A} e^{st} = 0$

Ⓑ

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

{ characteristic
equation

$$s^2 + 2\alpha s + \omega_o^2 = 0$$

$$\omega_o = \sqrt{\frac{1}{LC}}$$

$$\alpha = \frac{R}{2L}$$

Series RLC Circuits

② Homogeneous solution

Solution to $\frac{d^2v_H}{dt^2} + \frac{R}{L} \frac{dv_H}{dt} + \frac{1}{LC} v_H = 0$

(Cont'd)

③ Roots

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_o^2}$$
$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_o^2}$$

④ General solution

$$v_H = A_1 e^{(-\alpha + \sqrt{\alpha^2 - \omega_o^2})t} + A_2 e^{(-\alpha - \sqrt{\alpha^2 - \omega_o^2})t}$$

V-code: ???

Series RLC Circuits

③ Total solution

$$v(t) = v_P(t) + v_H(t)$$

$$v(t) = V_I + A_1 e^{(-\alpha + \sqrt{\alpha^2 - \omega_o^2})t} + A_2 e^{(-\alpha - \sqrt{\alpha^2 - \omega_o^2})t}$$

Find unknowns from initial conditions.

$$v(0) = 0 : 0 = V_I + A_1 + A_2$$

$$i(0) = 0 :$$

$$i(t) = C \frac{dv}{dt} = CA_1 (-\alpha + \sqrt{\alpha^2 - \omega_o^2}) e^{(-\alpha + \sqrt{\alpha^2 - \omega_o^2})t} +$$

$$CA_2 (-\alpha - \sqrt{\alpha^2 - \omega_o^2}) e^{(-\alpha - \sqrt{\alpha^2 - \omega_o^2})t}$$

$$\text{so, } 0 = A_1 (-\alpha + \sqrt{\alpha^2 - \omega_o^2}) + A_2 (-\alpha - \sqrt{\alpha^2 - \omega_o^2})$$

Mathematically: solve for unknowns
done.

Series RLC Circuits

V-code: ???


Let's stare at this a while longer...

3 cases:

$$\alpha > \omega_o$$

Overdamped
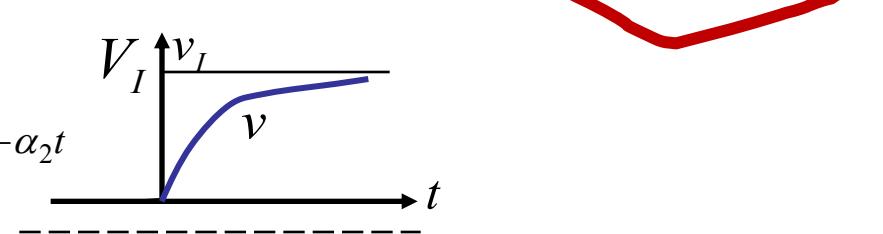
$$v(t) = V_I + A_1 e^{-\alpha t} e^{\left(\sqrt{\alpha^2 - \omega_o^2}\right)t} + A_2 e^{-\alpha t} e^{\left(-\sqrt{\alpha^2 - \omega_o^2}\right)t}$$



$$\alpha < \omega_o$$

Underdamped

$$v(t) = V_I + A_1 e^{-\alpha t} e^{\left(j\sqrt{\omega_o^2 - \alpha^2}\right)t} + A_2 e^{-\alpha t} e^{\left(-j\sqrt{\omega_o^2 - \alpha^2}\right)t}$$

$$= V_I + A_1 e^{-\alpha t} e^{j\omega_d t} + A_2 e^{-\alpha t} e^{-j\omega_d t}$$

$$= V_I + K_1 e^{-\alpha t} \cos \omega_d t + K_2 e^{-\alpha t} \sin \omega_d t$$

$$\omega_d = \sqrt{\omega_o^2 - \alpha^2}$$

$$e^{j\omega_d t} = \cos \omega_d t + j \sin \omega_d t$$

$$\alpha = \omega_o$$

Critically damped

Later...

Series RLC Circuits

V-code: ???

Let's stare at underdamped a bit longer...

$\alpha < \omega_o$ Underdamped contd...

$$v(t) = V_I + K_1 e^{-\alpha t} \cos \omega_d t + K_2 e^{-\alpha t} \sin \omega_d t$$

$$v(0) = 0 : K_1 = -V_I$$

$$\begin{aligned} i(0) = 0 : i(t) &= C \frac{dv}{dt} \\ &= -CK_1 \alpha e^{-\alpha t} \cos \omega_d t - CK_2 \omega_d e^{-\alpha t} \sin \omega_d t \\ &\quad - CK_1 \alpha e^{-\alpha t} \sin \omega_d t + CK_2 \omega_d e^{-\alpha t} \cos \omega_d t \end{aligned}$$

$$0 = -K_1 \alpha + K_2 \omega_d$$

$$K_2 = -\frac{V_I \alpha}{\omega_d}$$

$$v(t) = V_I - V_I e^{-\alpha t} \cos \omega_d t - V_I \frac{\alpha}{\omega_d} e^{-\alpha t} \sin \omega_d t$$

Note:

For $R = 0 \implies \alpha = 0$

$$v(t) = V_I - V_I \cos \omega_o t$$

Same as LC as expected

Series RLC Circuits

V-code: ???


Let's stare at underdamped a bit longer...

$\alpha < \omega_0$ Underdamped contd...

$$v(t) = V_I - V_I e^{-\alpha t} \cos \omega_d t - V_I \frac{\alpha}{\omega_d} e^{-\alpha t} \sin \omega_d t$$

Remember, scaled sum of sines (of the same frequency) are also sines! -- Appendix B.7
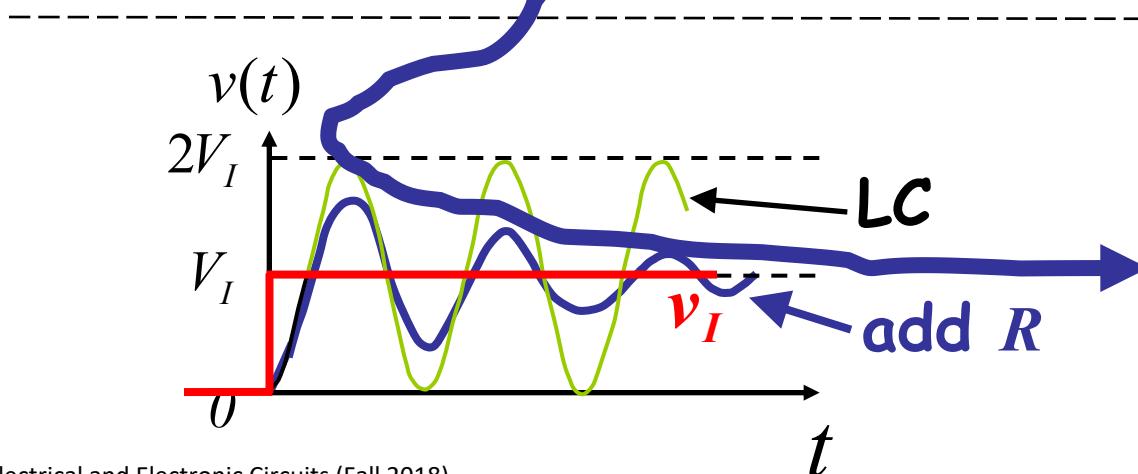
$$v(t) = V_I - V_I \frac{\omega_d}{\omega_d} e^{-\alpha t} \cos \left(\omega_d t - \tan^{-1} \frac{\alpha}{\omega_d} \right)$$



V-code: ???


Series RLC Circuits

$\alpha < \omega_o$ Underdamped contd...

$$v(t) = V_I - V_I e^{-\alpha t} \cos \omega_d t - V_I \frac{\alpha}{\omega_d} e^{-\alpha t} \sin \omega_d t$$

Remember, scaled sum of sines (of the same frequency) are also sines! -- Appendix B.7

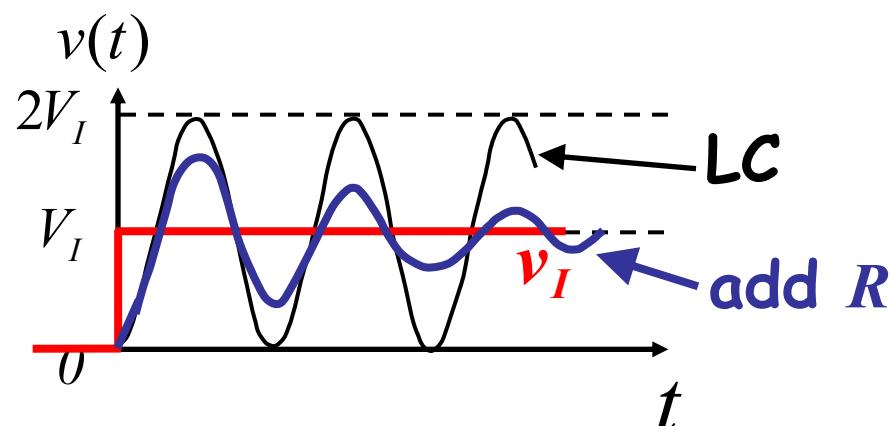
$$v(t) = V_I - V_I \frac{\omega_o}{\omega_d} e^{-\alpha t} \cos \left(\omega_d t - \tan^{-1} \frac{\alpha}{\omega_d} \right)$$



V-code: ???

Series RLC Circuits

$\alpha = \omega_o$ Critically damped

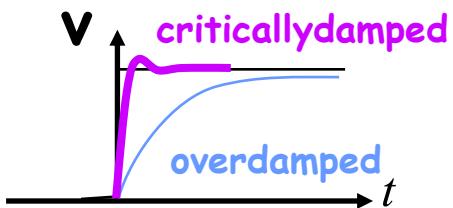


Section 12.2.3

V-code: ???

Series RLC Circuits

Remember this?
Closed the loop...

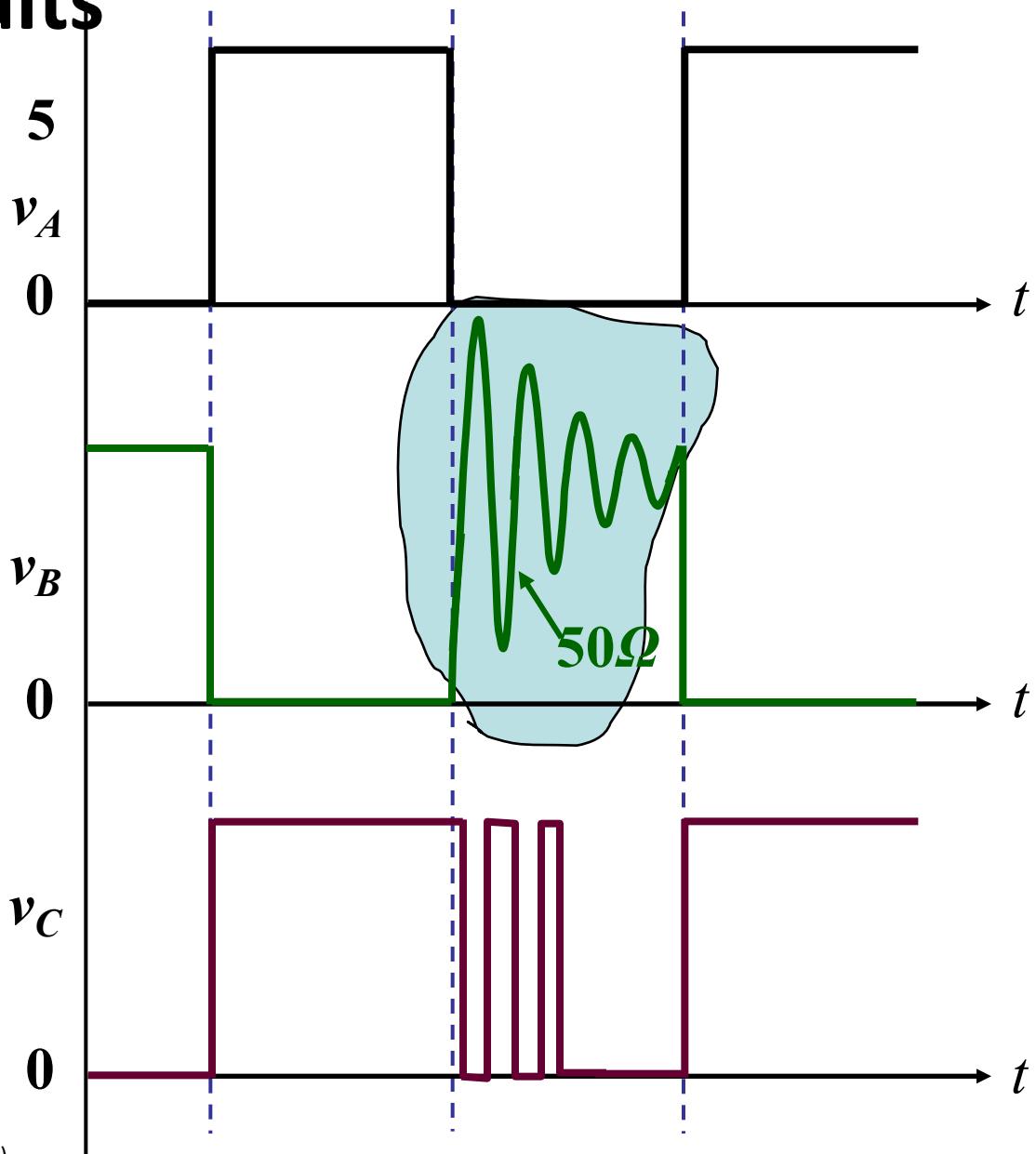

V-code: ???

Outline

Textbook: 12.1, 12.2, 12.3, 12.5, 12.7


- LC Circuits
- RLC Circuits
- Idealized Analysis

V-code: ???

Intuitive Analysis

Underdamped
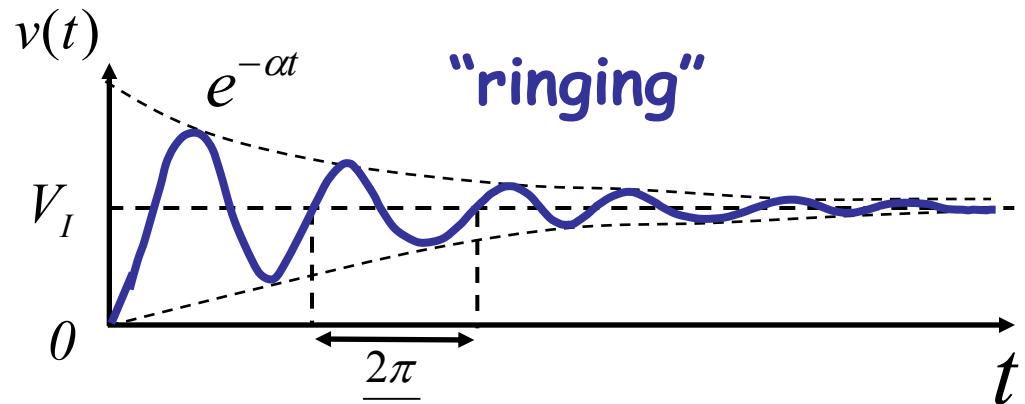
$$v(t) = V_I - V_I \frac{\omega_o}{\omega_d} e^{-\alpha t} \cos\left(\omega_d t - \tan^{-1} \frac{\alpha}{\omega_d}\right)$$



Characteristic equation

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

$$s^2 + 2\alpha s + \omega_o^2 = 0$$

ω_d : **Oscillation frequency**

$$\omega_d = \sqrt{\omega_o^2 - \alpha^2}$$

α : **Governs rate of decay**


V_I : **Final value**

$v(0)$: **Initial value**

$Q = \frac{\omega_o}{2\alpha}$: **Quality factor (approximately the number of cycles of ringing)**

V-code: ???

Intuitive Analysis

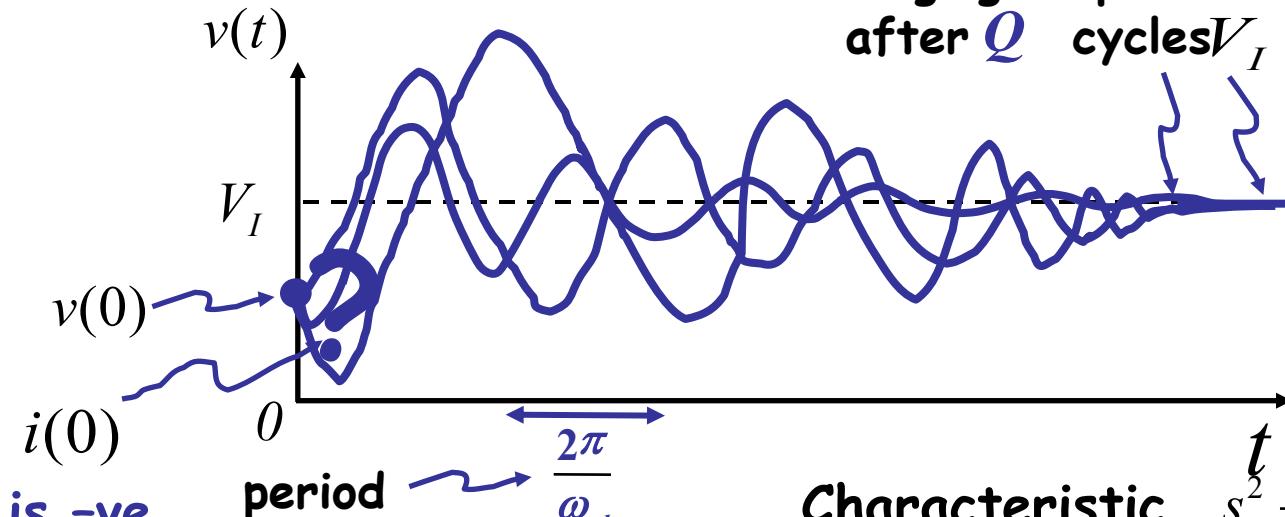

is -ve
so $v(t)$
must
drop


Characteristic
equation

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

$$s^2 + 2\alpha s + \omega_o^2 = 0$$

$$\omega_d = \sqrt{\omega_o^2 - \alpha^2}$$

$$Q = \frac{\omega_o}{2\alpha}$$

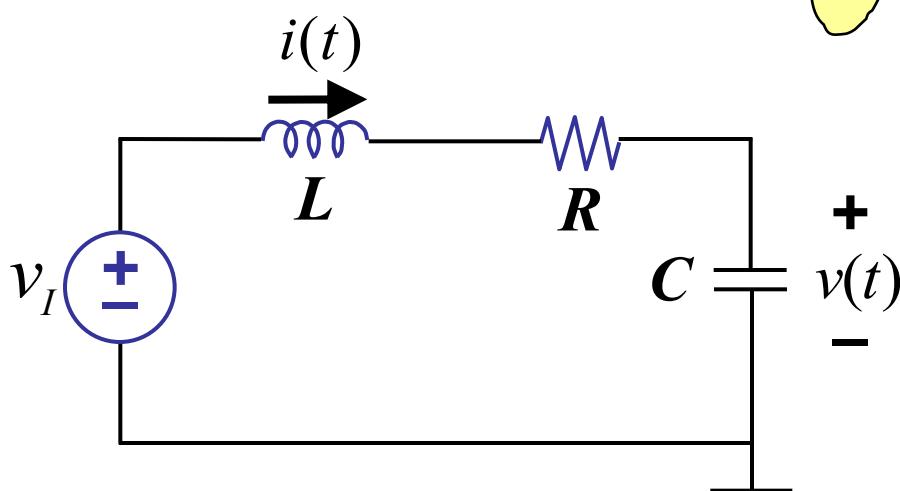

given
 $i(0)$ -ve
 $v(0)$ +ve