

4190.206A: Electrical and Electronic Circuits
(Prof. Jae Wook Lee)
Chapter 3. Network Theorems

Last Updated:
2018/9/21

<http://etl.snu.ac.kr/course/view.php?id=147773>

Solve the following exercise problems in the textbook (*Foundations of Analog and Digital Electronic Circuits*, Anant Agarwal and Jeffery H. Lang, 2005). Please submit your work **before** the class on the due date. We will grade it with pass/fail.

Due date: 10/2 (Tue) 3:30pm (Before class)

Place : Box at 301-554-1 or TAs

Example 2.28, Exercise 3.15, Exercise 3.25, Problem 3.8, Problem 3.9

* Example 2.28 is the one of web contents uploaded in the eTL. Please refer to eTL.