

Energy and Power in Digital Circuits

Lecture 14

November 9th, 2018

Jae W. Lee (jaewlee@snu.ac.kr)

Computer Science and Engineering

Seoul National University


Slide credits: Prof. Soonhoi Ha (SNU CSE)

Outline

Textbook: 11.1, 11.2, 11.3, 11.5

- **Power and Energy Relations for Simple RC Circuit**
- Average Power in an RC Circuit
- Power Dissipation in Logic Gates
- CMOS Logic

Power/Energy for Simple RC Circuit

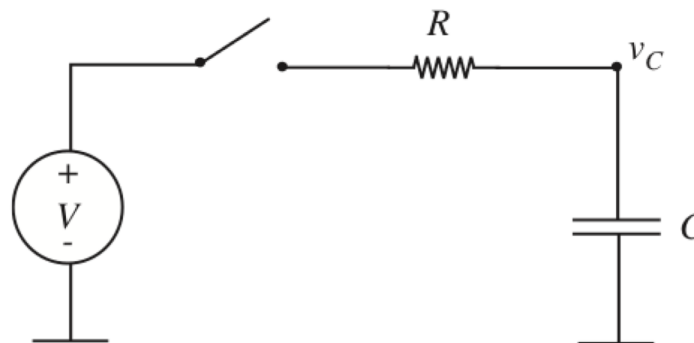

- Power delivered to a two-terminal element at any given instant of time t

$$p(t) = v(t)i(t)$$

- $i(t)$ is positive if the current enters into (+) terminal of the element
- e.g., if both $v(t)$ and $i(t)$ are positive:
 - A resistor dissipates energy.
 - A capacitor stores energy.

Power/Energy for Simple RC Circuit

- Energy supplied by the voltage source over an interval of time $0 \rightarrow T$:

$$w = \int_0^T p(t) dt.$$

- Example: if $p(t) = (V^2/R) * e^{-t/RC}$, total energy supplied over time $t=0 \rightarrow \infty$:

$$\begin{aligned} w &= \int_{t=0}^{t=\infty} \frac{V^2}{R} e^{\frac{-t}{RC}} dt \\ &= -\frac{V^2}{R} RC e^{\frac{-t}{RC}} \bigg|_{t=0}^{t=\infty} \\ &= CV^2. \end{aligned}$$


- Half of the energy dissipated by resistor; the other half stored in capacitor ($\frac{1}{2}CV^2$).

Outline


Textbook: 11.1, 11.2, 11.3, 11.5

- Power and Energy Relations for Simple RC Circuit
- **Average Power in an RC Circuit**
- Power Dissipation in Logic Gates
- CMOS Logic

RC Circuit with a Switch

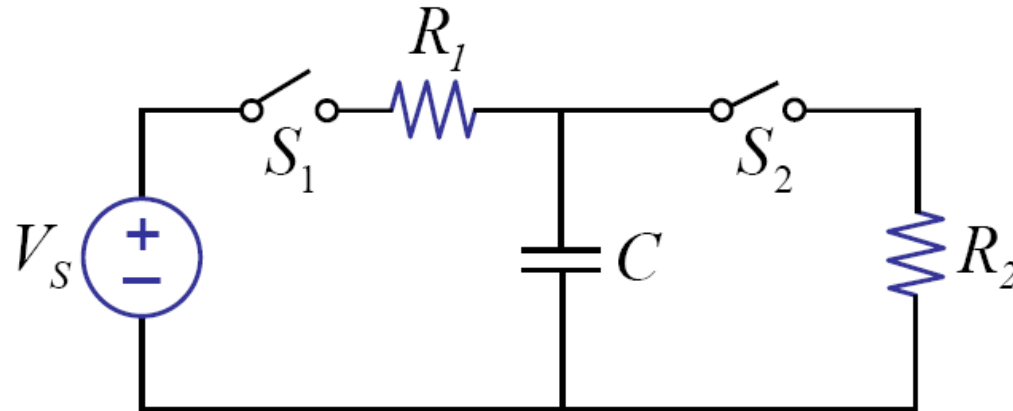


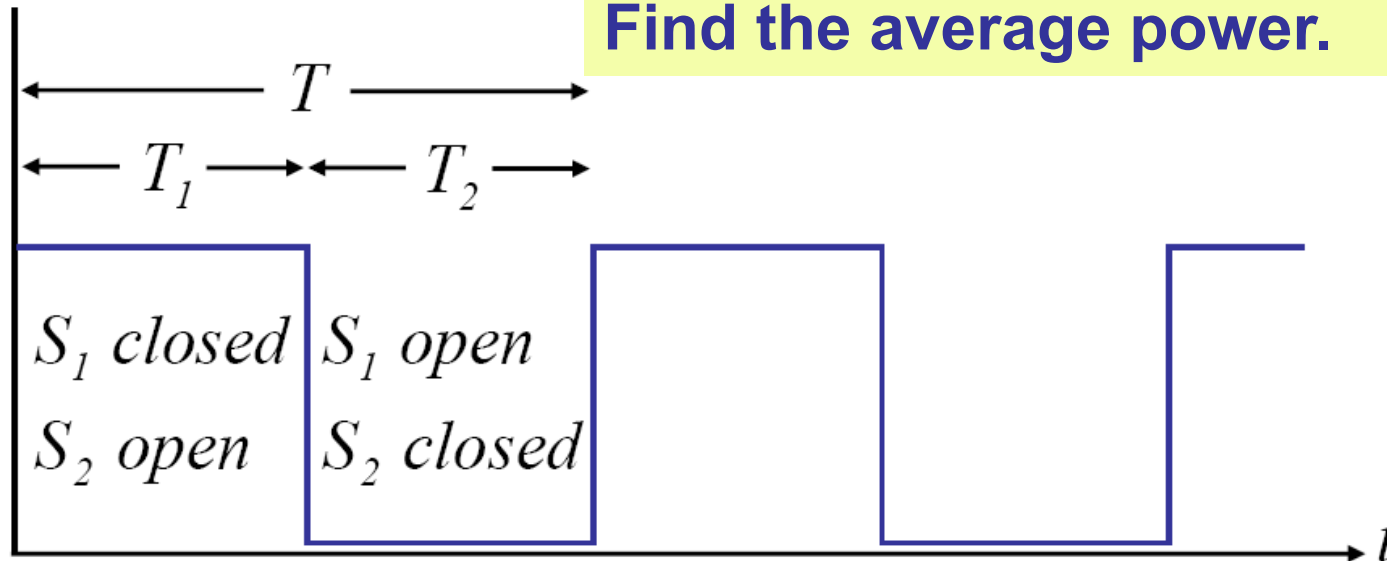Find energy dissipated in each cycle
Find the average power.





RC Circuit with a Switch

■ During T1

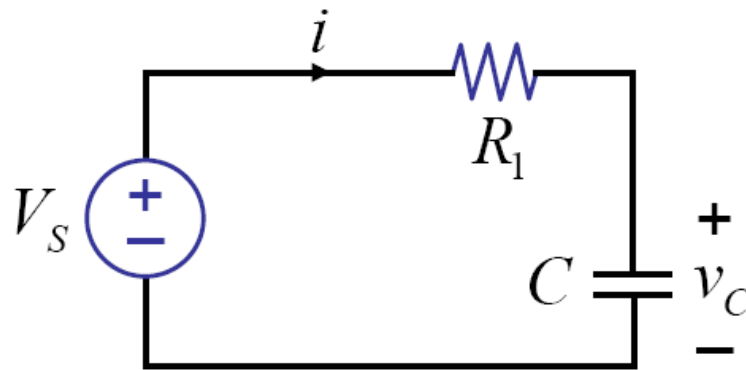

assume
 $v_C = 0$ at $t = 0$

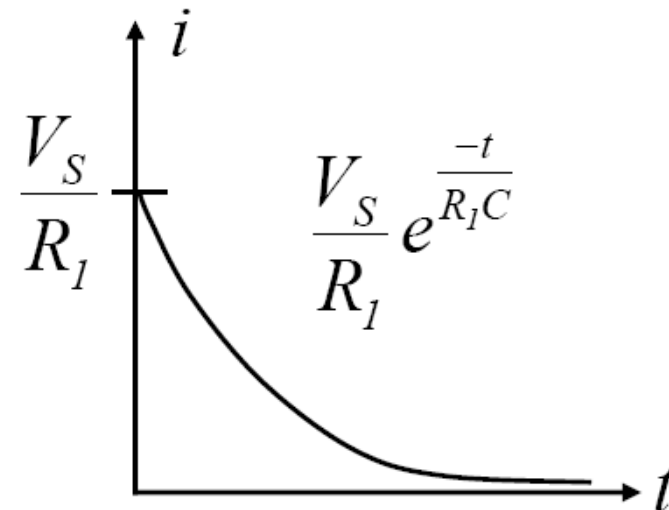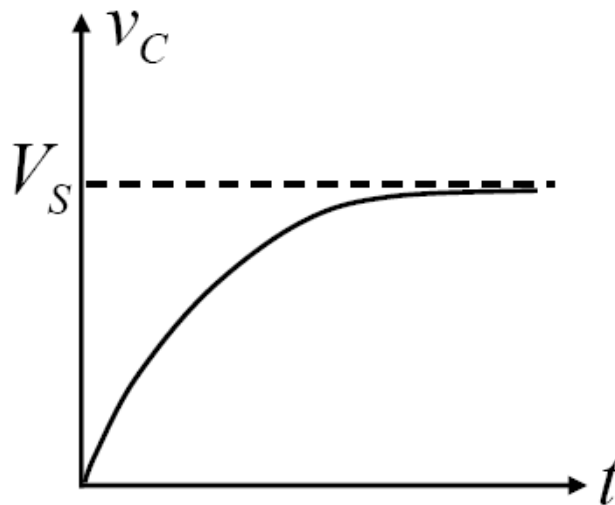

RC Circuit with a Switch

- **Energy Consumption: Total energy provided by the source during T_1**


$$E = \int_0^{T_1} V_S i dt = \int_0^{T_1} V_S \frac{V_S}{R_1} e^{-\frac{t}{R_1 C}} dt = C V_S^2 (1 - e^{-\frac{T_1}{R_1 C}})$$

$$\approx C V_S^2 \quad \text{if} \quad T_1 \gg R_1 C$$

- **Energy stored in the capacitor:** $E_C = \frac{1}{2} C V_S^2$
- **Energy dissipated in the resistor:** $E_1 = \frac{1}{2} C V_S^2$
 - Independent of R

RC Circuit with a Switch

■ During T2

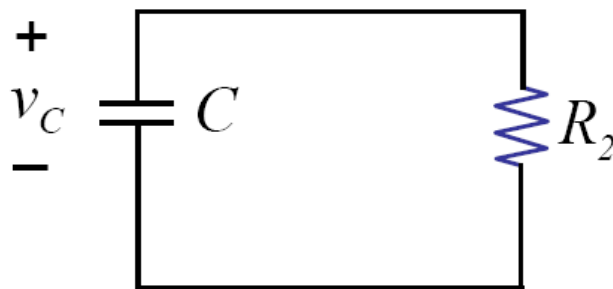

Initially, $v_C = V_s$ (recall $T_1 \gg R_1 C$)

If we assume $T_2 \gg R_2 C$

Capacitor energy is fully discharged =

Energy dissipated by the resistor: $E_2 = \frac{1}{2} C V_s^2$

- (again) independent of R

Putting Together

- **Energy dissipated in each cycle**

$$E = E_1 + E_2 = CV_s^2$$

- assuming that capacitor is fully charged and discharged during the period.

- **Average power**



$$\overline{P} = \frac{E}{T} = CV_s^2 f$$

Outline

Textbook: 11.1, 11.2, 11.3, 11.5



- Power and Energy Relations for Simple RC Circuit
- Average Power in an RC Circuit
- **Power Dissipation in Logic Gates**
- CMOS Logic

Power Dissipation of Inverter

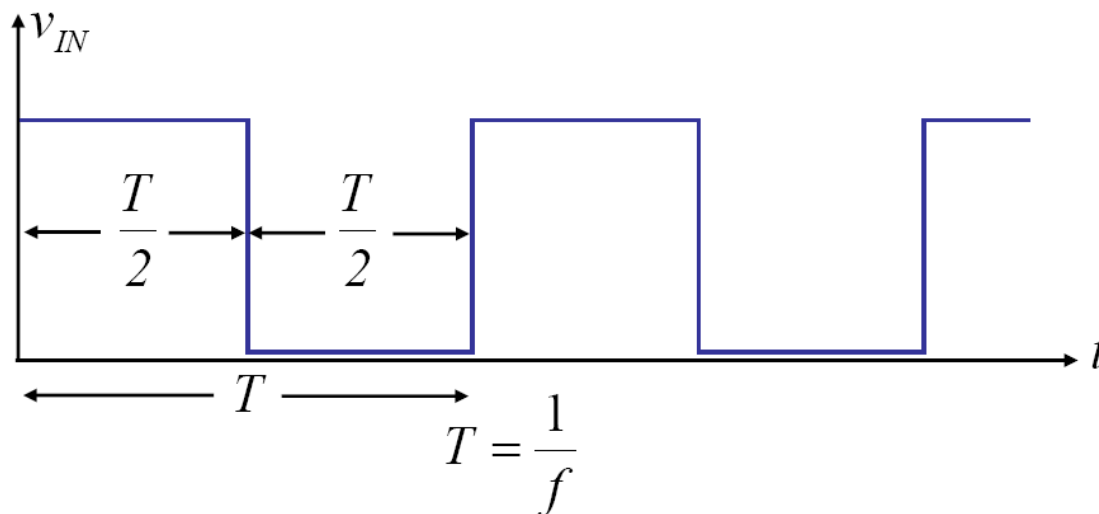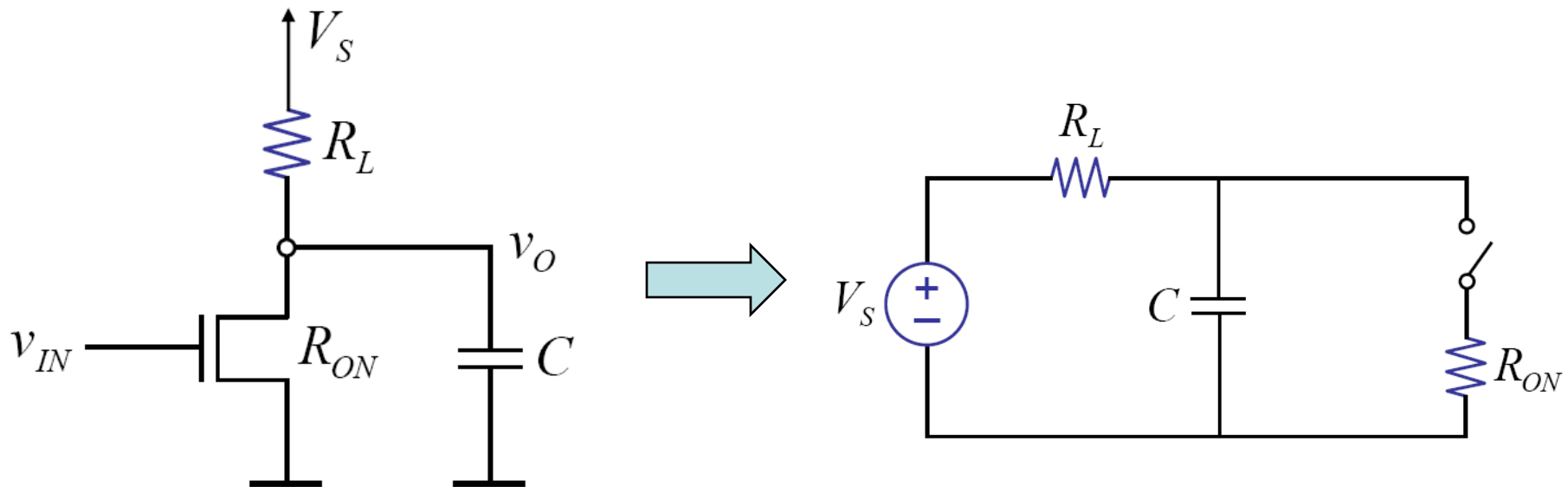

Power Dissipation of Inverter

■ During input is high

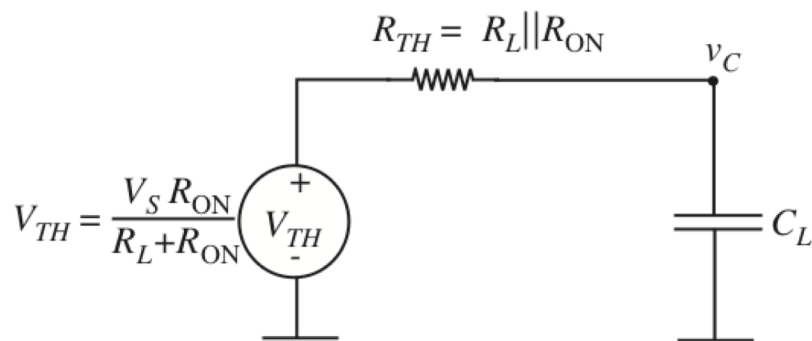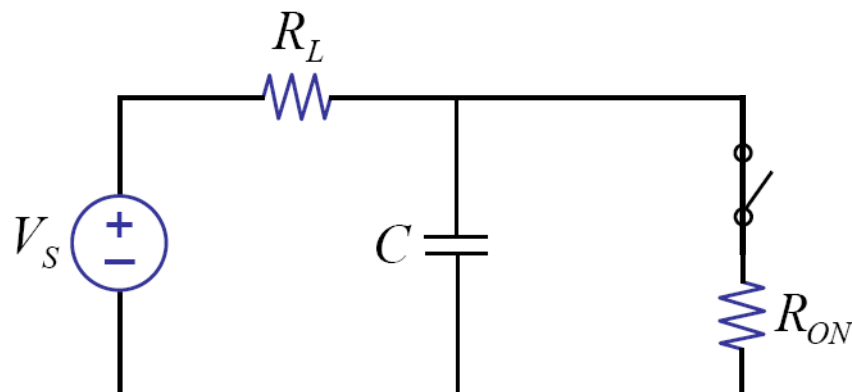

Assuming initial voltage on capacitor is 0:


$$v_C = V_{TH} + (V_S - V_{TH})e^{\frac{-t}{R_{TH}C_L}}$$

Thus, if $T \gg R_{TH}C_L$, the energy consumption w_1

$$w_1 = \frac{V_S^2}{R_L + R_{ON}} T_1 + \frac{V_S^2 R_L^2 C_L}{2(R_L + R_{ON})^2}.$$

Power Dissipation of Inverter

■ During input is low

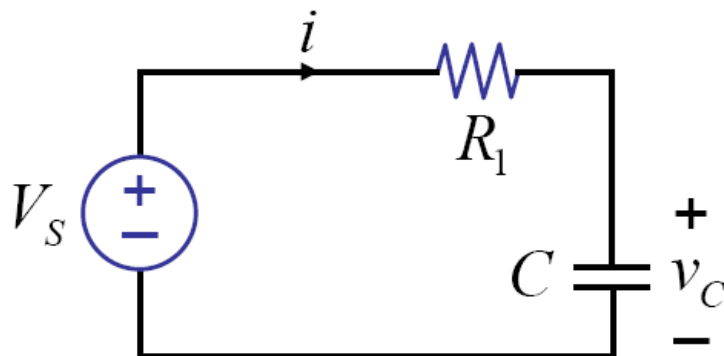

Assuming initial voltage on capacitor is V_{TH} and final voltage of V_S :

$$v_C = V_{TH} + (V_S - V_{TH}) \left(1 - e^{\frac{-t}{R_L C_L}} \right)$$

Thus, if $T \gg R_L C_L$, the energy consumption w_2

$$w_2 = \frac{V_S^2 R_L^2 C_L}{2(R_L + R_{ON})^2}.$$

Power Dissipation of Inverter

- **Average power = static power + dynamic power**
 - Static power: independent of the frequency
 - Power loss due to the static or continuous current drawn from the power supply
 - Dynamic power: dependent on the frequency
 - Power loss due to switching currents to charge and discharge capacitors

Power Dissipation of Inverter

■ Average Power

$$\bar{P} = \frac{V_s^2}{2(R_L + R_{ON})} + CV_s^2 f \frac{R_L^2}{(R_L + R_{ON})^2} \xrightarrow{R_L \gg R_{ON}} \frac{V_s^2}{2R_L} + CV_s^2 f$$

\downarrow \downarrow
Static power + dynamic power


- ✓ Static power: Independent of the switching frequency.
- ✓ Dynamic power: related to switching capacitor

$$\frac{P_{static}}{P_{dynamic}} = \frac{R_L + R_{ON}}{R_L} \times \frac{T}{2R_L C_L}$$

Worst Static Power Dissipation

■ Example 11.1
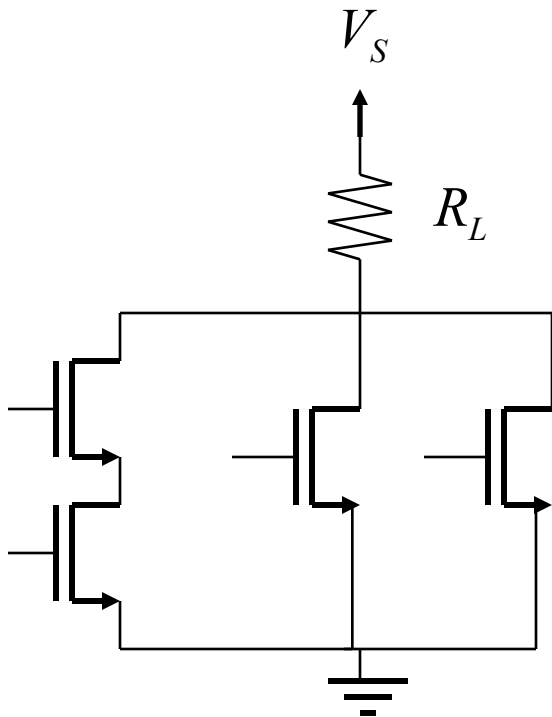
$$R_L = 100k\Omega, \quad R_{ON} = 10k\Omega$$



Dynamic vs. Static Power

■ Example



a chip with 10^6 gates clocking
at 100 MHz

$$C = 1 \text{ fF}$$

$$R_L = 10 \text{ k}\Omega$$

$$f = 100 \times 10^6$$

$$V_S = 5 \text{ V}$$

$$\frac{P_{static}}{P_{dynamic}} = \frac{R_L + R_{ON}}{R_L} \times \frac{T}{2R_L C_L}$$

Power Minimization

■ Dynamic power

- Reduce the supply voltage (5V \rightarrow 1.5V)
 - Change the voltage on need
- Reduce the capacitance
- Reduce the frequency
 - Turn off clock when not in use

■ Static power


- CMOS logic

Outline


Textbook: 11.1, 11.2, 11.3, 11.5

- Power and Energy Relations for Simple RC Circuit
- Average Power in an RC Circuit
- Power Dissipation in Logic Gates
- **CMOS Logic**

CMOS Logic (Complementary MOS)

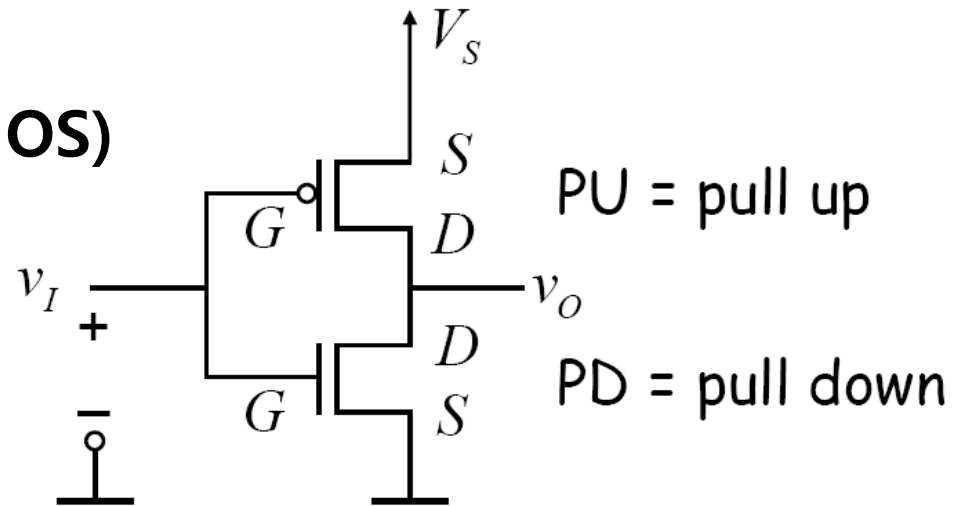


PMOS

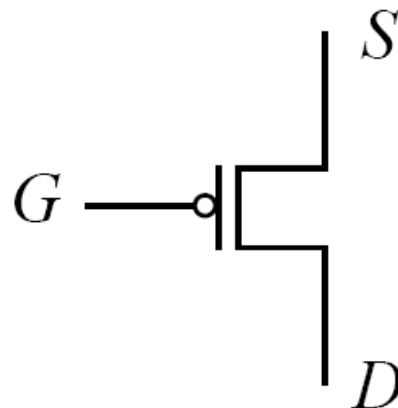

on when $v_{GS} \leq V_{TP}$
 off when $v_{GS} > V_{TP}$
 e.g. $V_{TP} = -1V$


CMOS Inverter

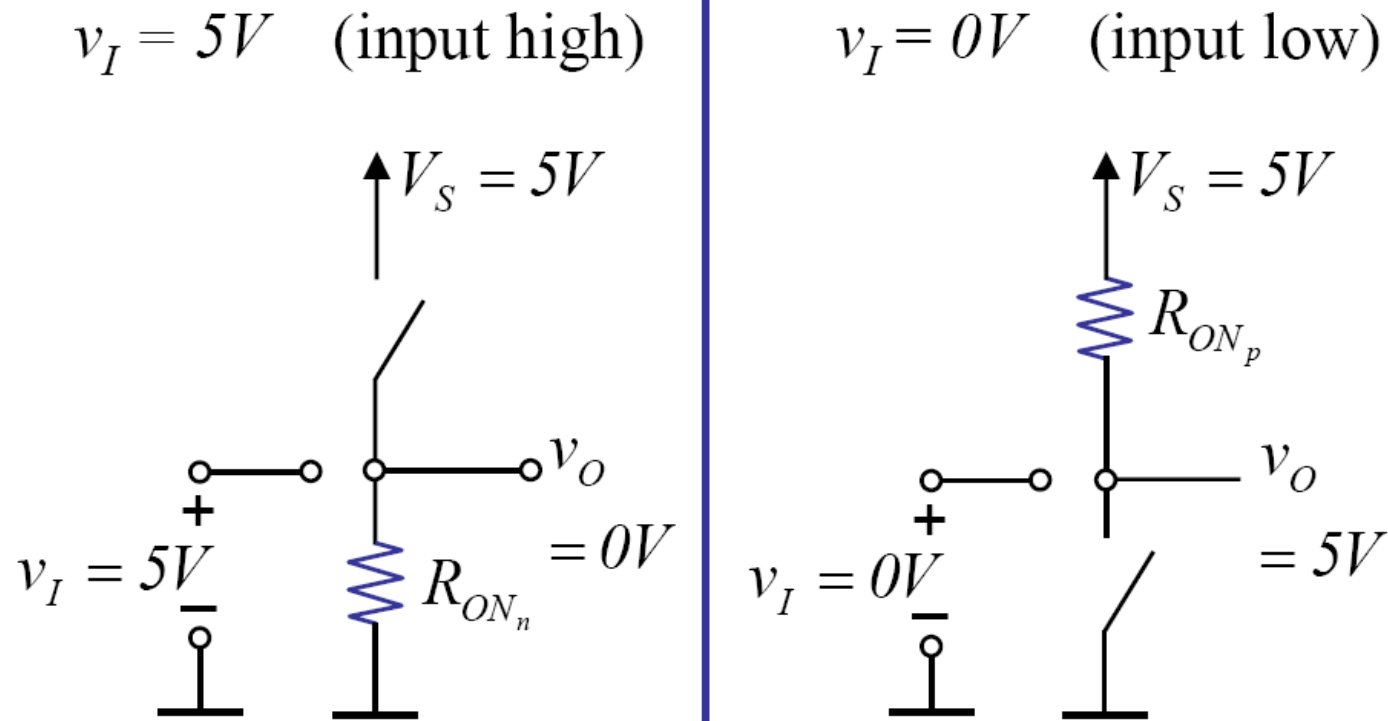

No static power!

- No direct path from the supply to ground


Dynamic Power of CMOS

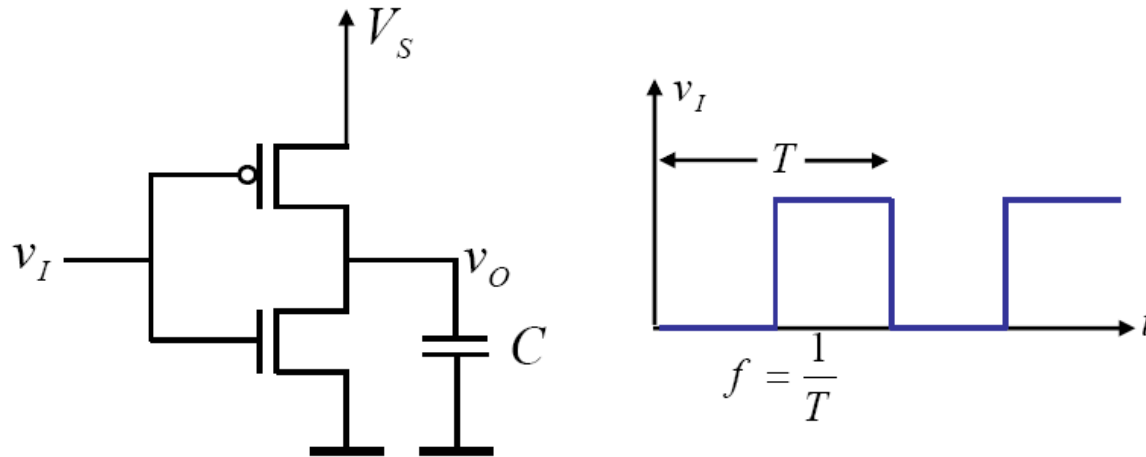

$$\overline{P} = CV_S^2 f$$

Static Power of CMOS

- Leakage power
- Transient current

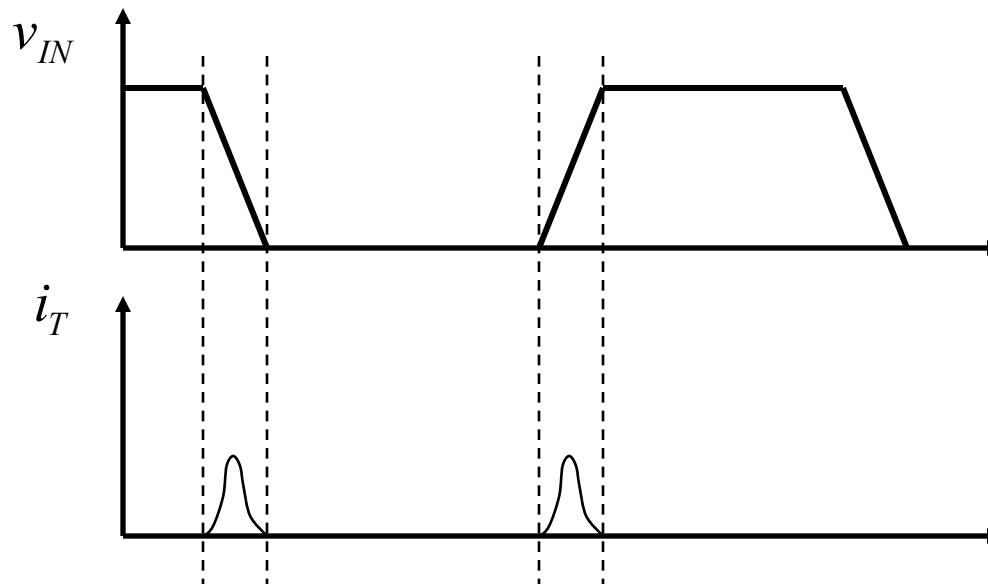

Examples

- ✓ **Example 11.6: Processor SA27E**
 - **# of gates = 3M, 25% activity**

$$C_L = 30\text{ fF}, \quad V_S = 1.5\text{ V}, \quad f = 425\text{ MHz}$$

$$P_{dynamic} = (Fraction\ switching) \times (\# gates) \times f C_L V_S^2$$

Examples

■ Exercise: Estimate the power of the following processor

- # of gates = 25M, 25% activity

$$C_L = 1fF, \quad V_S = 1.5V, \quad f = 3GHz$$

Summary

- Total power = static power + dynamic power
- CMOS does not exhibit static loss
- Dynamic power

$$P_{dynamic} = (Fraction\ switching) \times (\# gates) \times f C_L V_S^2$$

- Reduce the supply voltage
- Reduce the switching activities
- Turn off the logic not in use (clock gating)