4190.206A: Electrical and Electronic Circuits
(Prof. Jae Wook Lee)
Chapter 2. Resistive Networks

Last Updated:
2018/9/13

http://etl.snu.ac.kr/course/view.php?id=147773

Solve the following exercise problems in the textbook (*Foundations of Analog and Digital Electronic Circuits, Anant Agarwal and Jeffery H. Lang, 2005*). Please submit your work **before** the class on the due date. We will grade it with pass/fail.

Due date: 9/22 (Thu)

Exercise 2.3, Exercise 2.4, Problem 2.2, Problem 2.4, Exercise 2.9